

Analog IC Design

Lecture 20 Common-Mode Feedback (CMFB)

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University


Outline

- ❑ Well-defined and ill-defined output level
- ❑ Common-mode feedback (CMFB) loop
- ❑ Discrete-time CMFB
- ❑ CMFB loop practical aspects and examples
- ❑ Fully-differential OTA simulation example


Outline

- ❑ Well-defined and ill-defined output level
- ❑ Common-mode feedback (CMFB) loop
- ❑ Discrete-time CMFB
- ❑ CMFB loop practical aspects and examples
- ❑ Fully-differential OTA simulation example


Well-Defined Output Level

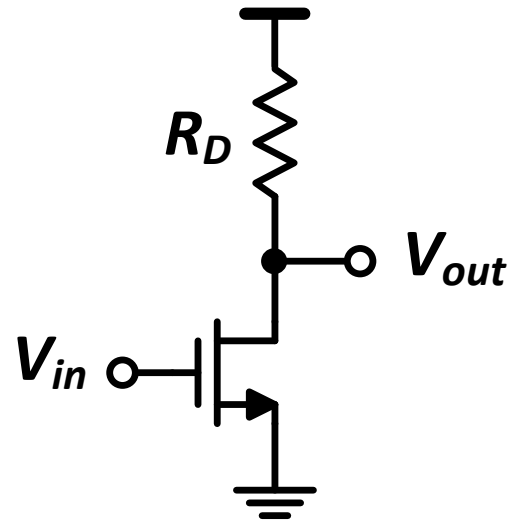


III-Defined Output Level

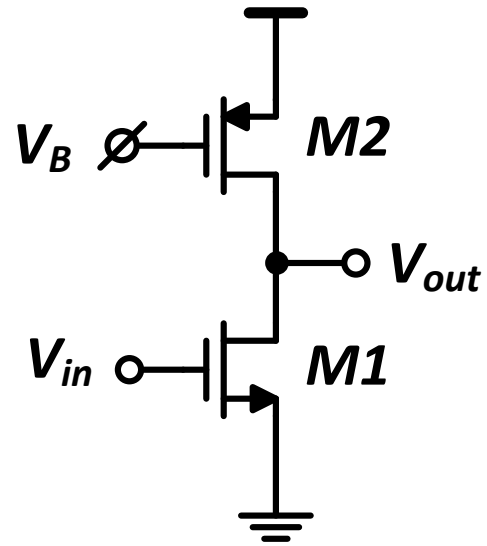


Is This Output Well-Defined?

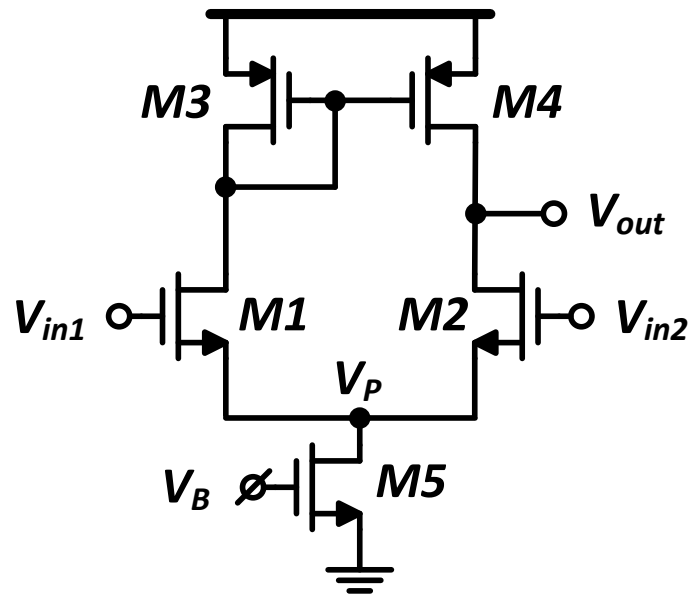

Is This Output Well-Defined?

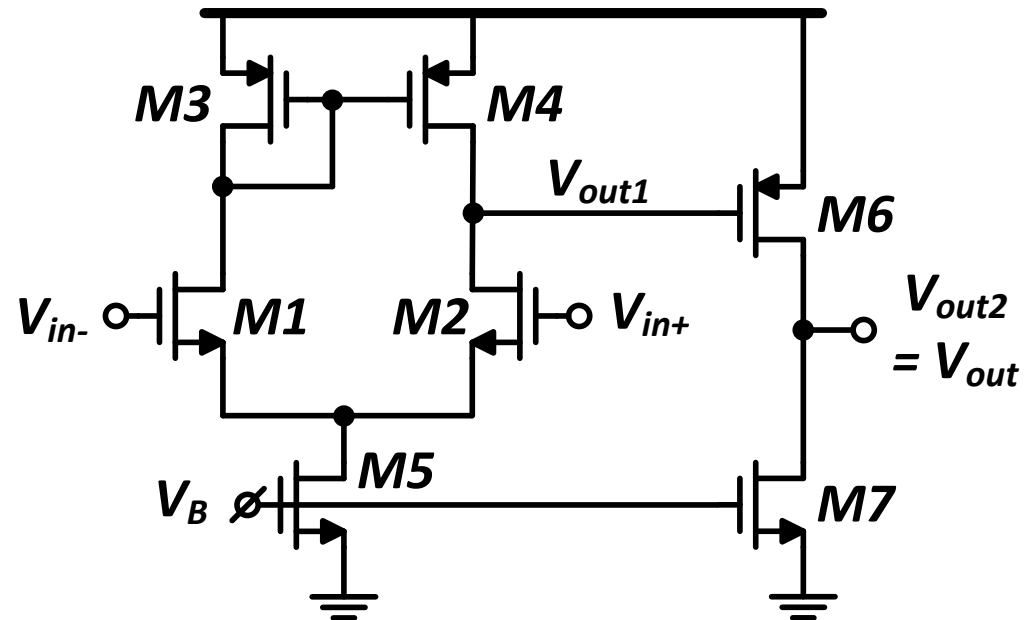


Well-Defined CM Level

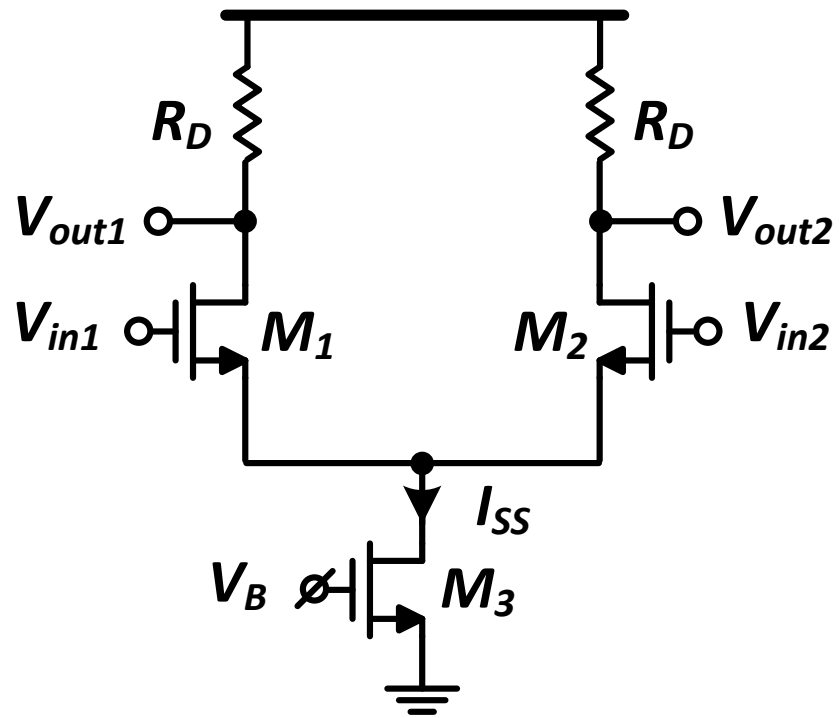

Ill-Defined CM Level

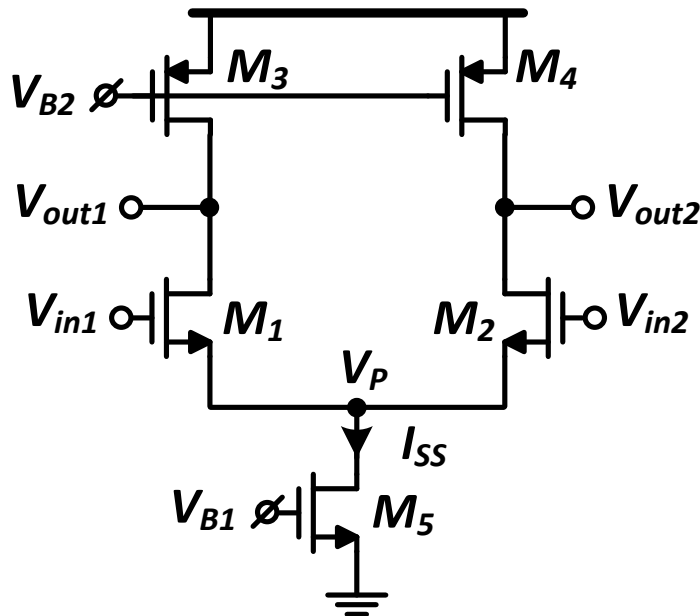- ❑ Mismatches ALWAYS create a finite error between $I_{D3,4}$ and $I_{SS}/2$
- ❑ $I_{D3,4} > I_{SS}/2$
 - $V_{out1,2}$ rise $\rightarrow I_{D3,4}$ fall to $I_{SS}/2 \rightarrow$ M3 and M4 enter triode
- ❑ $I_{D3,4} < I_{SS}/2$
 - $V_{out1,2}$ fall $\rightarrow I_{SS}/2$ fall to $I_{D3,4} \rightarrow$ M1, M2, and M5 enter triode



Why Fully Differential Circuits


- ❑ Fully differential vs diff input SE output
 - Larger output swing
 - No mirror poles (higher speed)
 - Better CMRR and PSRR
 - Better SNR
 - Better linearity (lower distortion)
 - Easy to analyze!
- ❑ But common-mode feedback (CMFB) circuit is required...

Outline

- ❑ Well-defined and ill-defined output level
- ❑ Common-mode feedback (CMFB) loop
- ❑ Discrete-time CMFB
- ❑ CMFB loop practical aspects and examples
- ❑ Fully-differential OTA simulation example


Common-Mode Feedback (CMFB)

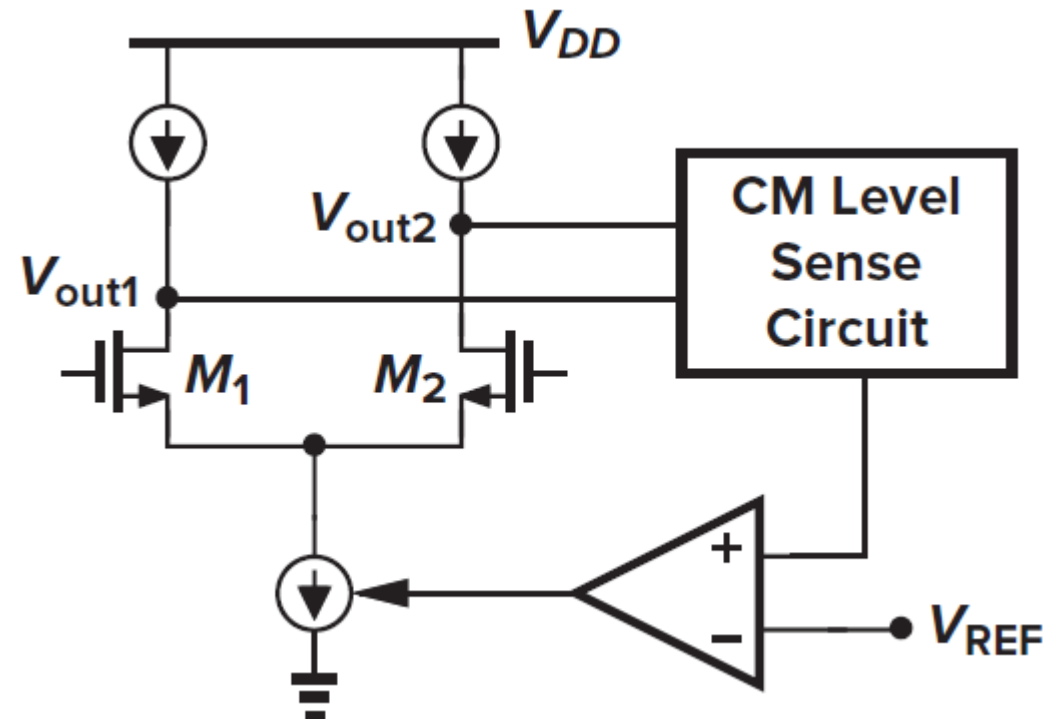- ❑ Negative FB system
 1. Sense CM level
 2. Compare it to a reference
 3. Return the error to the bias circuit




CM Sensing: Resistive Sensing

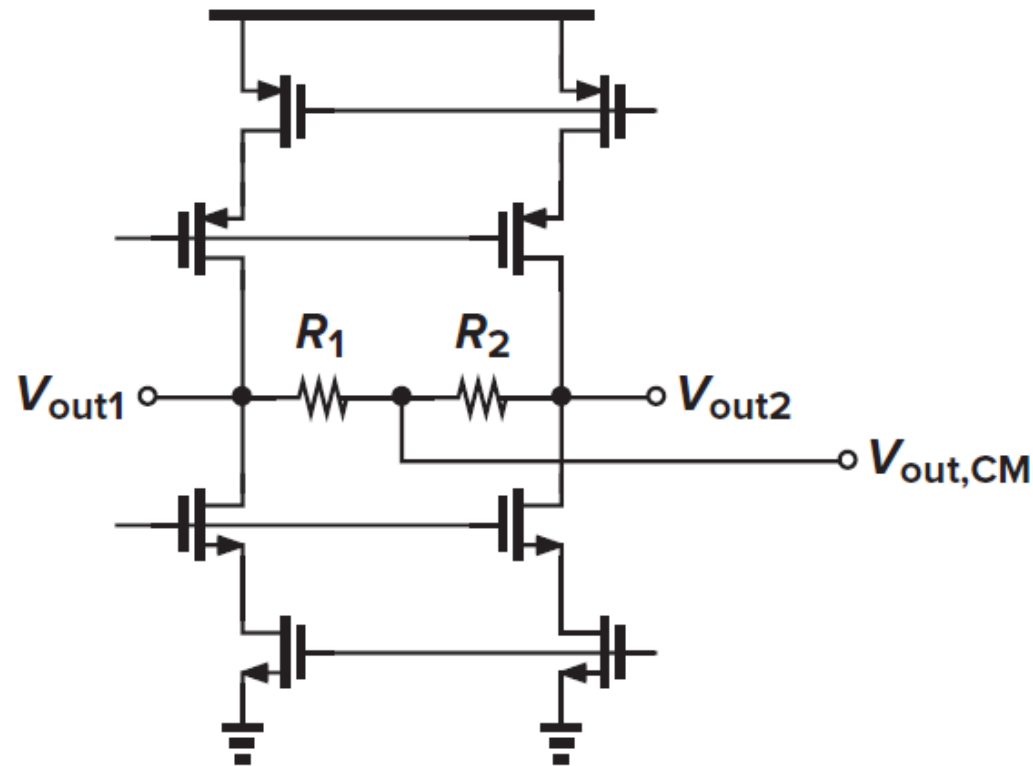- ❑ Small R will degrade the gain
- ❑ Large R occupies large area and has large parasitic capacitors
 - May degrade the CMFB loop stability!



CMFB Loop Example

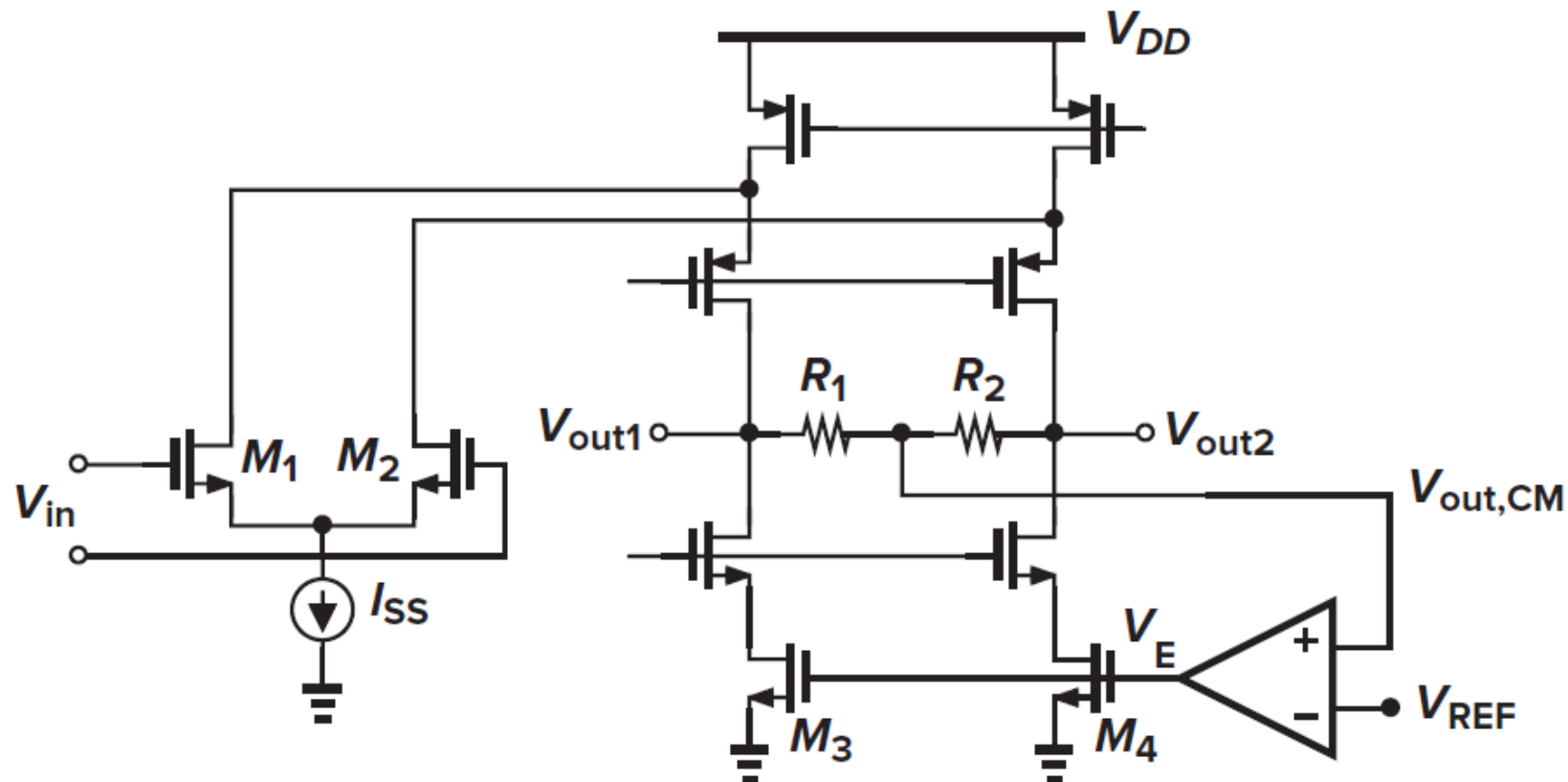
- ❑ Resistive sensing
- ❑ The feedback network forces the CM level of V_{out1} and V_{out2} to approach V_{REF}



[Razavi, 2017]


CMFB Loop Example

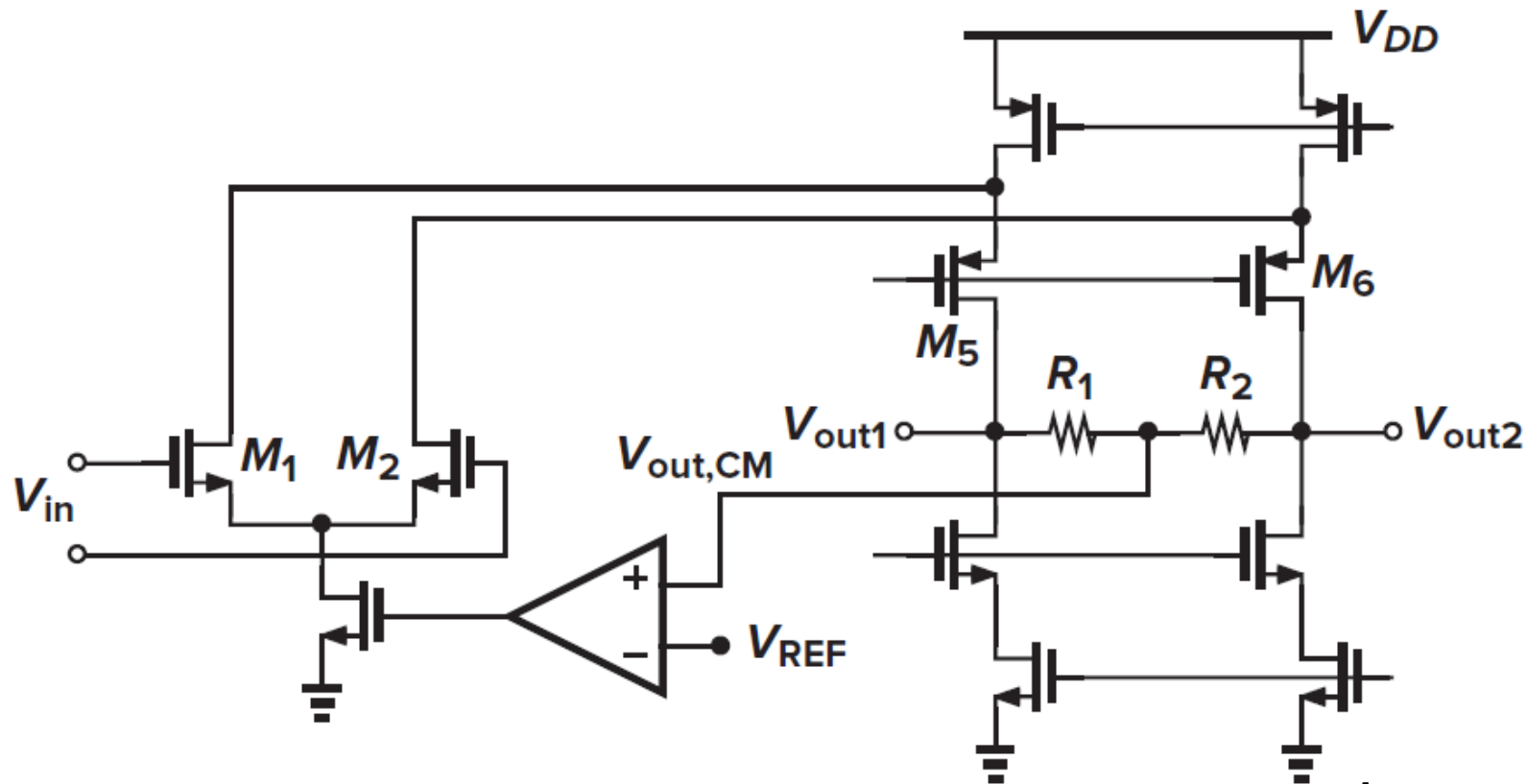- ❑ Resistive sensing
- ❑ The feedback network forces the CM level of V_{out1} and V_{out2} to approach V_{REF}




CM Sensing: Source Followers

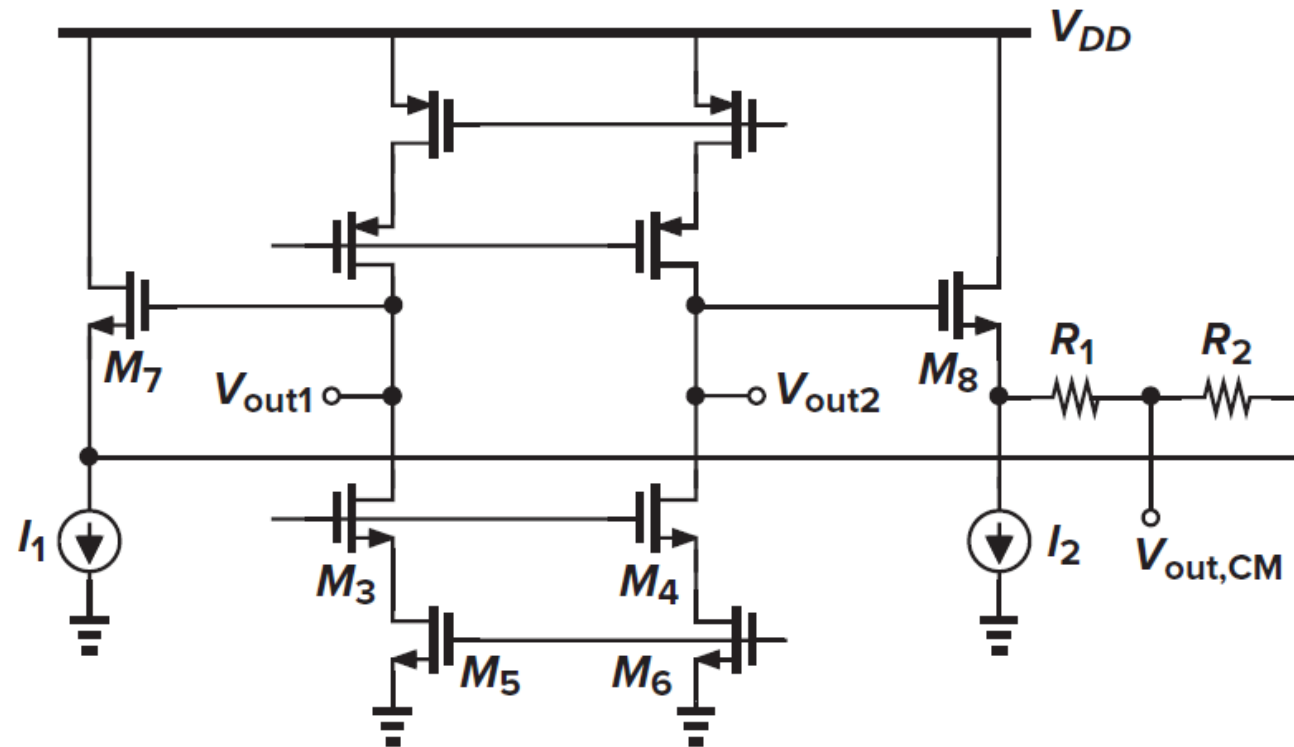- ❑ The CD stage introduces DC shift
 - Should be considered in the comparison step



CM Sensing: Source Followers

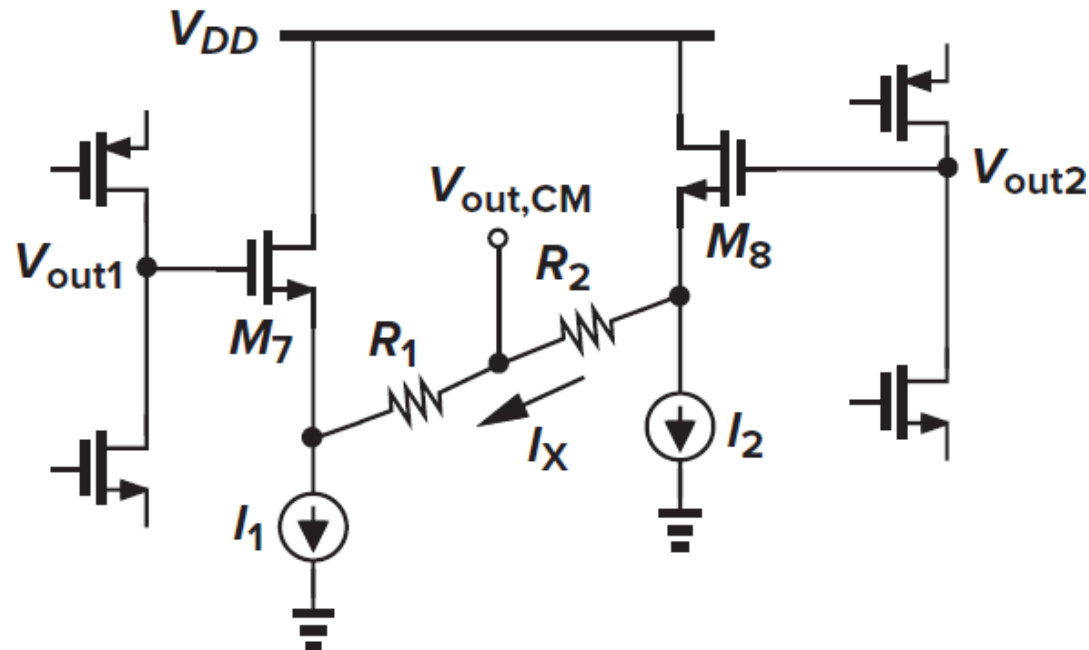- ❑ If $V_{out2} > V_{out1}$
 - I_1 must sink both $I_X \approx (V_{out2} - V_{out1})/(R_1 + R_2)$ and I_{D7} .
 - If $(R_1 + R_2)$ or I_1 are not sufficiently large: I_{D7} drops to zero
- ❑ Large $R_{1,2}$: more area and more capacitance
- ❑ Large $I_{1,2}$: more power consumption




CM Sensing: Source Followers

- ❑ Output swing is reduced

- Without CMFB: $V_{out,min} = V_{ov3} + V_{ov5}$

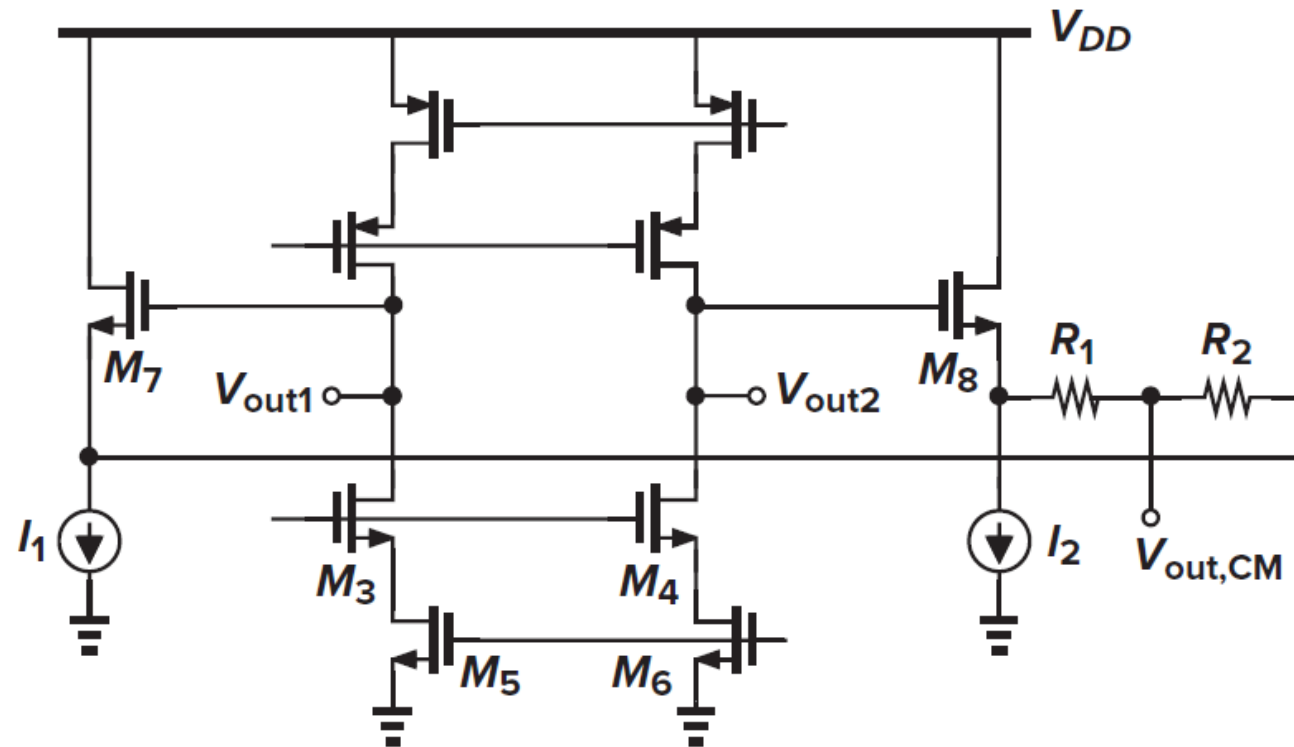- With CMFB: $V_{out,min} = V_{TH} + V_{ov7} + V_{I1}$



Continuous Time CMFB Summary

- ❑ Resistive sensing → Low voltage gain
- ❑ Source followers → Limited linear range and high power
- ❑ Other techniques exist
 - But also suffer from limited linear range
- ❑ Designing continuous-time (CT) CMFB circuits that are both linear and operate with low power-supply voltages is not an easy task
 - It is an area of continuing research!

Outline


- ❑ Well-defined and ill-defined output level
- ❑ Common-mode feedback (CMFB) loop
- ❑ Discrete-time CMFB
- ❑ CMFB loop practical aspects and examples
- ❑ Fully-differential OTA simulation example

Discrete Time CMFB

- ❑ Another popular CMFB technique is discrete-time switched-capacitor CMFB
 - Uses switches and capacitors
 - The circuit must be refreshed periodically
 - Suitable for discrete-time switched-capacitor circuits

Switched-Capacitor CMFB

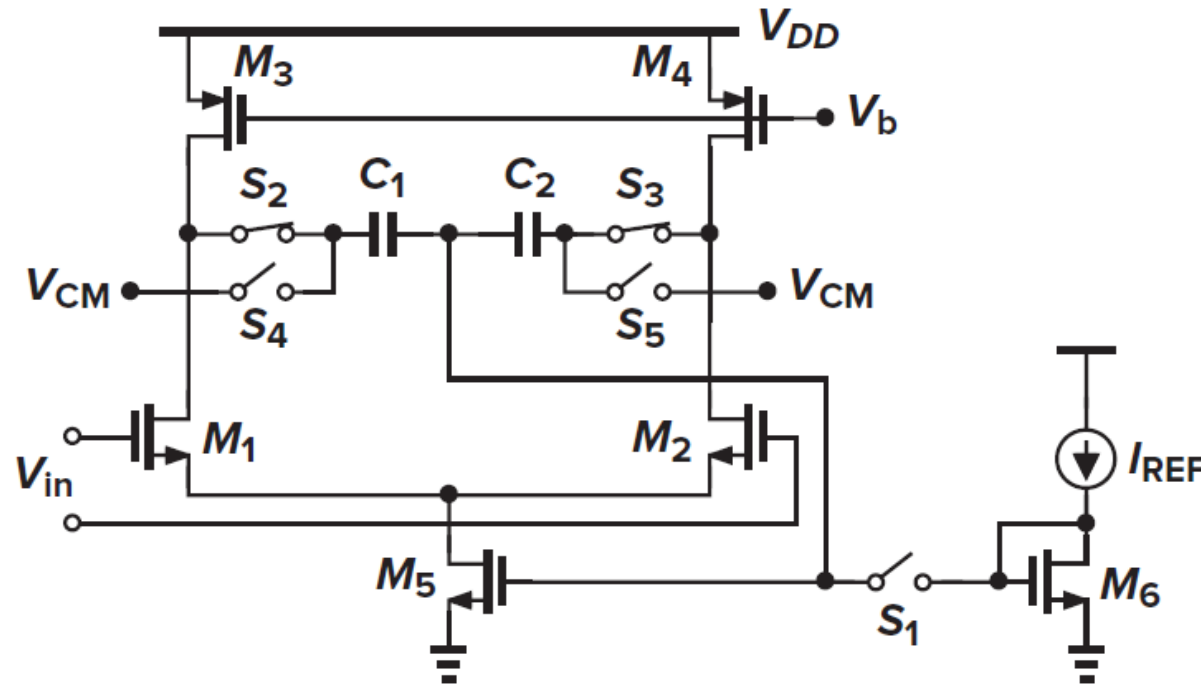- ❑ Reset phase: S1, S4, and S5 close
 - Capacitor charged: $V_C = V_{CM} - V_{GS6}$
- ❑ Amplification phase: S2 and S3 close
 - $V_{outCM} = V_C + V_{GS5} = V_{CM} - V_{GS6} + V_{GS5} \approx V_{CM}$



Outline


- ❑ Well-defined and ill-defined output level
- ❑ Common-mode feedback (CMFB) loop
- ❑ Discrete-time CMFB
- ❑ CMFB loop practical aspects and examples
- ❑ Fully-differential OTA simulation example

CMFB Loop Practical Aspects

- ❑ CMFB loop must be carefully analyzed
 - Draw small-signal model (use half-circuit principle)
 - Find LG, GX, PM, etc.
- ❑ We don't need high DC LG for CMFB loop (why?)
- ❑ Ideally CMFB loop BW should be close to differential loop BW
 - Recover quickly from CM disturbance (e.g., supply and coupling noise)
 - But this means high power consumption
- ❑ Practically set CMFB bandwidth to 30% of differential loop BW
 - For $10\tau_{diff}$ of differential settling, CM loop will have $3\tau_{CM}$
 - $\sim 95\%$ of CM disturbance is removed

CMFB Loop Capacitive Loading

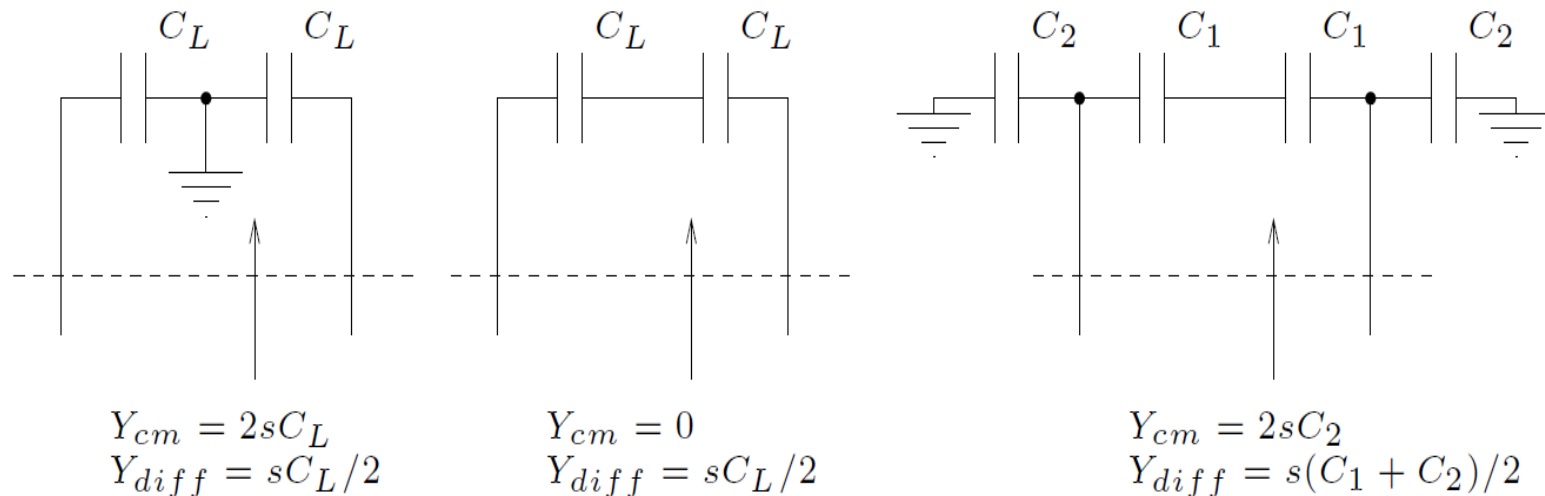- ❑ Single-stage OTAs are compensated by large C_L
- ❑ The same C_L can be used to compensate the CMFB loop
- ❑ **CAUTION:** The differential and CM capacitive loading are not necessarily the same!




CMFB Loop Example

- Typically the CMFB loop tunes 20% of the tail current (M_x)

$$LG_{o,CM} \approx \frac{1}{2} \times g_{mx} \times r_{op1} \times \frac{g_{mp2}}{g_{mx}} \times \frac{1}{2}$$
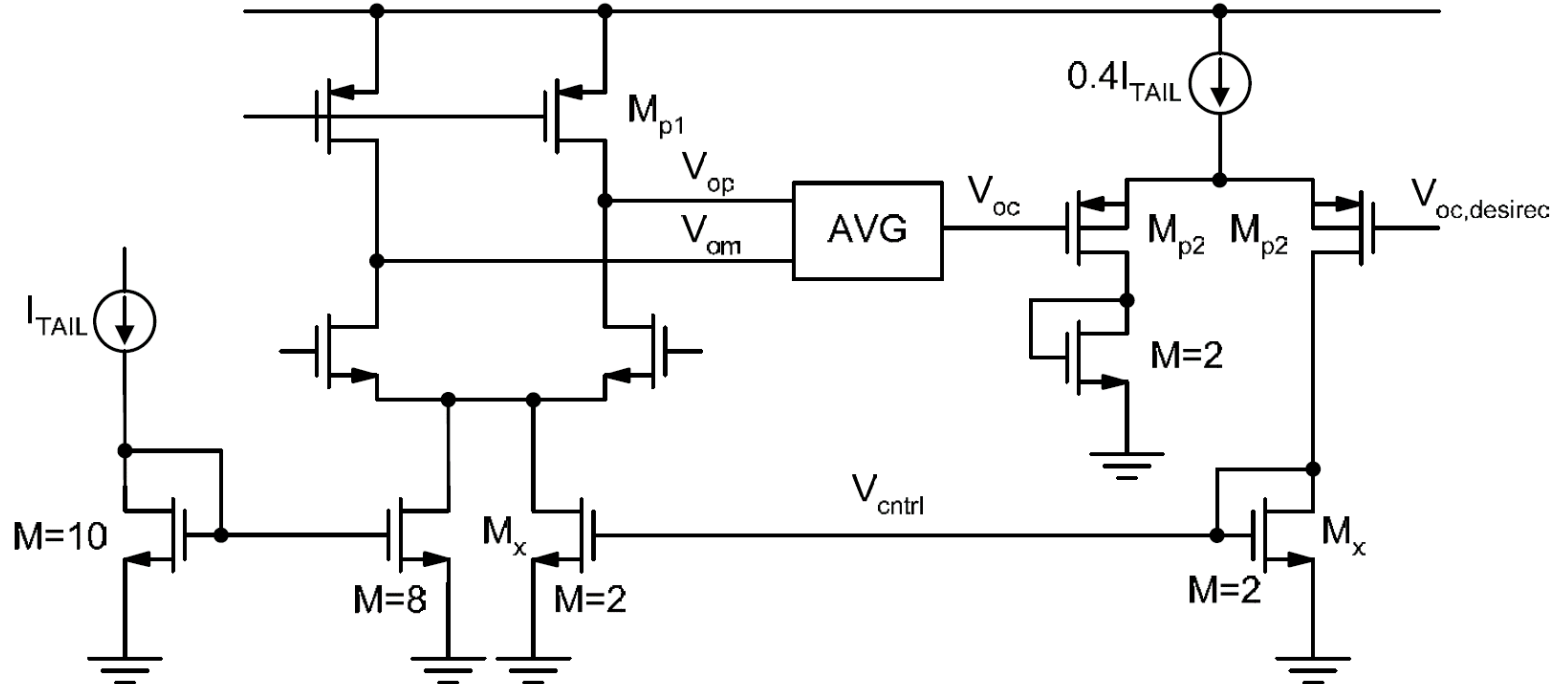
$$\omega_{u,CM} \approx LG_{o,CM} \times \frac{1}{r_{op1} C_L}$$




$C_m: LG = ?$
 $G_X = ?$
 V_{BP}

$V_{id} = 20mV$

$V_{out,cm} = 1.52V$

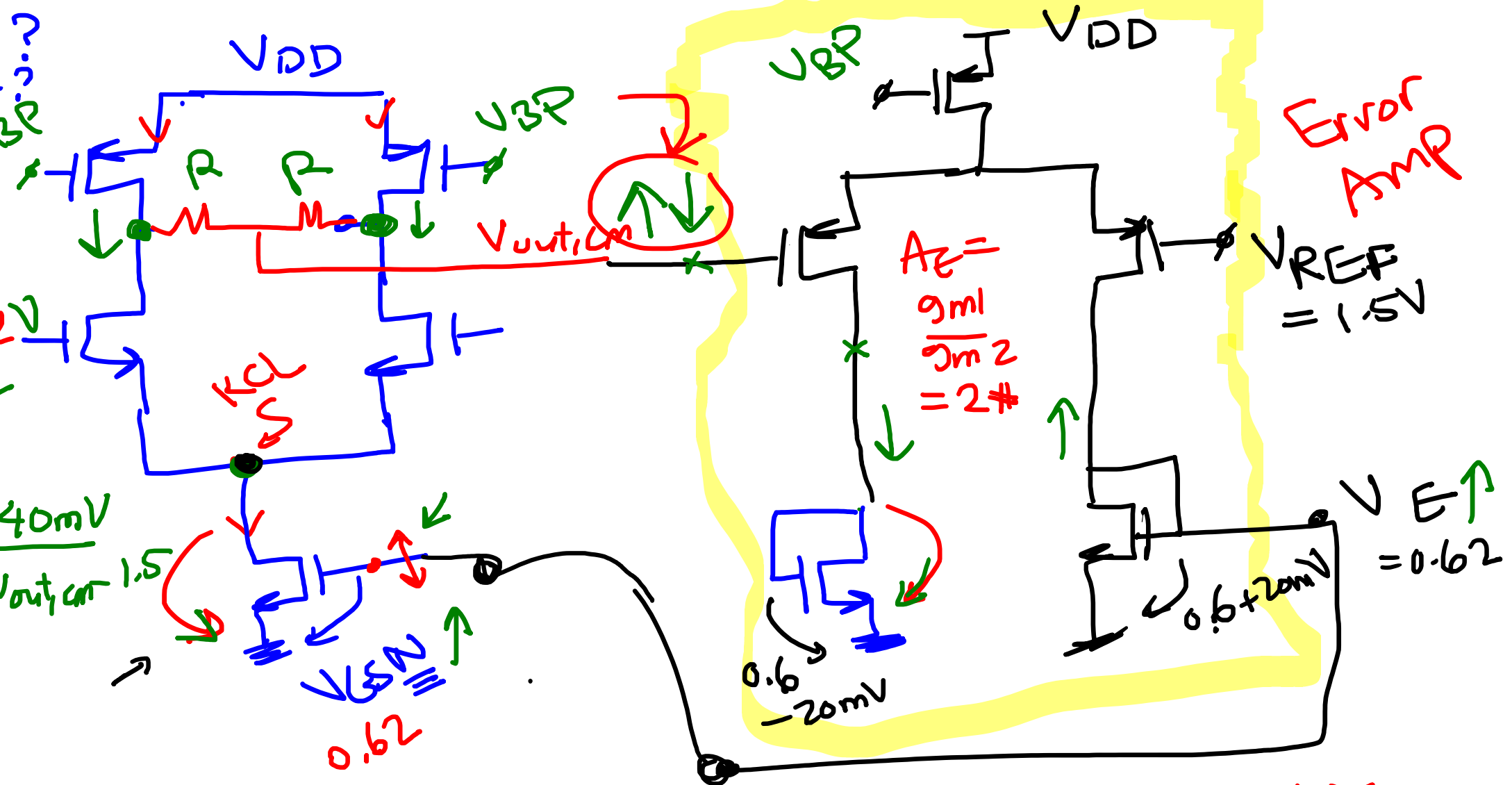$A_E = \frac{V_{od}}{V_{id}} = \frac{40mV}{V_{out,cm} - 1.5}$
 $= 2 \#$



$V_{EQ} = V_{GS,NQ}$
 $V_E = V_{EQ} + \Delta V_E$
 $V_{id} = \frac{\Delta V_E}{A_E}$

CMFB Loop Example

- ❑ Error amplifier replaced by a wire
- ❑ V_{CM} pinned to $V_{DD} - V_{GS2}$
- ❑ Max pk-to-pk diff swing $\sim 4V_T$


$$LG_{o,CM} \approx g_{m2}r_{o2}$$

$$LG_{o,diff} \approx g_{m1}(r_{o1}||r_{o2}||R)$$

$$\omega_{u,CM} \approx LG_{o,CM} \times \frac{1}{r_{o2}C_L} = \frac{g_{m2}}{C_L}$$

$$\omega_{u,diff} \approx LG_{o,diff} \times \frac{1}{(r_{o1}||r_{o2}||R)C_L} = \frac{g_{m1}}{C_L}$$
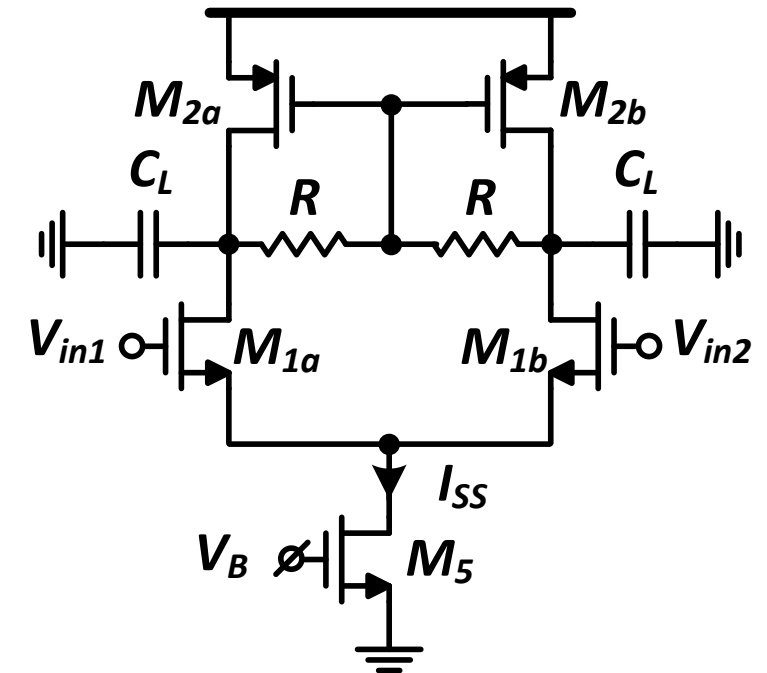
$$\omega_{p2,cm} \approx \frac{1}{RC_{gg2}}$$




Outline

- ❑ Well-defined and ill-defined output level
- ❑ Common-mode feedback (CMFB) loop
- ❑ Discrete-time CMFB
- ❑ CMFB loop practical aspects and examples
- ❑ Fully-differential OTA simulation example


Fully-Differential OTA

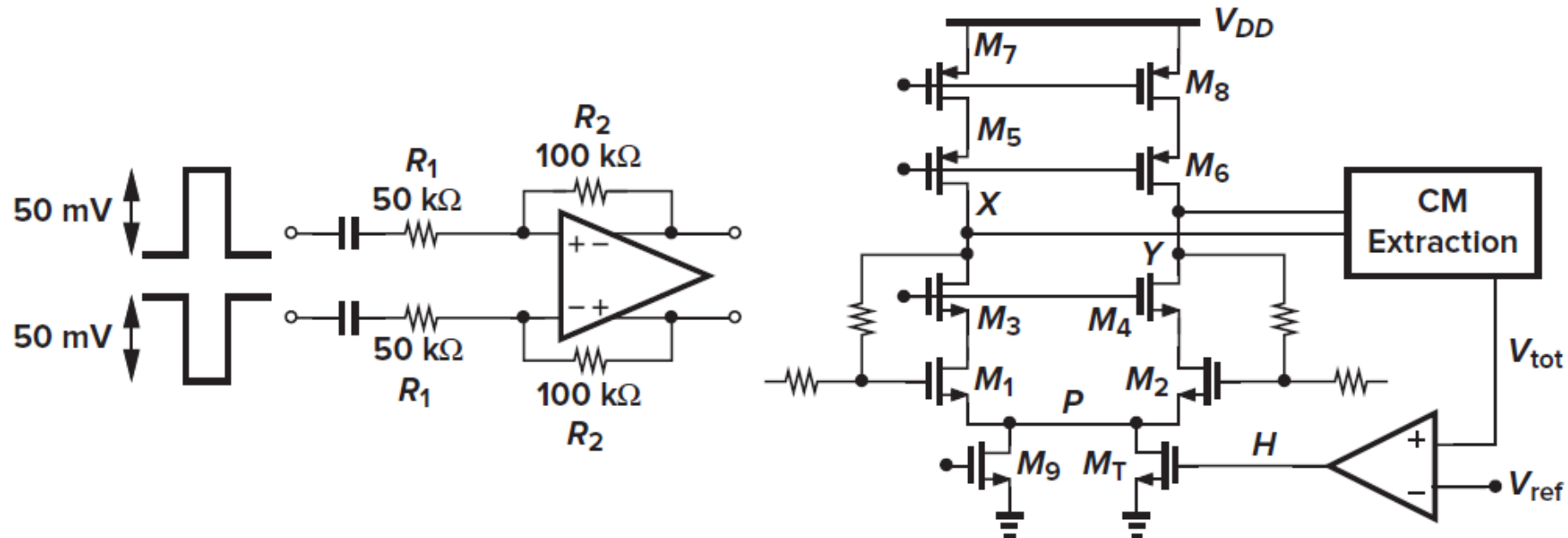- Typically M_9 carries 80% of I_{SS} \rightarrow CMFB tunes 20% in MT
- Capture large signal effects on differential and CMFB loop stability
 - Place the OTA in a closed-loop feedback system
 - Apply differential pulses (transient analysis)




Stability Analysis: Step Response

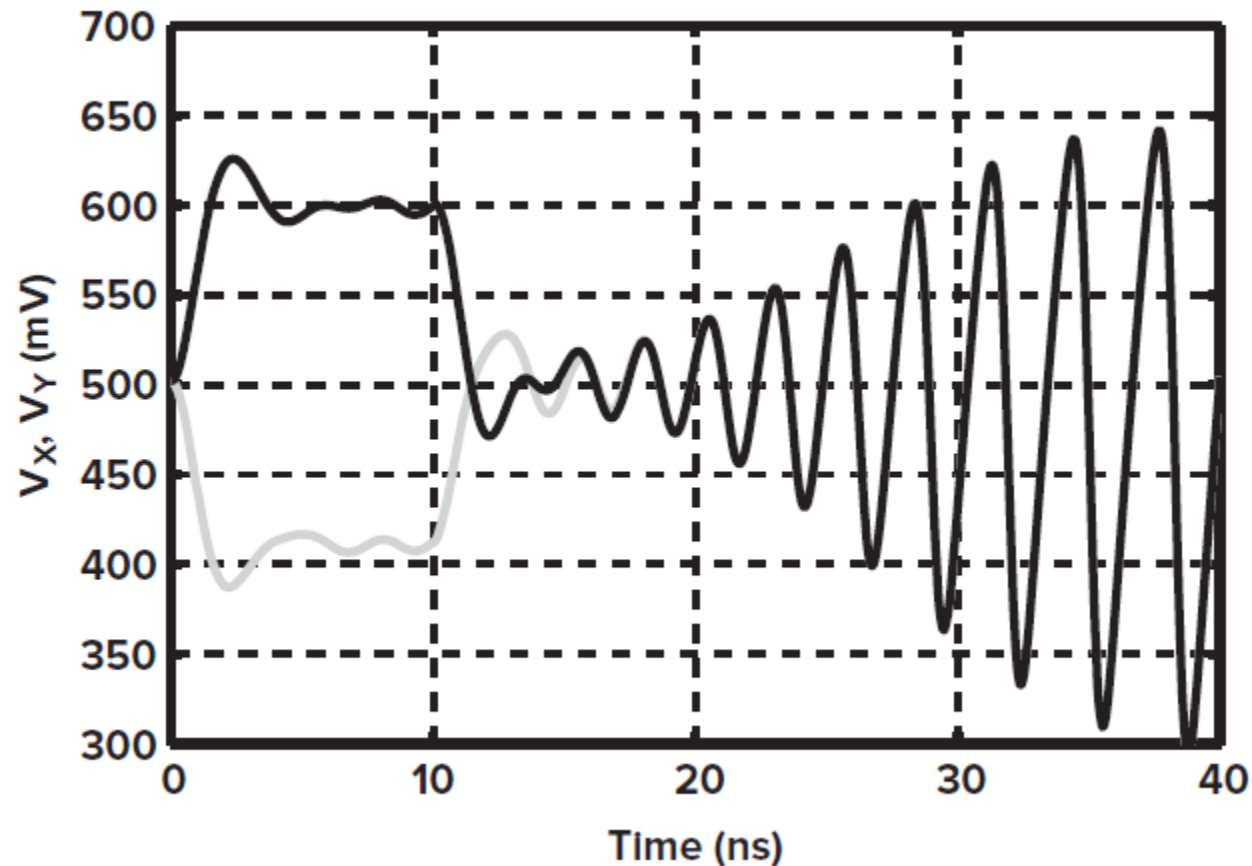- ❑ The CMFB loop is unstable!
 - Requires compensation




CMFB Loop Gain

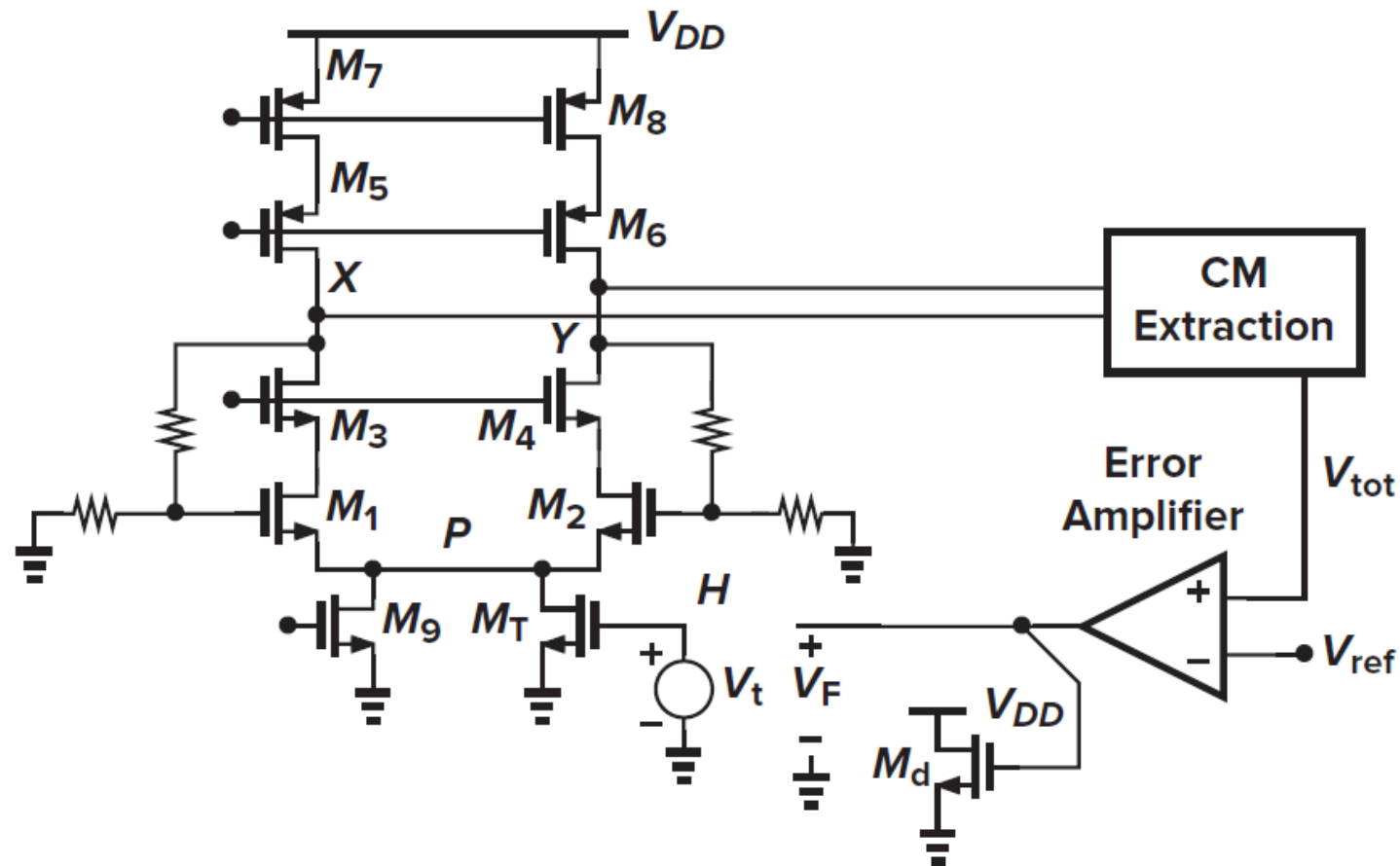- ❑ Hand analysis: Break the loop to analyze the CMFB loop gain
- ❑ Simulation: Better to use STB analysis (loading and bilateral effects considered)




Stability Analysis: LG

□ PM = -10°

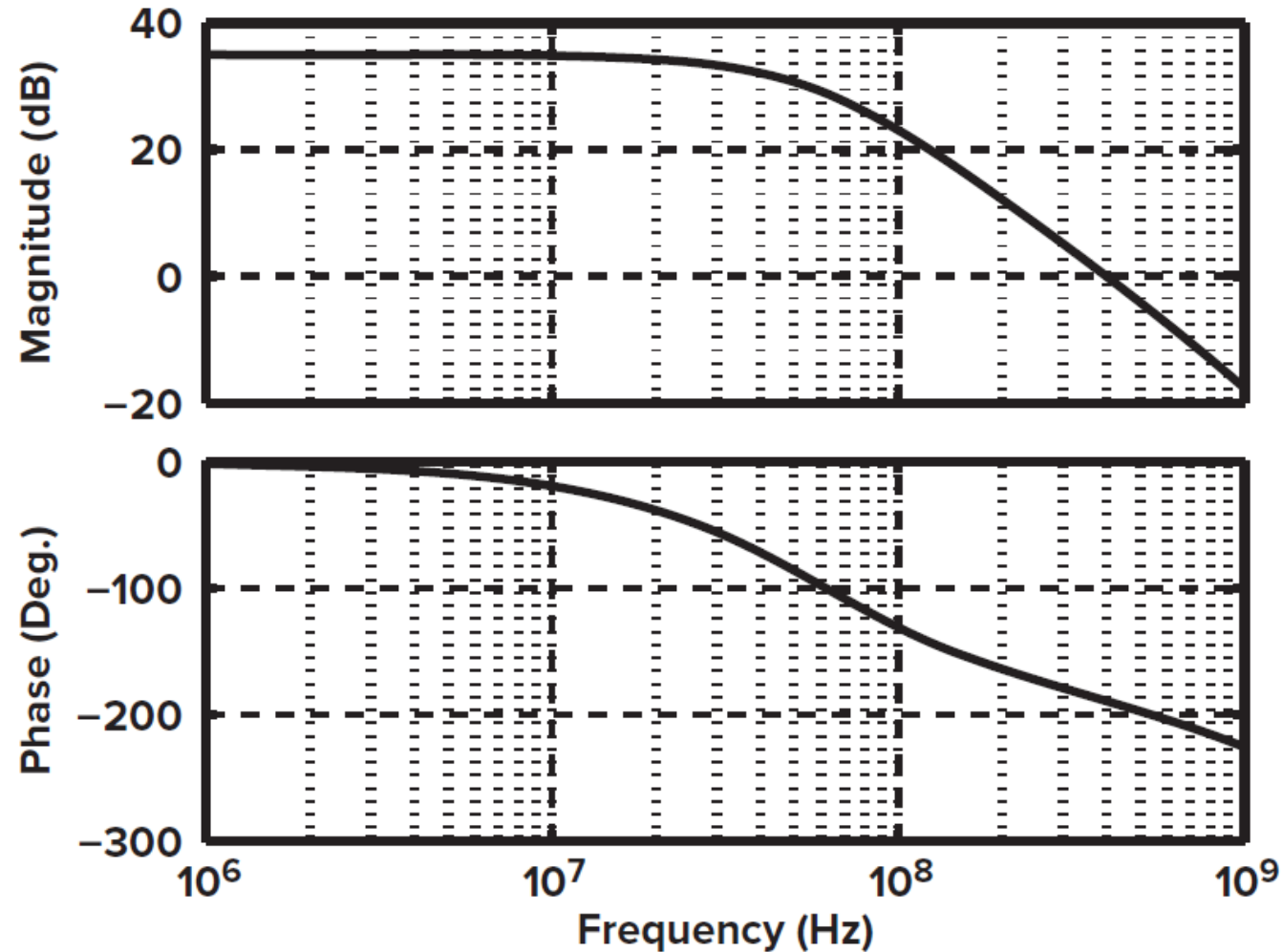


CMFB Loop Compensation

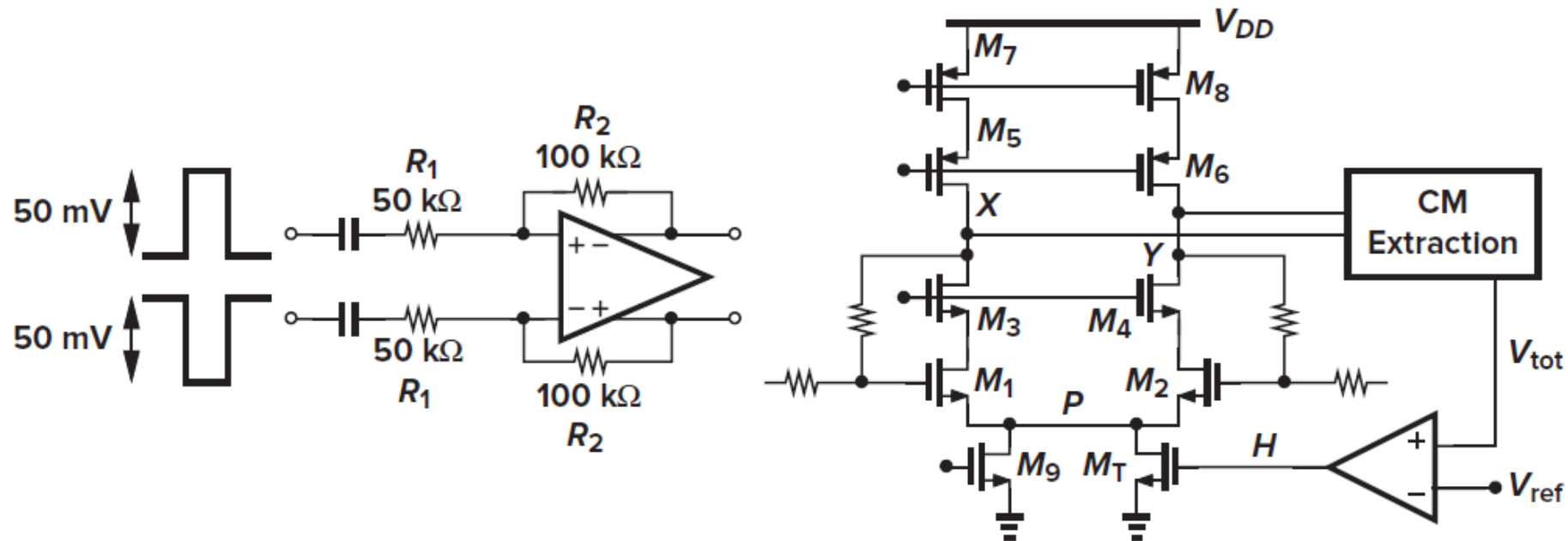- ❑ Add 3pF to the error amplifier output
 - Not the best design decision...




CMFB Loop Compensation

□ PM = 50°

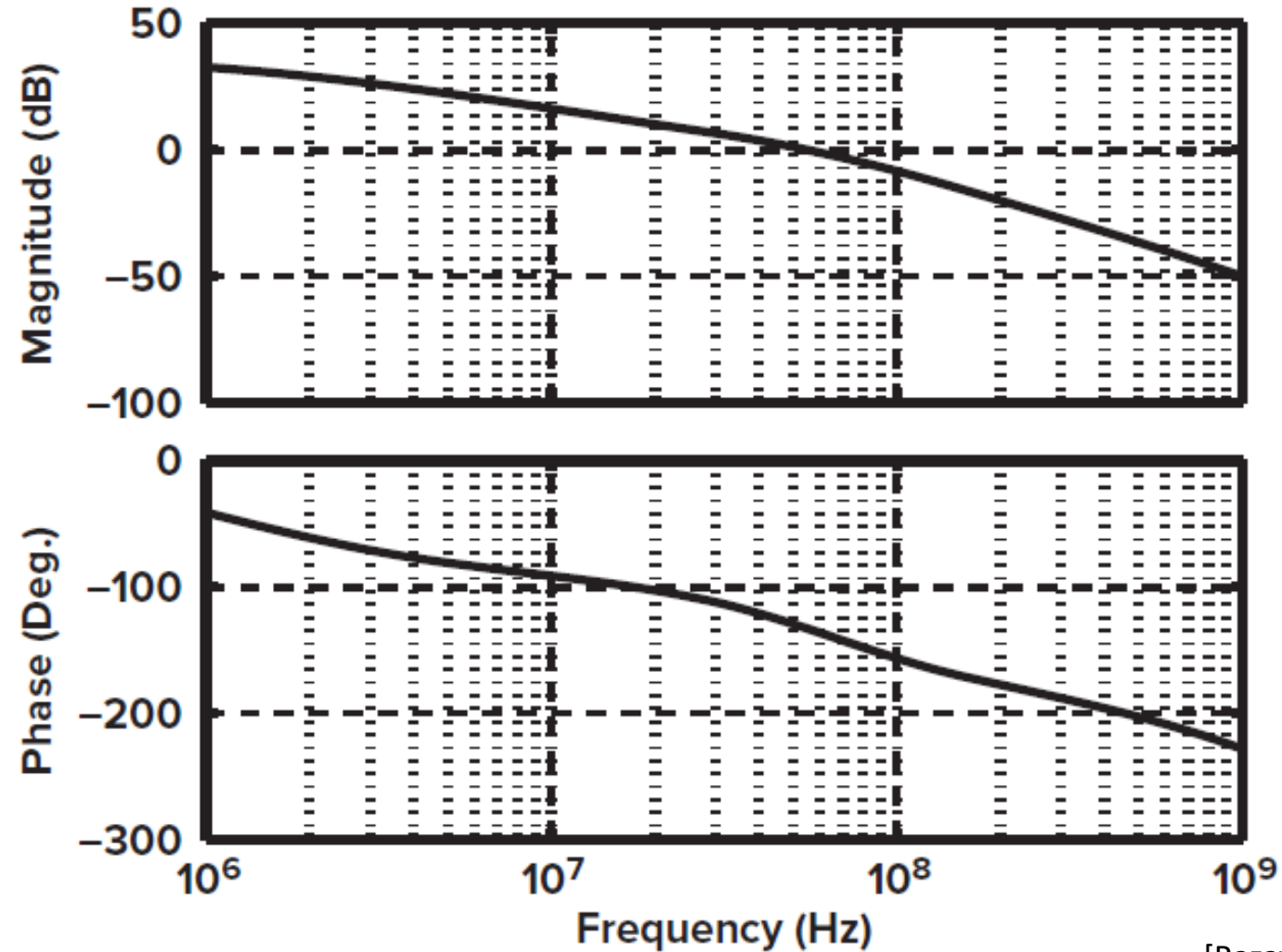


Stability Analysis: Step Response

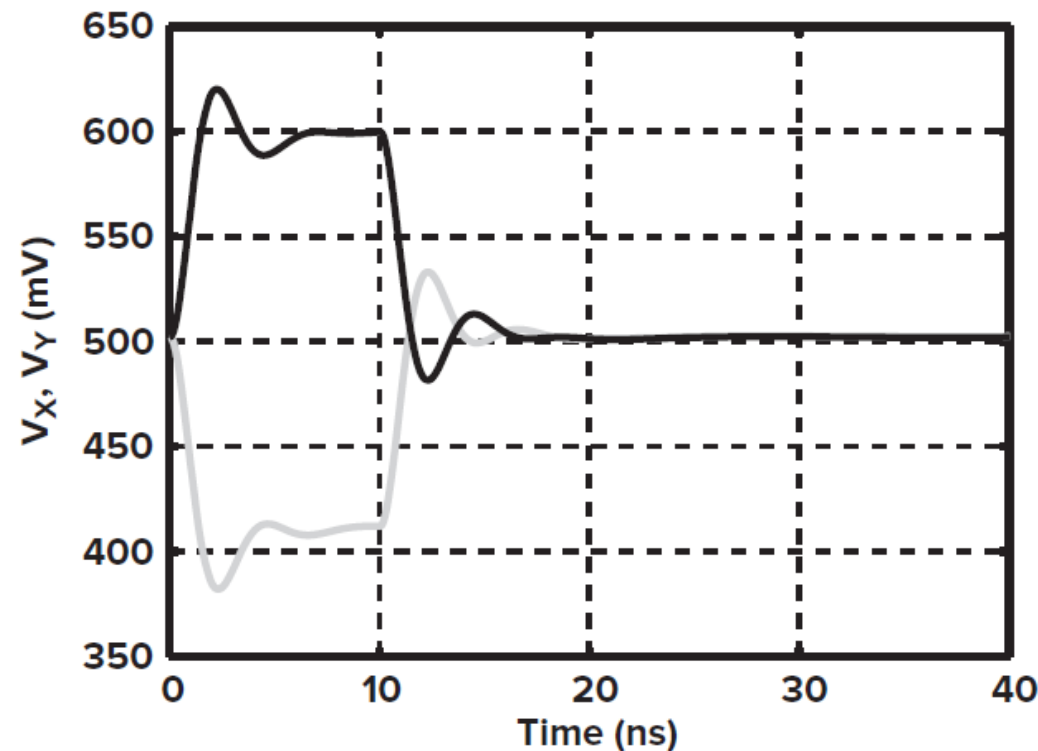- ❑ CMFB loop is stable
 - But the CMFB loop is not fast enough
- ❑ But there is differential ringing
 - The differential loop PM is not sufficient




Differential Loop Compensation

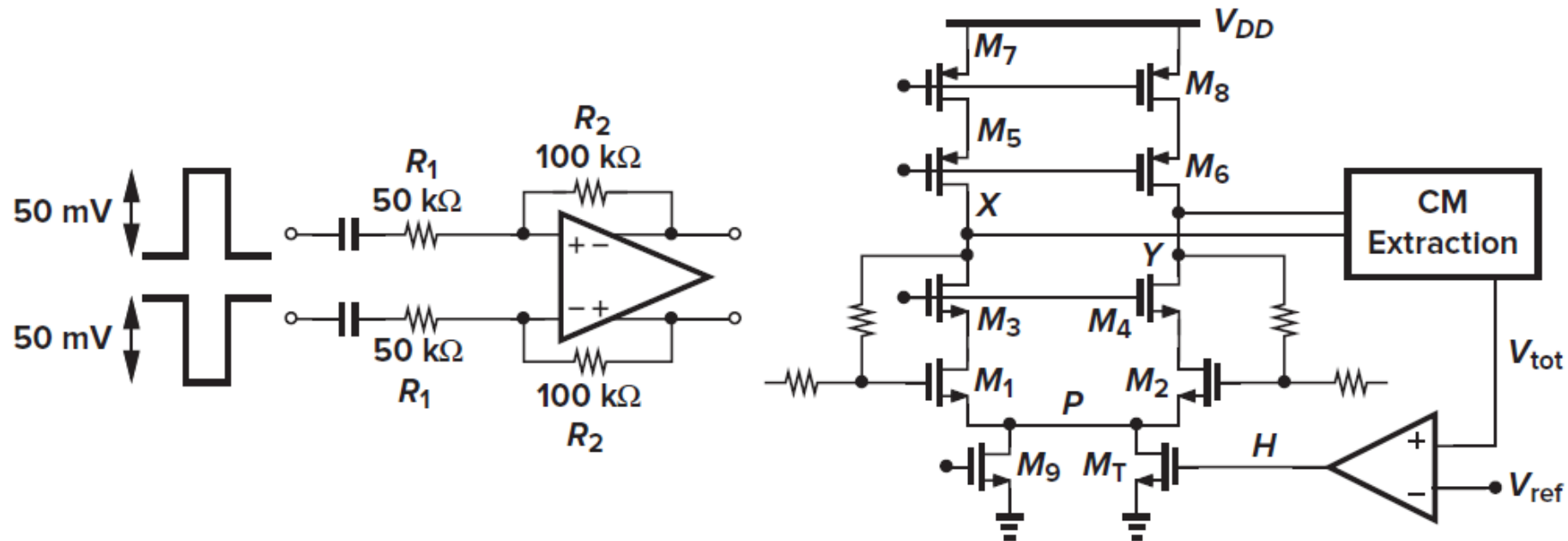- ❑ The feedback resistance and the OTA input cap add a pole
- ❑ Fixed by adding small cap parallel with the large feedback resistance
 - Usually required when using large feedback resistance



Stability Analysis: Step Response

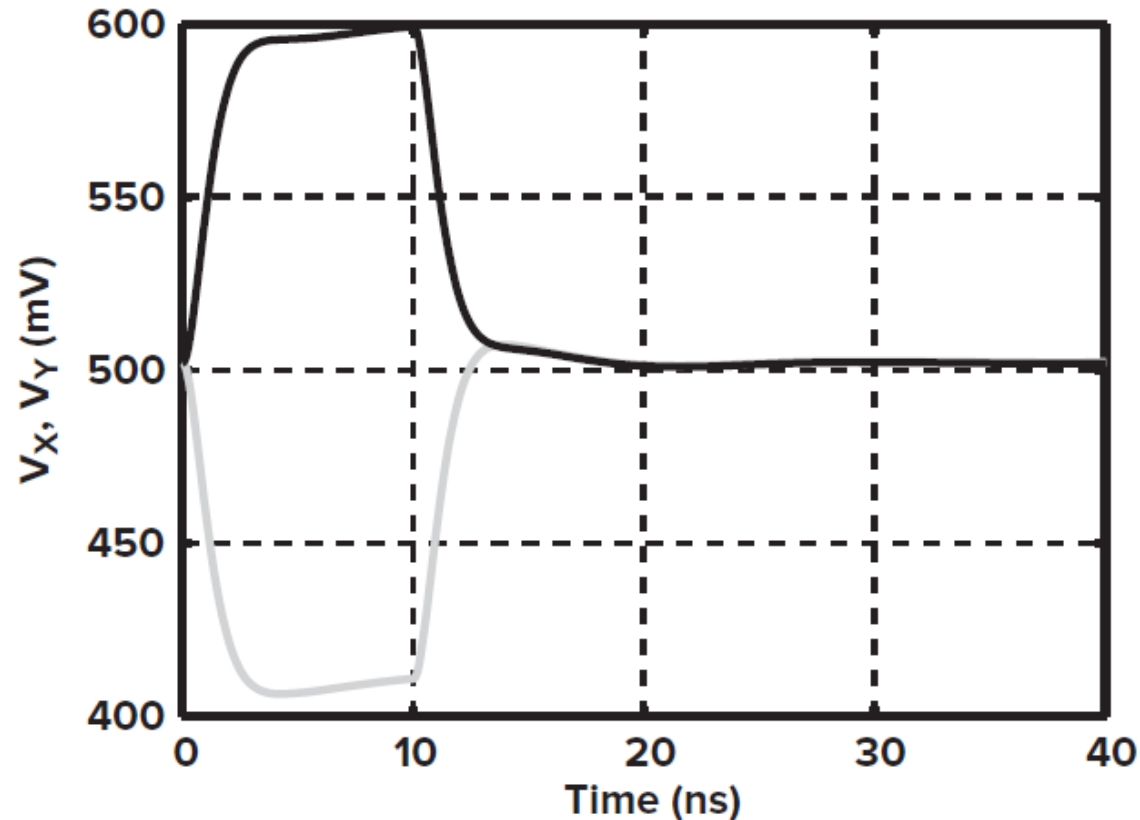- ❑ Differential ringing disappeared
 - But the CMFB loop is not fast enough



Thank you!

References

- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2nd ed., 2017.
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” 2nd ed., Wiley, 2012.
- ❑ B. Murmann, EE214 Course Reader, Stanford University.
- ❑ N. Krishnapura, EE539 Course Reader, IITM.