

# Analog IC Design

## Lecture 12 The Five-Transistor (5T) OTA

**Dr. Hesham A. Omran**

Integrated Circuits Laboratory (ICL)  
Electronics and Communications Eng. Dept.  
Faculty of Engineering  
Ain Shams University

# Outline

- ☐ Recapping previous key results
- ☐ Op-amp vs OTA
- ☐ Differential to single-ended conversion
- ☐ Five-transistor OTA Analysis
  - A. Small signal analysis
    - 1. Diff small signal analysis
    - 2. CM small signal analysis
  - B. Large signal analysis
    - 1. Diff large signal analysis
    - 2. CM large signal analysis
- ☐ Effect of mismatch
- ☐ 5T OTA frequency response

# Outline

- ❑ Recapping previous key results
- ❑ Op-amp vs OTA
- ❑ Differential to single-ended conversion
- ❑ Five-transistor OTA Analysis
  - A. Small signal analysis
    - 1. Diff small signal analysis
    - 2. CM small signal analysis
  - B. Large signal analysis
    - 1. Diff large signal analysis
    - 2. CM large signal analysis
- ❑ Effect of mismatch
- ❑ 5T OTA frequency response

# MOSFET in Saturation




- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \quad \text{OR} \quad V_{DS} \geq V_{ov}$$


- ❑ Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
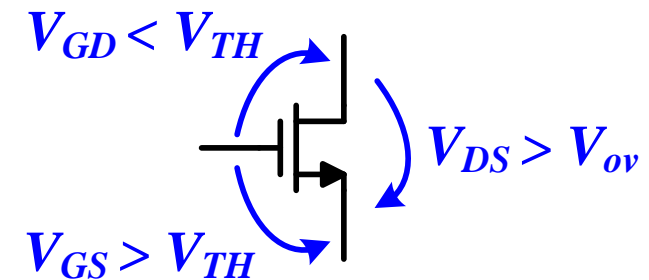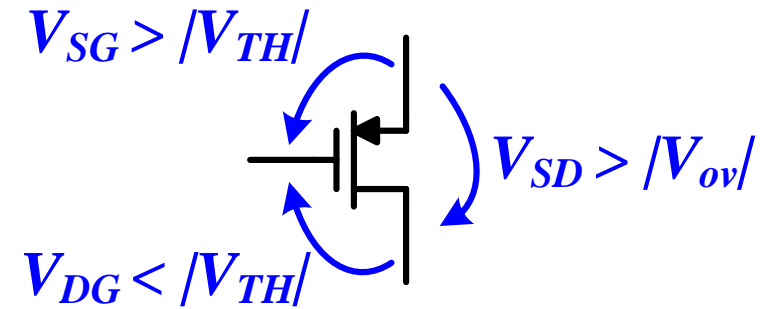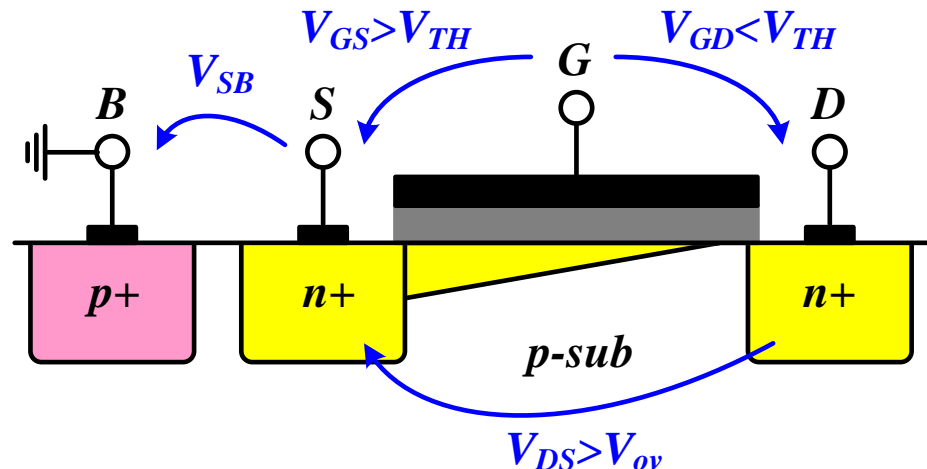
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$



# Regions of Operation Summary

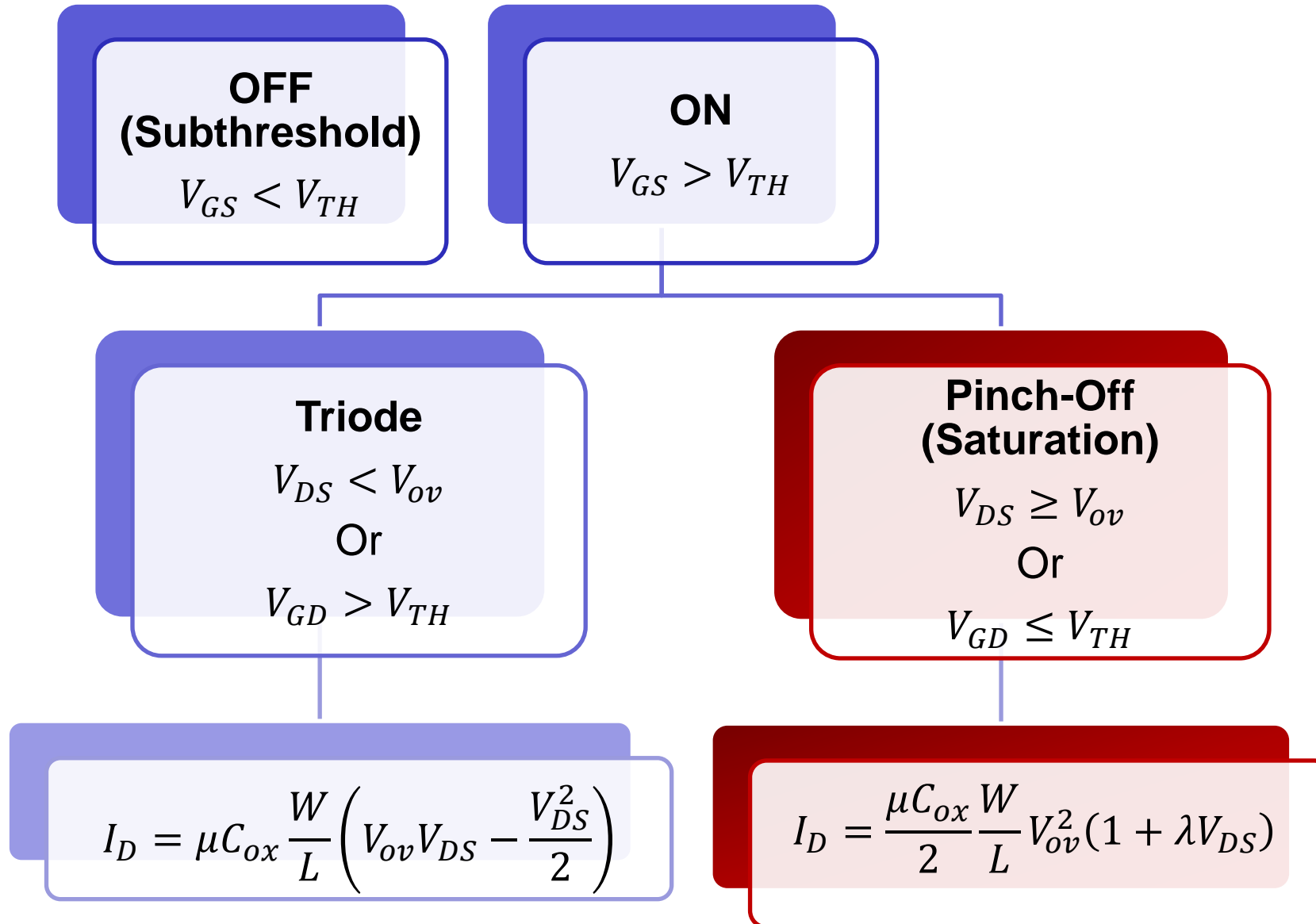

# High Frequency Small Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$


$$g_{mb} = \eta g_m \quad \eta \approx 0.1 - 0.25$$

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D} \quad V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L} \quad V_{DS} \uparrow V_A \uparrow$$


$$C_{gb} \approx 0$$

$$C_{gs} \gg C_{gd}$$




$$C_{sb} > C_{db}$$

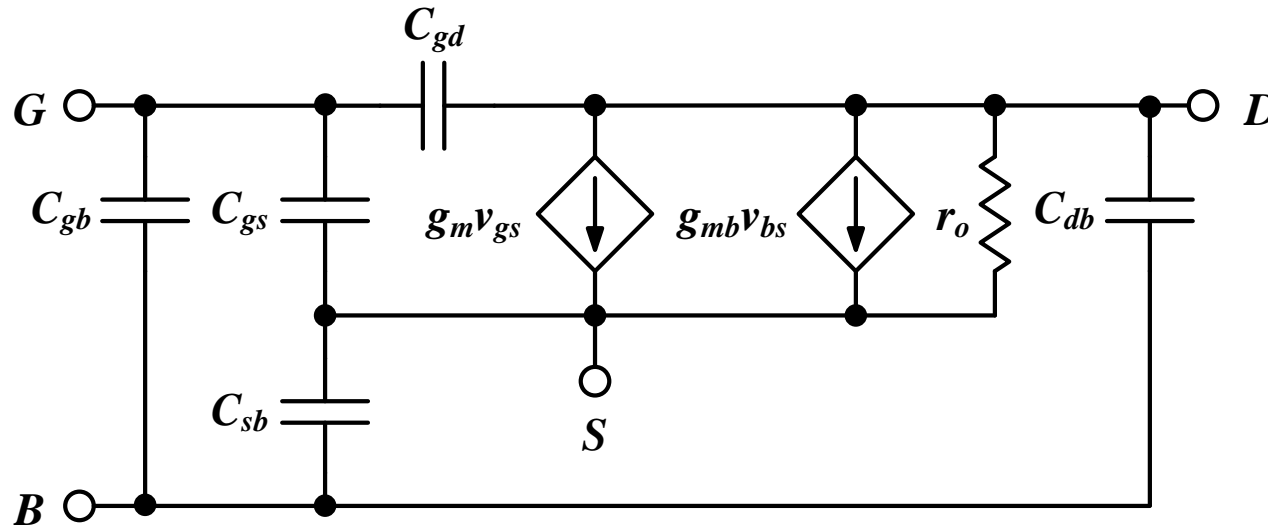

# Rin/out Shortcuts Summary

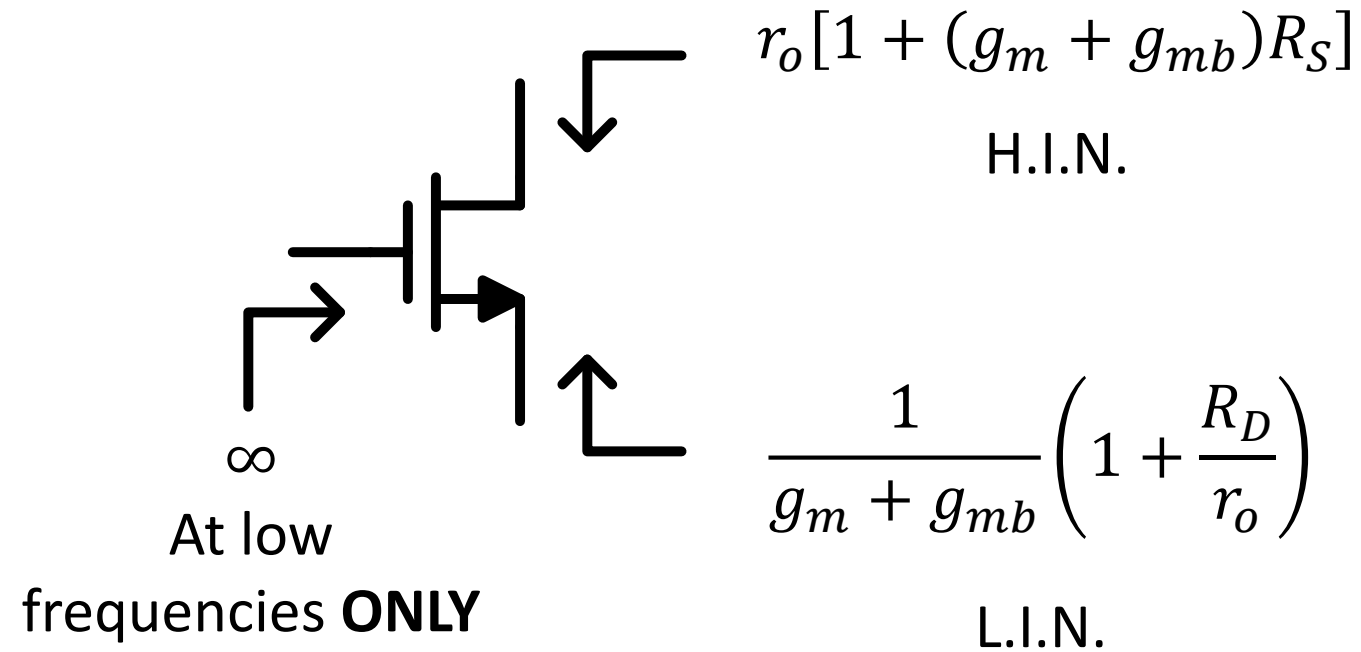

# Summary of Basic Topologies

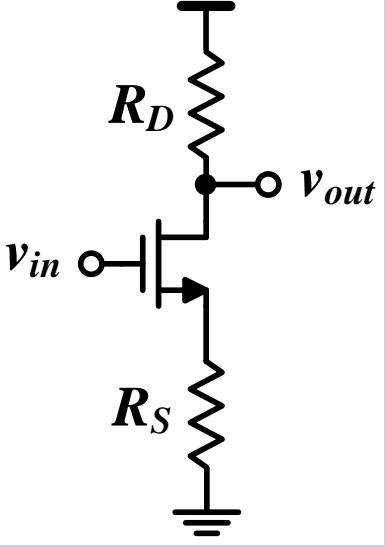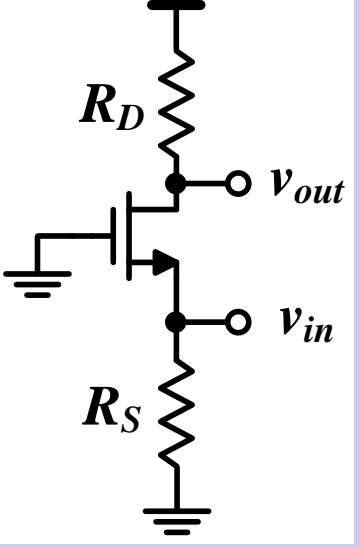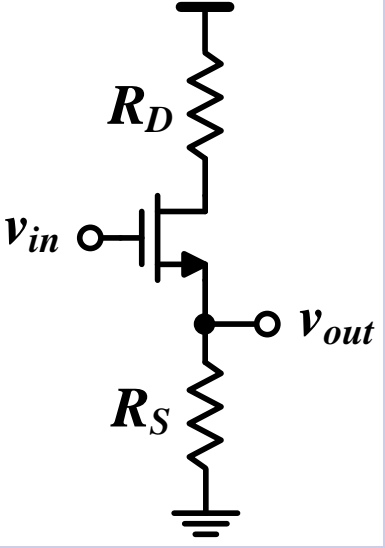	CS	CG	CD (SF)
			
	Voltage & current amplifier	Voltage amplifier Current buffer	Voltage buffer Current amplifier
<b>R<sub>in</sub></b>	$\infty$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$	$\infty$
<b>R<sub>out</sub></b>	$R_D \parallel r_o [1 + (g_m + g_{mb})R_S]$	$R_D \parallel r_o$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$
<b>G<sub>m</sub></b>	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$



# Differential Amplifier

	Pseudo Diff Amp	Diff Pair (w/ ideal CS)	Diff Pair (w/ $R_{SS}$ )
$A_{vd}$	$-g_m R_D$	$-g_m R_D$	$-g_m R_D$
$A_{vCM}$	$-g_m R_D$	0	$\frac{-g_m R_D}{1 + 2(g_m + g_{mb})R_{SS}}$
$A_{vd}/A_{vCM}$	1	$\infty$	$2(g_m + g_{mb})R_{SS} \gg 1$

$$A_{vCM2d} = \frac{v_{od}}{v_{iCM}} \approx \frac{\Delta R_D}{2R_{SS}} + \frac{\Delta g_m R_D}{2g_{m1,2}R_{SS}}$$



$$CMRR = \frac{A_{vd}}{A_{vCM2d}}$$

# Outline

- ☐ Recapping previous key results
- ☒ **Op-amp vs OTA**
- ☐ Differential to single-ended conversion
- ☐ Five-transistor OTA Analysis
  - A. Small signal analysis
    - 1. Diff small signal analysis
    - 2. CM small signal analysis
  - B. Large signal analysis
    - 1. Diff large signal analysis
    - 2. CM large signal analysis
- ☐ Effect of mismatch
- ☐ 5T OTA frequency response

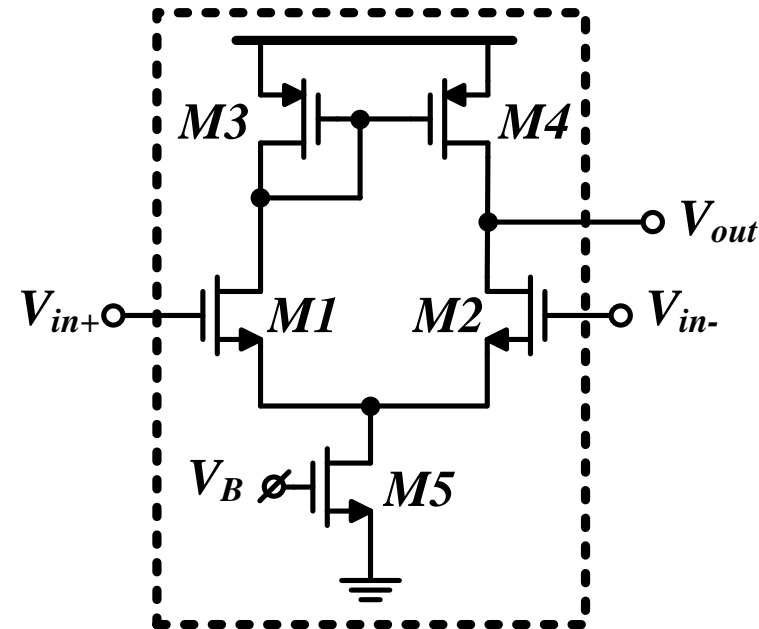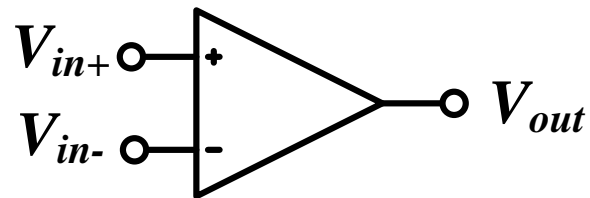
# Op-Amp

- ❑ An op-amp is simply a high gain differential amplifier
  - The gain can be increased by using cascodes and multi-stage amplification
- ❑ The diff amp is a key block in many analog and RF circuits
  - DEEP understanding of diff amp is ESSENTIAL








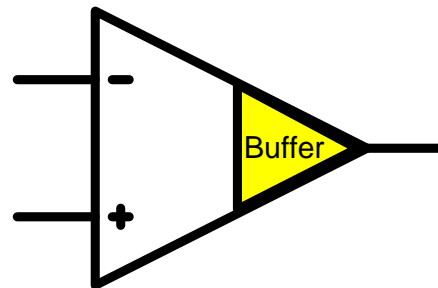
# Op-Amp vs OTA

- ❑ Ideal op-amp has infinite  $R_{in}$ , infinite gain, and zero  $R_{out}$
- ❑ Practical op-amp has HIGH  $R_{in}$ , HIGH gain, and LOW  $R_{out}$ 
  - LOW  $R_{out}$  required to avoid loading when driving resistive loads
  - The op-amp is usually implemented as a multistage amplifier
  - The last stage (output stage) is a buffer to provide LOW  $R_{out}$
- ❑ IC CMOS op-amps usually drive capacitive loads
  - Usually, there is no need for LOW  $R_{out}$
  - The output stage (buffer) is not required
  - These modern integrated op-amps are usually called Operational Transconductance Amplifiers (OTAs)



# Op-Amp vs OTA

- ❑ In short, an OTA is an op-amp without an output stage (buffer)
- ❑ Some designers just use op-amp name and symbol for both

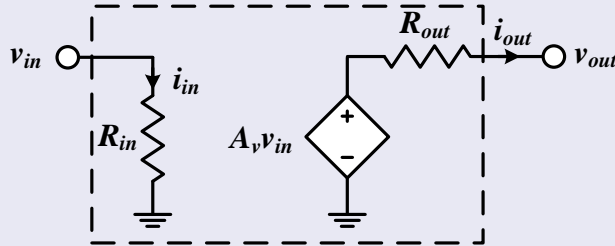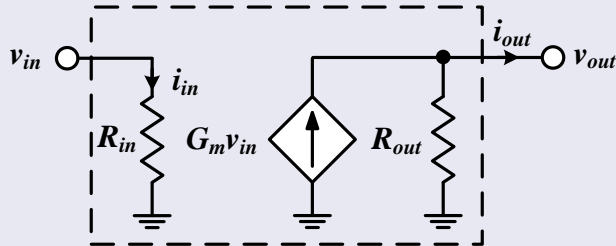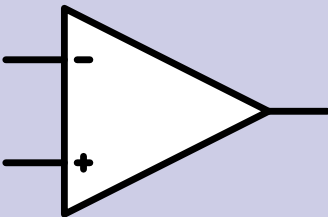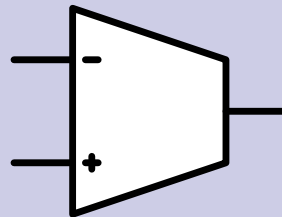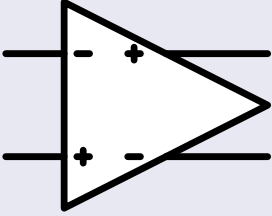
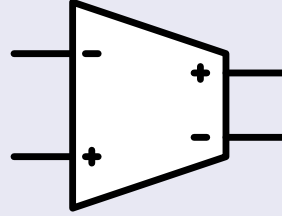
	Op-amp	OTA
Rout	LOW	HIGH
Model		
Diff input, SE output		
Fully diff		

# Outline

- ☐ Recapping previous key results
- ☐ Op-amp vs OTA
- ☐ Differential to single-ended conversion
- ☐ Five-transistor OTA Analysis
  - A. Small signal analysis
    - 1. Diff small signal analysis
    - 2. CM small signal analysis
  - B. Large signal analysis
    - 1. Diff large signal analysis
    - 2. CM large signal analysis
- ☐ Effect of mismatch
- ☐ 5T OTA frequency response

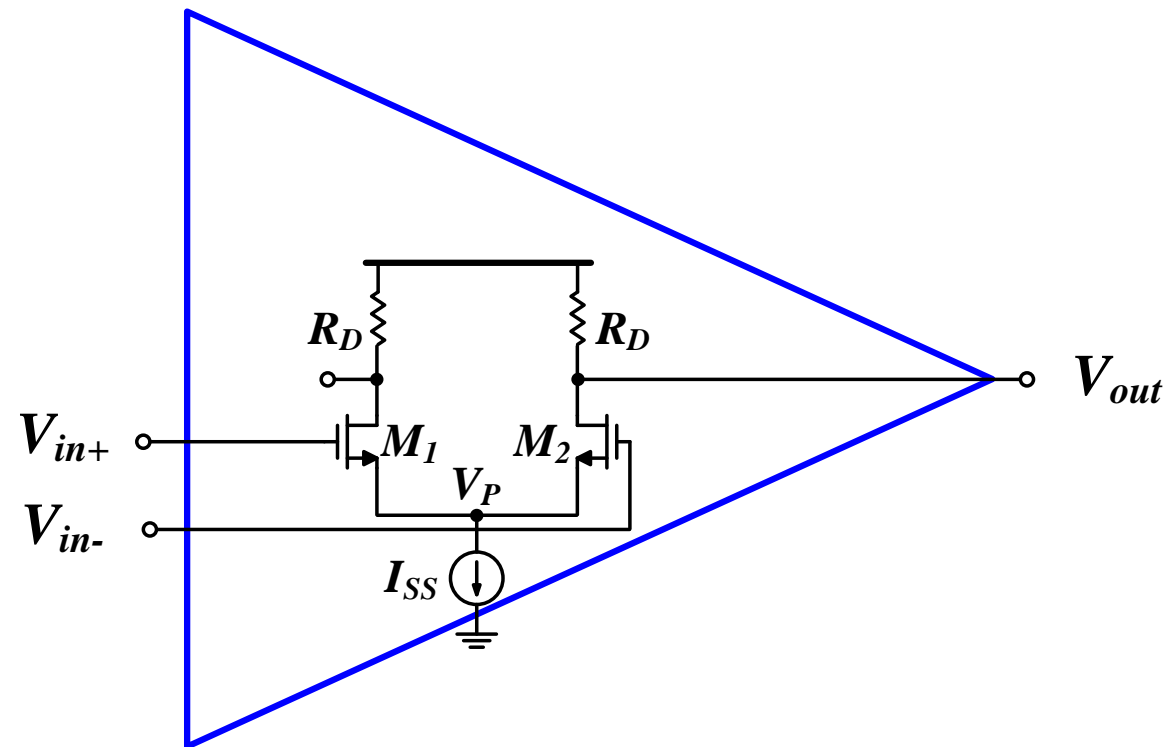
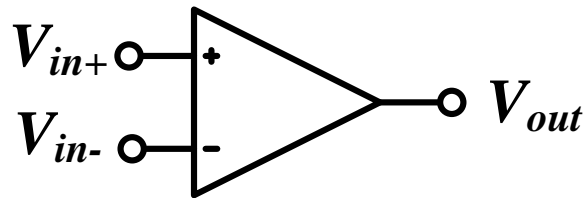
# How to Get SE Output?

- ❑ Trivial solution: discard one output!
  - But the gain is halved (and the CMRR is poor  $\sim g_m R_{SS}$ )
- ❑ Better solution: use a diff to single-ended (SE) converter (but how?!)


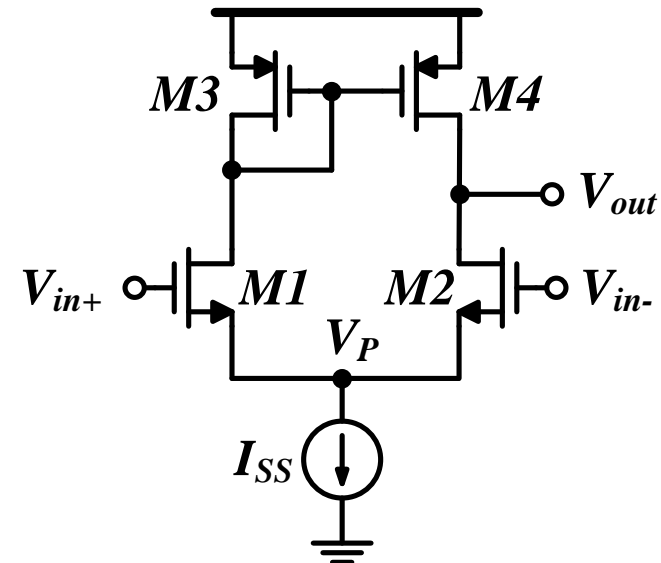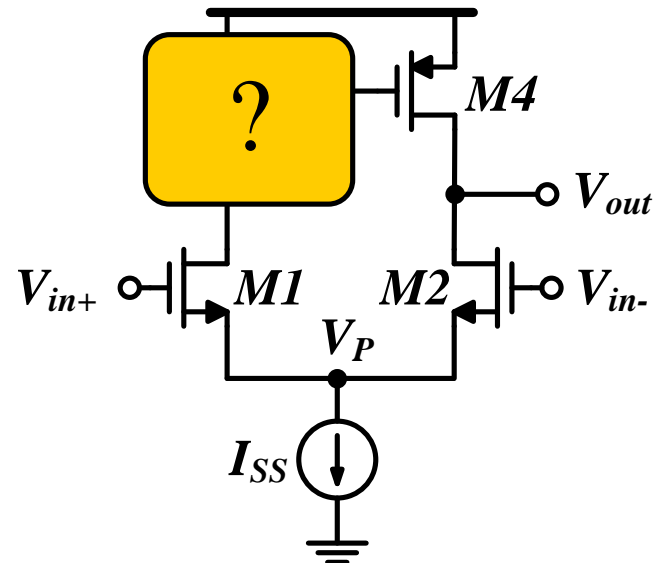
# 5T OTA

- ❑ A.k.a. diff pair with active load, diff pair with CM load, unbalanced diff pair.
- ❑ Can be viewed in two ways
  1. We use a current mirror to transfer the small signal current from the left side to the right side.
  2. M3 is a diode-connected load and M4 is a CS amplifier that transfers the small signal voltage from the left side to the right side.





# Outline

- ☐ Recapping previous key results
- ☐ Op-amp vs OTA
- ☐ Differential to single-ended conversion
- ☐ Five-transistor OTA Analysis
  - A. Small signal analysis
    1. Diff small signal analysis
    2. CM small signal analysis
  - B. Large signal analysis
    1. Diff large signal analysis
    2. CM large signal analysis
- ☐ Effect of mismatch
- ☐ 5T OTA frequency response

# 5T OTA Analysis

❑ In general, half-circuit principle cannot be used due to asymmetry


❑ Similar to diff amp, we carry four types of analysis:

A. Small signal analysis

1. Diff small signal analysis
2. CM small signal analysis

B. Large signal analysis

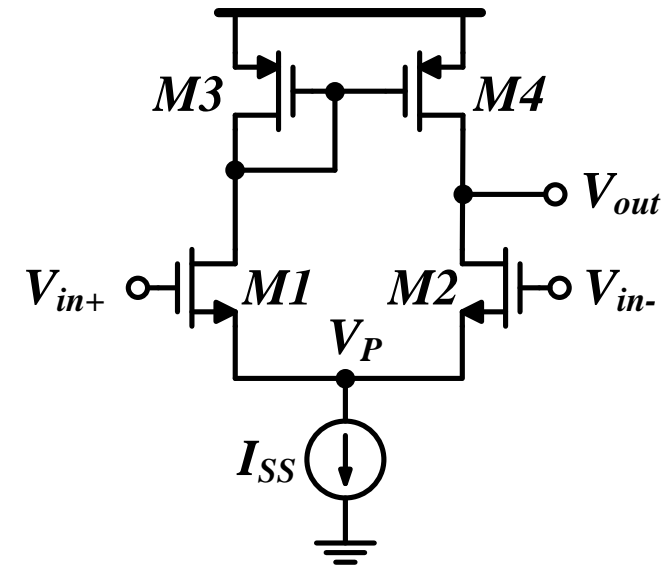1. Diff large signal analysis
2. CM large signal analysis





# A1. Diff Small Signal Analysis

- ❑ Solve it using superposition as a whole using GmRout (Can we use half-circuit? Why?)
- ❑ Each side contributes to  $i_{out}$  twice: directly and through the mirror

$$i_{out} = i'_{out} + i''_{out}$$

$$i_{out} \approx \frac{g_{m1}}{1 + g_{m1}(1/g_{m2})} \cdot \mathbf{2} \cdot \frac{v_{id}}{2} + \frac{g_{m2}}{1 + g_{m2}(1/g_{m1})} \cdot \mathbf{2} \cdot \frac{v_{id}}{2}$$
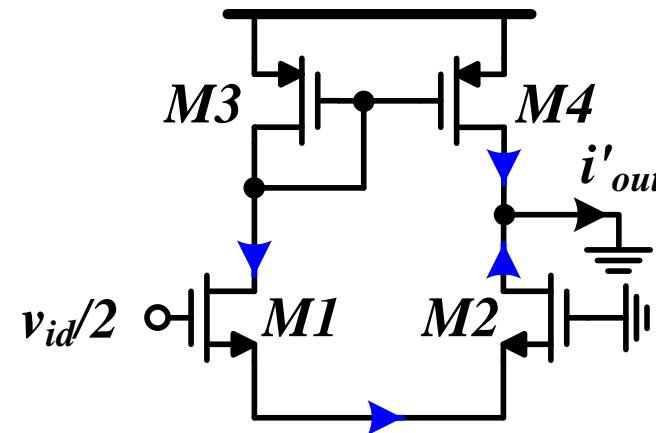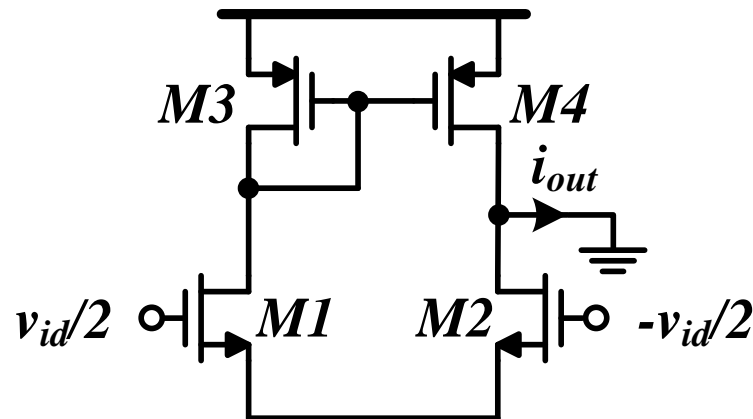
$$G_m = \frac{i_{out}}{v_{id}} \approx g_{m1,2}$$



# A1. Diff Small Signal Analysis


□ Can we use half-circuit? Why?

$$R_{out} = \frac{v_x}{i_x} = \frac{v_x}{2i_y} || r_{o4}$$

$$\frac{v_x}{i_y} = R_{LFD,M2} \approx r_{o2}(1 + g_{m2}R_{LFS,M1}) \approx 2r_{o2}$$

$$R_{out} \approx r_{o2} || r_{o4}$$



$$A_{vd} = \frac{v_{out}}{v_{id}} \approx g_{m1,2}(r_{o2} || r_{o4})$$

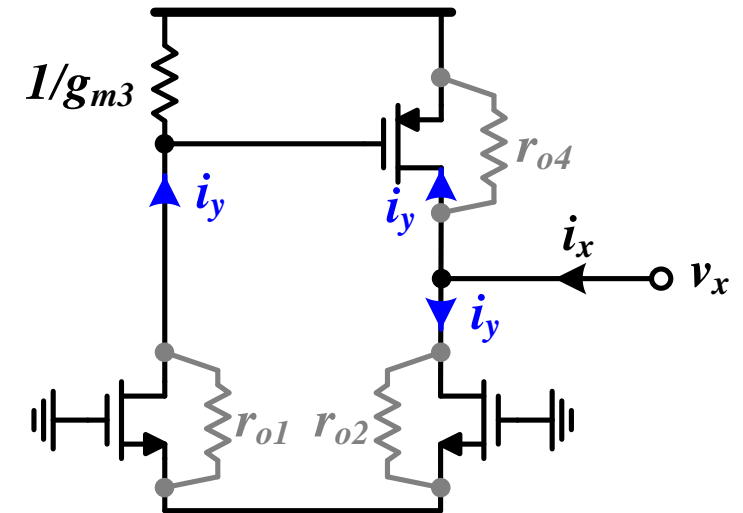
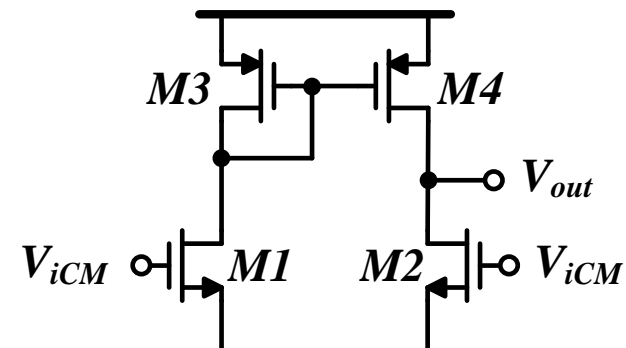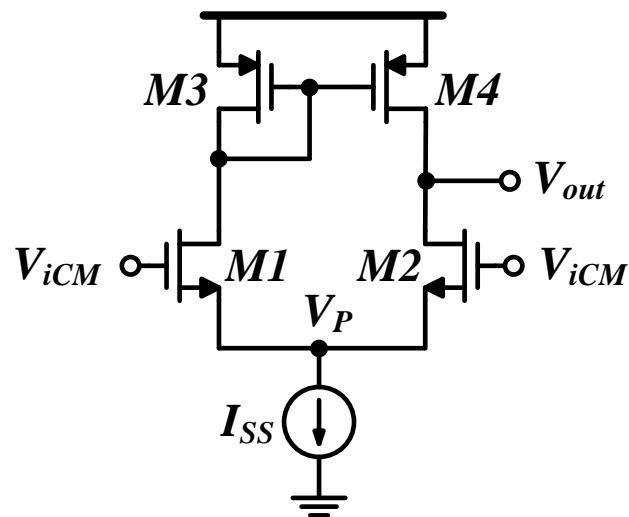
## A2. CM Small Signal Analysis

- If the tail CS is ideal
  - The two sides will generate current in the same direction
  - Thus both currents must be zero

$$v_{out} = 0 \Rightarrow A_{vCM} = \frac{v_{out}}{v_{iCM}} = 0 \Rightarrow CMRR = \frac{A_{vd}}{A_{vCM}} \rightarrow \infty$$




# A2. CM Small Signal Analysis

- ❑ For non-ideal tail CS:  $A_{vCM} \neq 0$  and  $CMRR \neq \infty$
- ❑ The presence of  $R_{SS}$  complicates the analysis. Using SLiCAP yields:

$$H_s = - \frac{1.0 g_{m12} r_{o12} r_{o34}}{2.0 R_{SS} + r_{o12} + r_{o34} + 2.0 R_{SS} g_{m12} r_{o12} + 2.0 R_{SS} g_{m34} r_{o34} + g_{m34} r_{o12} r_{o34} + 2.0 R_{SS} g_{m12} g_{m34} r_{o12} r_{o34}}$$



$$A_{vCM} \approx - \frac{1}{2 g_{m3,4} R_{SS}}$$

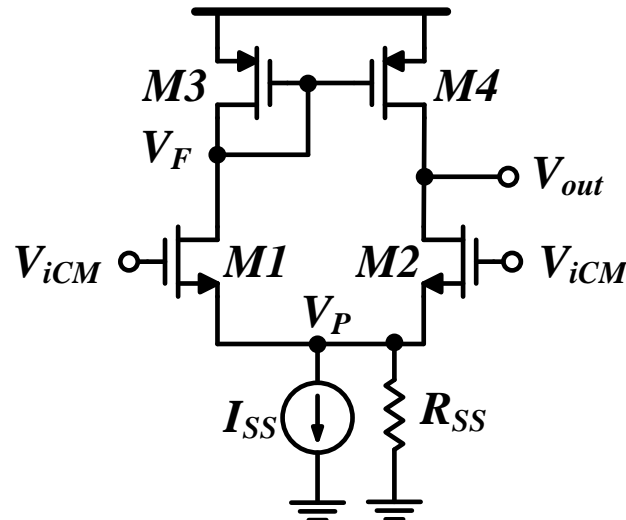- ❑ Can we derive the same result intuitively?


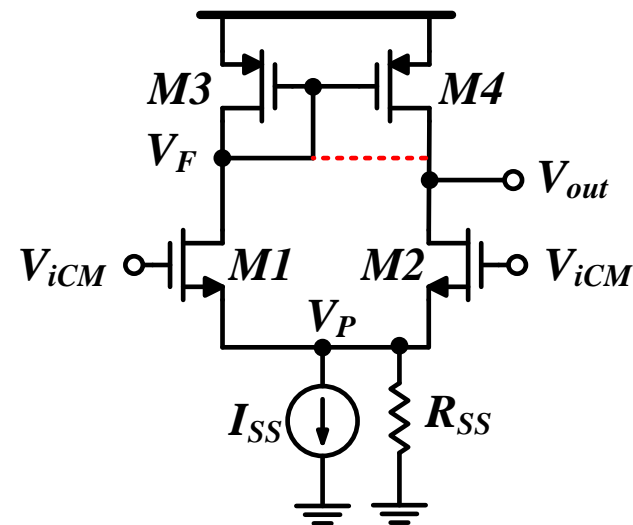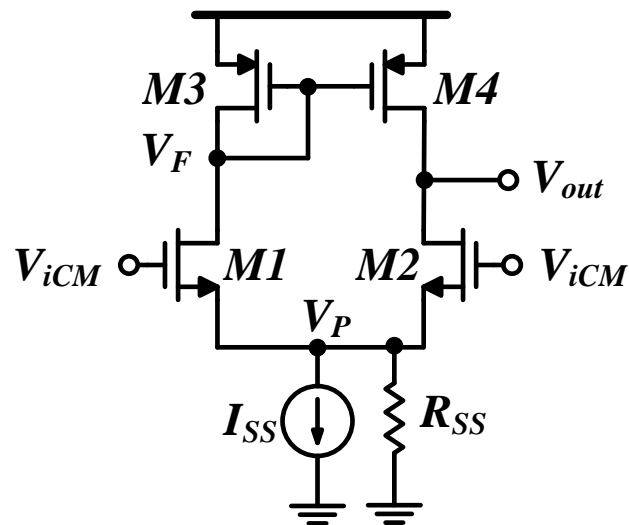
## A2. CM Small Signal Analysis

- ❑ M1 and M2 have the same  $V_{GS}$ : Difference in  $I_D$  depends on  $V_{DS}$
- ❑ M3 and M4 have the same  $V_{GS}$ : Difference in  $I_D$  depends on  $V_{DS}$
- ❑ Assume  $V_F < V_{out}$ 
  - $I_{D1} < I_{D2}$  and  $I_{D3} > I_{D4} \rightarrow$  Not a valid assumption
- ❑ Assume  $V_F > V_{out}$ 
  - $I_{D1} > I_{D2}$  and  $I_{D3} < I_{D4} \rightarrow$  Not a valid assumption
- ❑ The only valid assumption is  $V_F = V_{out} \rightarrow$  As if there is a s.c.!




## A2. CM Small Signal Analysis

- ❑ For CM input,  $V_{out}$  follows  $V_F \rightarrow$  As if there is a s.c. between them
- ❑ The circuit becomes symmetric  $\rightarrow$  Apply half circuit principle

$$A_{vCM} = \frac{V_{out}}{V_{iCM}} = G_m R_{out} \approx \frac{-g_{m1,2}}{1 + 2g_{m1,2}R_{SS}} \frac{1}{g_{m3,4}} \approx -\frac{1}{2g_{m3,4}R_{SS}}$$

- ❑ Same as SLiCAP's result 😊


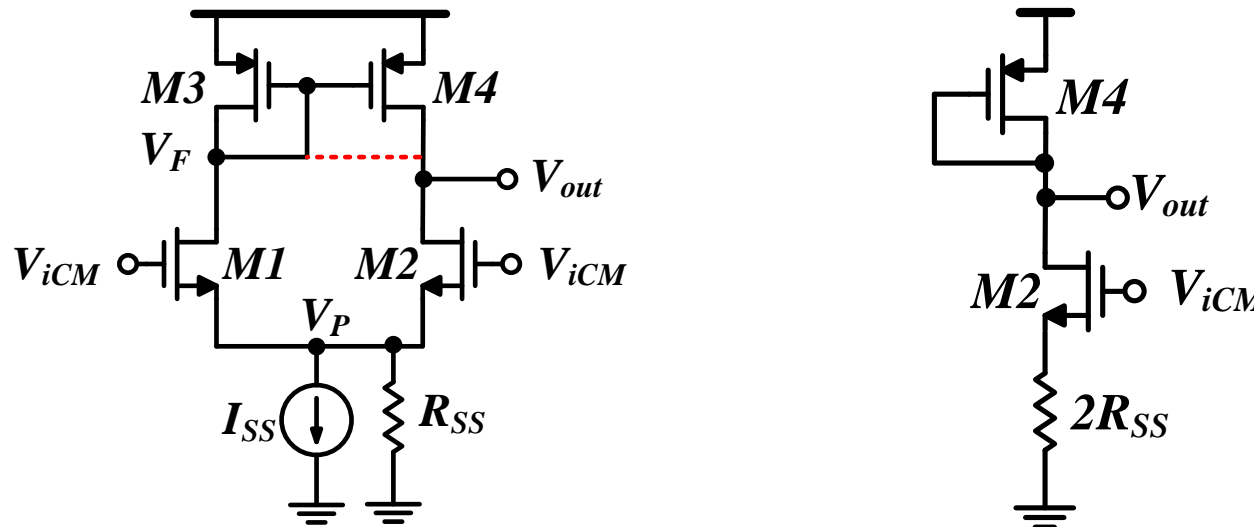



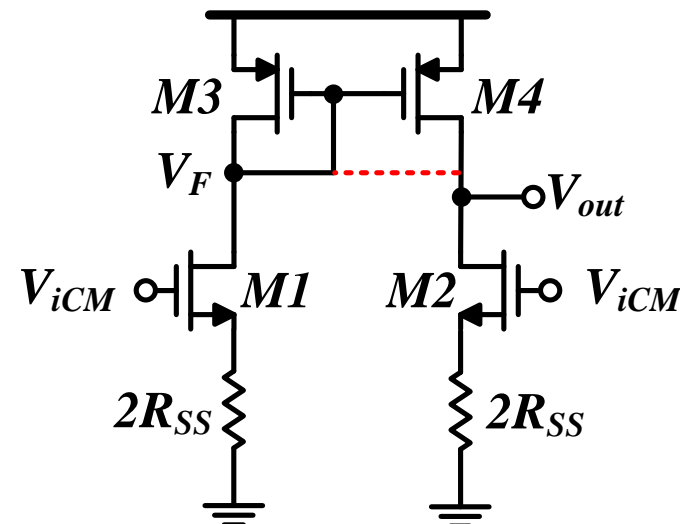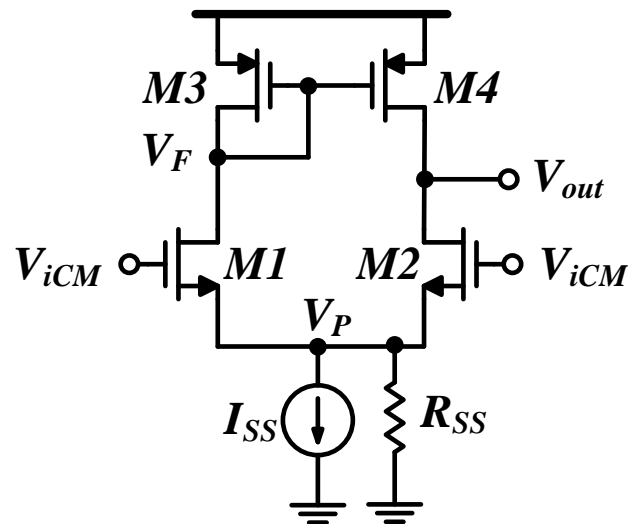
# A2. CM Small Signal Analysis

- ❑ **Method #2:** Ignore  $r_{o1,2}$  for simplicity (CLM of M1,2 ignored)  $\rightarrow$  apply half-circuit at the sources
- ❑ M1 and M2 generate the same current ( $\Delta i_d$ )  $\rightarrow \therefore$  M3 and M4 have the same current  $\rightarrow \therefore$  Not just their  $V_{GS}$  is equal, but their  $V_{DS}$  must be equal  $\rightarrow \therefore V_{out} = V_F$
- ❑ s.c. between  $V_{out}$  and  $V_F \rightarrow$  apply half-circuit at the drains

$$A_{vCM} = \frac{V_{out}}{V_{iCM}} = G_m R_{out} \approx \frac{-g_{m1,2}}{1 + 2g_{m1,2}R_{SS}} \frac{1}{g_{m3,4}} \approx -\frac{1}{2g_{m3,4}R_{SS}}$$



## A2. CM Small Signal Analysis



- Strictly speaking,  $R_{out}$  for diff and cm must be the same!
  - $R_{out}$  is independent of input type and location (we already deactivate the input when we calculate  $R_{out}$ )

$$R_{out} \approx r_{o2} || r_{o4}$$

- It can be shown that  $G_m$  is actually given by

$$G_m \approx \frac{-g_{m1,2}}{1 + 2g_{m1,2}R_{SS}} \frac{1}{g_{m3,4}(r_{o2} || r_{o4})} \approx -\frac{1}{2g_{m3,4}R_{SS}(r_{o2} || r_{o4})}$$

- An intuitive derivation is not very easy.


$$A_{vCM} = \frac{V_{out}}{V_{iCM}} = G_m R_{out} \approx -\frac{1}{2g_{m3,4}R_{SS}}$$

## A2. CM Small Signal Analysis



❑ **Method #3:** Use GmRout (Neglect  $r_{o1,2}$  BUT do NOT neglect  $r_{o3}$ , otherwise  $A_{vCM} \rightarrow 0$ )

$$\begin{aligned} G_m &= \frac{i_{o,sc}}{v_{iCM}} = \frac{g_{m1}}{1 + 2g_{m1}R_{SS}} \cdot \left( \frac{1}{g_{m3}} || r_{o3} \right) \cdot g_{m4} - \frac{g_{m2}}{1 + 2g_{m2}R_{SS}} \\ &= \frac{g_{m1,2}}{1 + 2g_{m1,2}R_{SS}} \left( \frac{g_{m3,4}r_{o3,4}}{1 + g_{m3,4}r_{o3,4}} - 1 \right) \approx \frac{-1}{2g_{m3,4}r_{o3,4}R_{SS}} \\ A_{vCM} &= G_m R_{out} \approx \frac{-1}{2g_{m3,4}r_{o3,4}R_{SS}} \cdot r_{o4} = -\frac{1}{2g_{m3,4}R_{SS}} \end{aligned}$$

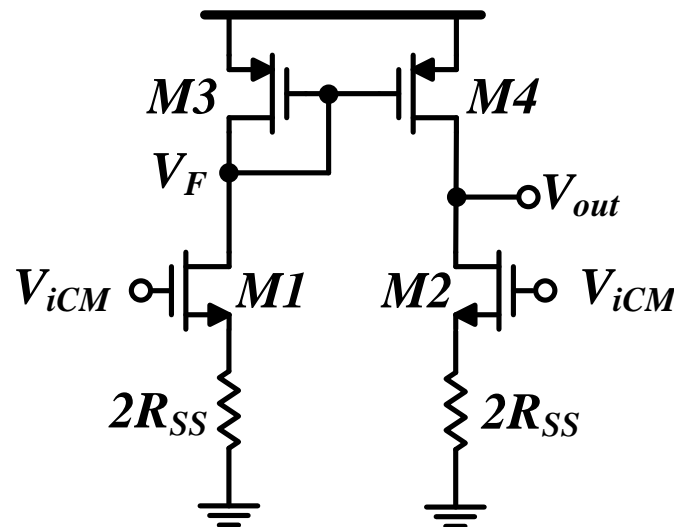

# CMRR

$$A_{vd} = \frac{V_{out}}{V_{id}} \approx g_{m1,2}(r_{o2} // r_{o4})$$

$$A_{vCM} = \frac{V_{out}}{V_{iCM}} \approx -\frac{1}{2g_{m3,4}R_{SS}}$$

$$CMRR \approx g_{m1,2}(r_{o2} // r_{o4}) \cdot 2g_{m3,4}R_{SS} \sim (g_m r_o)^2$$



- ❑ The CMRR is much better than the trivial case of getting SE output by dropping one differential output
  - For the trivial case  $CMRR \approx g_m R_{SS} \sim g_m r_o$
- ❑ CM noise will affect the SE output even in the case of perfect symmetry
  - A clear disadvantage compared to fully diff OTA
- ❑ The effective  $R_{SS}$  degrades at high frequency

# Outline

- ☐ Recapping previous key results
- ☐ Op-amp vs OTA
- ☐ Differential to single-ended conversion
- ☐ **Five-transistor OTA Analysis**
  - A. Small signal analysis
    1. Diff small signal analysis
    2. CM small signal analysis
  - B. Large signal analysis**
    1. Diff large signal analysis
    2. CM large signal analysis
- ☐ Effect of mismatch
- ☐ 5T OTA frequency response

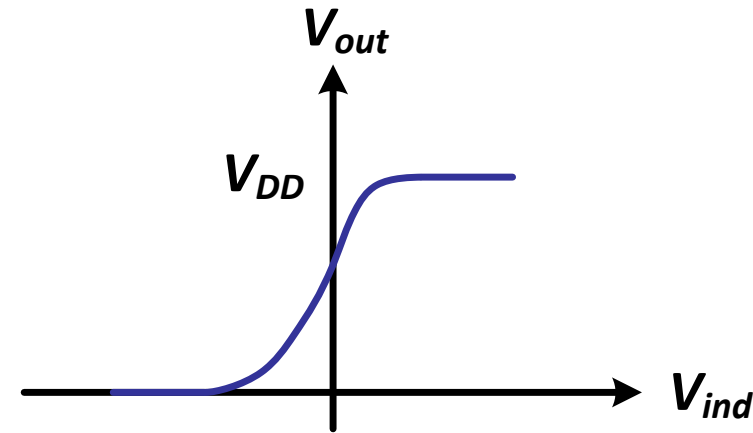
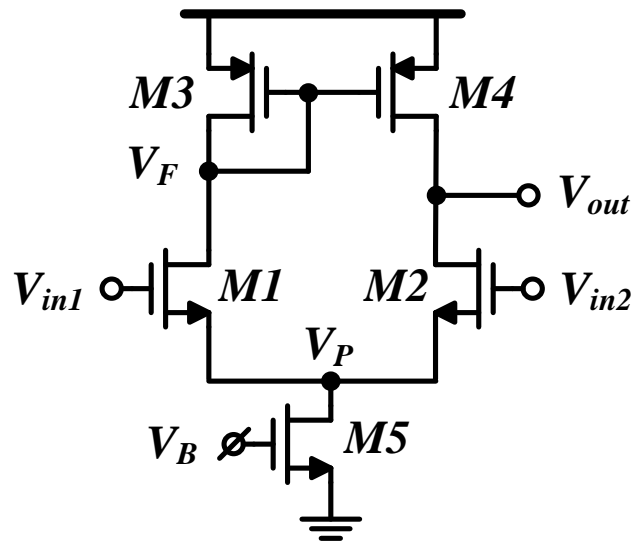
# B1. Diff Large Signal Analysis

- $V_{id} = (V_{in1} - V_{in2}) \gg 0$ 
  - M1 and M3 ON  $\rightarrow$  M4 ON (triode)  $\rightarrow$  small resistance
  - M2 OFF  $\rightarrow$  large resistance
  - $V_{out} \approx V_{DD}$



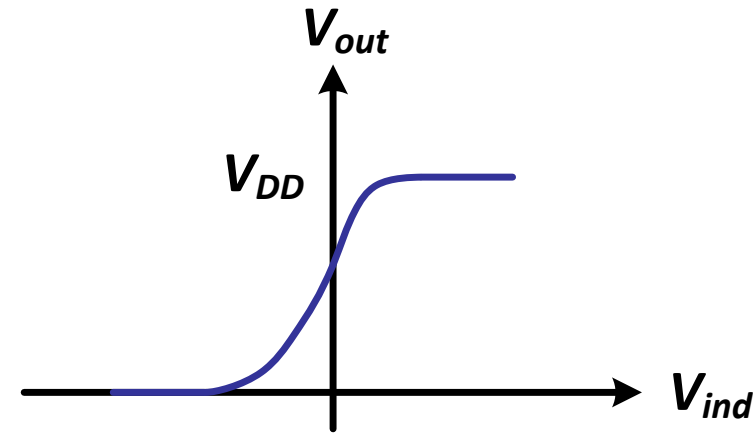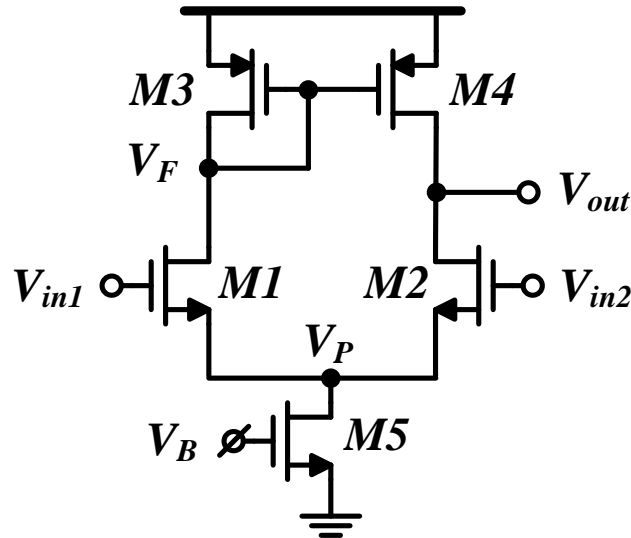
# B1. Diff Large Signal Analysis

- $V_{id} = (V_{in1} - V_{in2}) \ll 0$ 
  - M1 and M3 OFF  $\rightarrow$  M4 OFF  $\rightarrow$  large resistance
  - M2 and M5 ON (triode)  $\rightarrow$  small resistance
  - $V_{out} \approx 0$



## B2. CM Large Signal Analysis

- All transistors must be in saturation

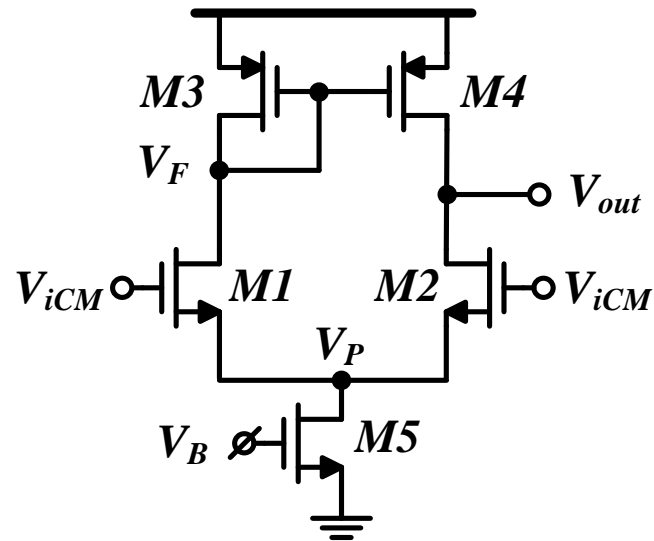

- Tail CS in sat

$$V_{iCM} \geq V_{THN} + V_{ov1} + V_{ov5}$$

- Input pair in sat

$$V_{iCM} \leq V_{DD} - |V_{THP}| - |V_{ov3}| + V_{THN}$$



# Outline


- ❑ Recapping previous key results
- ❑ Op-amp vs OTA
- ❑ Differential to single-ended conversion
- ❑ Five-transistor OTA Analysis
  - A. Small signal analysis
    - 1. Diff small signal analysis
    - 2. CM small signal analysis
  - B. Large signal analysis
    - 1. Diff large signal analysis
    - 2. CM large signal analysis
- ❑ Effect of mismatch
- ❑ 5T OTA frequency response

# Effect of Mismatch (in Input Pair)

□ Use superposition (left + right)

$$A_{vCM} = \frac{v'_{out}}{v_{iCM}} + \frac{v''_{out}}{v_{iCM}} \approx \left( \frac{2g_{m1}}{1 + g_{m1} \left( \frac{1}{g_{m2}} \parallel R_{SS} \right)} - \frac{2g_{m2}}{1 + g_{m2} \left( \frac{1}{g_{m1}} \parallel R_{SS} \right)} \right) R_{out}$$
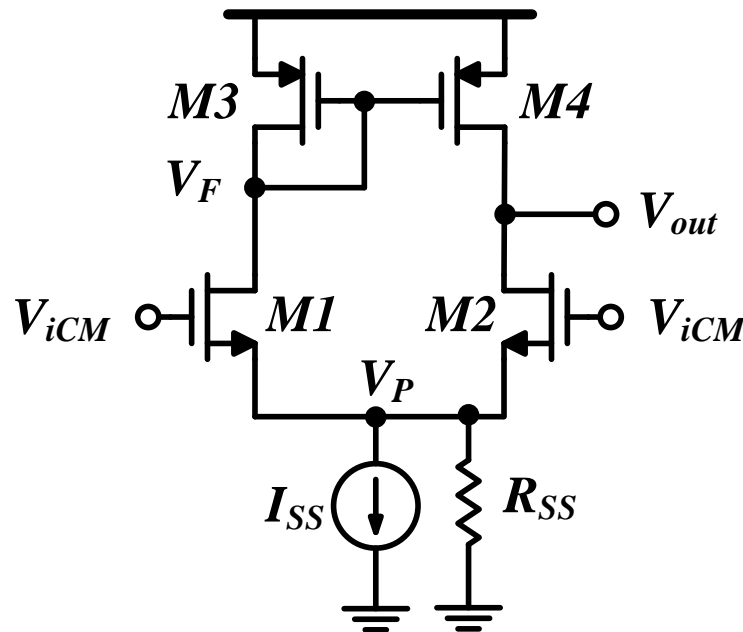
$$= \frac{2\Delta g_m R_{out}}{1 + (g_{m1} + g_{m2})R_{SS}} \approx \frac{\Delta g_m R_{out}}{g_{m1,2} R_{SS}}$$



# CMRR with Mismatch

- Overall CM small signal response (matched + mismatch)

$$A_{vCM} \approx \frac{-\frac{g_{m1,2}}{g_{m3,4}}}{1 + 2g_{m1,2}R_{SS}} + \frac{2\Delta g_m R_{out}}{1 + 2g_{m1,2}R_{SS}} \approx \frac{-\frac{g_{m1,2}}{g_{m3,4}} + 2\Delta g_m R_{out}}{2g_{m1,2}R_{SS}}$$

- Common-mode rejection ratio (CMRR) (@low frequency!)

$$A_{vd} = g_{m1,2}R_{out}$$

$$CMRR = \frac{A_{vd}}{A_{vCM}} \approx \frac{2g_{m1,2}R_{SS}}{-\frac{1}{g_{m3,4}R_{out}} + 2\frac{\Delta g_m}{g_{m1,2}}}$$

# Outline

- ☐ Recapping previous key results
- ☐ Op-amp vs OTA
- ☐ Differential to single-ended conversion
- ☐ Five-transistor OTA Analysis
  - A. Small signal analysis
    - 1. Diff small signal analysis
    - 2. CM small signal analysis
  - B. Large signal analysis
    - 1. Diff large signal analysis
    - 2. CM large signal analysis
- ☐ Effect of mismatch
- ☐ 5T OTA frequency response

# Differential Frequency Response: Poles


□ Output pole:  $C_{out} \approx C_{db4} + C_{db2} + f(C_{gd4}) + C_{gd2} + C_L$

$$\omega_{p1} \approx \frac{1}{R_{out} C_{out}}$$

□ Mirror pole:  $C_{mirr} \approx C_{gs3} + C_{gs4} + C_{db3} + C_{db1} + C_{gd1} + f(C_{gd4})$

$$\omega_{p2} \approx \frac{g_{m3}}{C_{mirr}}$$

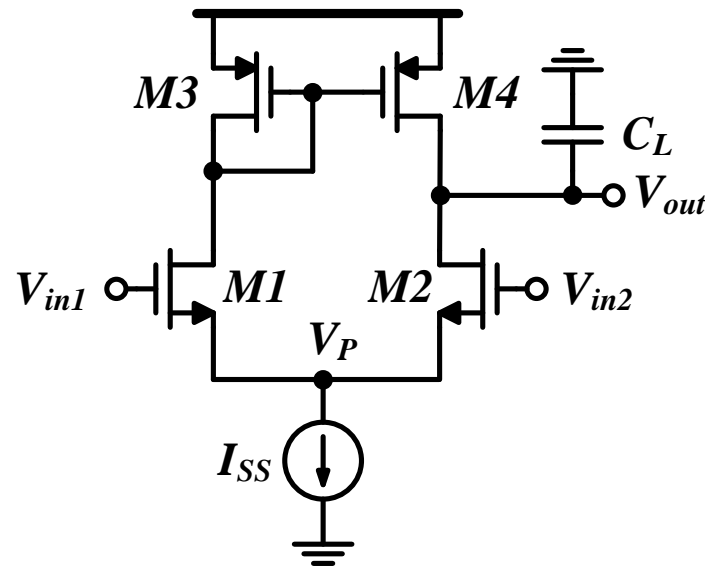$v_p$  acts as virtual ground  
at high frequency (why?)



# Differential Frequency Response: LHP Zero


□ At  $s_z$ :  $v_{out} = 0 \Rightarrow i_{out} = 0 \Rightarrow g_{m4}v_{sg4} = g_{m2}v_{gs2}$

$$g_{m1} \left( \frac{1}{g_{m3}} \parallel \frac{1}{s_z C_{mirr}} \right) \cdot g_{m4} \cdot v_{in1} = g_{m2} \cdot v_{in2}$$

$$s_z = -\frac{2g_{m3,4}}{C_{mirr}} \Rightarrow \omega_z = 2\omega_{p2}$$

□ Can we get same result by inspection?

- What happens to  $i_{out,sc}$ ?

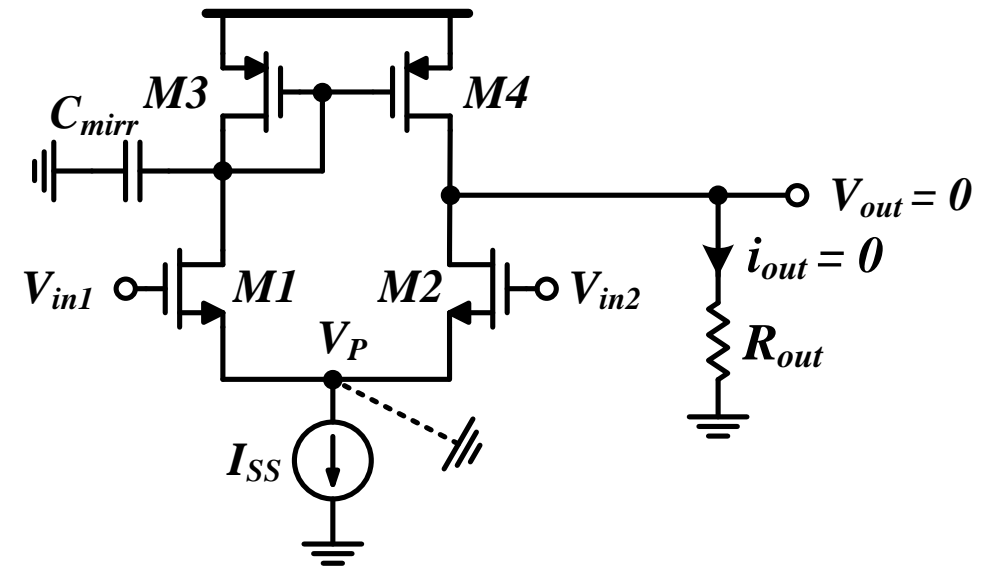

$v_p$  acts as virtual ground at high frequency (why?)

---

**Thank you!**

# References

- ❑ A. Sedra and K. Smith, “Microelectronic Circuits,” 7th ed., Oxford University Press, 2015
- ❑ B. Razavi, “Fundamentals of Microelectronics,” 2nd ed., Wiley, 2014
- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2nd ed., 2017
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” 2nd ed., Wiley, 2012