

Lab 2

MOSFET Sizing and CS Amplifier

Part 1: Sizing Chart

Required Spec:

DC Gain	-12
Supply	3v
Current Consumption	200uA

Analytic Calculations:

$$|A_v| \approx gmR_D = \frac{2I_D}{V_{ov}} = \frac{2V_{RD}}{V_{ov}}$$

In Simulation $V_{ov} \neq \frac{2I_D}{gm}$ all the time, Instead use $V^ = \frac{2I_D}{gm}$*

$$|A_v| = \frac{2V_{RD}}{V^*}$$

To get Large Output Swing: Assume CM output = $V_{RD} = \frac{V_{DD}}{2} = 1.5$

$$R = \frac{V_{RD}}{I_D} = \frac{1.5}{200\mu} = 7.5K\Omega \quad (\text{first design parameter calculated})$$

$$V_Q^* = \frac{2V_{RD}}{|A_v|} = 2 * \frac{1.5}{12} = 0.25 V$$

This concludes the initial Gain Calculation, We will use the obtained results on a sizing testbench to get the remaining required design parameters to meet the required Spec.

Testbench Schematic:

Using $W/L = 10\mu/2\mu$ and $V_{DS} = 1.5$, The choice for Dimension does not really matter right now as we will use cross multiplication later to calculate the required sizing values for the amplifier.

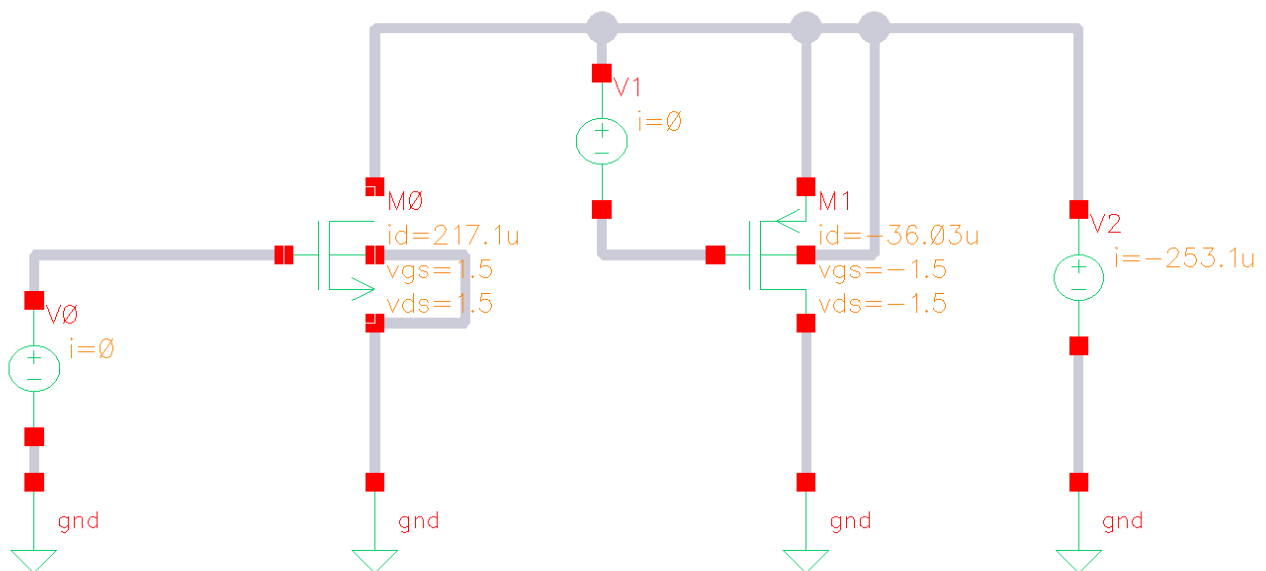


Figure 1 Sizing Testbench Schematic

Sweeping VGS from 0:10mV:(Vth + 0.4):

I ran a simple DC Op run once to determine the value of V_{TH}

$$V_{th} = 669.2mV$$

Sweep Range $\rightarrow 0: 10mV: 1.0692V$

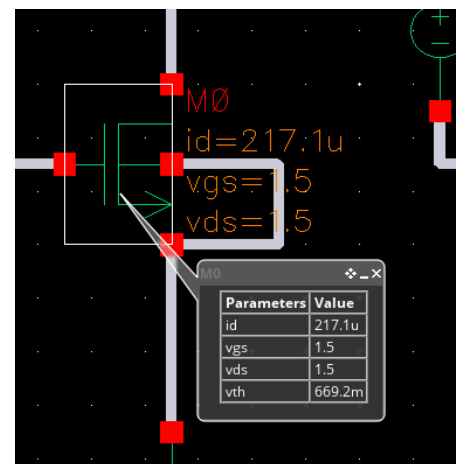


Figure 2 Value of V_{th} from simulation

V* and Vov Overlaid vs VGS:

Vov NMOS	expr	(v("M0:vgs" ?result "dc") - v("M0:vth" ?result "dc"))
V* NMOS	expr	((2 * getData("M0:id" ?result "dc")) / getData("M0:gm" ?result "dc"))
Vov PMOS	expr	(v("M1:vgs" ?result "dc") - v("M1:vth" ?result "dc"))
V* PMOS	expr	((2 * getData("M1:id" ?result "dc")) / getData("M1:gm" ?result "dc"))

Figure 3 Output Setup and Expressions for Vov and V*

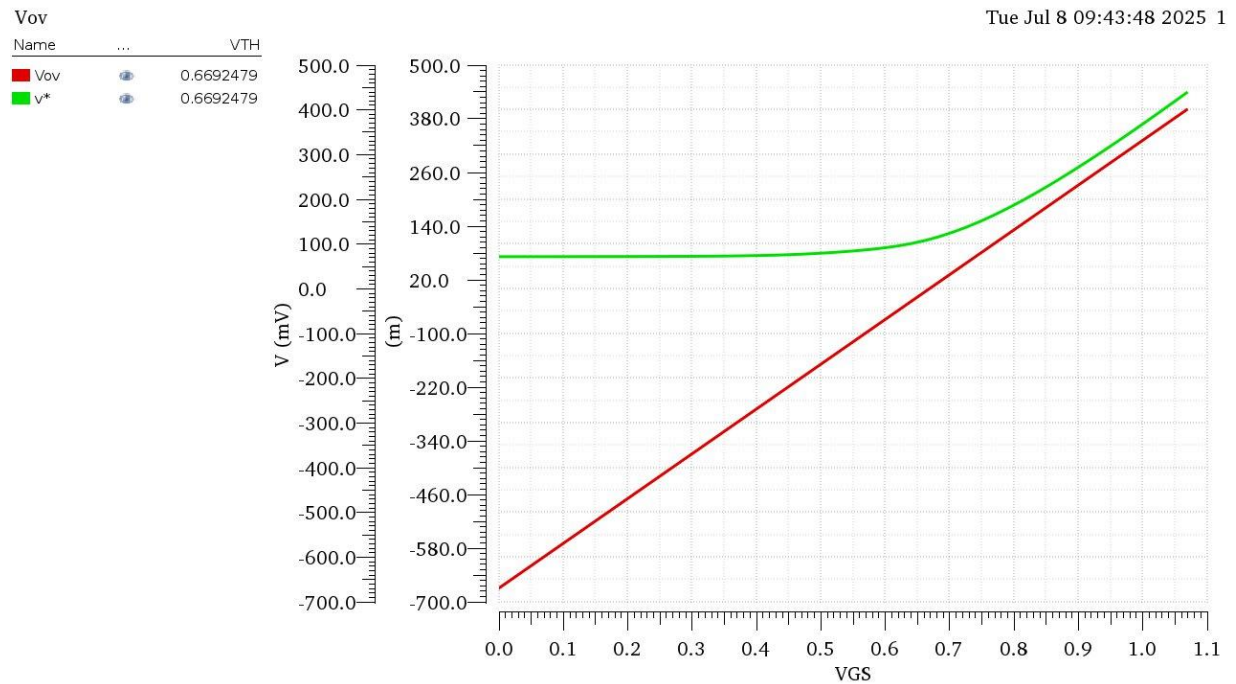


Figure 4 Vov and V* vs VGS NMOS

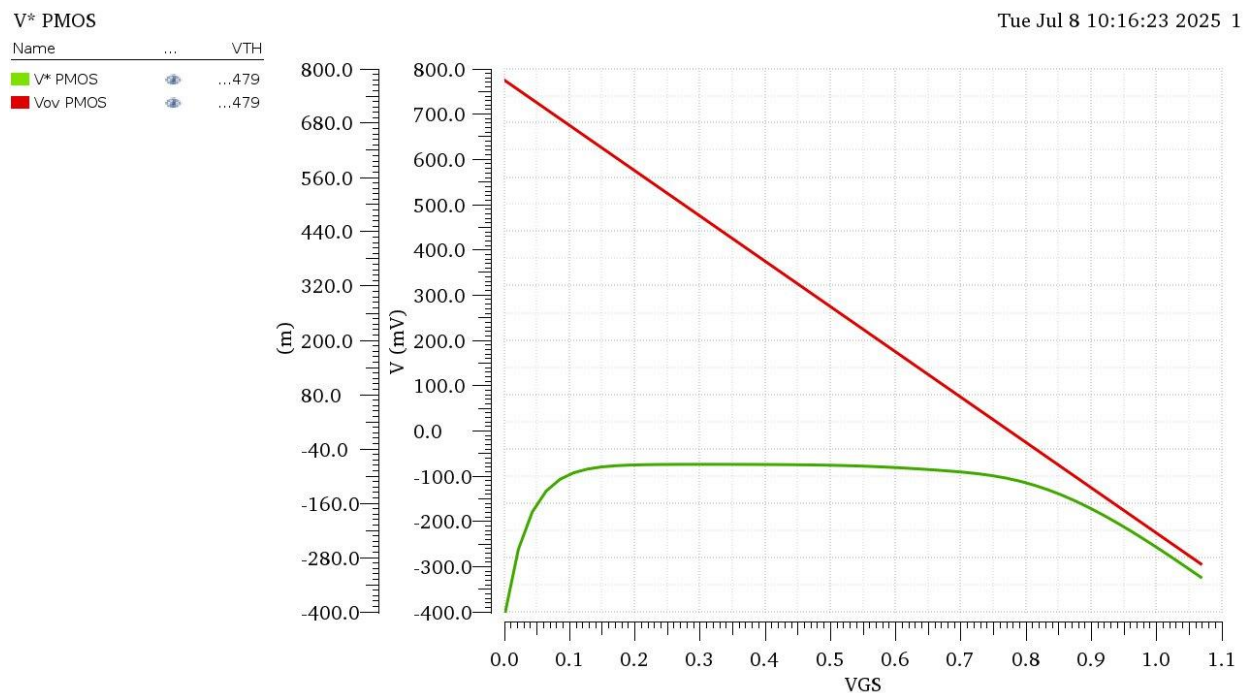


Figure 5 Vov and V* vs VGS PMOS

Comment: V_{ov} and V^* are relatively close in value to each other at the beginning of the Strong Inversion region meaning the square law is relatively valid in that region. But for Deep Strong inversion (Large V_{ov}) or weak inversion, the behavior is quite far despite using a Long Channel Length.

Locating V^*_Q and V_{GSQ} , V_{ovQ} :

V^* NMOS

Tue Jul 8 10:16:23 2025 1

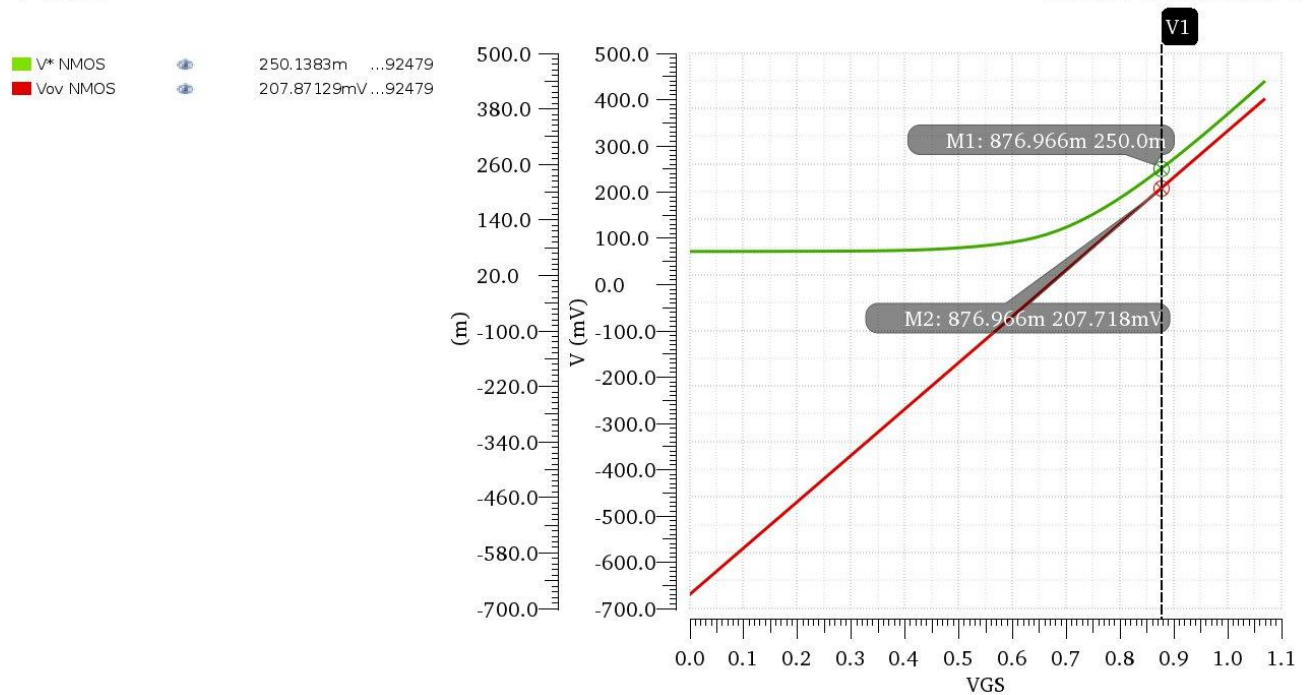


Figure 6 V^*_Q , V_{ovQ} and V_{GSQ} NMOS

$$@V^*_Q = 250\text{mV}, \quad V_{ovQ} = 207.72\text{mV}, \quad V_{GSQ} = 876.97\text{mV}$$

Plotting I_D , g_m , g_{ds} vs V_{GS} :

DC Analysis `dc`: $V_{GS} = (0 \rightarrow 1.06925)$

1

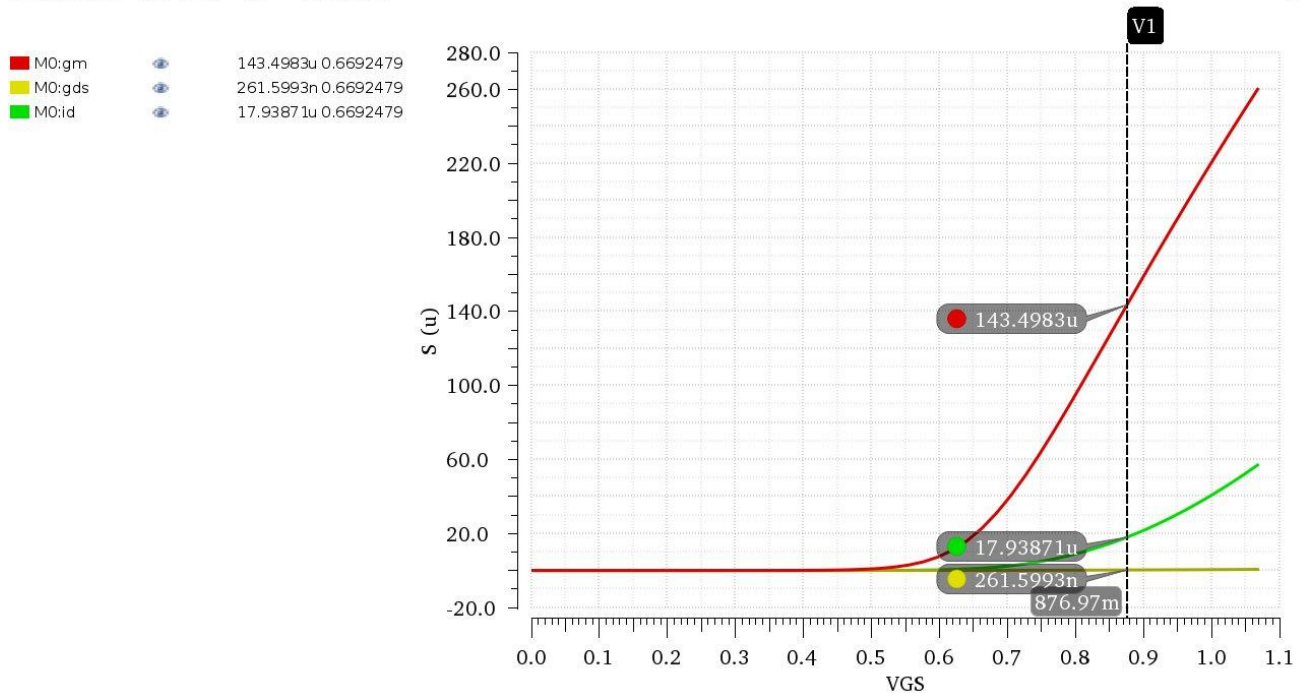


Figure 7 I_D , g_m , g_{ds} vs V_{GS} and their corresponding values at V_{gsq}

IDx	17.94uA
gm_x	143.5uS
gds_x	261.6nS

Getting the Value of W:

These Values were Calculated at $W=10\mu m$, to get the actual value of W for the design we can simply do cross multiplication since I_D is directly proportional to W regardless square law is valid or no.

W	I_D
$10\mu m$	$I_{DX} @ V_{Q*}$ (from the chart)
?	$I_{DQ} = 200\mu A$ (from the specs)

$$W = W * \frac{I_{DQ}}{I_{DX}} = \frac{10\mu * 200\mu}{17.94\mu} = \mathbf{111.48\mu m}$$

W is greater than W_{max} of the technology prompting us to use multipliers to achieve the required dimensions

Calculating the remaining Design parameters and verifying results analytically:

Using cross-multiplication we can get the values of gmQ and gdsQ as follows...

W	gm	gds
10 μm	gm _x = 143.5 μS	gds _x = 261.6nS
111.48 μm	gm _q	gds _q

$$gm_q = \frac{143.5\mu * 111.48\mu}{10\mu} \approx 1.6\text{mS} \quad , \quad gds_q = \frac{261.6n * 111.48\mu}{10\mu} = 2.916\mu\text{S}$$

$$ro = \frac{1}{gds} = \frac{1}{2.916\mu\text{S}} = 342.9\text{K}\Omega$$

Verifying Gain:

$$A_v = -gm(R_D // ro) = -1.6\text{m} * \frac{7.5\text{K} * 342.9\text{K}}{7.5\text{K} + 342.9\text{K}} = -11.743 \approx -12$$

The parameters are correct!

Final Parameter List:

W	111.48 μm
L	2 μm
gm	1.6 mS
gds	2.916 μS
ro	342.9 k Ω
R _D	7.5 k Ω
V _{gs}	876.97 mV

Part 2: CS Amplifier

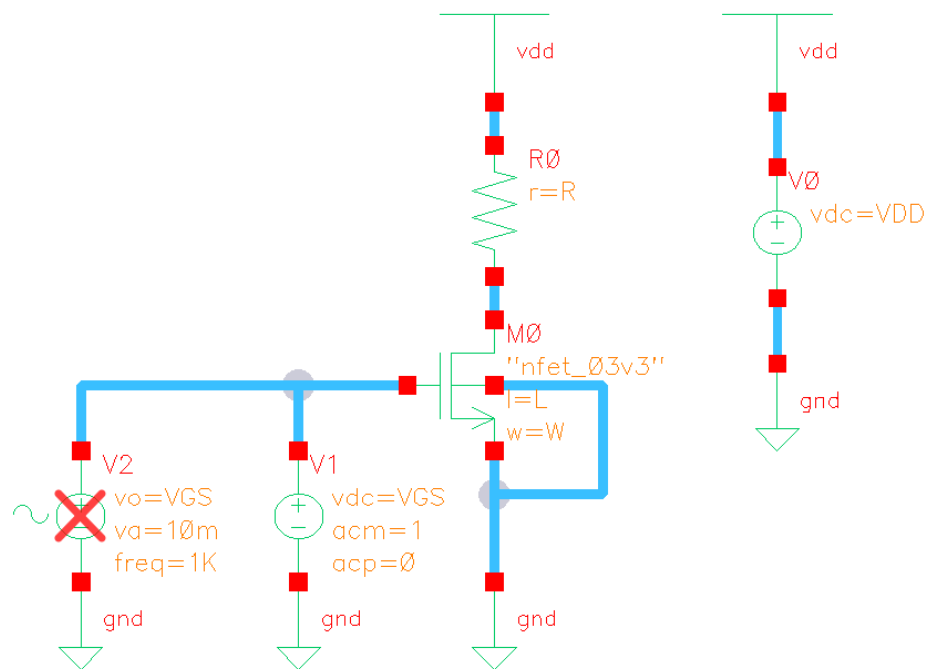


Figure 8 CS Amplifier Schematic Ready for DC, AC and Transient analyses

DC Operating Point Check:

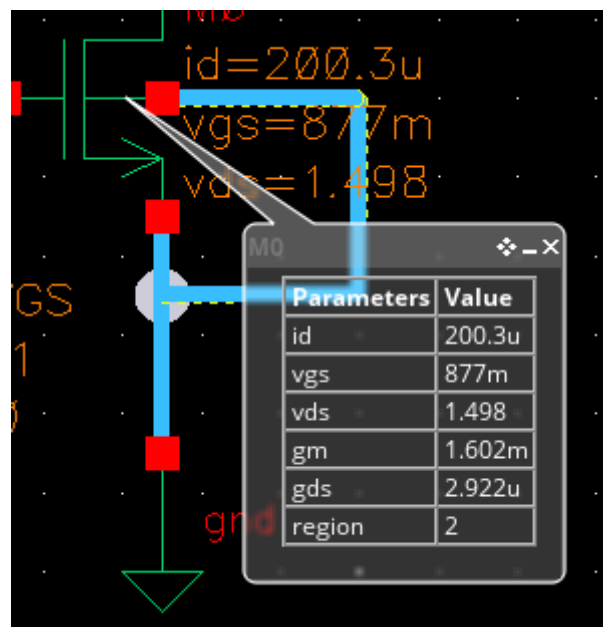


Figure 9 OP Point using Ballons

Comparing Analytic and Simulation Results for OP Point:

Parameter	Simulation	Analytic
Vgs	877 mV	876.96 mV
Id	200.3 uA	200 uA
gm	1.602 mS	1.6 mS
gds	2.922 uS	2.916 uS
ro	342.23 KΩ	342.935 KΩ

The results are almost identical due to using a chart-based approach.

- **Compare r_o and R_D . Is the assumption of ignoring r_o justified in this case? Do you expect the error to remain the same if we use min L ?**

$$R_D = 7.5 \text{ K}\Omega, \quad r_o \approx 342 \text{ K}\Omega, \quad r_o \gg R_D$$

Therefore, It is safe to neglect r_o in this case.

In case of using min L , Since r_o and L are directly proportional, r_o will massively decrease by decreasing L to a point where it is no longer valid to neglect it as it will have a value comparable with R_D .

- **Calculate the intrinsic gain of the transistor.**

$$\text{Intrinsic Gain } |A_v| = g_m * r_o = 1.6\text{m} * 342\text{K} = 547.2$$

- **Calculate the amplifier gain analytically. What is the relation (\ll , $<$, \approx , $>$, \gg) between the amplifier gain and the intrinsic gain?**

$$\text{Amplifier Gain } |A_v| = g_m(R_D // r_o) = 1.6\text{m} * (7.6\text{K} // 342\text{K}) = 11.757 \ll 547.2$$

Amplifier Gain is much less than (\ll) Intrinsic Gain.

AC Analysis:

Av AC

Tue Jul 8 13:18:09 2025 1

Name	M
Av AC	2

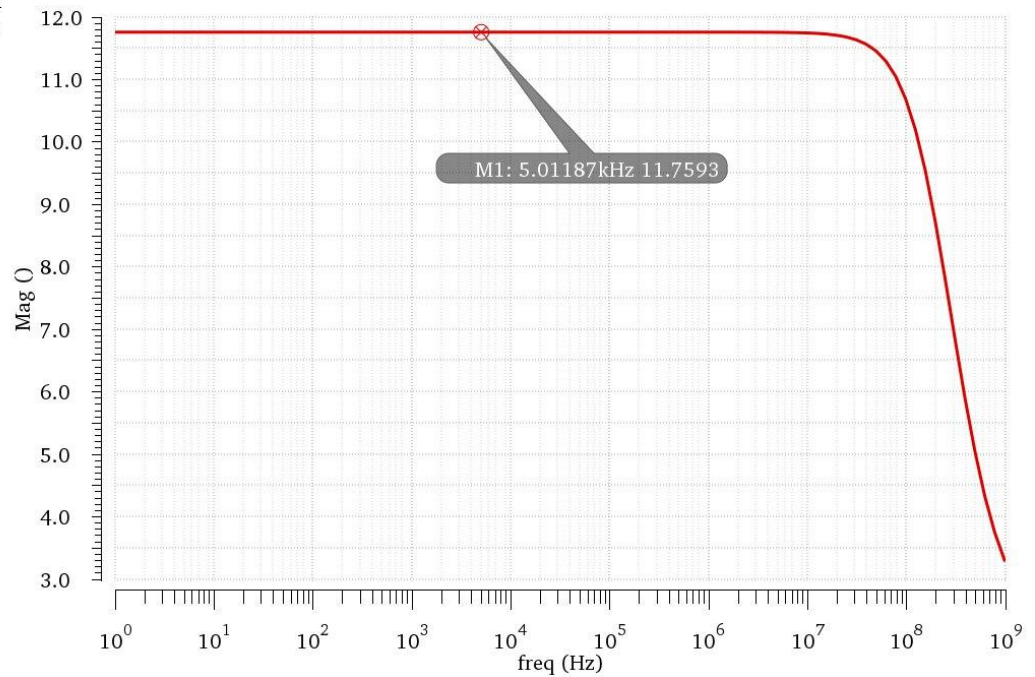


Figure 10 DC Gain from AC Analysis

Gain = 11.7593, Agrees with Analytical Results and approximately equal to the required spec.

VOUT vs VIN:

VOUT

Tue Jul 8 13:24:58 2025 1

Name	M
VOUT	2

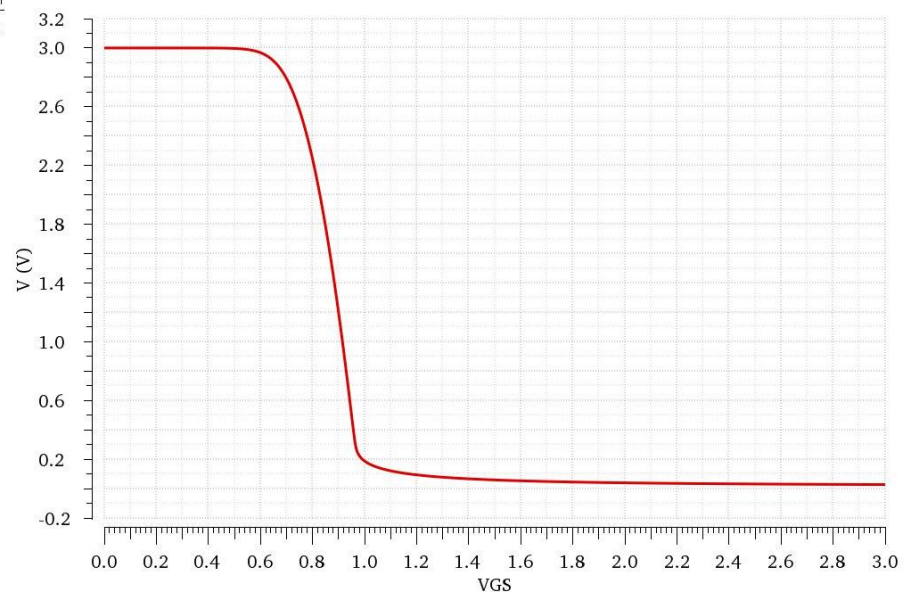


Figure 11 VOUT vs VIN graph

The relation between V_{IN} and V_{OUT} differs according to the region of operation of the transistor:

V_{OUT} is given by $V_{OUT} = V_{DD} - I_D \cdot R_D$

@ $V_{in} < V_{th}$: Cutoff region, $I_D = 0$ thus $V_{OUT} = V_{DD}$

@ $V_{in} > V_{th}$ & $V_{out} > V_{ov}$: Saturation region, The relation is quadratic according to the Square Law.

Notice: Due to the big slope in that area, if a small signal is applied around the Operational point it could be approximated that the relation is linear in that case. Hence that's the preferred region to operate the amplifier.

@ $V_{in} > V_{th}$ & $V_{out} < V_{ov}$: Triode Region, The relation is almost linear according to the triode current equation.

Though with a much smaller slope than the one in the saturation region.

Derivative of V_{OUT} vs V_{IN} :

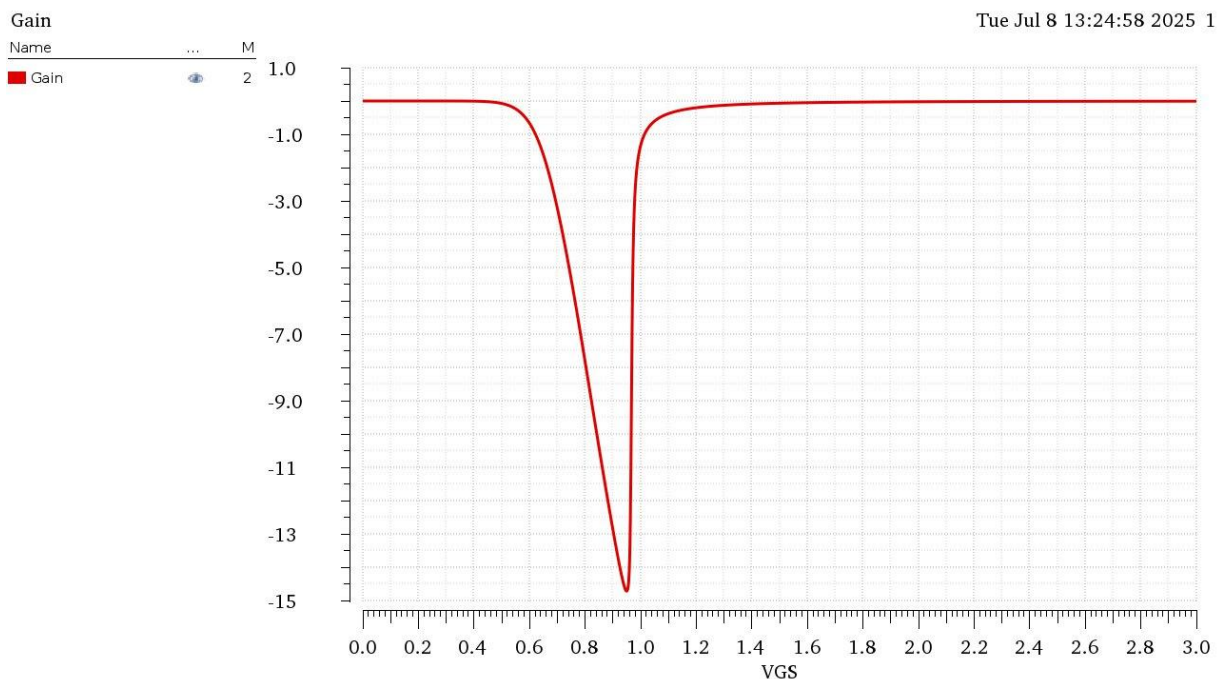


Figure 12 Derivative of V_{OUT} vs V_{IN} graph

Is the Gain Linear?

Since $V_{IN} = V_{GS}$, $g_m = 2 \cdot I_D / V_{ov} = k \cdot V_{ov}$ depends on V_{GS} and the gain $A_v = g_m \cdot R_d$ (Depends on g_m)

The Gain is the function of the input and as seen from the graph it is not linear. Though if zoomed in for a small signal it can be approximated to be linear in that case.

Transient Analysis:

gm vs time

Tue Jul 8 14:13:46 2025 1

Name	...	M
gm vs time		2

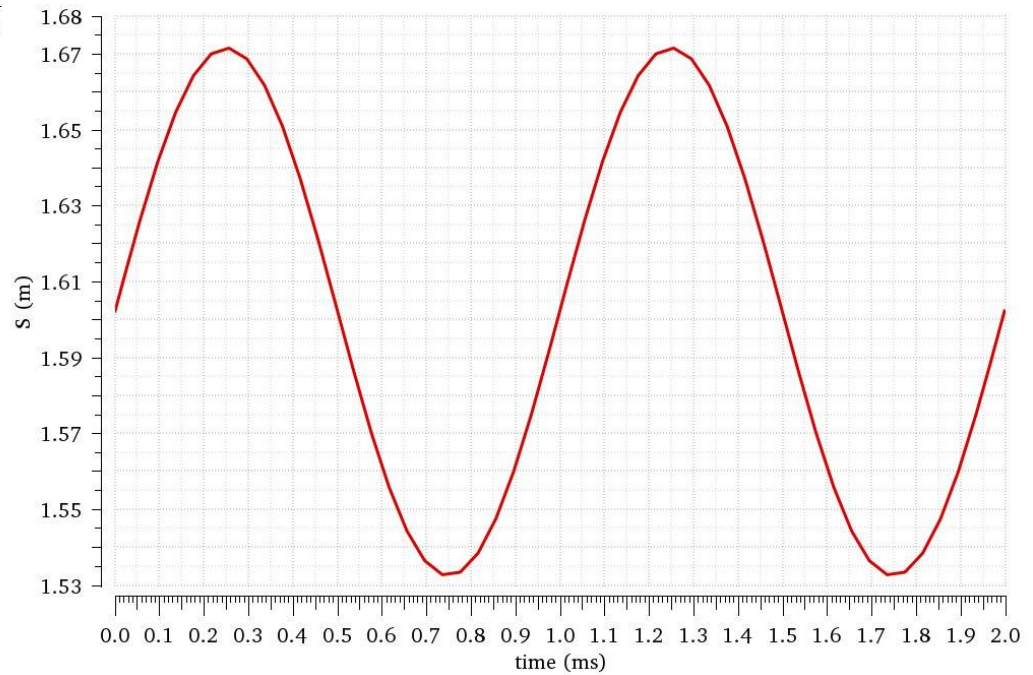


Figure 13 g_m vs Time (Transient Analysis)

VIN

Tue Jul 8 14:13:46 2025 1

Name	...	M
VIN		2

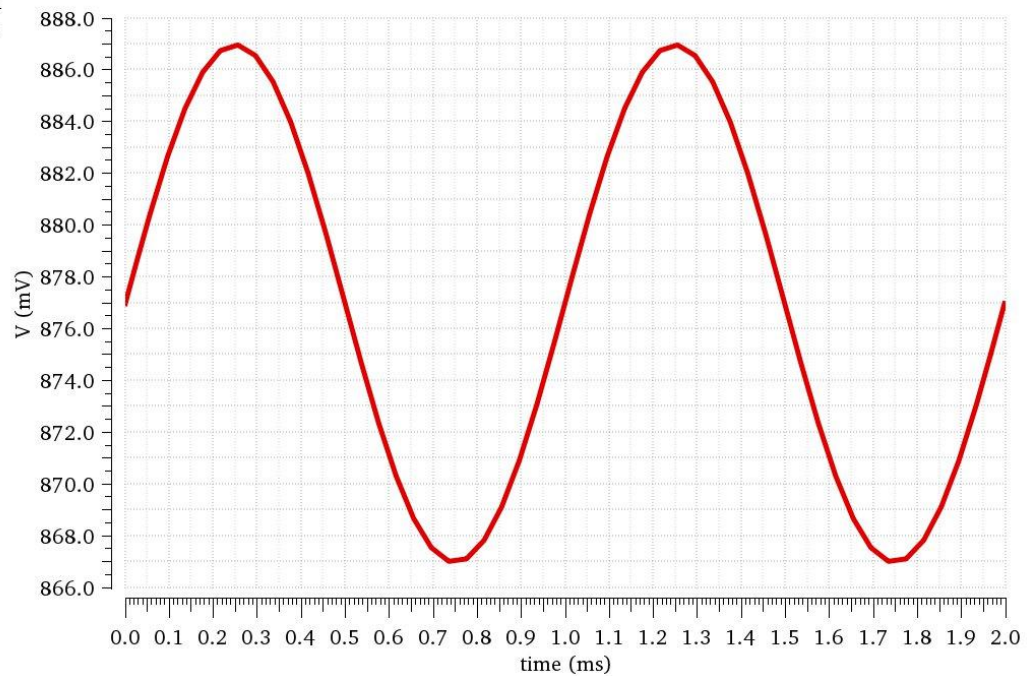


Figure 14 V_{IN} vs Time (Transient Analysis)

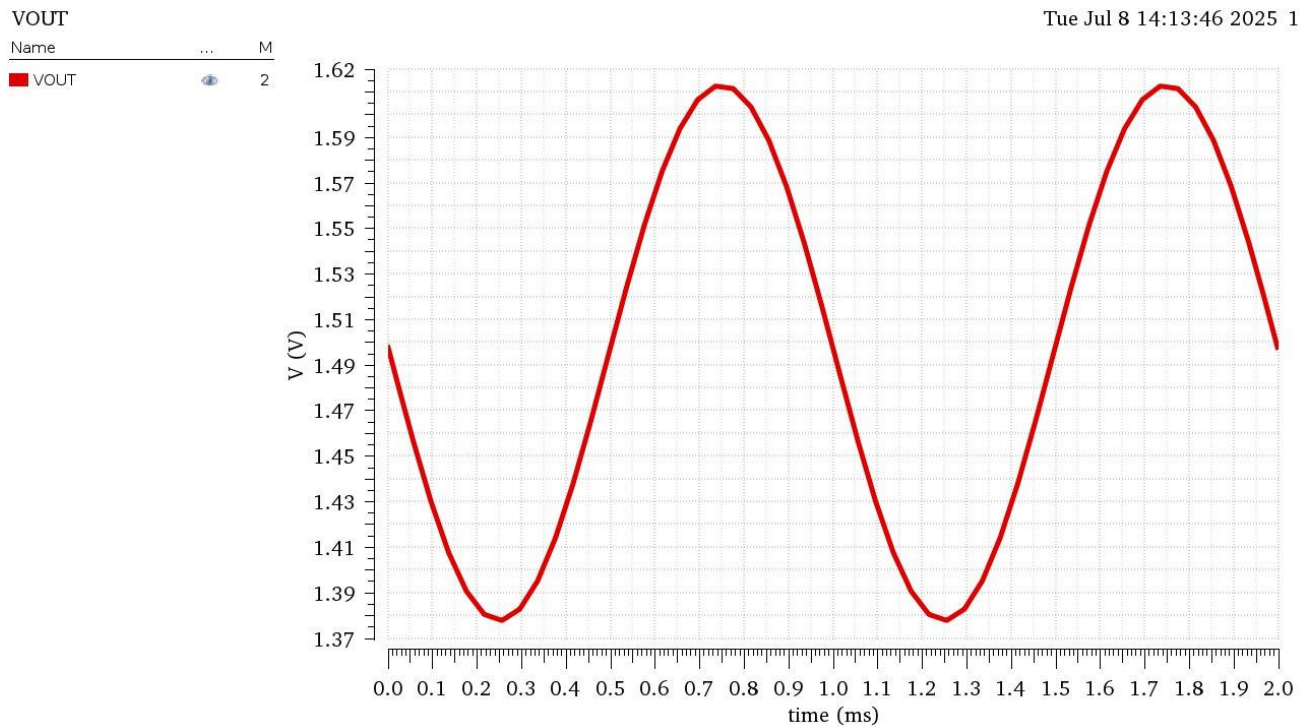


Figure 15 VOUT vs Time (Transient Analysis)

- **Does gm vary with the input signal? What does that mean?**

gm does vary across time as it is a function of the input. Which means the gain also varies with the input signal

- **Is this amplifier linear? Comment.**

No, The amplifier is not Linear.

While some linear behavior can be noticed on very small signals, those are merely approximations and do not show the entire picture. Vout varies with Vin which affects different parameters and makes the gain non-linear as well.