

# Analog IC Design

## Lecture 16 OTA Frequency Compensation

**Dr. Hesham A. Omran**

Integrated Circuits Laboratory (ICL)  
Electronics and Communications Eng. Dept.  
Faculty of Engineering  
Ain Shams University

# Outline

---

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
  - Miller compensation
  - The feedforward zero

# Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
  - Miller compensation
  - The feedforward zero

# MOSFET in Saturation




- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \text{ or } V_{DS} \geq V_{ov}$$


- ❑ Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
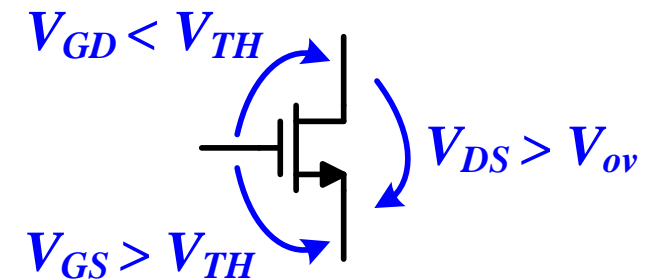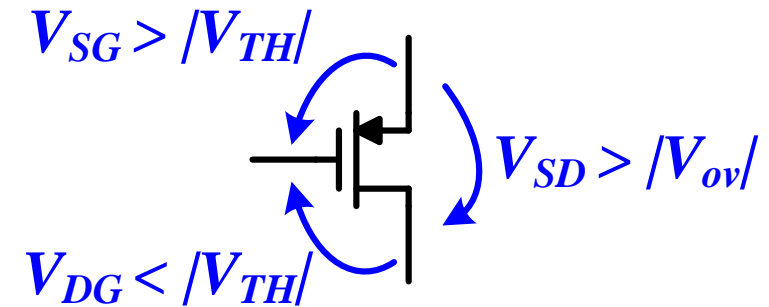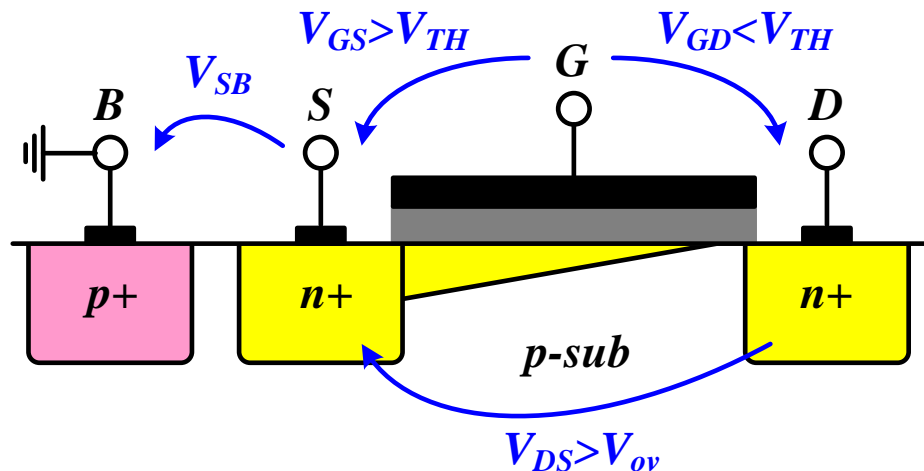
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$



# Regions of Operation Summary

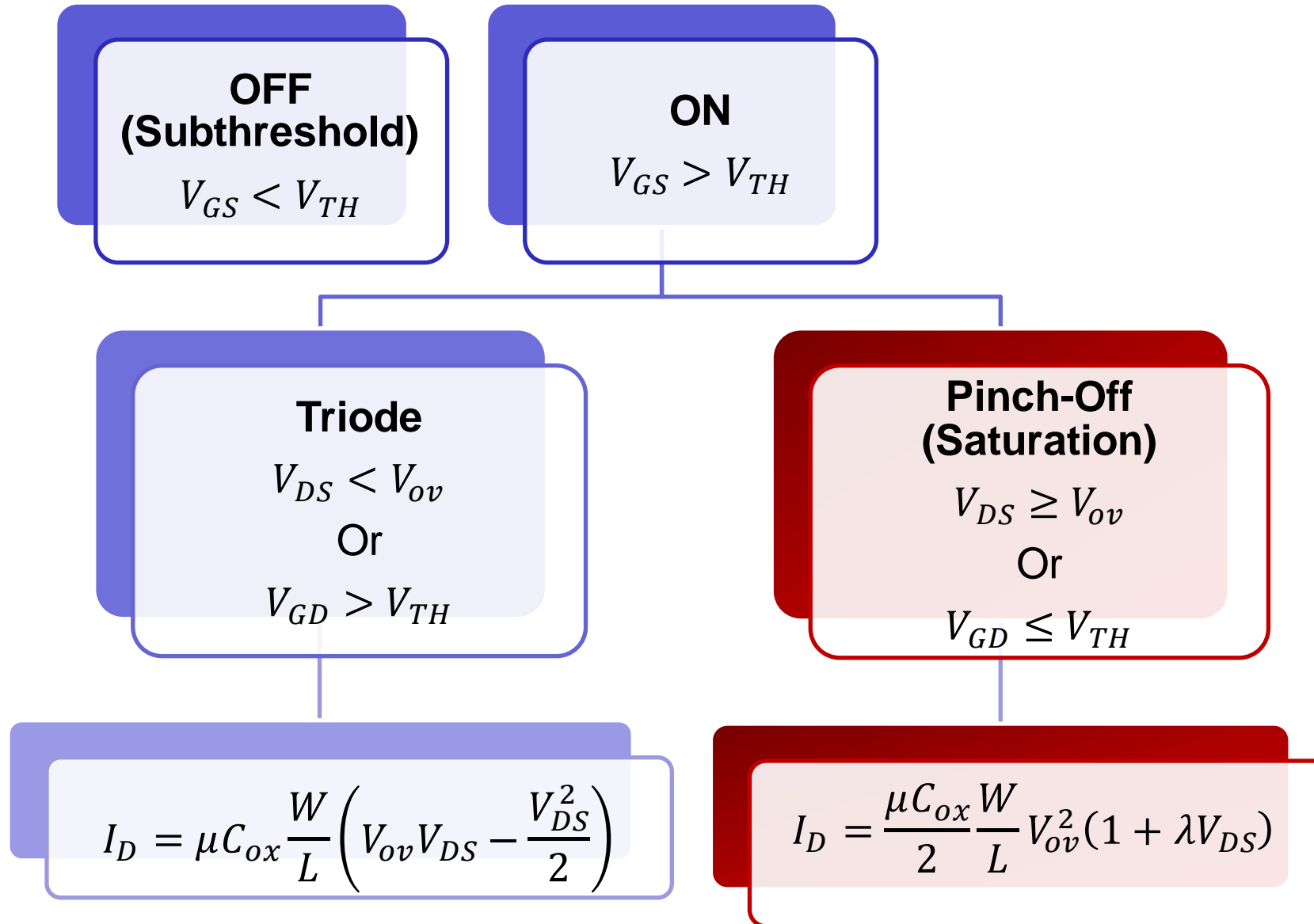

# High Frequency Small Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$

$$g_{mb} = \eta g_m$$

$$\eta \approx 0.1 - 0.25$$

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D}$$


$$V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L}$$

$$V_{DS} \uparrow V_A \uparrow$$


$$C_{gb} \approx 0$$

$$C_{gs} \gg C_{gd}$$




$$C_{sb} > C_{db}$$

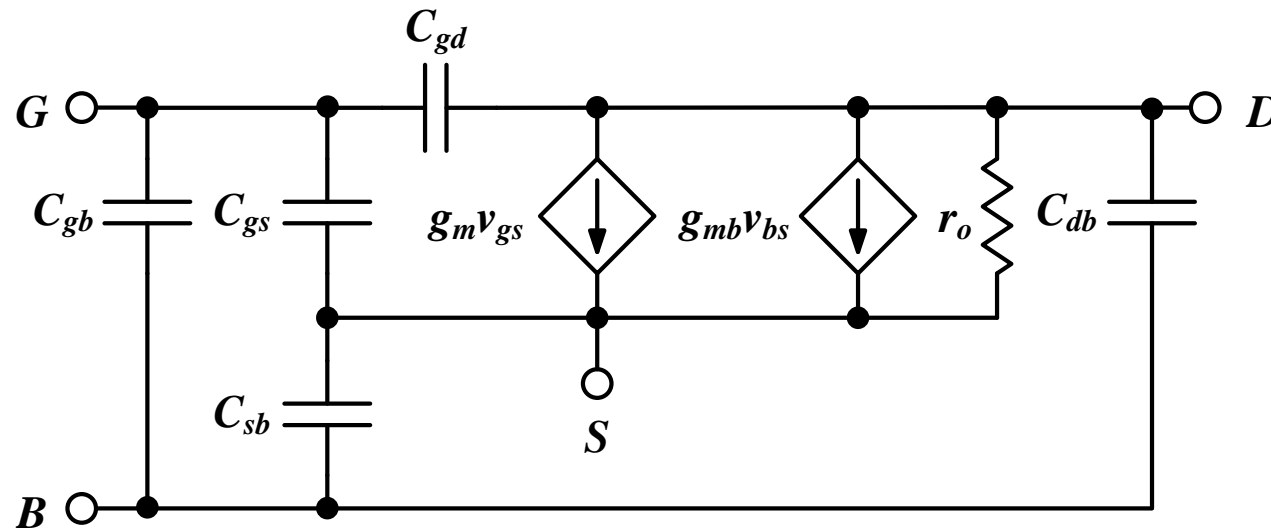

# Rin/out Shortcuts Summary

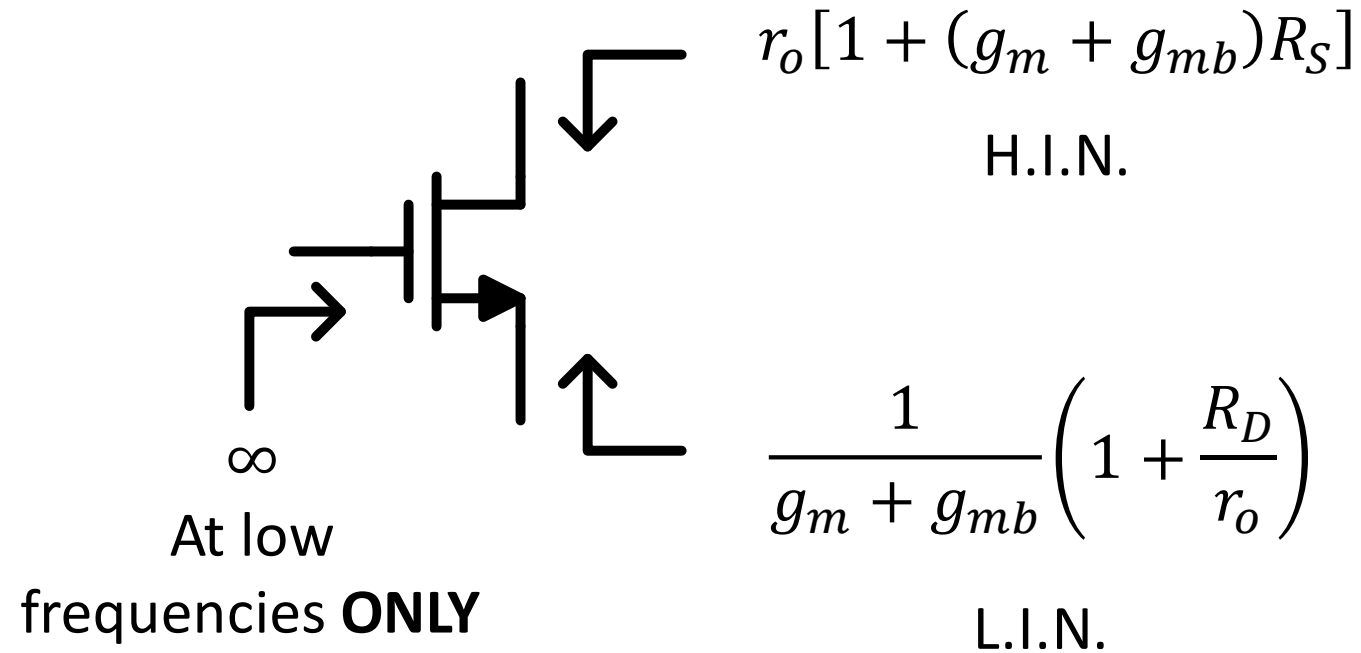

# Summary of Basic Topologies

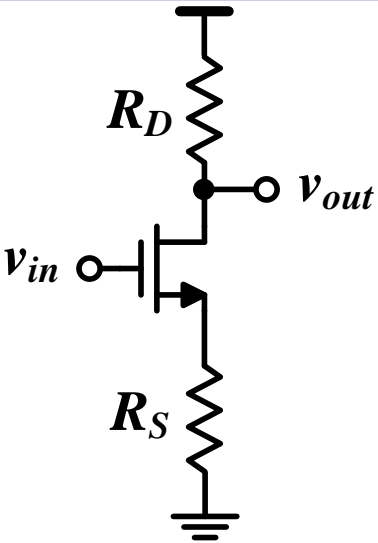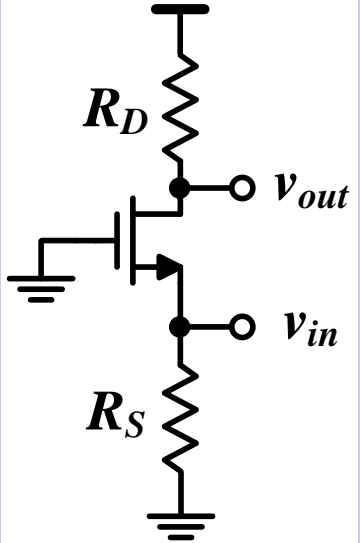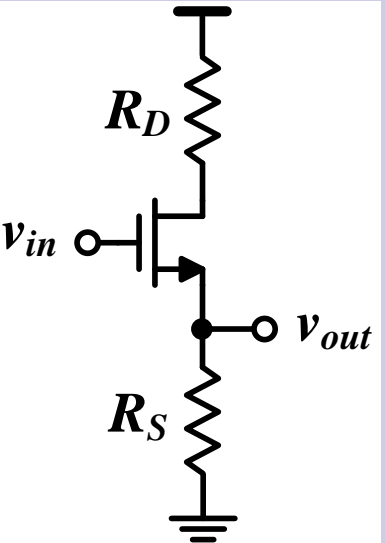	CS	CG	CD (SF)
			
	Voltage & current amplifier	Voltage amplifier Current buffer	Voltage buffer Current amplifier
<b>R<sub>in</sub></b>	$\infty$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$	$\infty$
<b>R<sub>out</sub></b>	$R_D \parallel r_o [1 + (g_m + g_{mb}) R_S]$	$R_D \parallel r_o$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left( 1 + \frac{R_D}{r_o} \right)$
<b>G<sub>m</sub></b>	$\frac{-g_m}{1 + (g_m + g_{mb}) R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$



# Differential Amplifier



	Pseudo Diff Amp	Diff Pair (w/ ideal CS)	Diff Pair (w/ $R_{SS}$ )
$A_{vd}$	$-g_m R_D$	$-g_m R_D$	$-g_m R_D$
$A_{vCM}$	$-g_m R_D$	0	$\frac{-g_m R_D}{1 + 2(g_m + g_{mb})R_{SS}}$
$A_{vd}/A_{vCM}$	1	$\infty$	$2(g_m + g_{mb})R_{SS} \gg 1$

$$A_{vCM2d} = \frac{v_{od}}{v_{iCM}} \approx \frac{\Delta R_D}{2R_{SS}} + \frac{\Delta g_m R_D}{2g_{m1,2}R_{SS}}$$

$$CMRR = \frac{A_{vd}}{A_{vCM2d}}$$





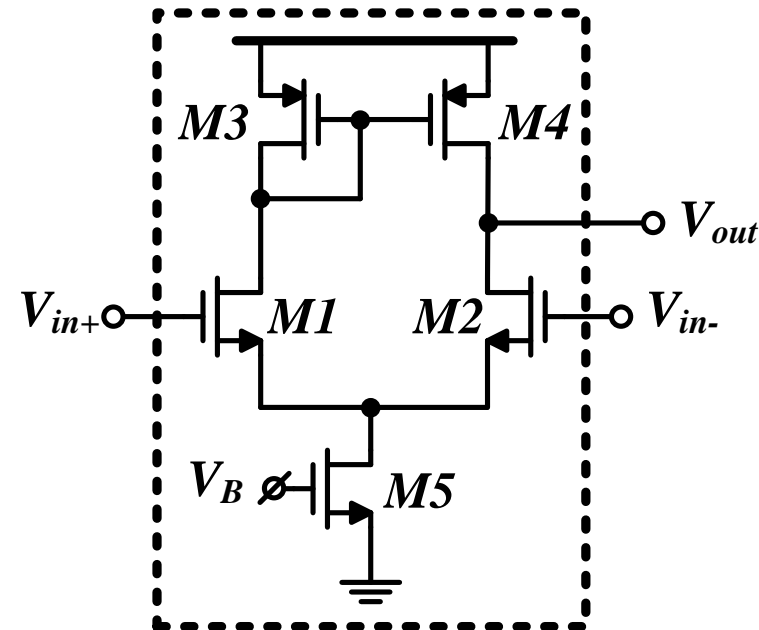
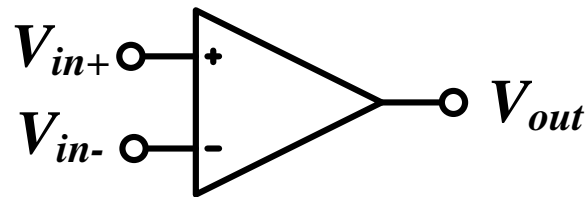
# Op-Amp

- ❑ An op-amp is simply a high gain differential amplifier
  - The gain can be increased by using cascodes and multi-stage amplification
- ❑ The diff amp is a key block in many analog and RF circuits
  - DEEP understanding of diff amp is ESSENTIAL



# Op-Amp vs OTA

- ❑ In short, an OTA is an op-amp without an output stage (buffer)
- ❑ Some designers just use op-amp name and symbol for both

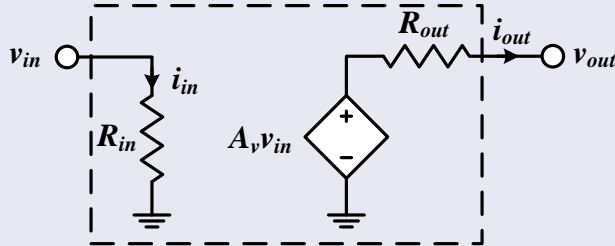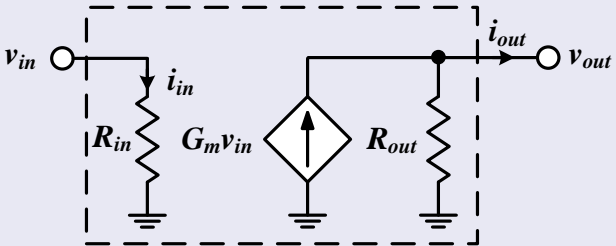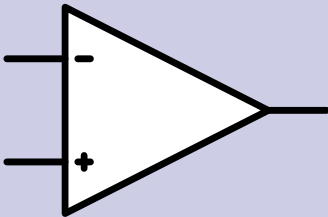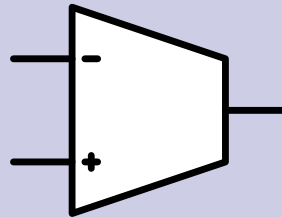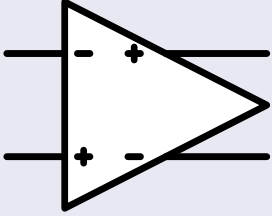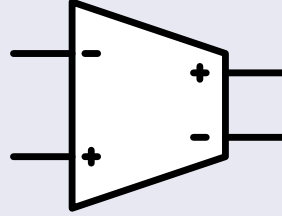	Op-amp	OTA
Rout	LOW	HIGH
Model		
Diff input, SE output		
Fully diff		

# V-star ( $V^*$ )

- V-star ( $V^*$ ) is inspired by  $V_{ov}$  but calculated from actual simulation data

$$g_m = \frac{2I_D}{V^*} \leftrightarrow V^* = \frac{2I_D}{g_m} = \frac{2}{g_m/I_D}$$

- Figures-of-merit in terms of  $V^*$

$$g_m r_o = \frac{2I_D}{V^*} \cdot \frac{1}{\lambda I_D} = \frac{2}{\lambda V^*}$$

$$f_T = \frac{g_m}{2\pi C_{gg}} = \frac{1}{2\pi} \cdot \frac{2I_D}{V^*} \cdot \frac{1}{C_{gg}}$$

$$\frac{g_m}{I_D} = \frac{2}{V^*}$$

- The boundary between weak and strong inversion ( $n = 1.2 \rightarrow 1.5$ )



$$V_{ov}(SI) = V^*(WI) = 2nV_T \approx 60 \rightarrow 80mV$$

# Negative Feedback

$$\beta = \frac{R_2}{R_1 + R_2}$$

$$A_{CL} = \frac{V_{out}}{V_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}} = \frac{A_{OL}}{1 + \beta A_{OL}} \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$
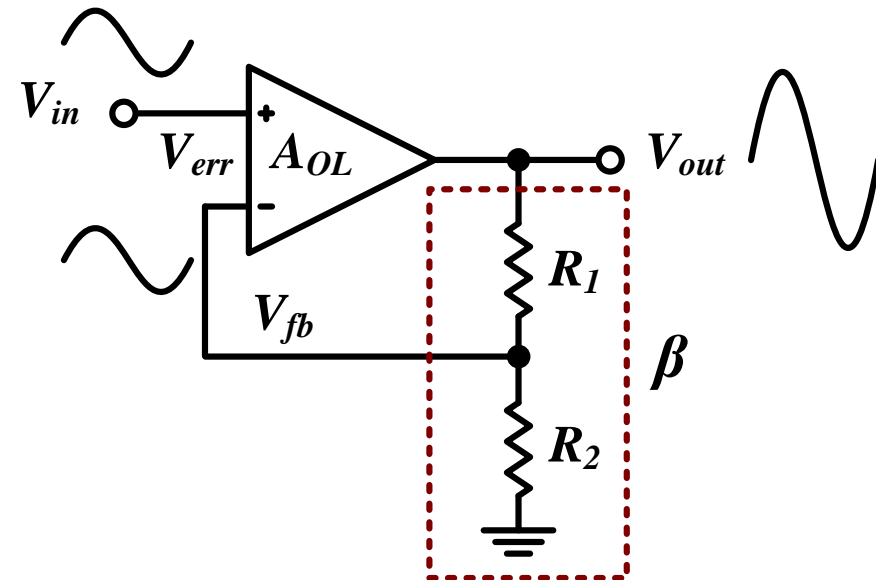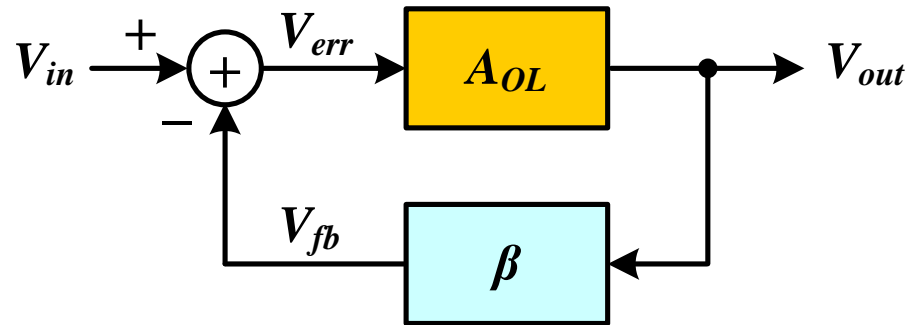
$$\omega_{p,CL} = (1 + \beta A_{OLo}) \omega_{p,OL}$$




# Outline

- ❑ Recapping previous key results
- ❑ **Frequency compensation**
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
  - Miller compensation
  - The feedforward zero
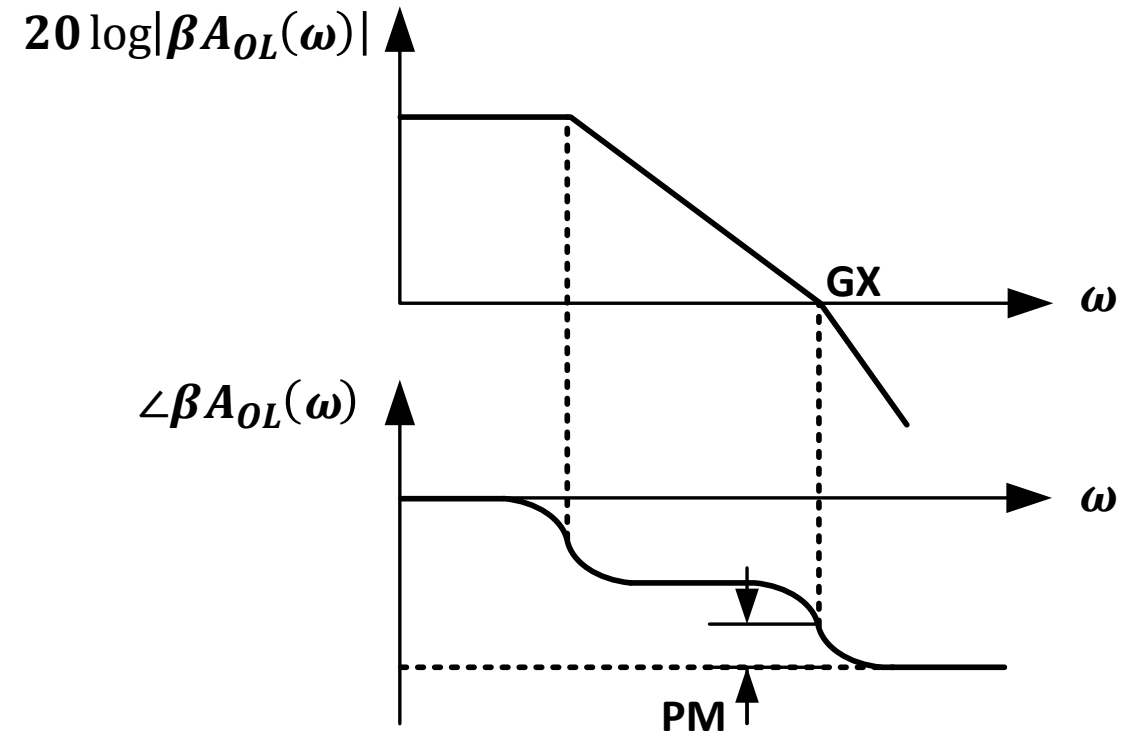
# Phase Margin and the Ultimate GBW


- If  $\omega_{p2} = \omega_u$ : PM = 45°
  - Typically inadequate (peaking/ringing)
- Thus  $\omega_{p2}$  should be  $> \omega_u \rightarrow \omega_{p1} \ll \omega_u < \omega_{p2}$ 
  - $\omega_{p1}$  defines OL BW and  $\omega_{p2}$  defines ultimate GBW (max CL BW)

Frequency domain peaking  
→ noise amplification  
Time domain ringing  
→ poor settling time


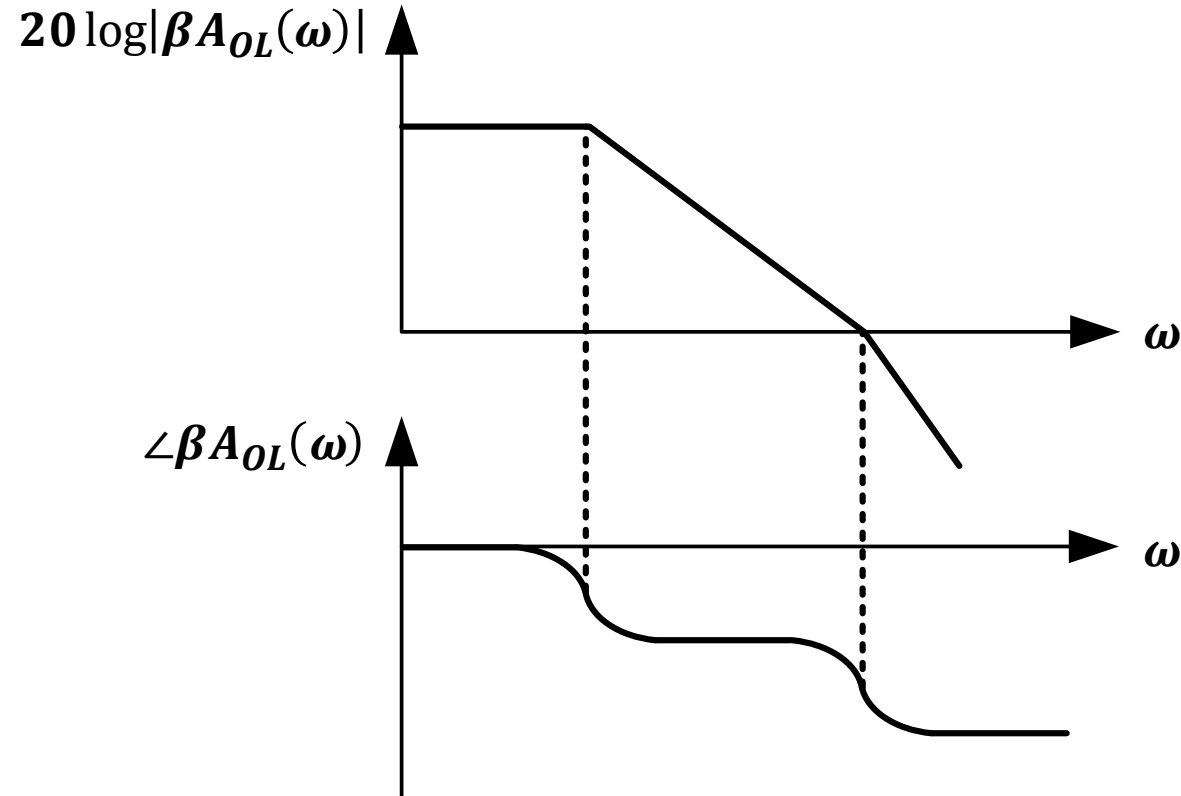
# Frequency Compensation


- ❑ Frequency compensation: Modify the system to achieve a specific PM to control frequency domain peaking and time domain ringing
- ❑  $G_X < P_X$  is not enough: We actually need  $\omega_u < \omega_{p2}$





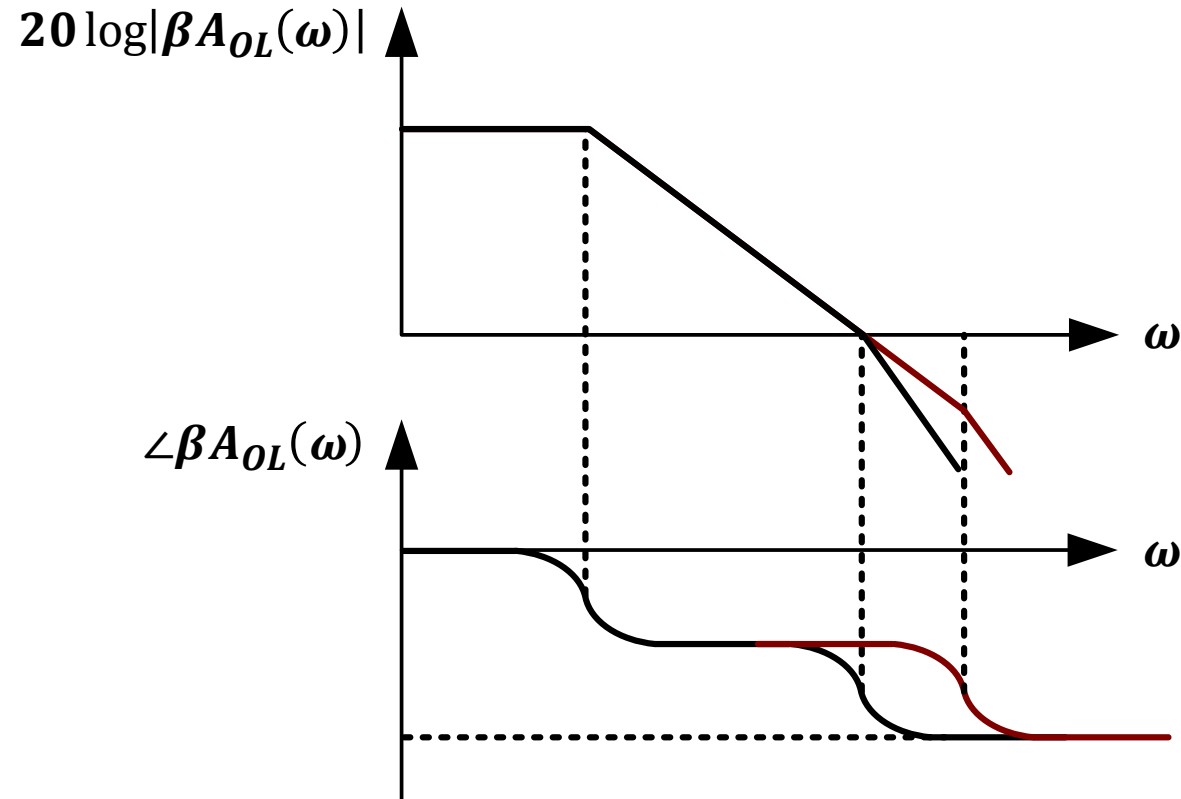
# Frequency Compensation

- We need  $G_X < P_X$  (actually  $\omega_u < \omega_{p2}$ )
  - Push  $\omega_{p2}$  **outwards**: lower resistance/capacitance
    - Not always feasible for free


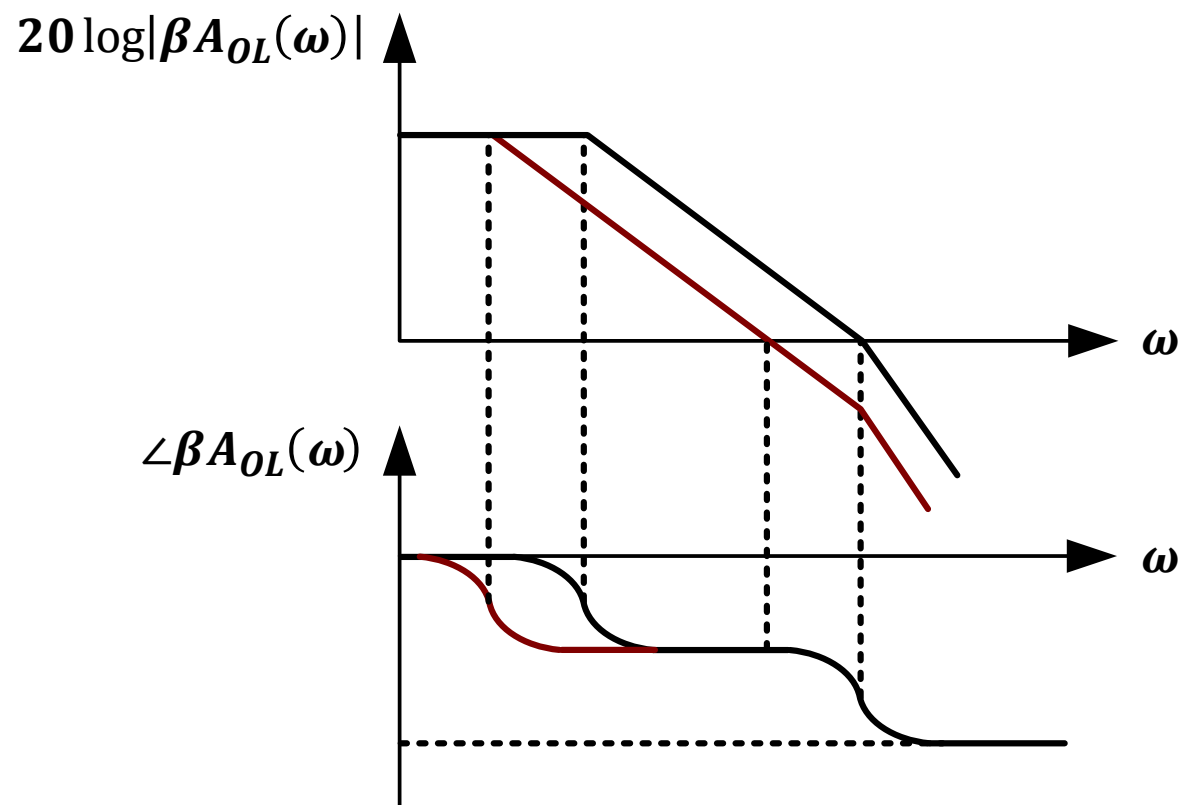
# Frequency Compensation

- We need  $G_X < P_X$  (actually  $\omega_u < \omega_{p2}$ )
  - Push  $G_X / \omega_u / \omega_{p1}$  **inwards**: lower GBW



# Compensation of Popular OTA Topologies

- ❑ Single-stage OTAs
  - 5T OTA
  - Telescopic cascode OTA
  - Folded cascode OTA
- ❑ Two-stage OTA
- ❑ Three-stage OTA
- ❑ Gain boosted OTA

# Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
  - Miller compensation
  - The feedforward zero

# 5T OTA

- $\omega_{p1} \ll \omega_u < \omega_{p2}$
- The H.I.N. sets  $BW_{OL}$


$$\omega_{p1} = \omega_{pout} \approx \frac{1}{R_{out} C_{out}}$$

- The first non-dominant pole (mirror node) sets the ultimate GBW
  - Ultimate CL bandwidth (buffer)

$$\omega_{p2} = \omega_{pM} \approx \frac{g_{m3}}{C_M} \sim \frac{\omega_T}{3}$$


- LHP zero:

$$\omega_z = 2\omega_{p2}$$

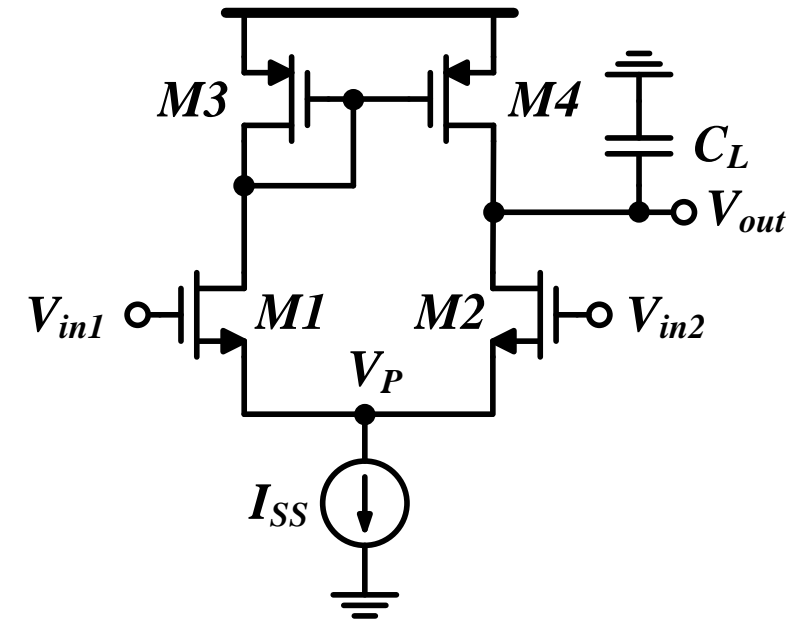

# 5T OTA


☐ Fully differential?

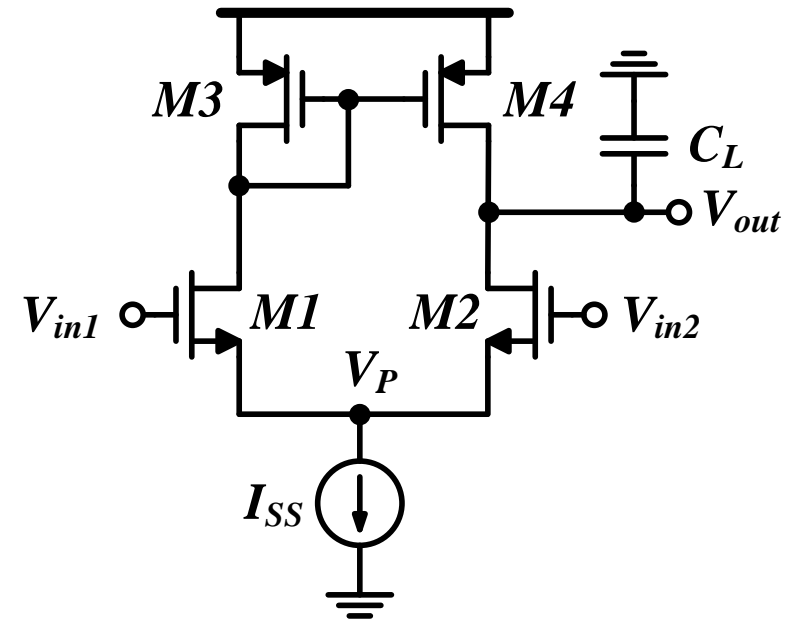
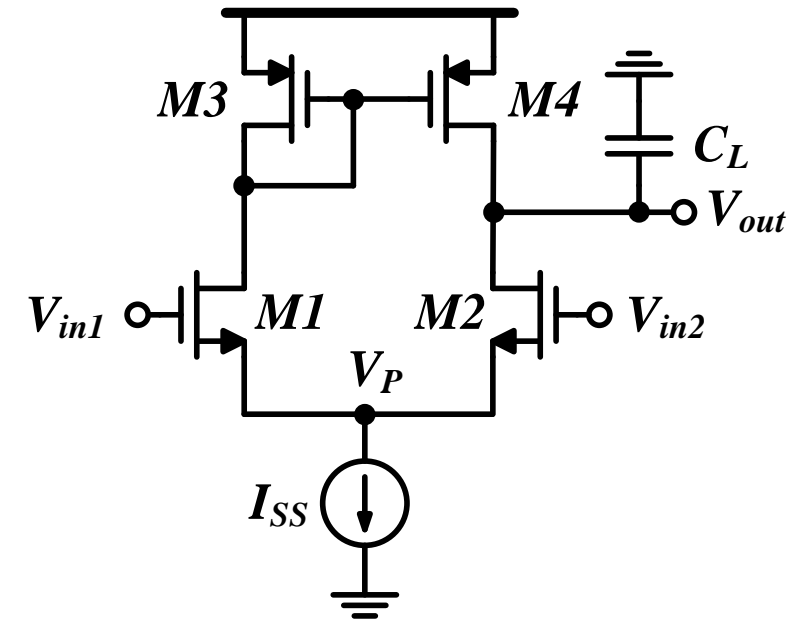
# 5T OTA


□ Fully differential with mismatch?

$$\begin{aligned} H(s) &= \frac{A_o/2}{1 + \frac{s}{\omega_{p1}}} + \frac{A_o/2}{1 + \frac{s}{\omega_{p1} + \Delta\omega}} \\ &= \frac{A_o \left\{ 1 + \frac{s}{2} \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p1} + \Delta\omega} \right) \right\}}{\left( 1 + \frac{s}{\omega_{p1}} \right) \left( 1 + \frac{s}{\omega_{p1} + \Delta\omega} \right)} \\ &= \frac{A_o \left( 1 + \frac{s}{\omega_z} \right)}{\left( 1 + \frac{s}{\omega_{p1}} \right) \left( 1 + \frac{s}{\omega_{p1} + \Delta\omega} \right)} \end{aligned}$$


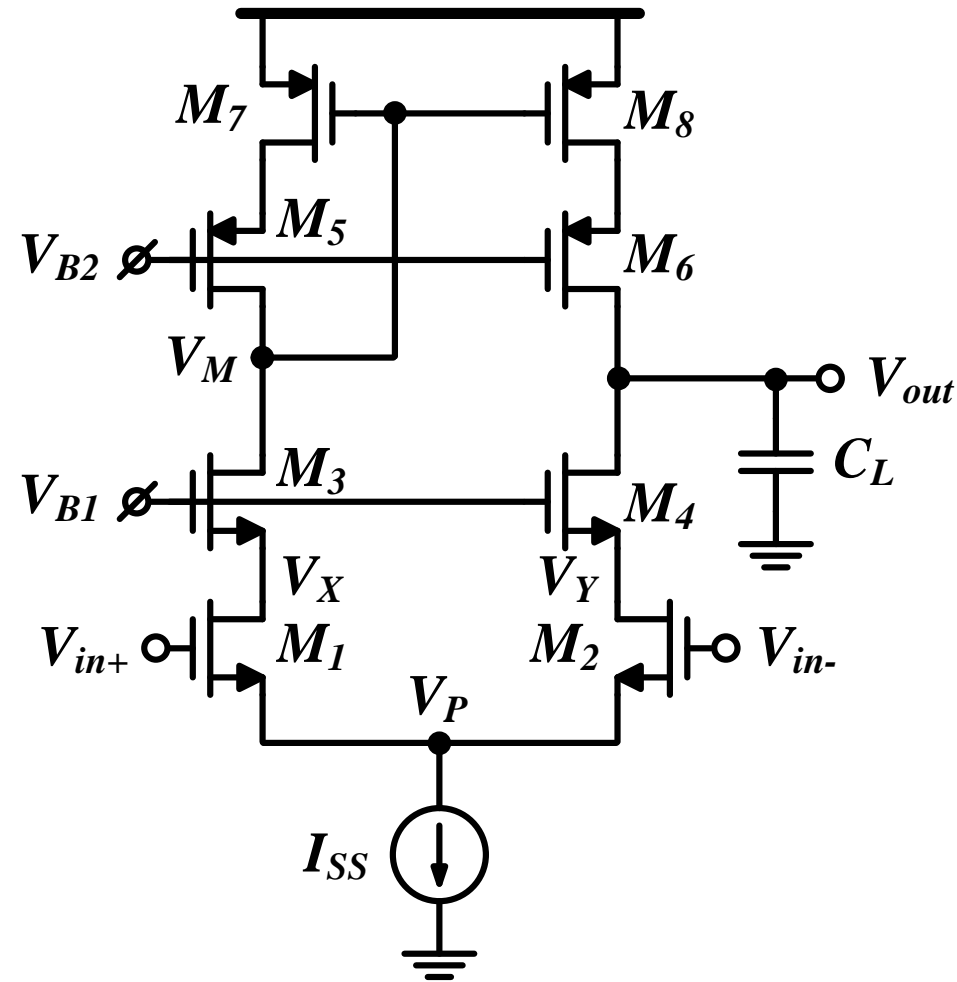
# Telescopic Cascode

- Higher DC gain, but limited swing and additional poles






# Telescopic Cascode: Poles

- ❑  $\omega_{p1} \ll \omega_u < \omega_{p2}$
- ❑ The H.I.N. sets  $BW_{OL}$

$$\omega_{p1} = \omega_{pout} = \frac{1}{R_{out} C_{out}}$$


- ❑  $V_X$  and  $V_Y$  contribute a single pole
- ❑ Non-dominant poles considerations:
  - $C_{gs}$  is larger than other caps
  - PMOS contributes larger capacitances (lower  $I_D/W$ )
- ❑ The first non-dominant pole (mirror node) sets the ultimate GBW
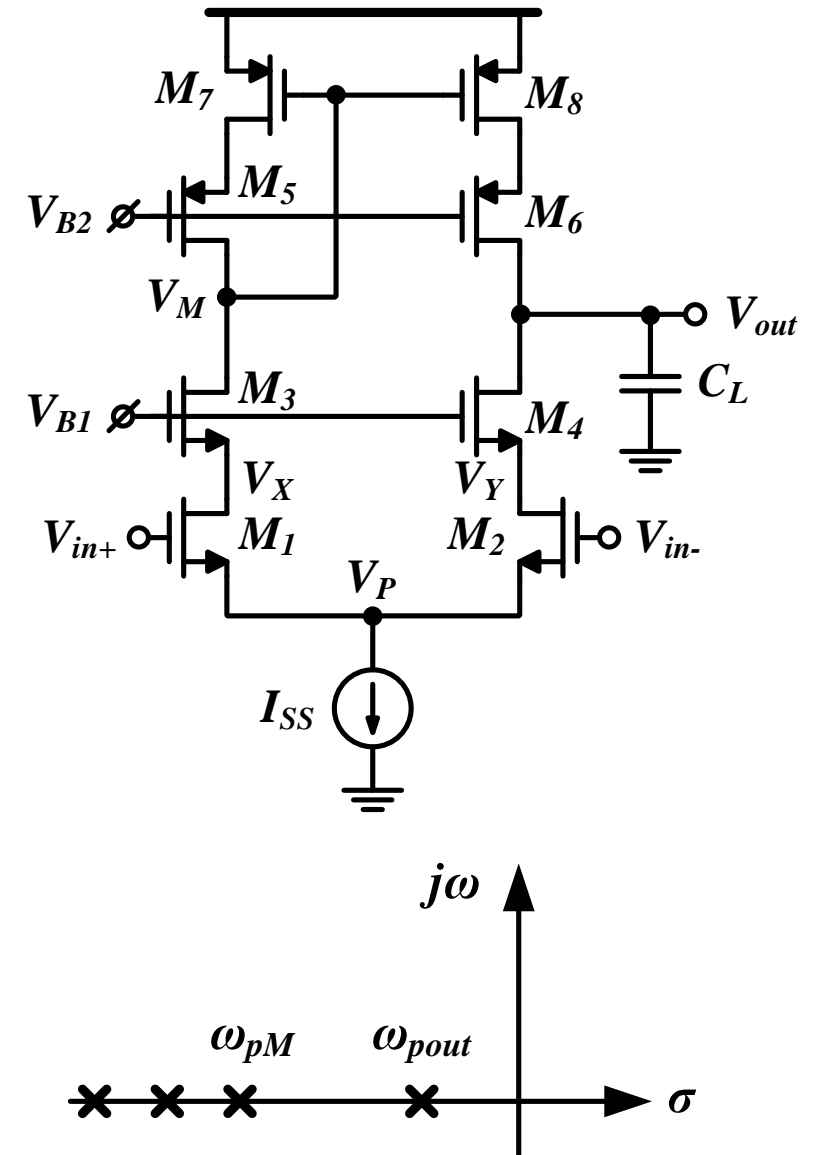
$$\omega_{p2} = \omega_{pM} \approx \frac{g_{m7}}{C_M} \sim \frac{\omega_T}{4}$$



# Folded Cascode

- ❑ Two possible implementations for SE output
- ❑ Compared to telescopic cascode:
  - More power ( $\sim 2x$ )
  - Lower gain ( $r_{o1} || r_{o2}$ )
  - More nodes/poles
  - More complex
  - But input and output ranges decoupled

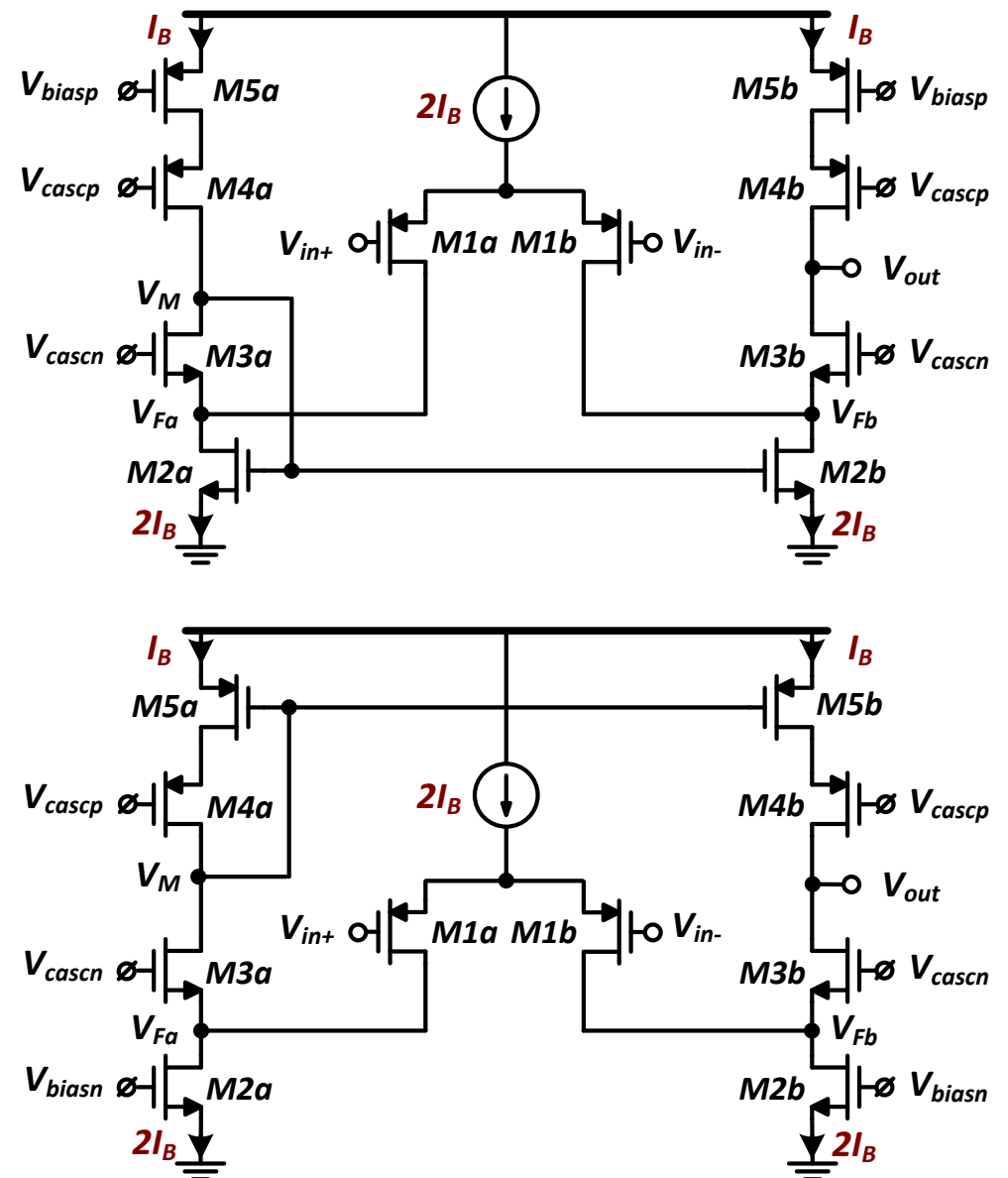

# Folded Cascode: Poles

- ❑  $\omega_{p1} \ll \omega_u < \omega_{p2}$
- ❑ The H.I.N. sets  $BW_{OL}$

$$\omega_{p1} = \omega_{pout} = \frac{1}{R_{out}C_{out}}$$

- ❑ The first non-dominant pole sets the ultimate GBW

- Mirror node ( $V_M$ )

$$\omega_{p2} = \omega_{pM} \approx \frac{g_{m5}}{C_M}$$


- Or folding node ( $V_F$ )

$$\omega_{p2} = \omega_{pF} \approx \frac{g_{m3}}{C_F}$$

- $V_{Fa}$  and  $V_{Fb}$  contribute a single pole



- ❏ Considerations:

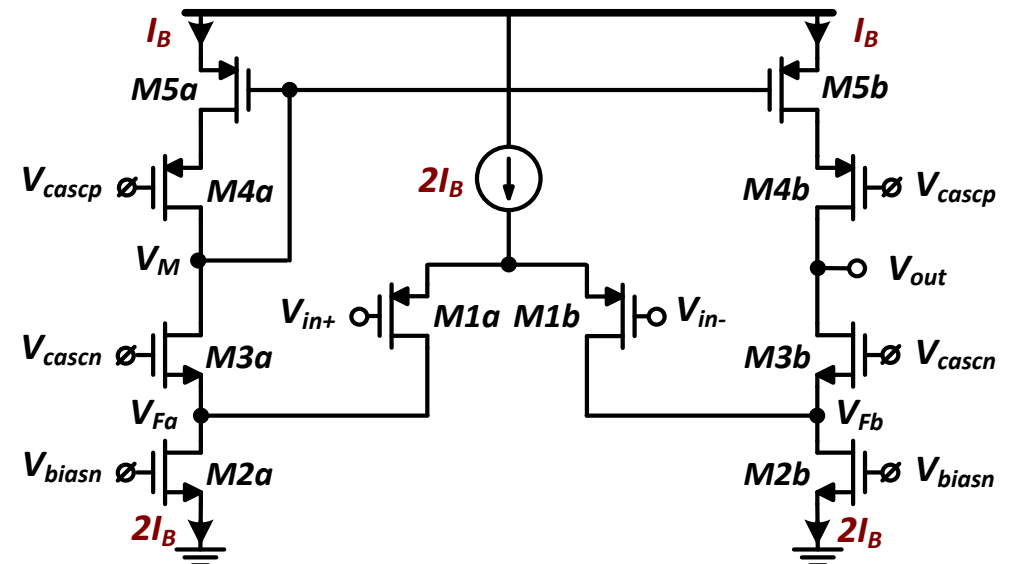- $C_{gs}$  larger than other caps
- PMOS larger than NMOS
- M2 has large capacitance (double the current)



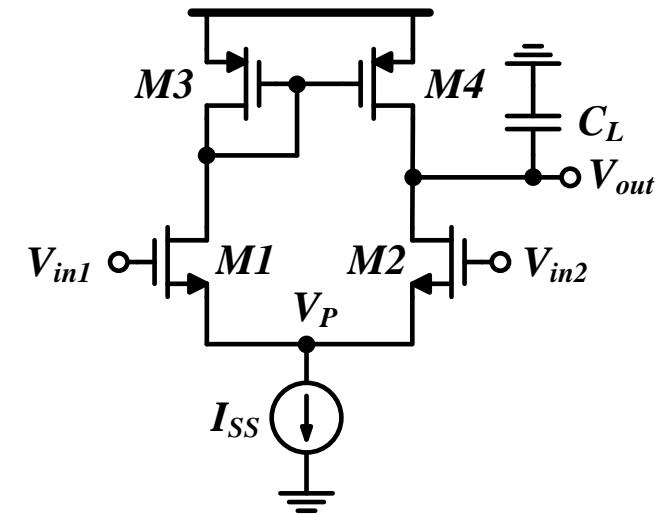
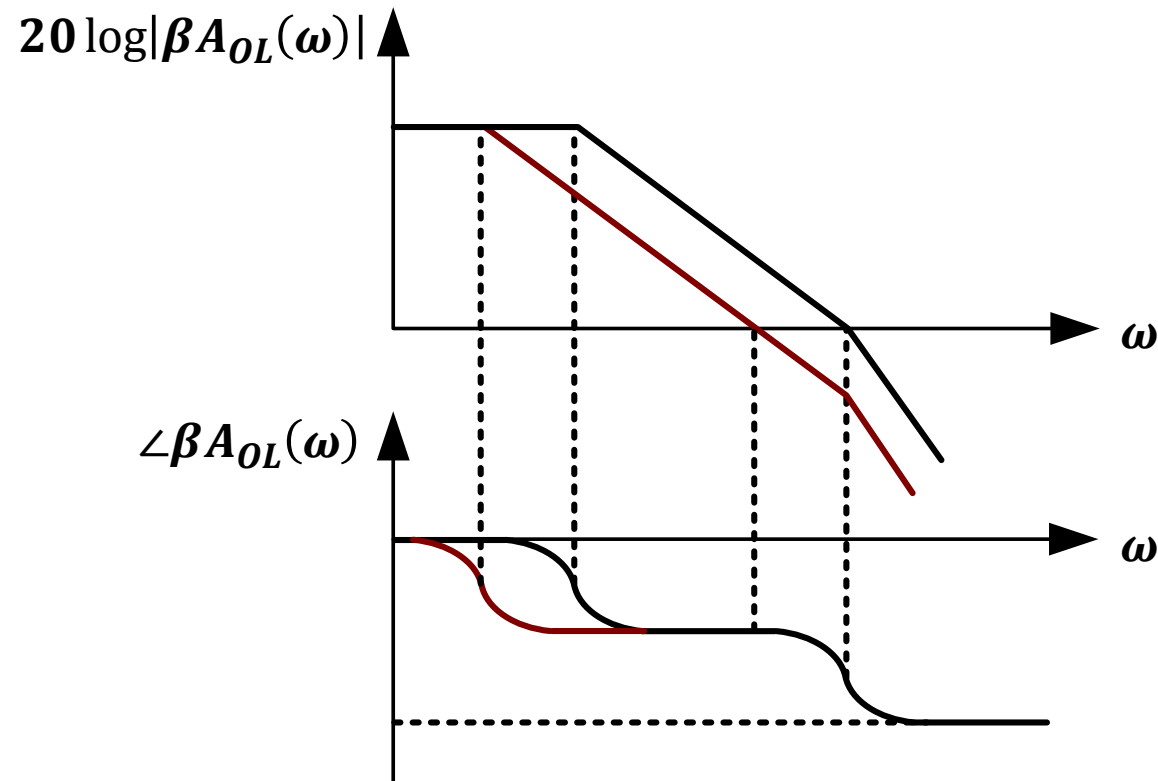
# Single-Stage OTAs: Compensation

- ❑ Push  $G_X / \omega_u / \omega_{p1}$  **inwards**: lower GBW
  - Increase  $C_L$
  - **Single-stage OTAs are compensated by large load capacitance**


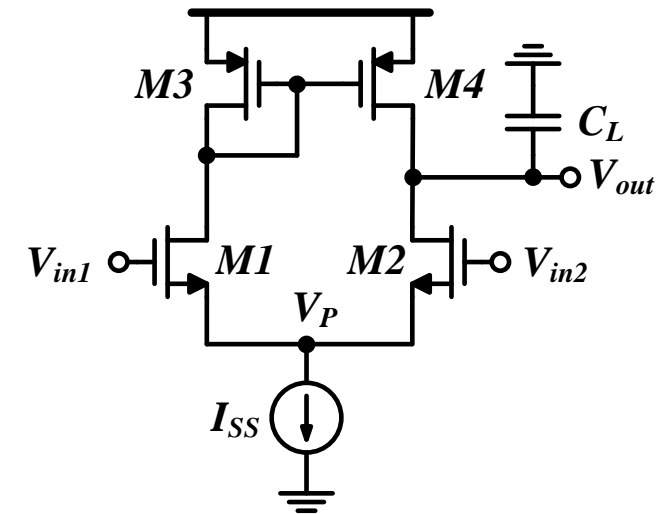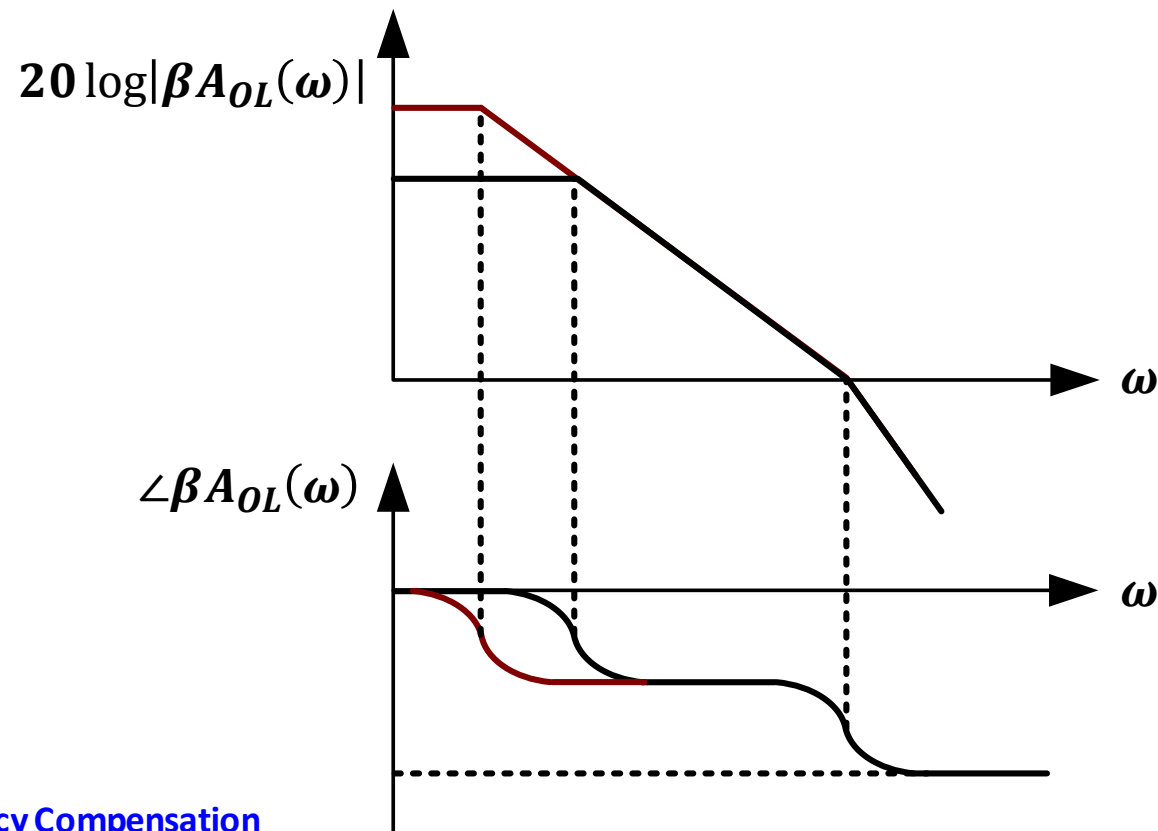
# Single-Stage OTAs: Compensation

- ❑ Push  $G_X / \omega_u / \omega_{p1}$  **inwards**: lower GBW
  - Increase  $C_L$
  - **Single-stage OTAs are compensated by large load capacitance**
- ❑ Increasing  $R_{out}$  does not affect PM




# Outline

---

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
  - Miller compensation
  - The feedforward zero

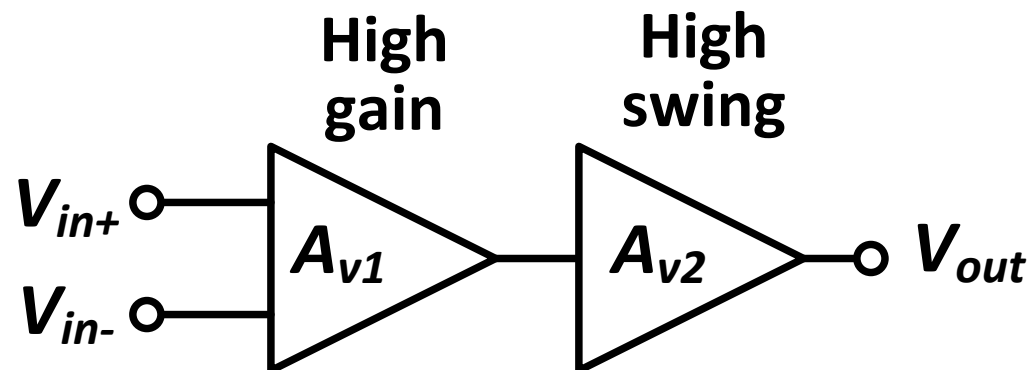
# Two-Stage OTA

- ❑ Isolates the gain and swing requirements
  - But much more power consumption
  - And complicates stability requirements
- ❑ Three-stage OTA exists, but quite difficult to stabilize
- ❑ First stage can be 5T-OTA or cascode
- ❑ Second stage is typically a simple common-source
  - Allows maximum output swing


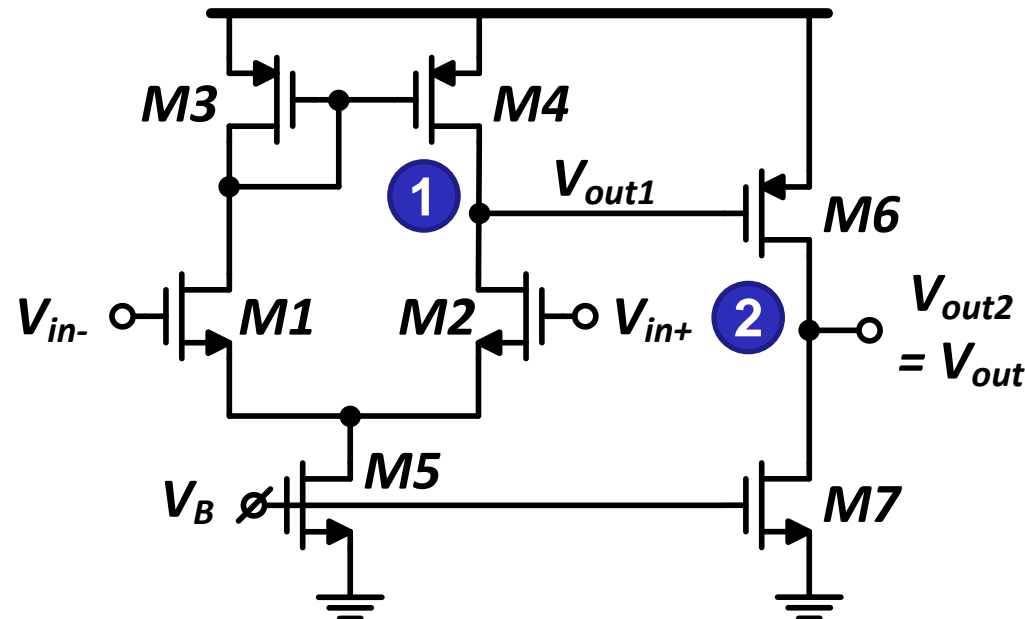
# Two-Stage OTA: Poles

- ❑ Two gain stages  $\rightarrow$  Two H.I.N.s
  - Two dominant poles!
- ❑ Internal pole:  $\omega_{p1} = \frac{1}{R_{out1}C_1}$
- ❑ Output pole:  $\omega_{p2} = \frac{1}{R_{out2}C_2}$







# Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
  - Miller compensation
  - The feedforward zero
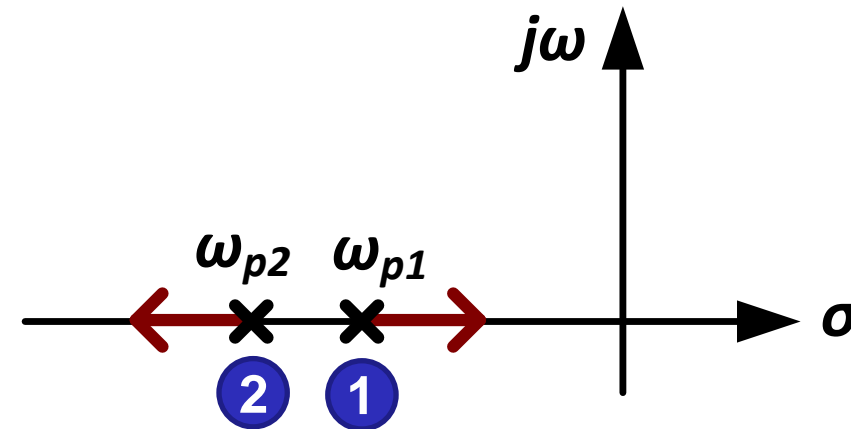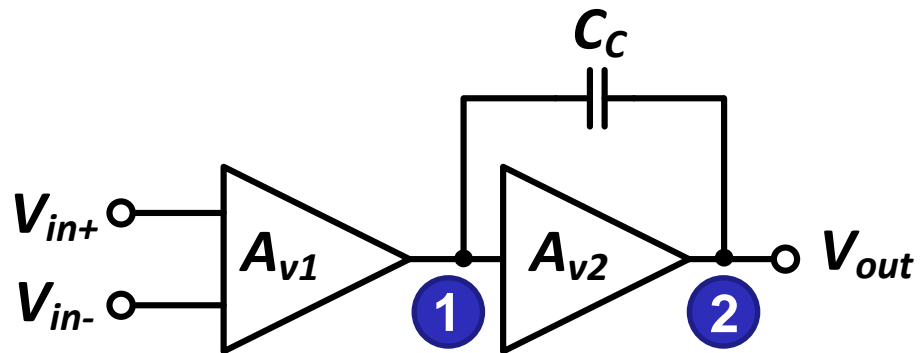
# Two-Stage OTA: Miller Compensation

- ❑ Exploit Miller capacitance multiplication
- ❑ Pole splitting
  - Push  $\omega_{p1}$  inwards  $\rightarrow$  push GX inwards
  - Push  $\omega_{p2}$  outwards  $\rightarrow$  push PX outwards



# CS HFR: Reminder

- ❑ Surprisingly, exact analysis gives a quite complex expression
  - See [Johns & Martin 2012] or [Razavi 2017]
- ❑ If dominant pole approximation is applied

$$\omega_{pd} \approx \frac{1}{b_1} = \frac{1}{R'_{sig}[C_{gs} + C_{gd}(1 + g_m R_{out})] + R_{out}(C_{out} + C_{gd})}$$

- Same result as OCTC (both based on same approximation)
- ❑ Additionally, dominant pole approx gives an expression for  $\omega_{pnd}$

$$\omega_{pnd} \approx \frac{1}{b_2 \omega_{p1}} = \frac{b_1}{b_2} = \frac{g_m C_{gd}}{C_{gd}(C_{gs} + C_{out}) + C_{gs} C_{out}}$$

- If a large cap is connected parallel to  $C_{gd}$ :  $\omega_{pnd} \approx \frac{g_m}{C_{gs} + C_{out}}$ 
    - Can be derived intuitively without analysis (how?)

# Two-Stage OTA: Miller Compensation



❑ Before compensation

$$\omega_{p1} = \frac{1}{R_{out1}C_1} \quad \& \quad \omega_{p2} = \frac{1}{R_{out2}C_2}$$

❑ After compensation: Pole splitting

$$\omega_{p1} \approx \frac{1}{R_{out1}[(G_{m2}R_{out2})C_C + C_1] + R_{out2}(C_2 + C_C)} \approx \frac{1}{R_{out1}(G_{m2}R_{out2})C_C}$$
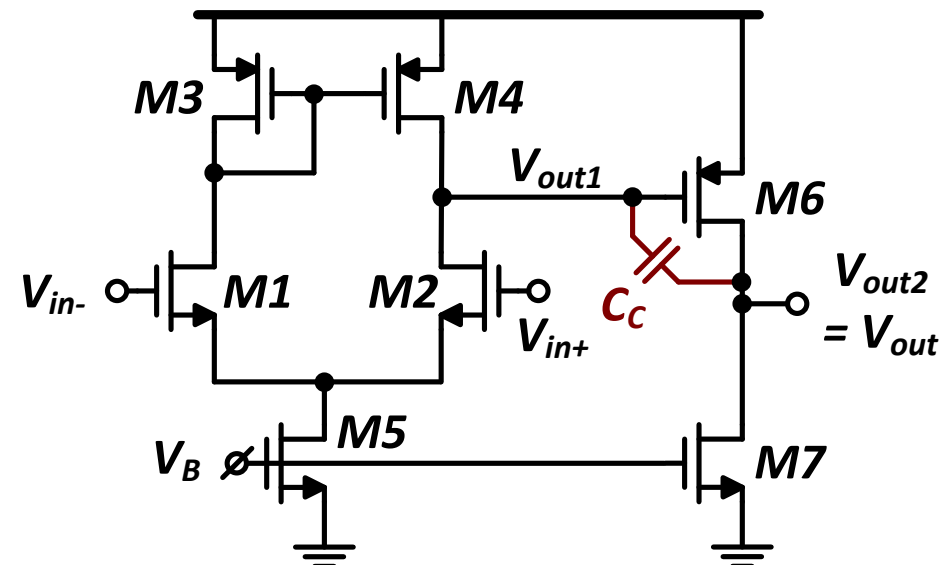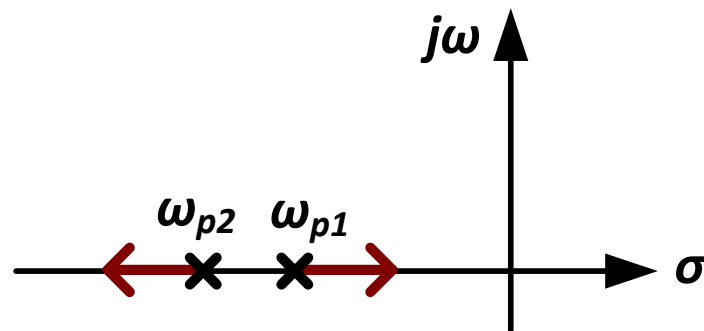
$$\omega_{p2} \approx \frac{G_{m2}C_C}{C_C(C_1 + C_2) + C_1C_2} \approx \frac{G_{m2}}{C_1 + C_2}$$



# Stability Requirement: $\omega_u$ and $\omega_{p2}$

$$\omega_{p1} \approx \frac{1}{R_{out1}(G_{m2}R_{out2})C_C}$$

$$\omega_{p2} \approx \frac{G_{m2}}{C_1 + C_2} \approx \frac{G_{m2}}{C_L}$$


$$GBW \approx G_{m1}R_{out1}G_{m2}R_{out2} \cdot \frac{1}{R_{out1}(G_{m2}R_{out2})C_C}$$

$$GBW = \omega_u \approx \frac{G_{m1}}{C_C}$$

□ For critical damped response:  $\zeta = 1$ ,

$Q = 0.5$ , and  $PM \approx 76^\circ$
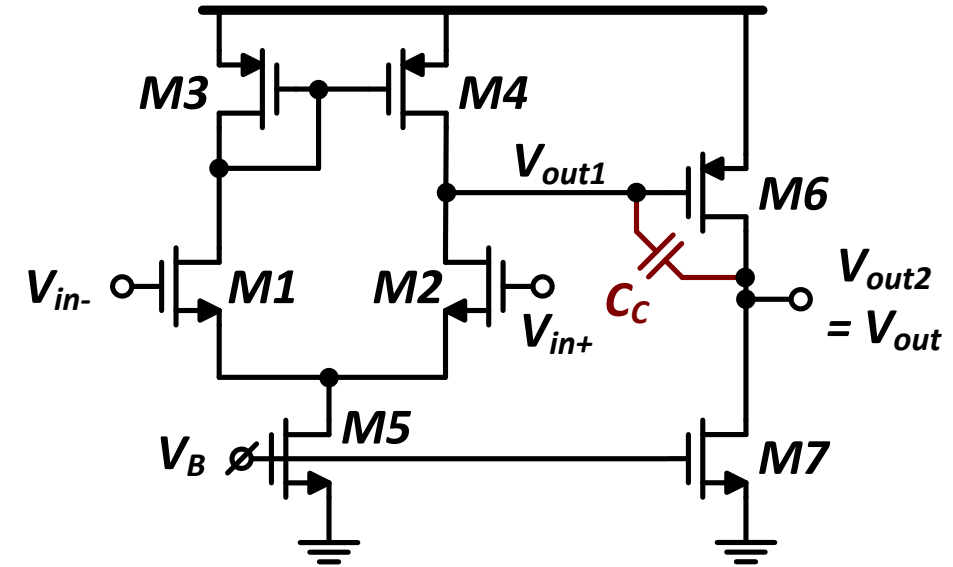
$$\omega_{p2} \approx 4\omega_u \rightarrow \frac{G_{m2}}{C_L} \approx \frac{4G_{m1}}{C_C}$$



# Bias Current in 1<sup>st</sup> and 2<sup>nd</sup> Stages

$$\frac{G_{m2}}{C_L} \approx \frac{4G_{m1}}{C_C}$$

- Assume  $C_L = 4pF$  and  $C_C = C_L/2 = 2pF$


$$\frac{G_{m2}}{G_{m1}} = 4 \times \frac{4}{2} = 8$$

- If both stages use the same gm/ID

- Note that  $I_{B1} = 2 \times I_{D1,2}$



$$\frac{I_{B2}}{I_{B1}} = 4$$

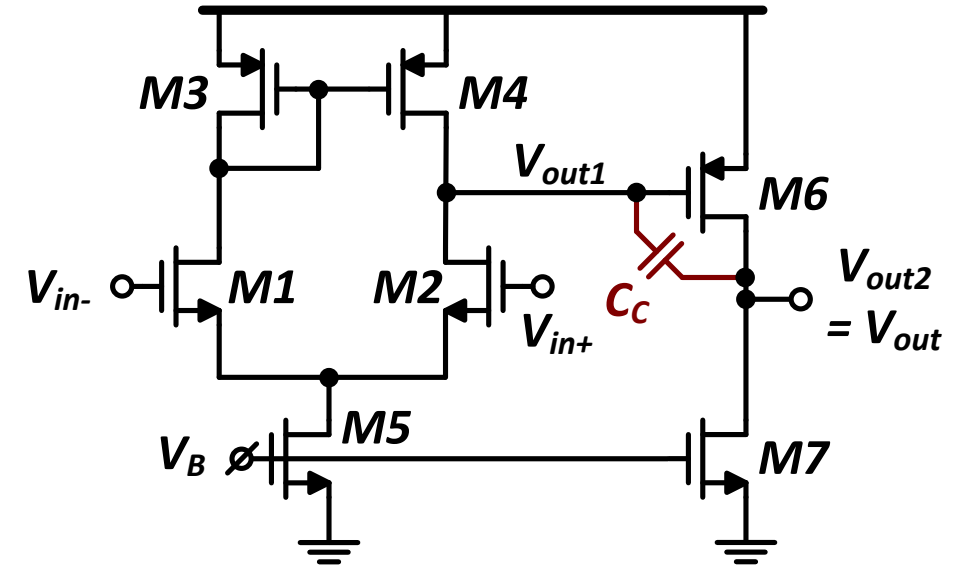- 80% of the power is consumed in the second stage to achieve stability
  - 80% of bias current do not contribute (directly) to GBW
  - Miller OTA is very energy inefficient!



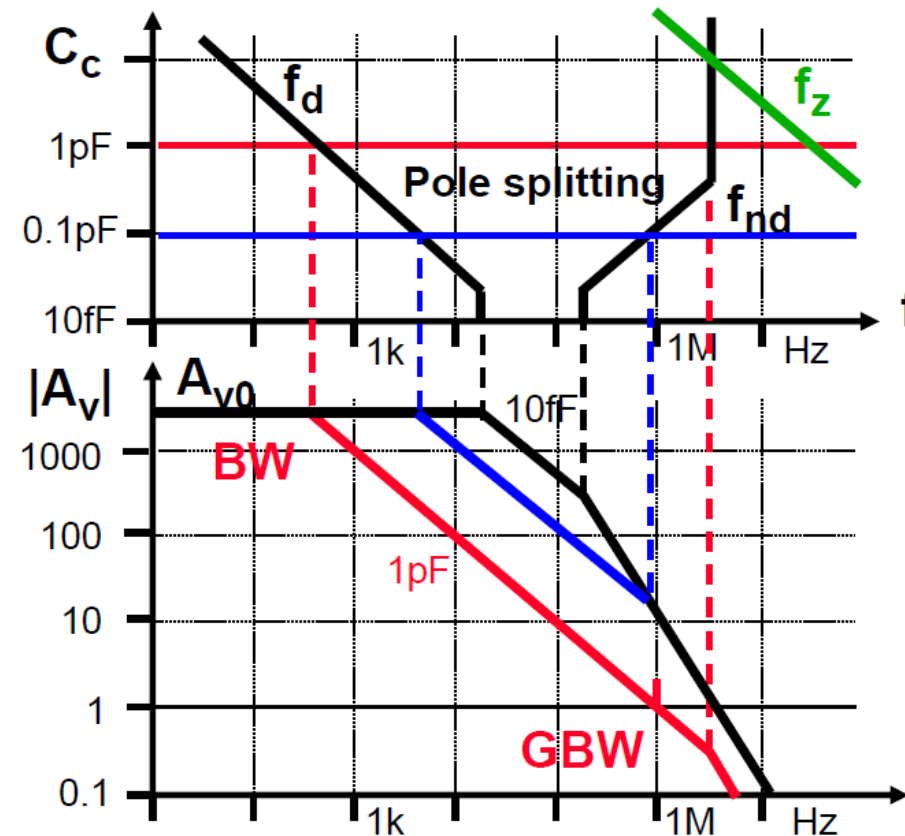
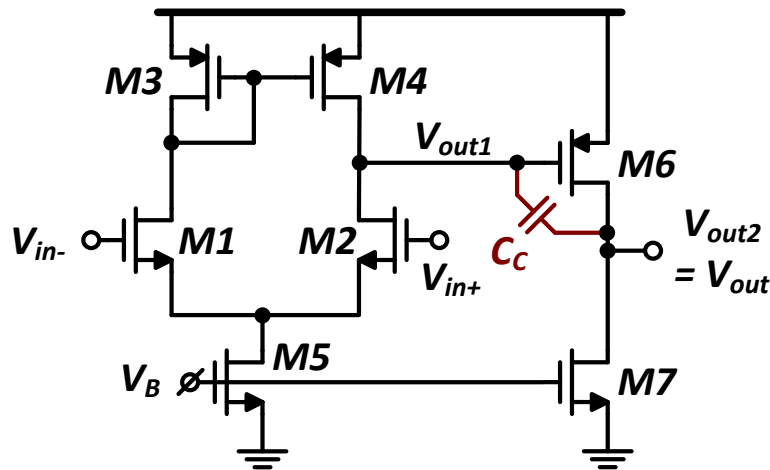
# Miller OTA: Pole Splitting with $C_C$

- ❑ Too large  $C_C$  does not give more pole splitting: just smaller GBW
  - Usually we choose  $C_1 < C_C < C_L$
  - Reasonable starting point:  $C_C \approx (0.3 \rightarrow 0.5) \times C_L$



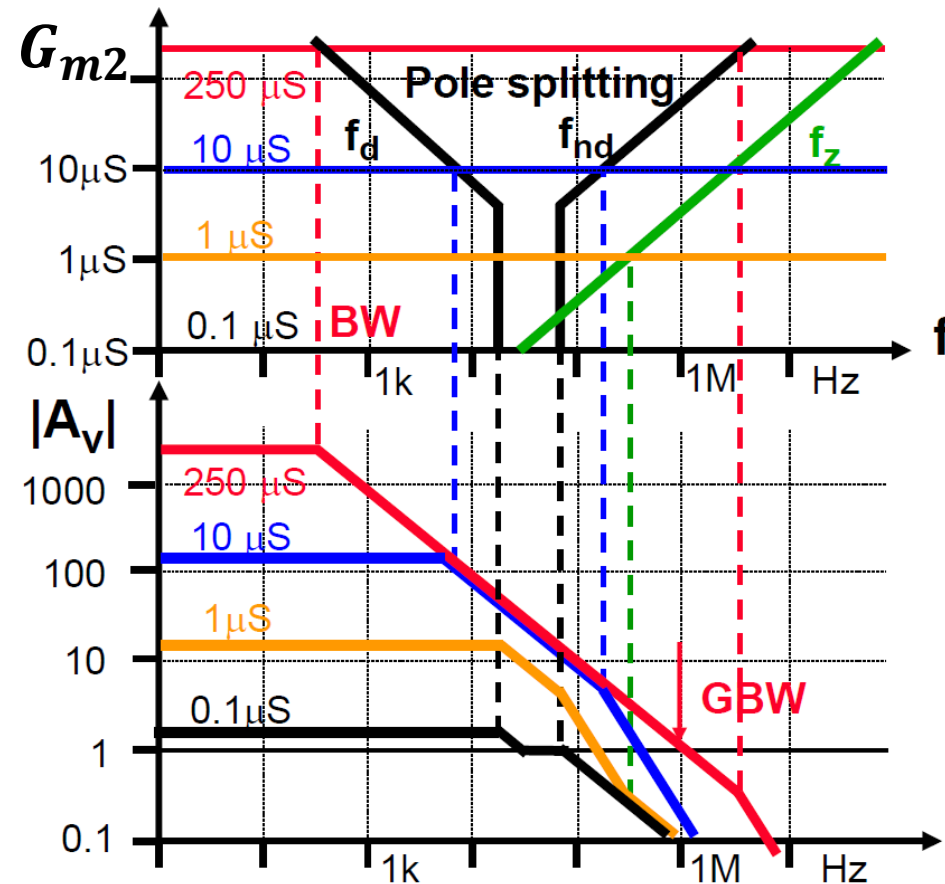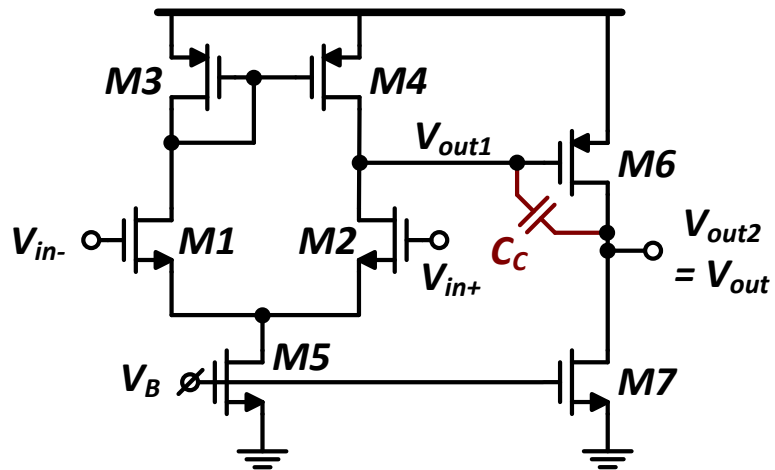
# Miller OTA: Pole Splitting with $G_{m2}$

- Increasing  $G_{m2}$  works even better than increasing  $C_c$ 
  - But more power consumption in the 2<sup>nd</sup> stage




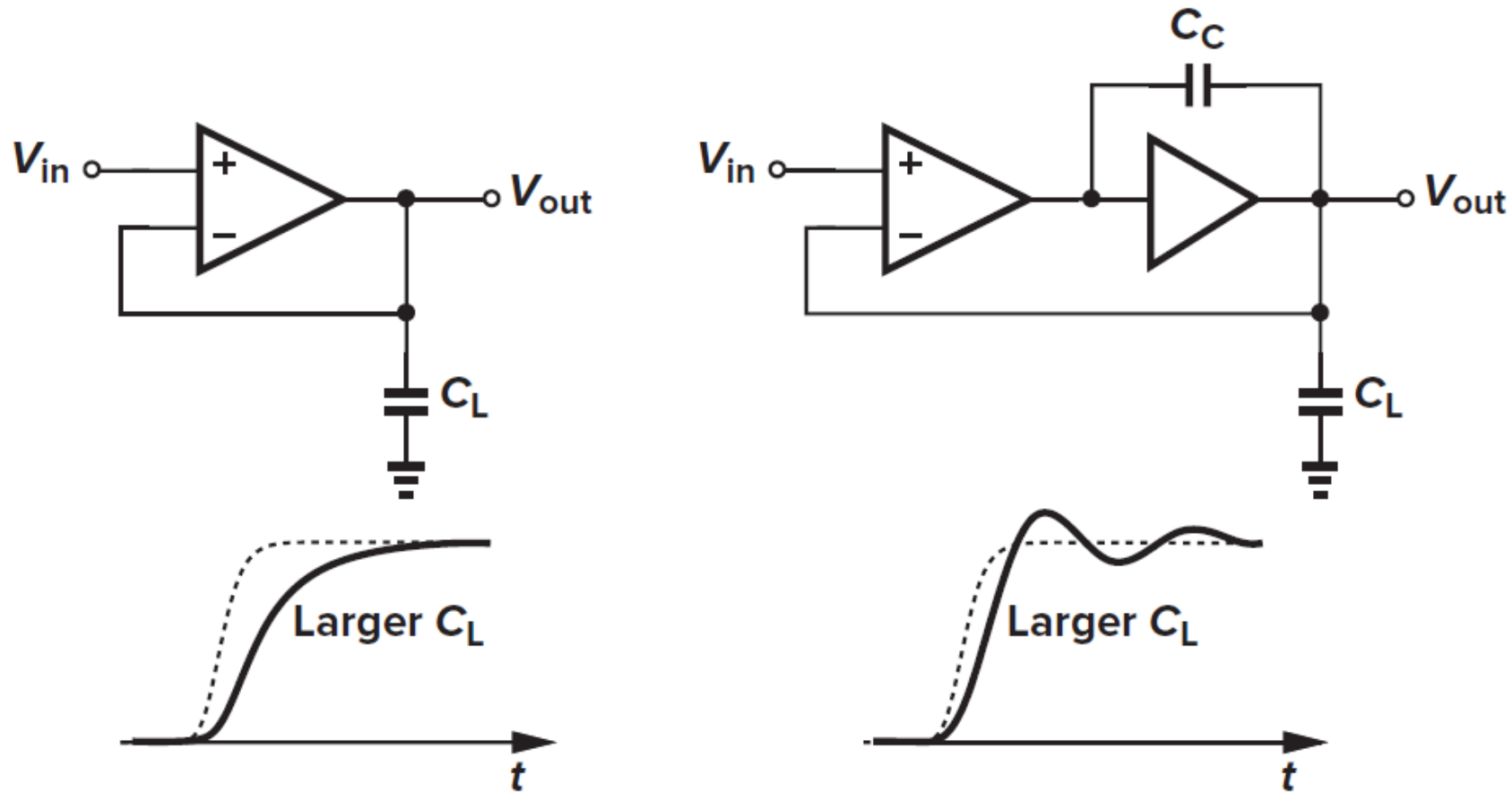
# Single vs Two-Stage OTA: Sensitivity to $C_L$



# Outline

- ❑ Recapping previous key results
- ❑ Frequency compensation
- ❑ Compensation of single-stage OTAs
- ❑ Compensation of two-stage OTA
  - Miller compensation
  - The feedforward zero

# The Feedforward Zero: **Reminder**

□  $v_{out} = 0 \rightarrow i_{out} = 0$



□  $v_{in} s C_F = -G_m v_{in}$

$$s_z = -\frac{G_m}{C_F}$$

□ LHP zero if  $G_m$  is +ve (e.g. CD)

□ **RHP zero if  $G_m$  is -ve (e.g. CS)**

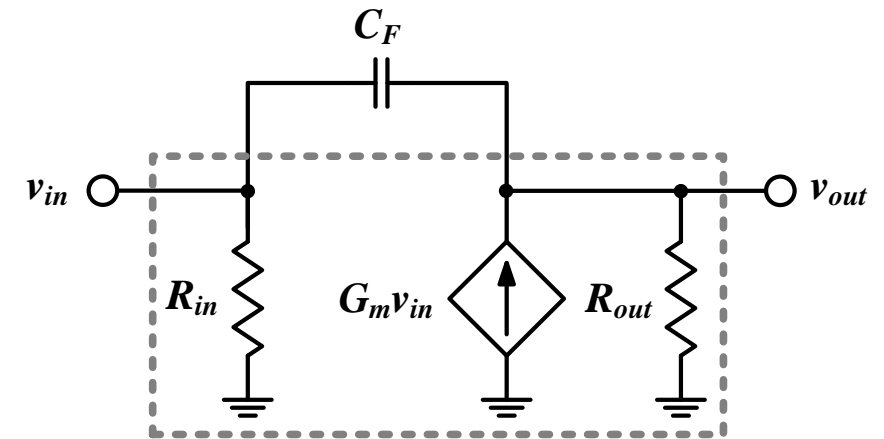
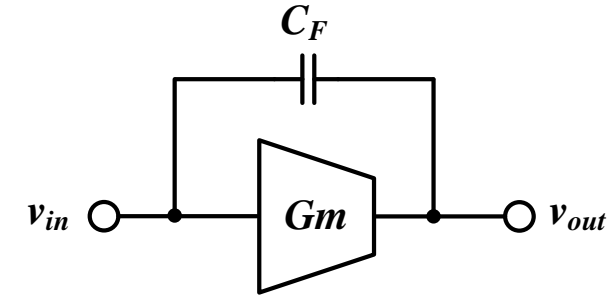
- Mag inc and phase drops
- Very bad for FB loop stability


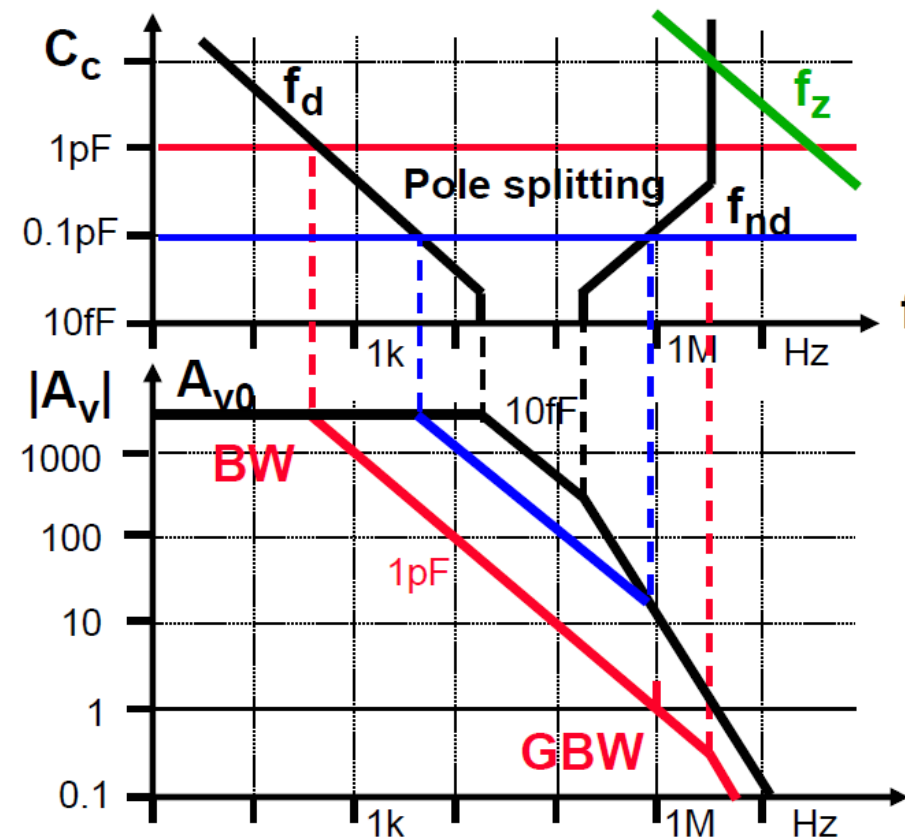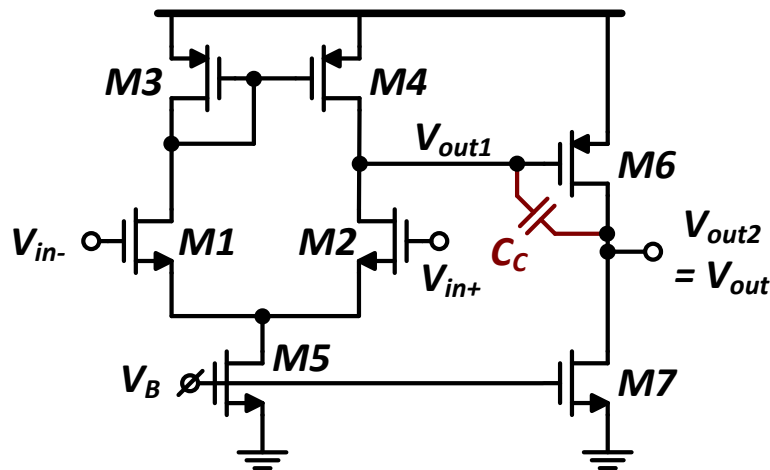
# Miller OTA: The RHP Zero

- ❑ RHP zero is bad for both magnitude and phase
  - Pushes GX outwards and pushes PX inwards
  - Increasing  $C_C$  may hurt stability!

$$\omega_z = \frac{g_{m6}}{C_C + C_{gd}} \approx \frac{G_{m2}}{C_C}$$




# Handling the RHP Zero

- Add a resistance to control the value of the zero (other tricks exist)

$$\frac{v_{out1}}{R_Z + \frac{1}{s_Z C_C}} = g_{m6} v_{out1}$$
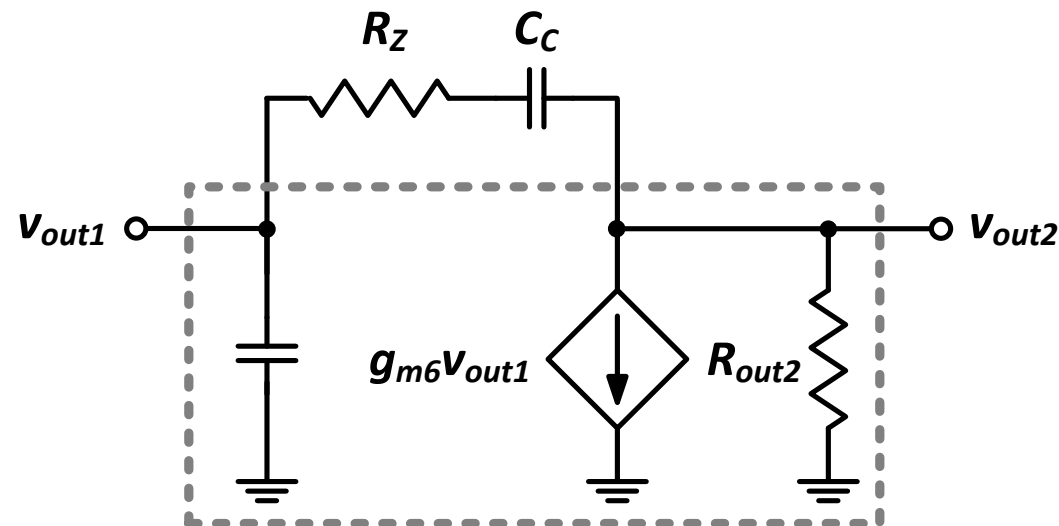
$$s_Z = \frac{1}{C_C \left( \frac{1}{g_{m6}} - R_Z \right)}$$



# Miller Zero Placement

- Place the zero at  $\infty$

$$\omega_z = \frac{1}{C_C \left( \frac{1}{G_{m2}} - R_Z \right)} \rightarrow R_Z = \frac{1}{G_{m2}}$$


- Some designers try to move the zero to the LHP to cancel the first non-dominant pole and/or improve the PM

$$\frac{1}{C_C \left( R_Z - \frac{1}{G_{m2}} \right)} = \frac{G_{m2}}{C_L} \rightarrow R_Z = \frac{C_L + C_C}{G_{m2} C_C}$$

- Practically never achieved due to variations
- Actually does not lead to faster response (why?)
- Pushing the LHP zero to lower frequencies is even worse
  - Very poor settling time (a.k.a. pole-zero doublet)
  - Noise amplification

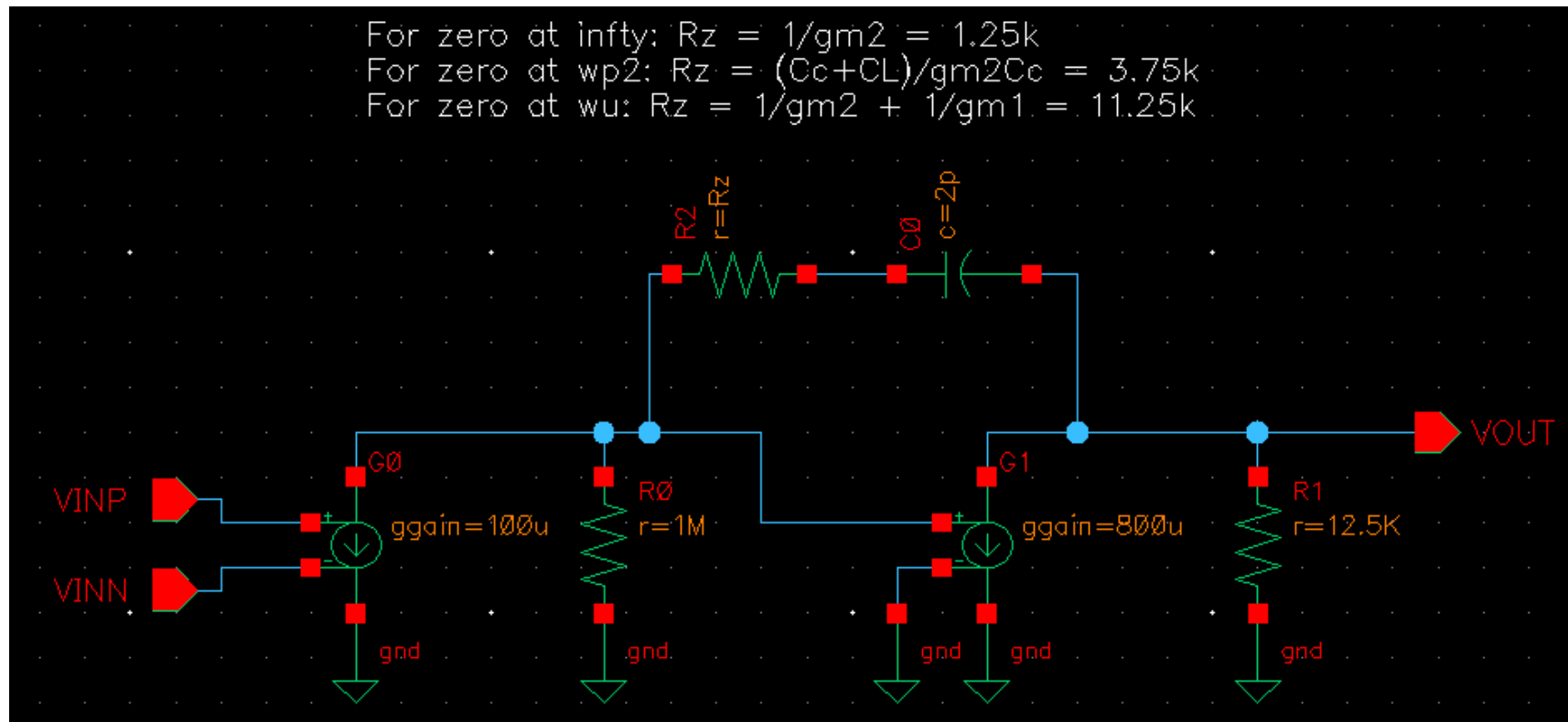
# Miller OTA Behavioral Model

- Try three different strategies for Miller zero placement
  - $\infty$
  - Cancel  $\omega_{p2}$
  - At  $\omega_u$  (this is a designer mistake rather than a valid strategy!)




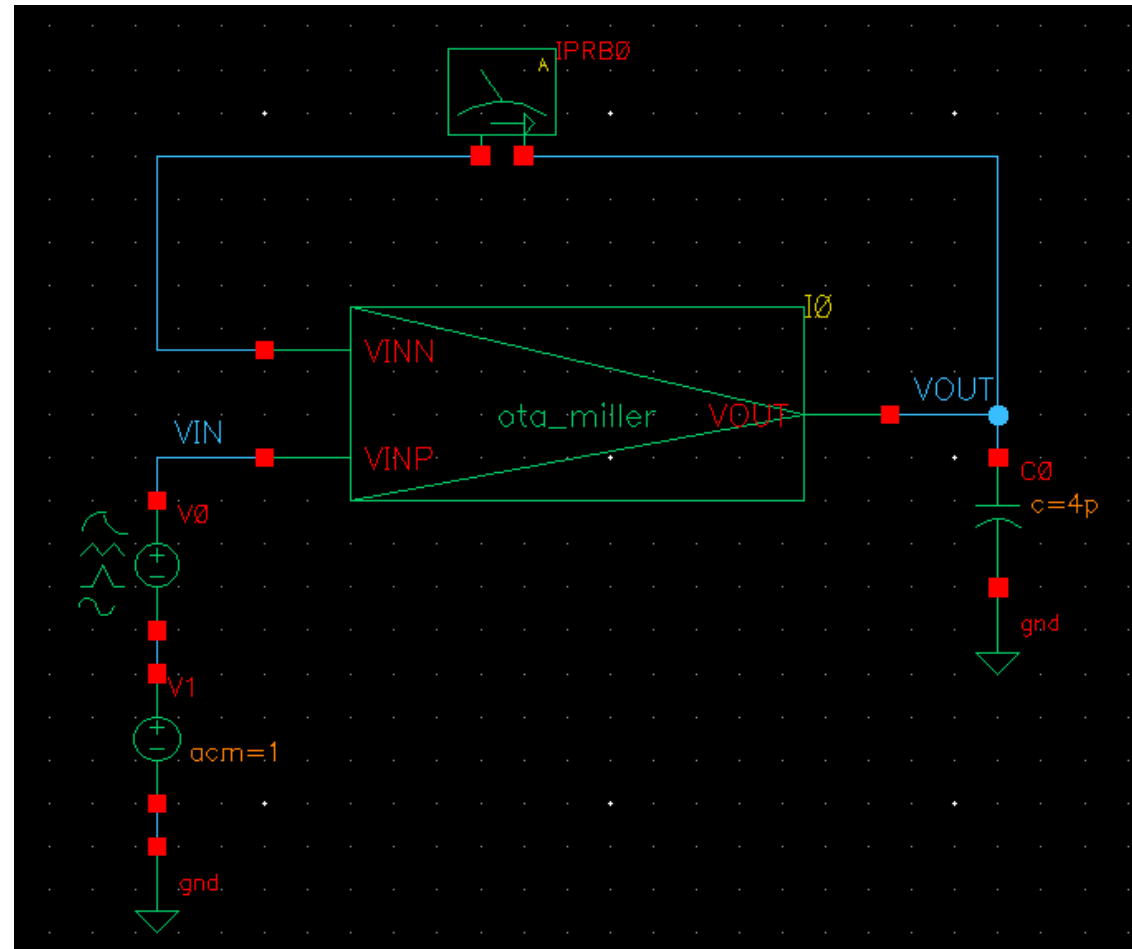
# TB for LG and Step Response

- Verify stability, ac response, and transient response in unity-gain buffer configuration.






# LG and Step Response

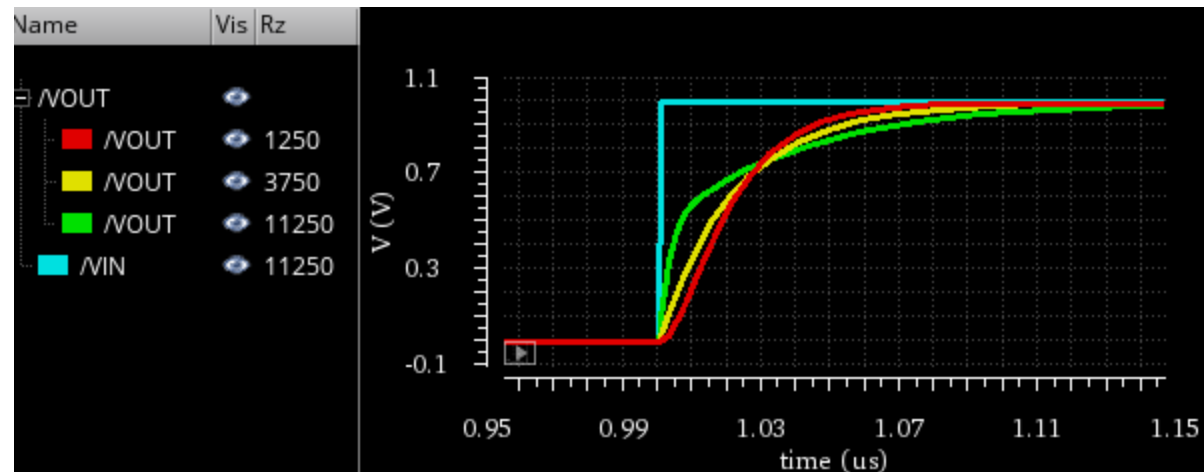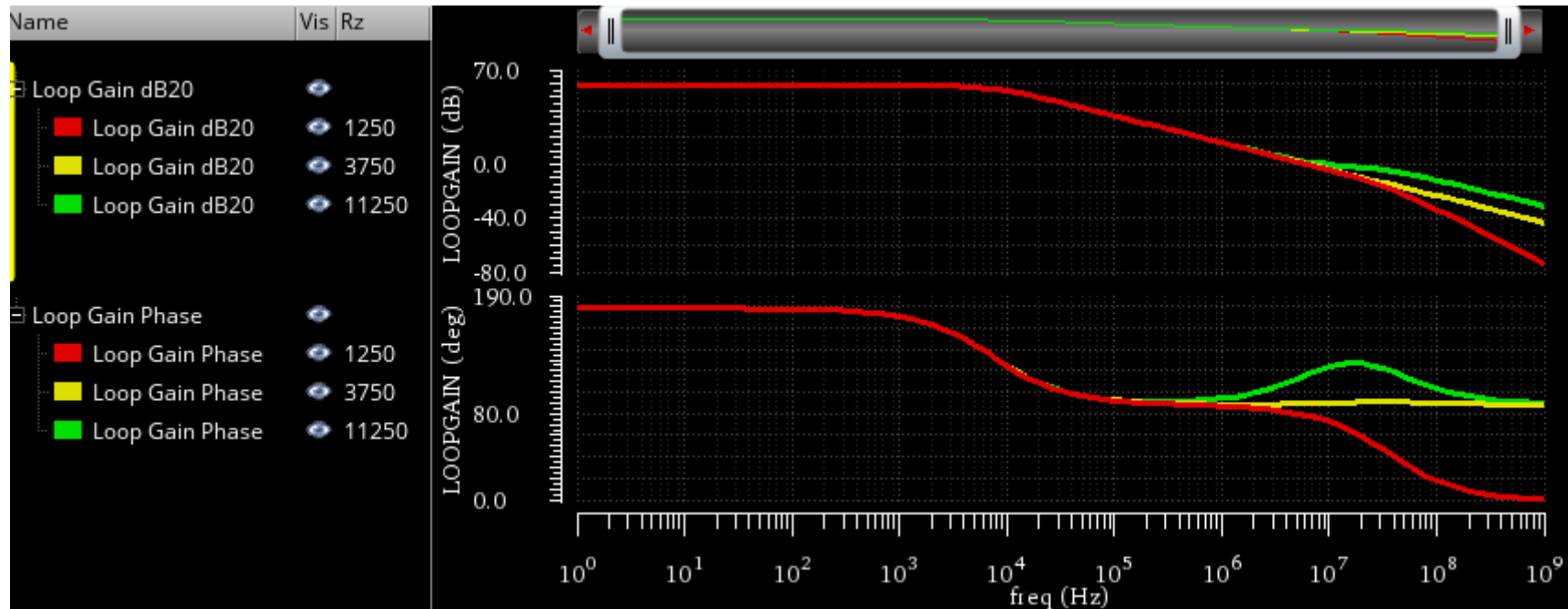


# LG and CL Gain

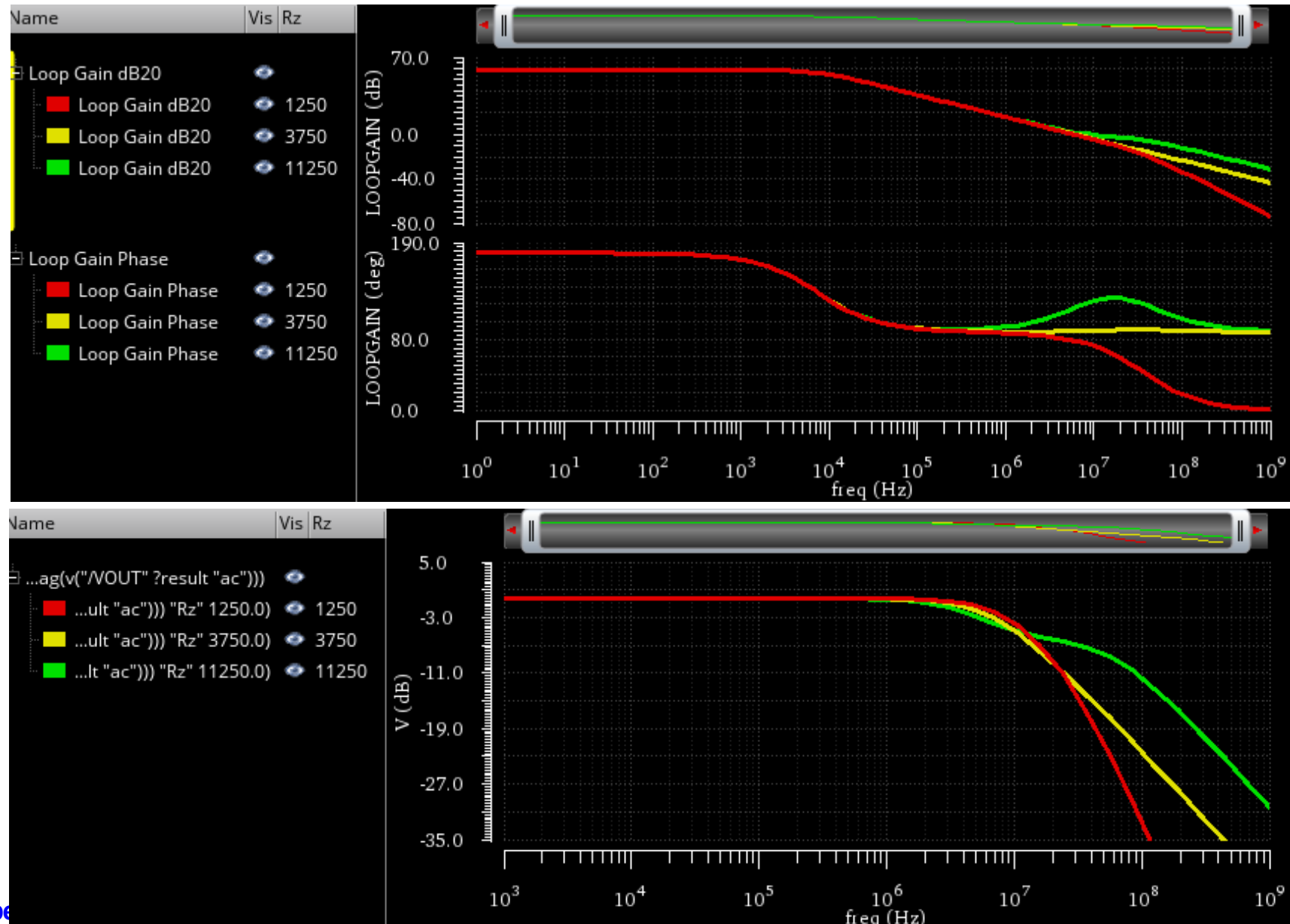
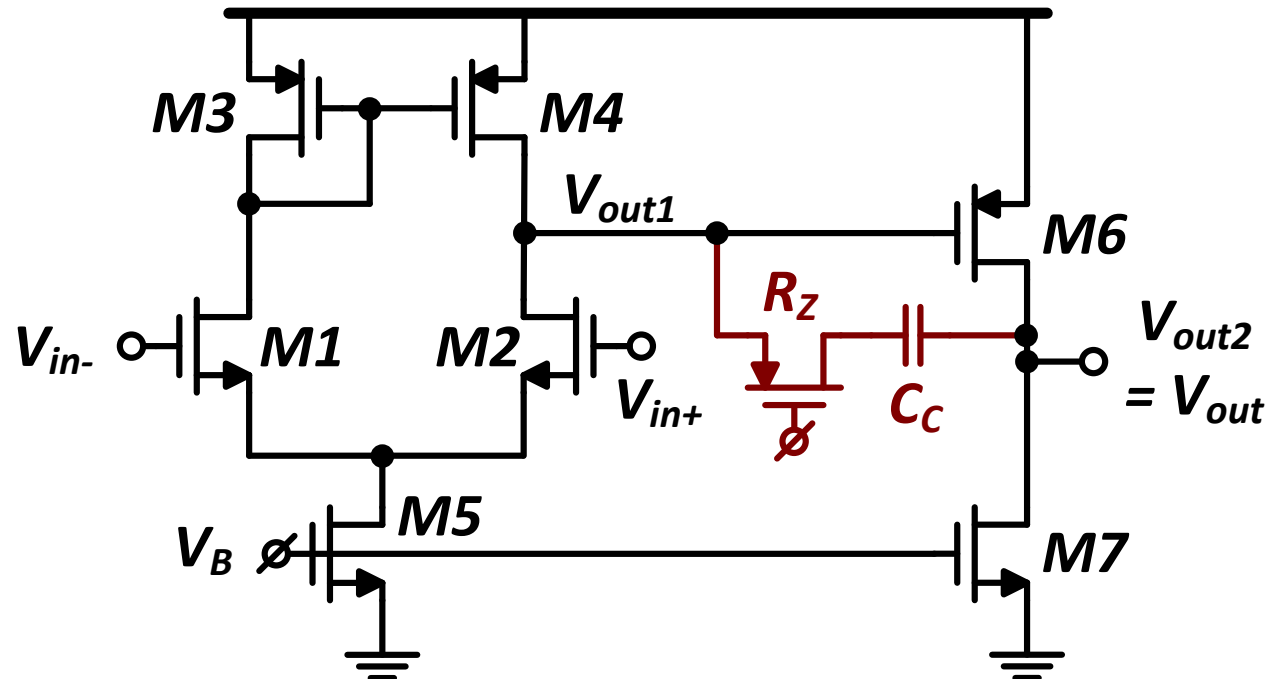
# $R_Z$ Implementation

- $R_Z$  can be implemented as a simple resistor or using a transistor in the linear region
  - Clever biasing can make it track variations (maintain  $R_Z \approx \frac{1}{g_{m6}}$ )
  - Why  $R_Z$  is implemented as PMOS?



---

**Thank you!**

# References

- ❑ A. Sedra and K. Smith, “Microelectronic Circuits,” Oxford University Press, 7<sup>th</sup> ed., 2015
- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2<sup>nd</sup> ed., 2017.
- ❑ W. Sansen, “Analog design essentials,” Springer, 2006.
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” 2<sup>nd</sup> ed., Wiley, 2012.
- ❑ B. Murmann, EE214 Course Reader, Stanford University.