

Analog IC Design

Lecture 06 Basic Amplifier Stages

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Outline

- ❑ Recapping previous key results
- ❑ Why amplifiers?
- ❑ Basic amplifier operation
- ❑ Basic amplifier analysis
- ❑ R_{in}/R_{out} shortcuts
 - Looking from drain
 - Looking from source
- ❑ GmRout method
- ❑ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ❑ Large signal behavior

Outline

- ❑ Recapping previous key results
- ❑ Why amplifiers?
- ❑ Basic amplifier operation
- ❑ Basic amplifier analysis
- ❑ R_{in}/R_{out} shortcuts
 - Looking from drain
 - Looking from source
- ❑ GmRout method
- ❑ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ❑ Large signal behavior

MOSFET in Saturation




- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \quad OR \quad V_{DS} \geq V_{ov}$$


- ❑ Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
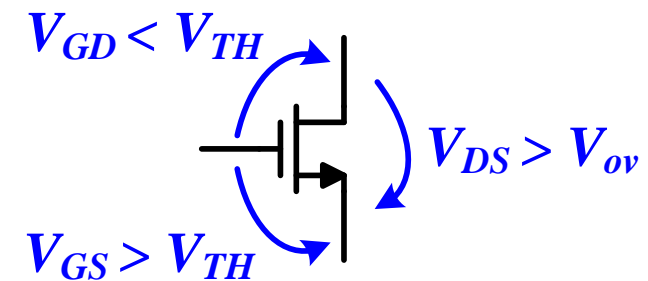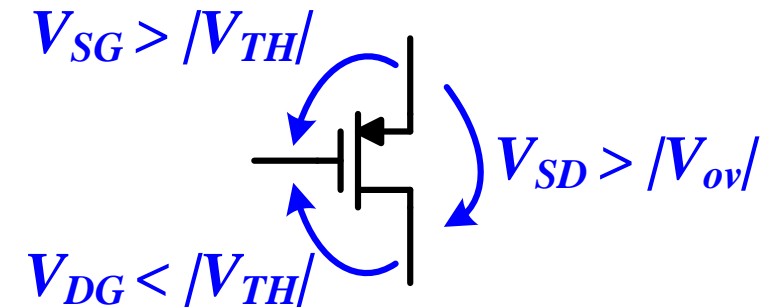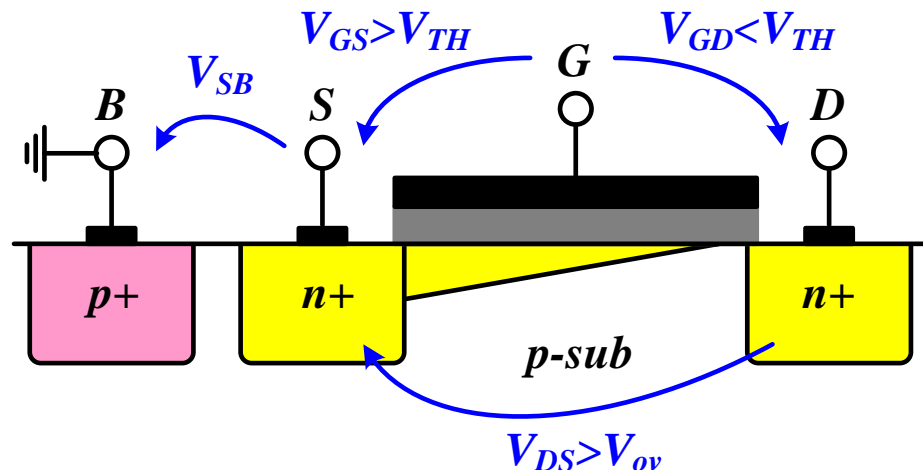
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$



Regions of Operation Summary

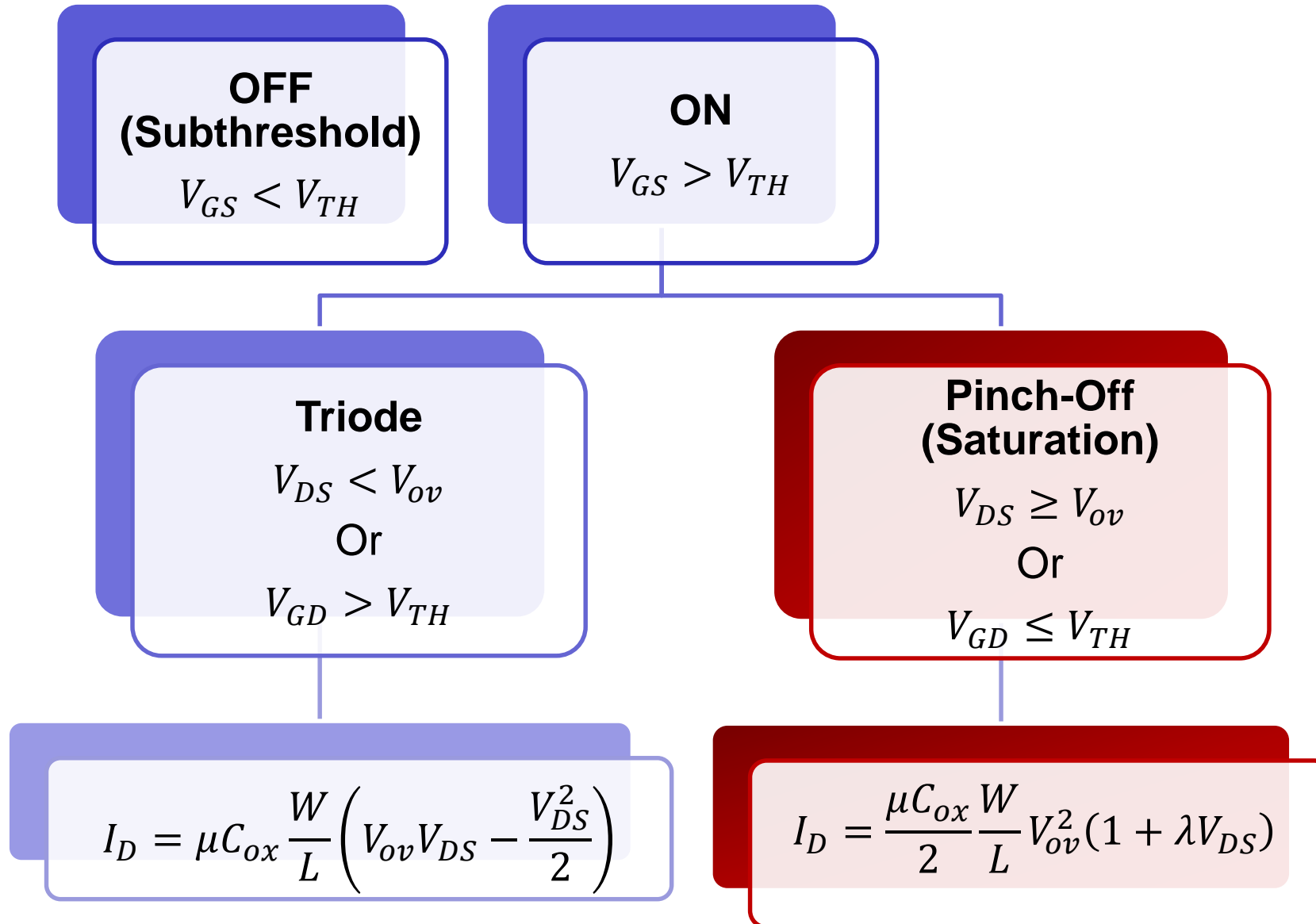


Low-Frequency Small-Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$
$$g_{mb} = \eta g_m \quad \eta \approx 0.1 - 0.25$$

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D}$$

$$V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L}$$

$$V_{DS} \uparrow \quad V_A \uparrow$$

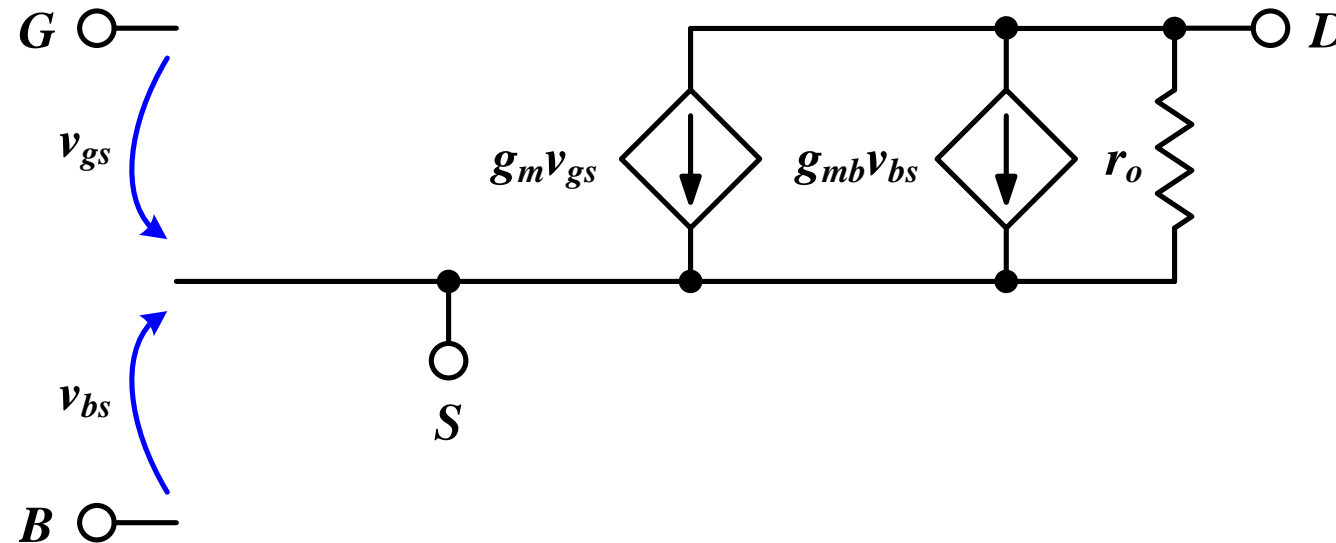


Outline




- ❑ Recapping previous key results
- ❑ Why amplifiers?
- ❑ Basic amplifier operation
- ❑ Basic amplifier analysis
- ❑ Rin/out shortcuts
 - Looking from drain
 - Looking from source
- ❑ GmRout method
- ❑ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ❑ Large signal behavior

Why Amplifiers?

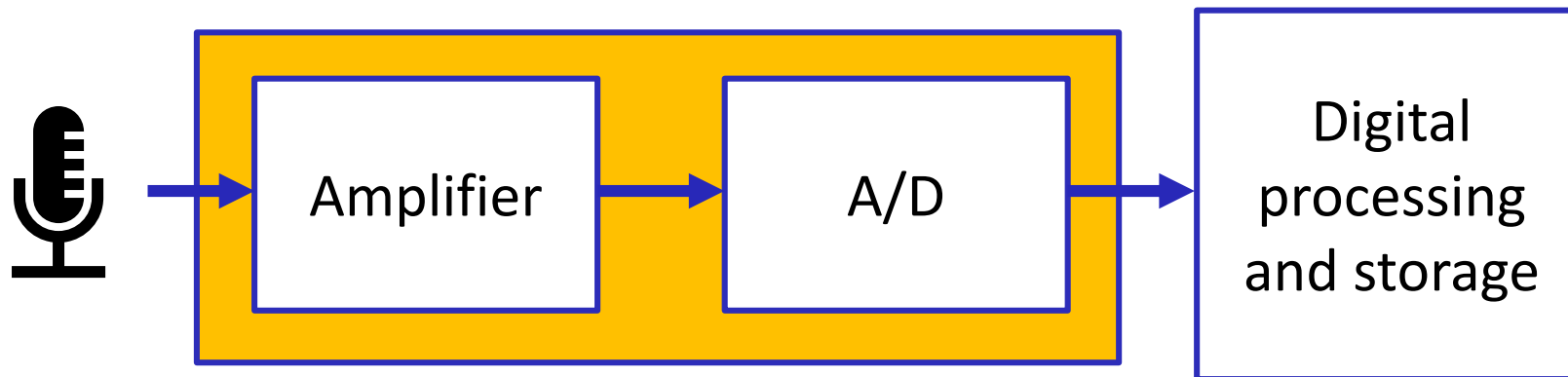- ❑ All the physical signals in the world around us are analog
 - Voice, light, temperature, pressure, etc.
- ❑ We (will) always need an “analog” interface circuit to connect between our physical world and our digital electronics
- ❑ The physical signals are usually very weak
 - They must be amplified before any kind of processing
- ❑ Amplifiers are also needed in many other applications




Basic MOSFET Amplifier Topologies
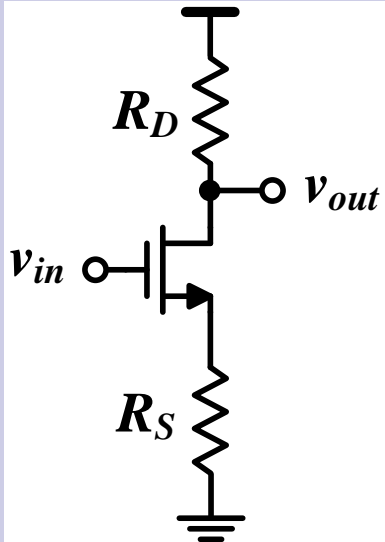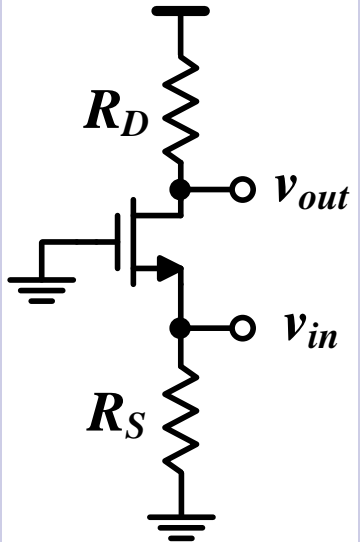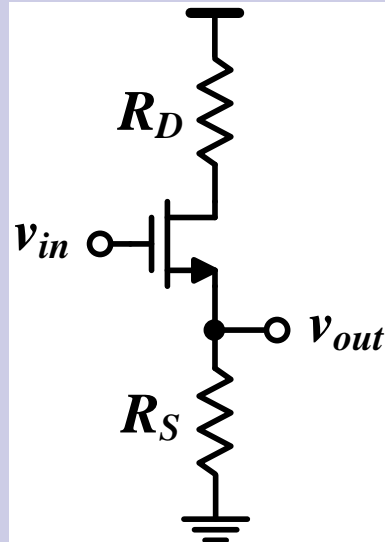
| | Common Source (CS) | Common Gate (CG) | Common Drain (CD) Source Follower (SF) |
|-----|---|---|---|
| |  |  |  |
| | Voltage & current amplifier | Voltage amplifier Current buffer | Voltage buffer Current amplifier |
| In | G | S | G |
| Out | D | D | S |


Outline

- ☐ Recapping previous key results
- ☐ Why amplifiers?
- ☒ **Basic amplifier operation**
- ☐ Basic amplifier analysis
- ☐ Rin/out shortcuts
 - Looking from drain
 - Looking from source
- ☐ GmRout method
- ☐ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ☐ Large signal behavior

CS Amplifier Example

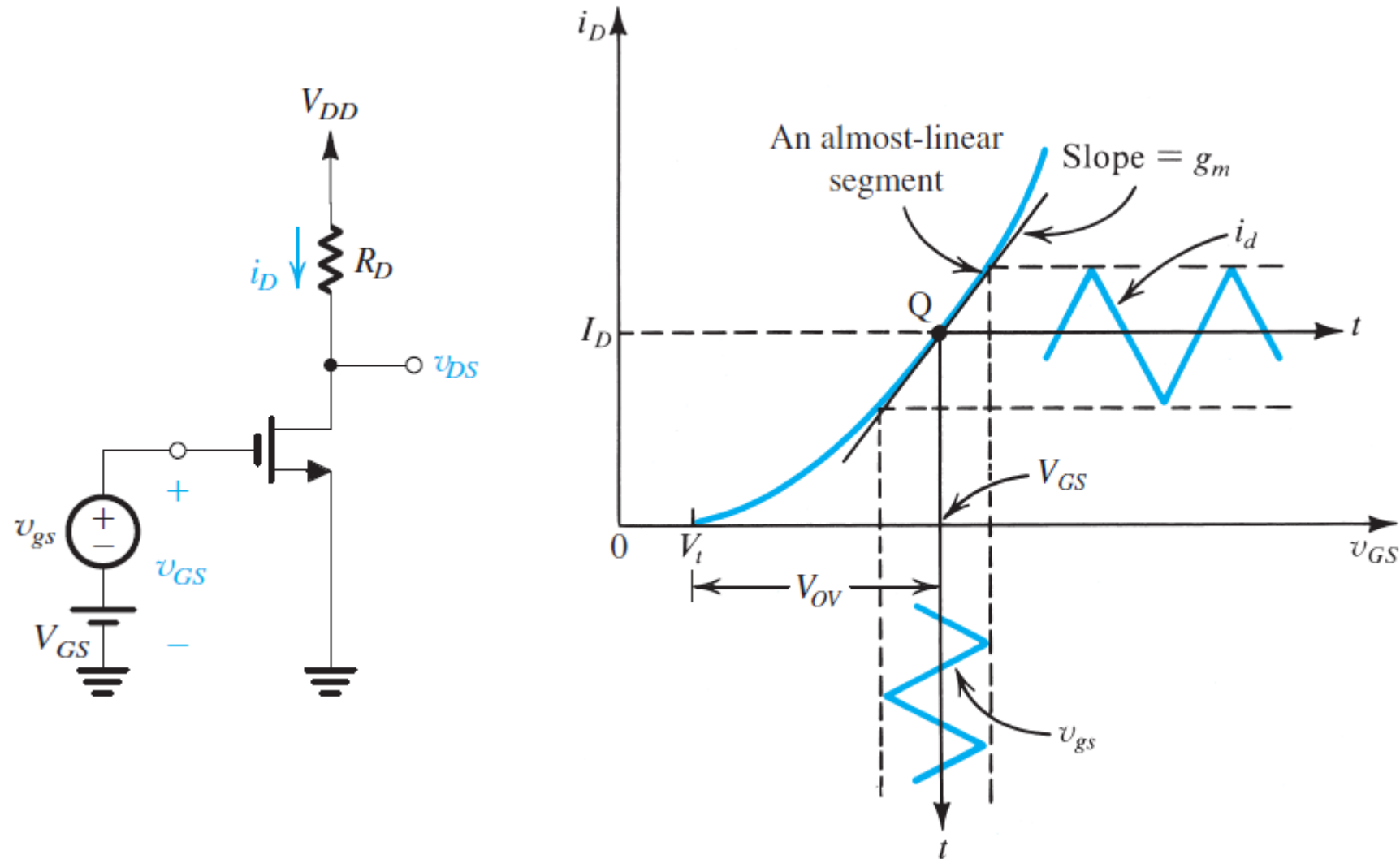

CS Amplifier Example

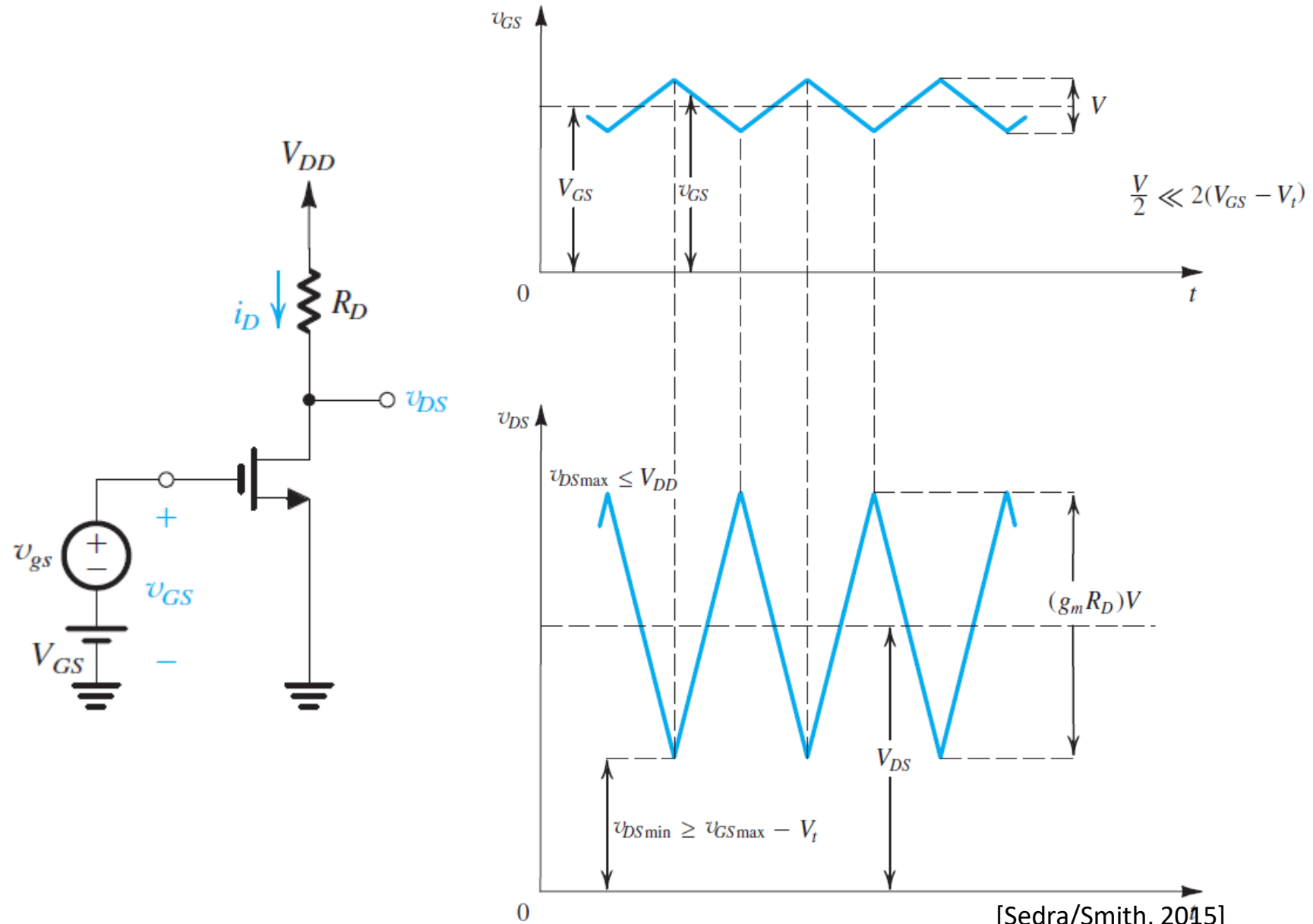


Outline

- ❑ Recapping previous key results
- ❑ Why amplifiers?
- ❑ Basic amplifier operation
- ❑ **Basic amplifier analysis**
- ❑ Rin/out shortcuts
 - Looking from drain
 - Looking from source
- ❑ GmRout method
- ❑ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ❑ Large signal behavior

Amplifier Analysis Steps

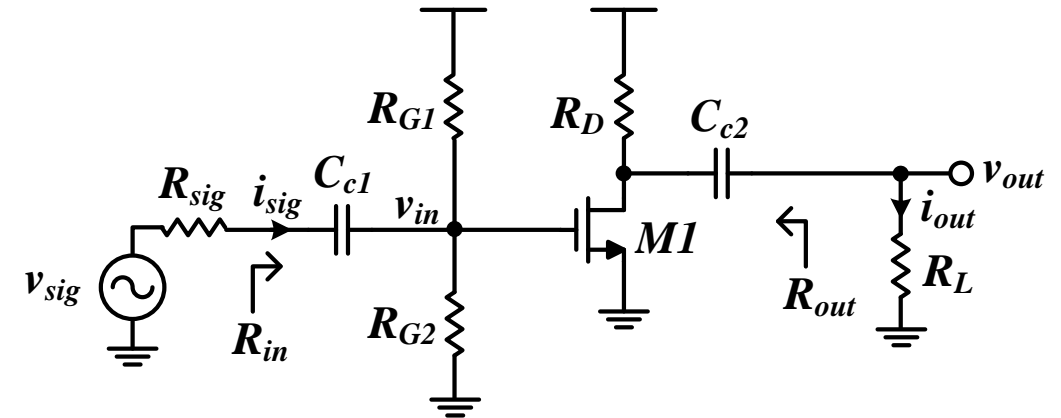1. DC analysis
 - Coupling and bypass capacitors \rightarrow open-circuit (o.c)
 - Calculate Q-point and check operation in saturation
($V_{DS} > V_{ov}$)
2. Calculate small signal parameters (g_m, r_o)
3. Draw the small signal equivalent circuit
 - DC voltage source \rightarrow short-circuit (s.c.)
 - DC current source \rightarrow open-circuit (o.c.)
 - Coupling and bypass capacitors \rightarrow short-circuit (s.c)
4. Determine the amplifier parameters
 - Input resistance and output resistance
 - Voltage gain and current gain




Amplifier Parameters

$$\square R_{in} = \frac{v_{in}}{i_{in}} = \frac{v_{in}}{i_{sig}}$$

$$\square R_{out} = \frac{v_x}{i_x} @ v_{sig} = 0$$

$$\square \text{Voltage gain} = A_v = \frac{v_{out}}{v_{sig}} = \frac{v_{in}}{v_{sig}} \cdot \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_{sig} + R_{in}} \cdot \frac{v_{out}}{v_{in}}$$
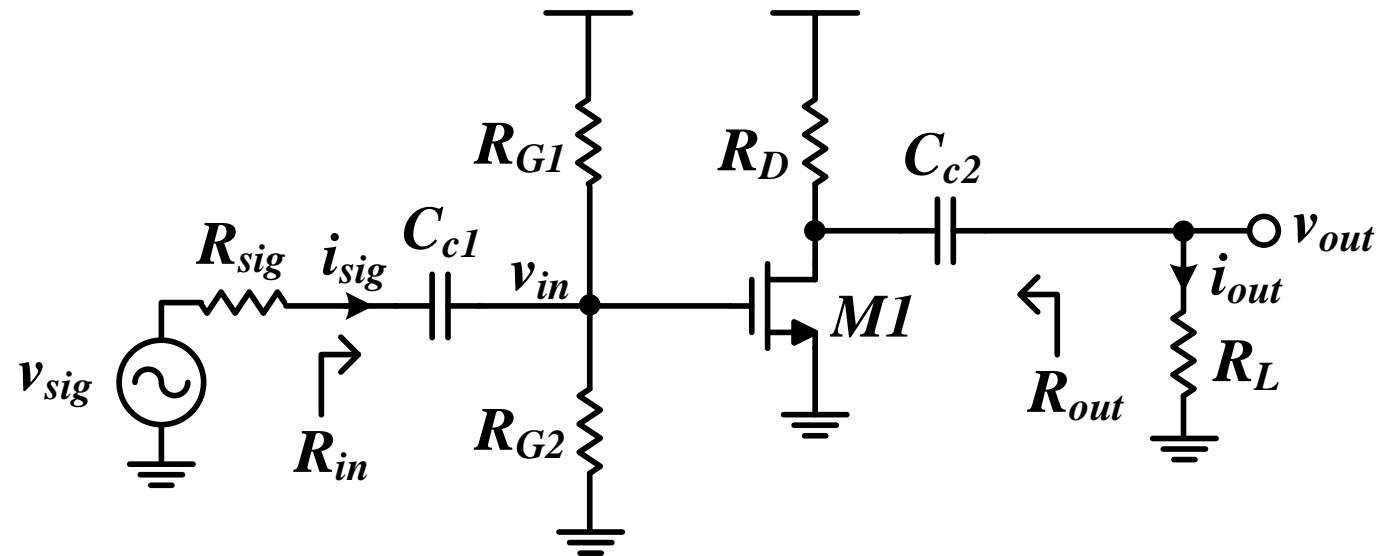
$$\square \text{Current gain} = A_i = \frac{i_{out}}{i_{sig}} = \frac{v_{out}/R_L}{v_{in}/R_{in}} = \frac{v_{out}}{v_{in}} \cdot \frac{R_{in}}{R_L}$$



Large and Small Signal Analysis



| | Large Signal Analysis | Small Signal Analysis |
|------------|--|--|
| Model | Large signal model | Small signal model |
| Linearity | Non-linear | Linear |
| Simulation | DC and transient analysis | AC analysis |
| Purpose | Calculate bias point, signal swing, distortion, etc. | Calculate A_v , R_{in} , R_{out} , BW , etc. |
| VDC | ✓ | s.c. |
| IDC | ✓ | o.c. |
| Capacitor | o.c. (in DC) | $1/\omega C$ |
| Inductor | s.c. (in DC) | ωL |

Amplifier Analysis Example

$$v_{out} = -(g_m v_{in}) r_o$$


$$|A_v| = \left| \frac{v_{out}}{v_{in}} \right| = g_m r_o$$

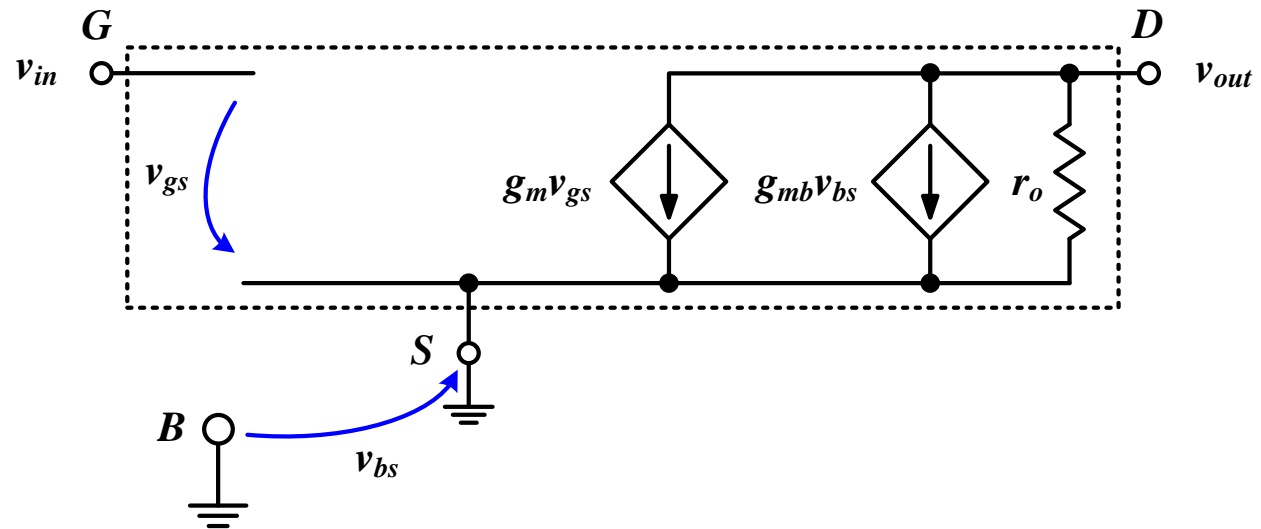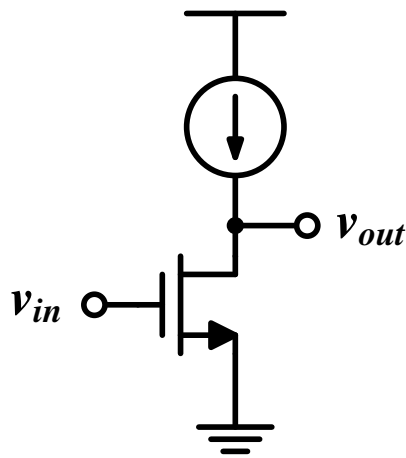□ $g_m r_o$ is the max gain that can be obtained from a single transistor: a.k.a. intrinsic gain




Direct Analysis on Schematics

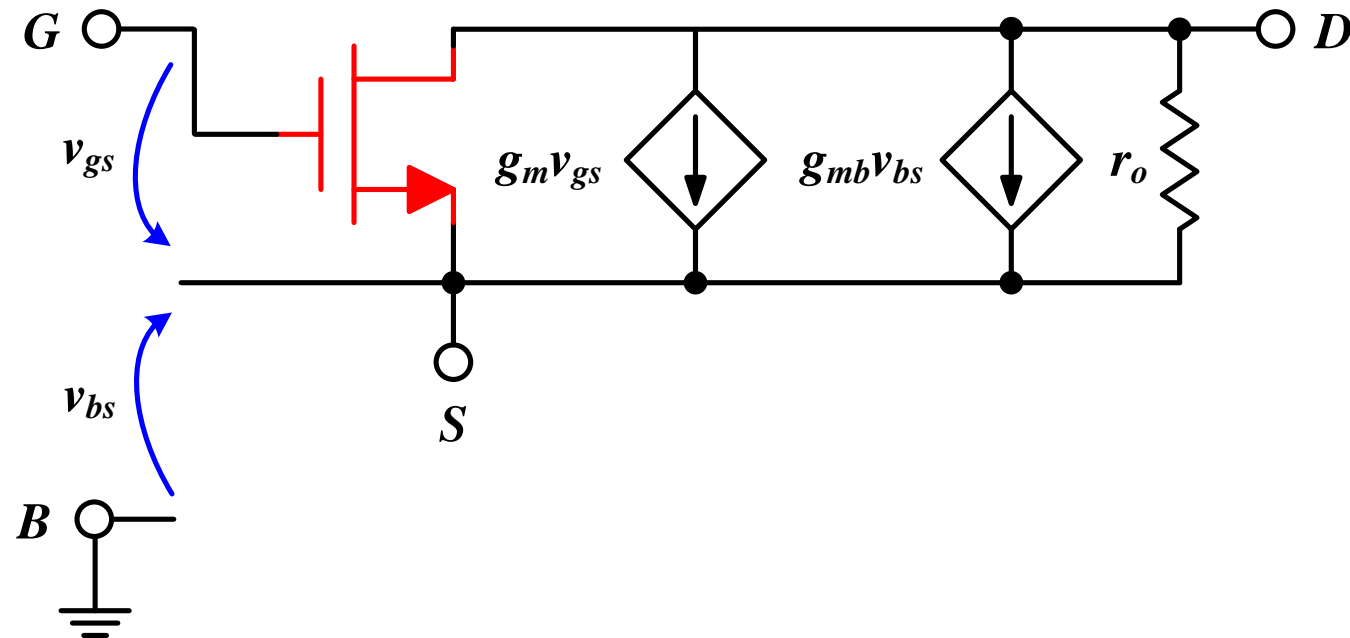- ❑ No need to draw the small signal model every time
- ❑ Just remember we have two VCCSs and r_o between D and S
- ❑ If G is ac gnd, then $v_{bs} = v_{gs} \rightarrow g_m$ and g_{mb} add
 - $g_m \rightarrow g_m + g_{mb}$



Direct Analysis on Schematics

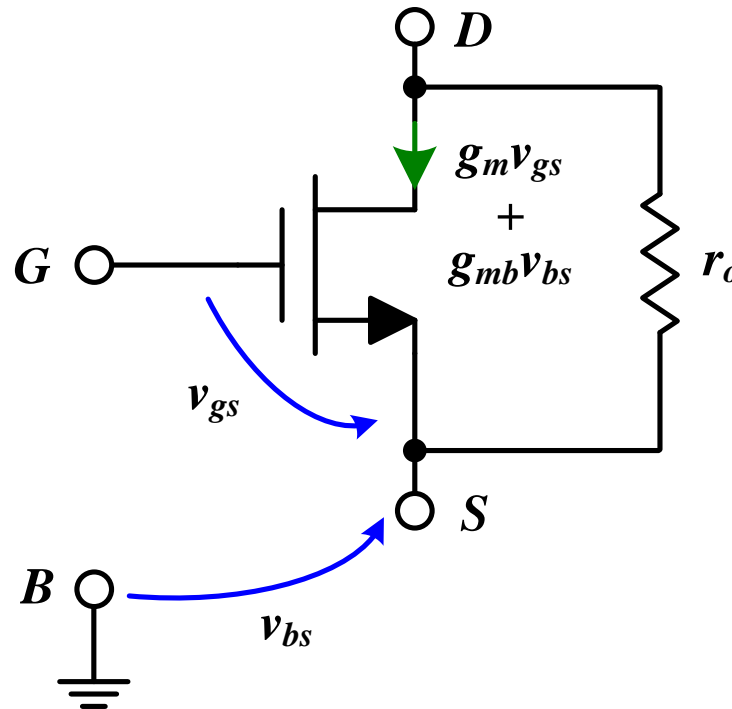- ❑ No need to draw the small signal model every time
- ❑ Just remember we have two VCCSs and r_o between D and S
- ❑ If G is ac gnd, then $v_{bs} = v_{gs} \Rightarrow g_m$ and g_{mb} add
 - $g_m \rightarrow g_m + g_{mb}$



Intrinsic Gain

$$v_{out} = -(g_m v_{in}) r_o$$

$$|A_v| = \left| \frac{v_{out}}{v_{in}} \right| = g_m r_o$$


- $g_m r_o$ is the max gain that can be obtained from a single transistor
- Common approximations that we usually use

$$g_m r_o \gg 1$$

$$r_o \gg \frac{1}{g_m}$$

$$g_m + \frac{1}{r_o} \approx g_m$$
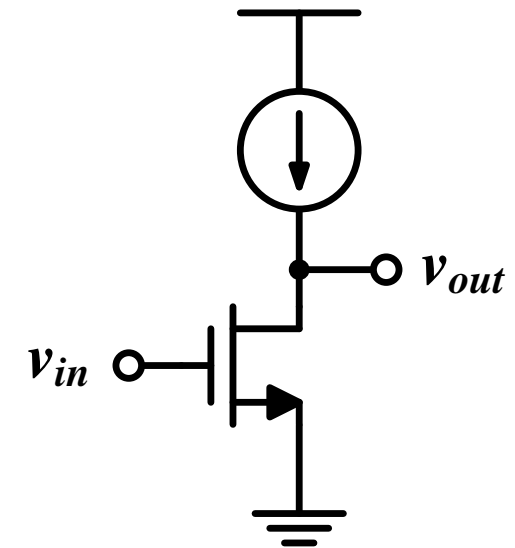
$$r_o // \frac{1}{g_m} \approx \frac{1}{g_m}$$




Outline

- ☐ Recapping previous key results
- ☐ Why amplifiers?
- ☐ Basic amplifier operation
- ☐ Basic amplifier analysis
- ☐ **Rin/out shortcuts**
 - Looking from drain
 - Looking from source
- ☐ GmRout method
- ☐ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ☐ Large signal behavior

Rin/out Shortcuts

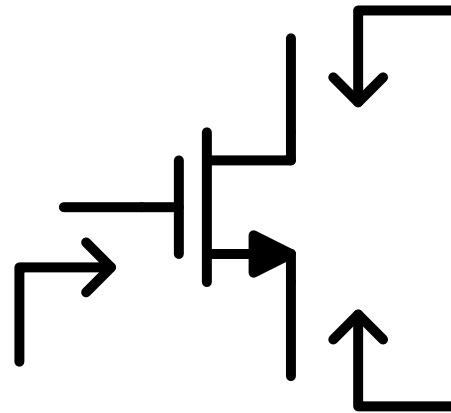- Find equivalent impedance looking from Gate, Source, and Drain




Looking From Drain

- If G is ac gnd, then $v_{bs} = v_{gs} \rightarrow g_m$ and g_{mb} add
- $v_{gs} = -i_x R_S$ and $g_m r_o \gg 1$
- Apply KCL at D

$$i_x = (g_m + g_{mb})(-i_x R_S) + \frac{v_x - i_x R_S}{r_o}$$
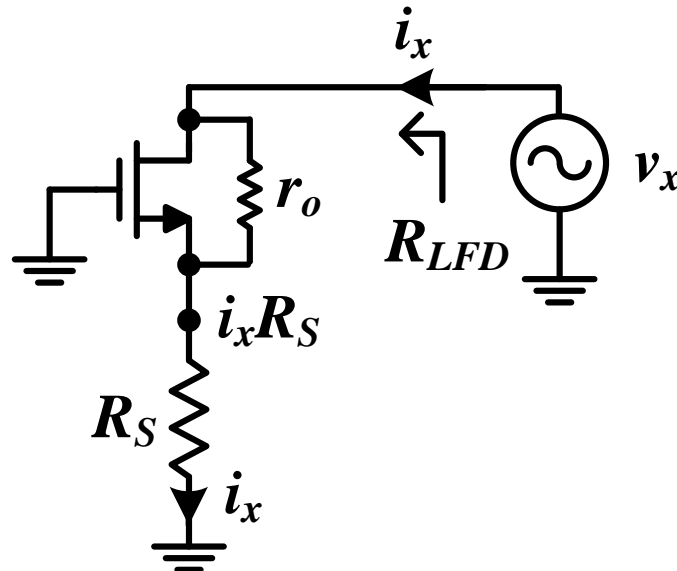
$$R_{LFD} = \frac{v_x}{i_x} = r_o + [(g_m + g_{mb})r_o + 1]R_S \approx r_o[1 + (g_m + g_{mb})R_S]$$




Looking From Drain

$$R_{LFD} \approx r_o [1 + (g_m + g_{mb})R_S]$$


- ❑ Special case: $R_S = 0$ (G and S ac s.c.) → **active load**

$$R_{LFD} = r_o$$

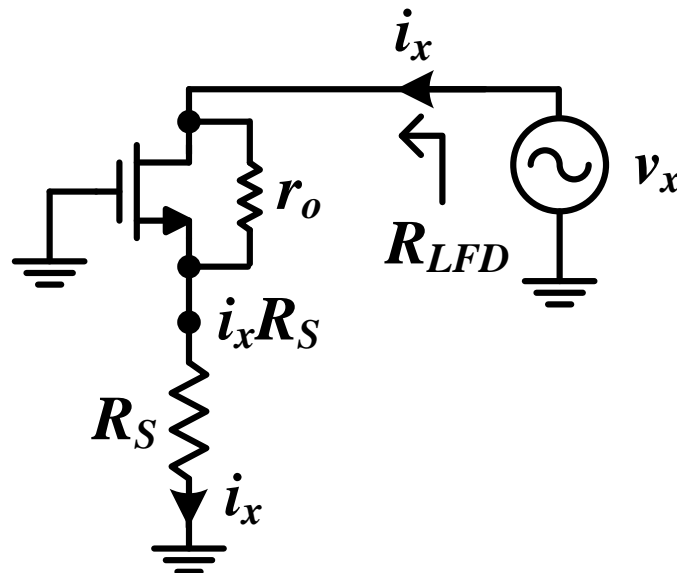- ❑ **Drain is a high-impedance node (H.I.N.)**




Active Load (Source OFF)

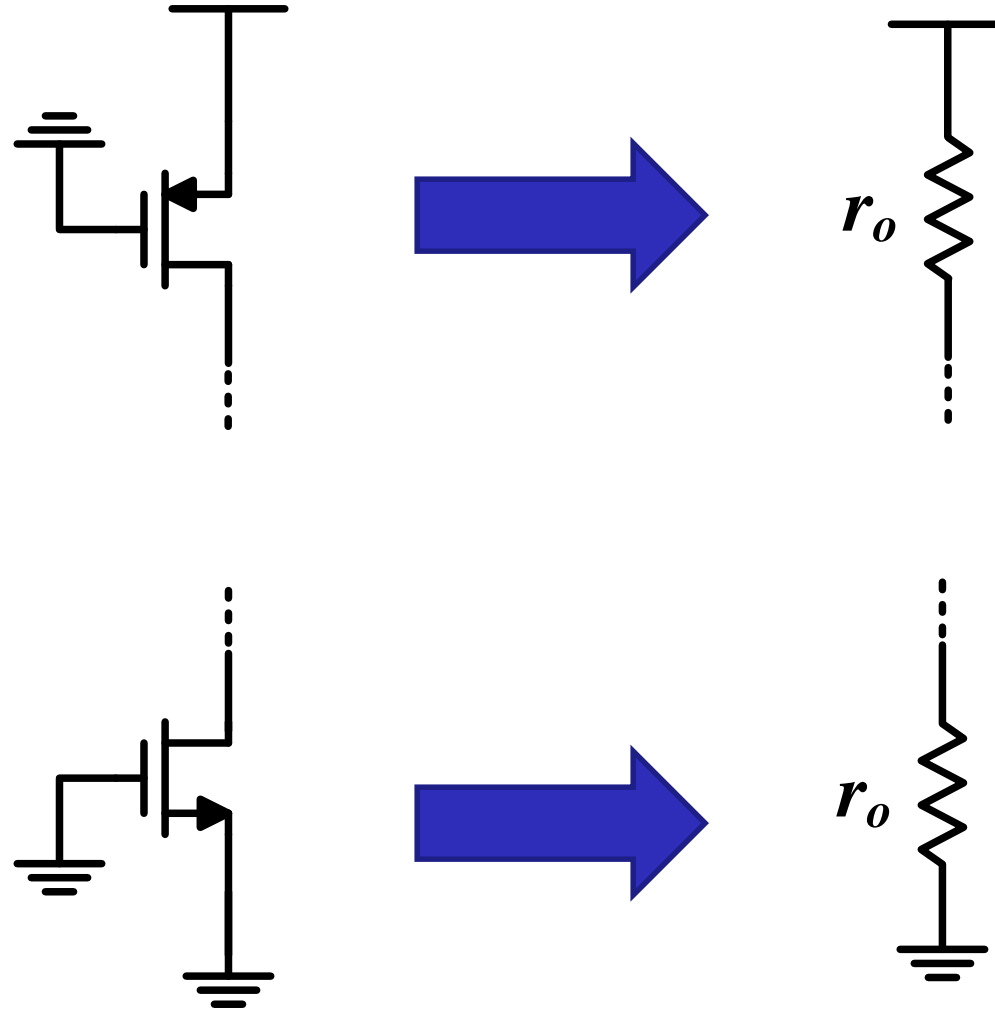

Quiz

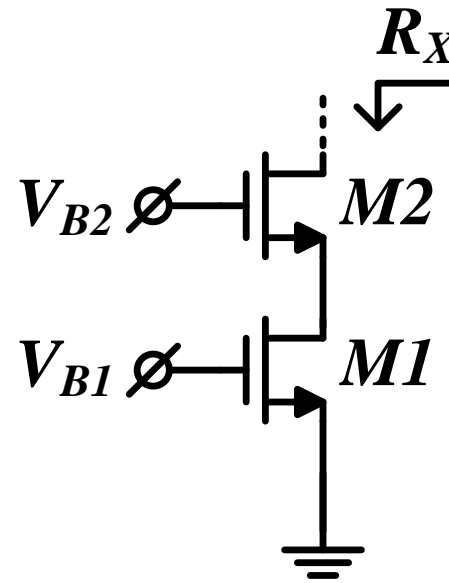
- ❑ Assume M1 and M2 have the same g_m and r_o , $g_m r_o \gg 1$, and neglect body effect
- ❑ Find R_X



Looking From Source

- $v_{gs} = -v_x$, g_m and g_{mb} add, and $g_m r_o \gg 1$
- Apply KCL at S
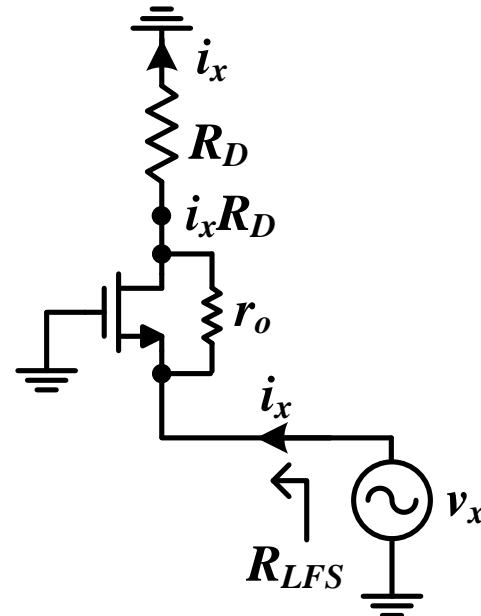
$$i_x = (g_m + g_{mb})v_x + \frac{v_x - i_x R_D}{r_o}$$
$$R_{LFS} = \frac{v_x}{i_x} = \frac{1}{g_m + g_{mb} + \frac{1}{r_o}} \left(1 + \frac{R_D}{r_o} \right) \approx \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$$




Looking From Source

$$R_{LFS} \approx \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$$

❑ Special case: $R_D = 0 \rightarrow$ **diode connected**





$$R_{LFS} \approx \frac{1}{g_m + g_{mb}}$$

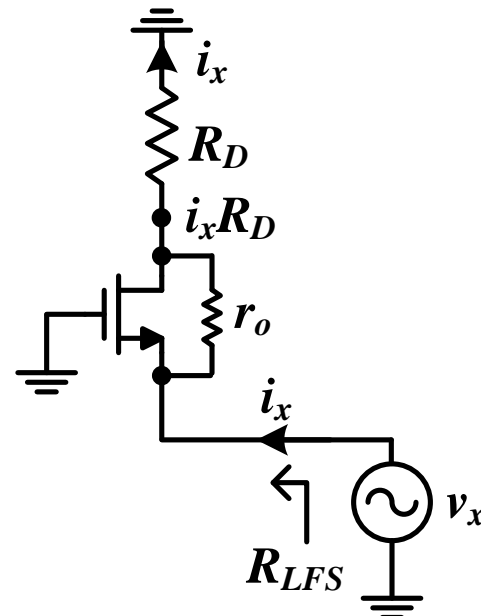❑ **Source is a low impedance node (L.I.N.)**




Diode Connected (Source Absorption)

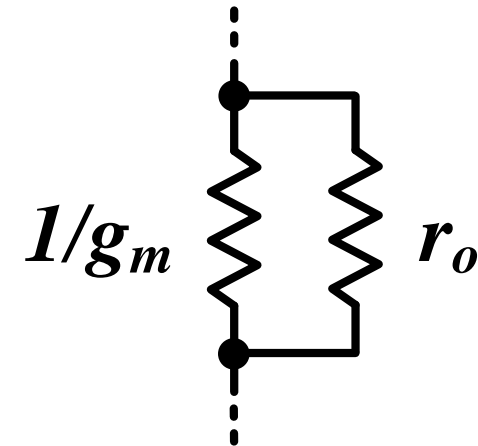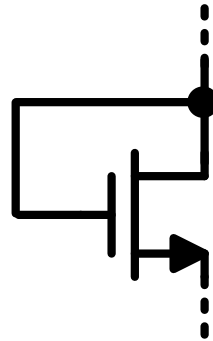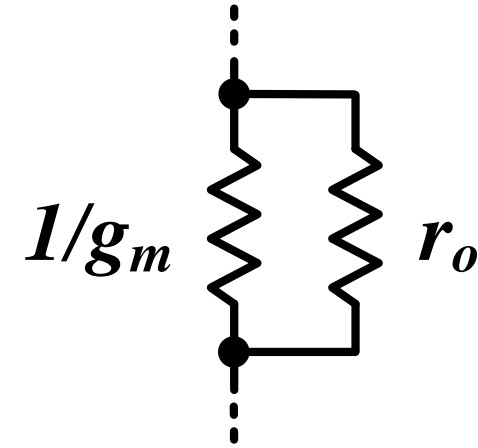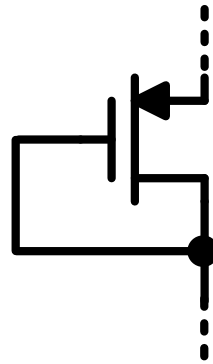- ❑ Always in saturation ($V_{DS} = V_{GS} > V_{ov}$)
- ❑ Body effect: $g_m \rightarrow g_m + g_{mb}$ (if G is ac gnd)




Quiz

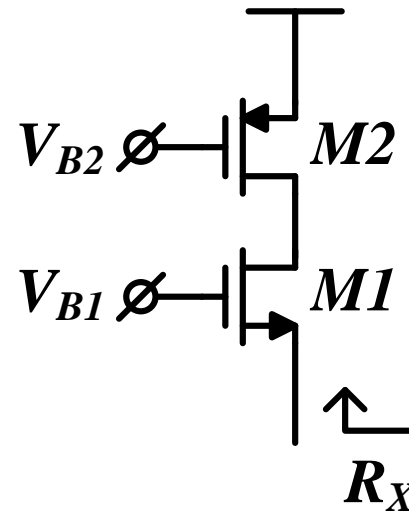- ❑ Assume M1 and M2 have the same r_o , $g_m r_o \gg 1$, and neglect body effect
- ❑ Find R_X




Quiz

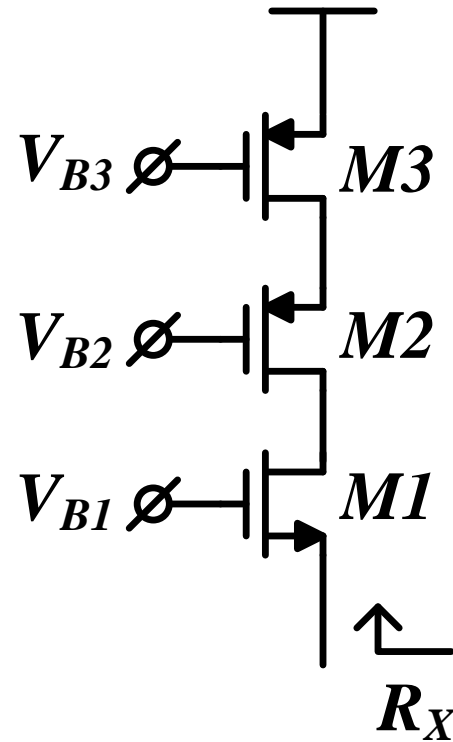- ❑ Assume M1, M2, and M3 have the same g_m and r_o , $g_m r_o \gg 1$, and neglect body effect
- ❑ Find R_X



Rin/out Shortcuts Summary

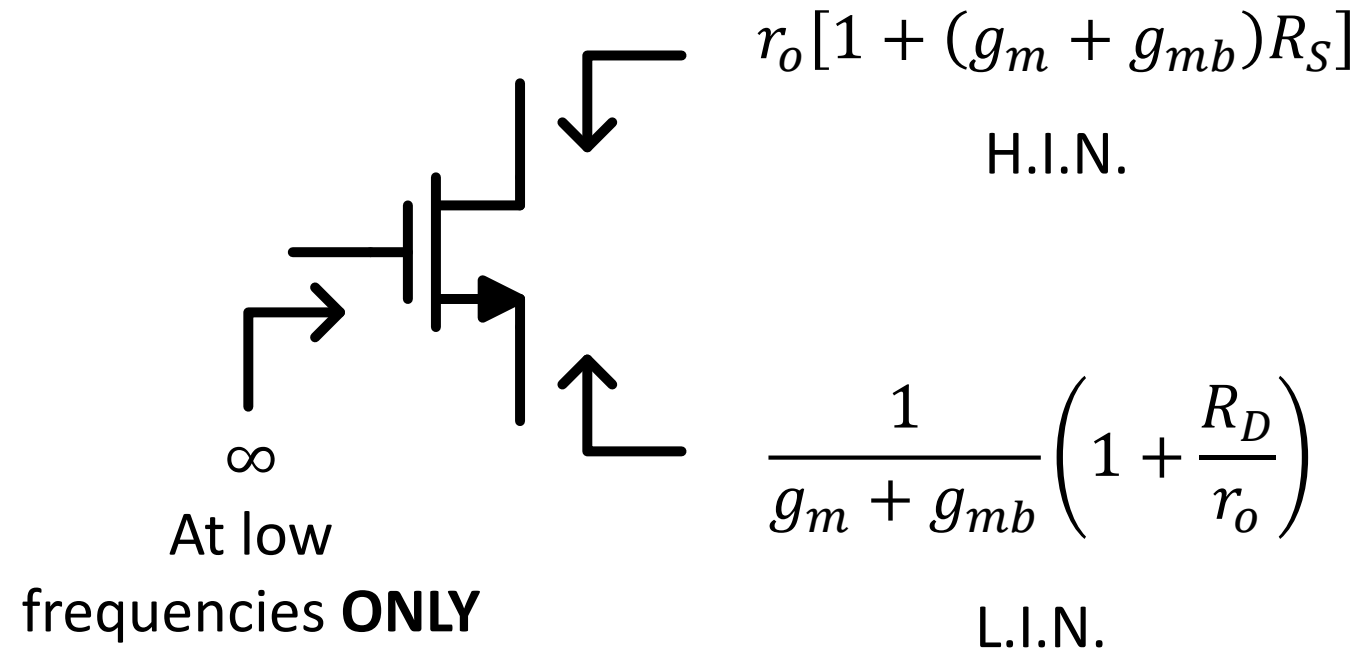

Outline


- ☐ Recapping previous key results
- ☐ Why amplifiers?
- ☐ Basic amplifier operation
- ☐ Basic amplifier analysis
- ☐ R_{in}/R_{out} shortcuts
 - Looking from drain
 - Looking from source
- ☐ **GmRout method**
- ☐ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ☐ Large signal behavior

Amplifier Model

□ Rin/out

$$R_{in} = \frac{v_{in}}{i_{in}}$$
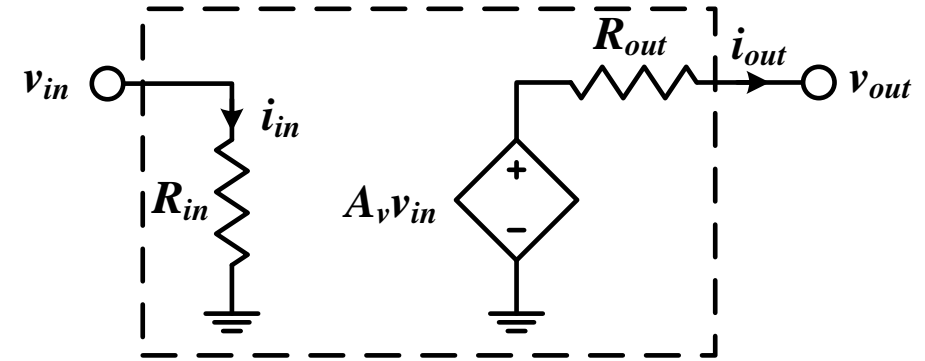
$$R_{out} = \frac{v_x}{i_x} @ v_{in} = 0$$



□ O.C. voltage gain (Thevenin model)

$$v_{out,oc} = v_{Thevenin} = A_v v_{in}$$


$$A_v = \frac{v_{out,oc}}{v_{in}}$$

Amplifier Model

□ Transconductance (Norton model)

$$i_{out,sc} = i_{Norton} = G_m v_{in}$$

$$G_m = \frac{i_{out,sc}}{v_{in}}$$

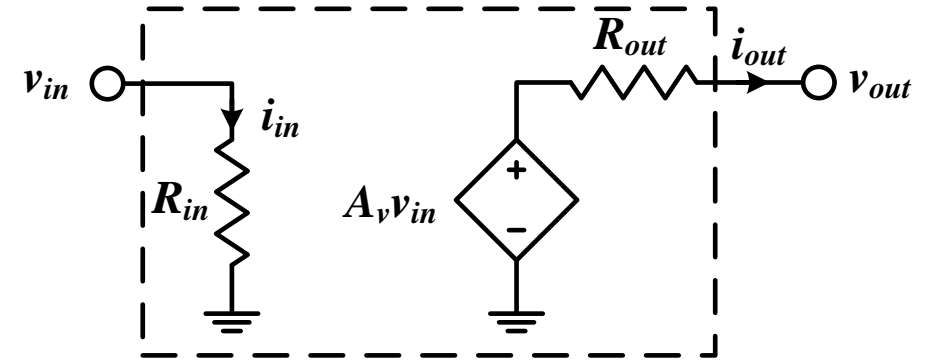


□ Thevenin \Leftrightarrow Norton

$$v_{out,oc} = A_v v_{in} = (G_m v_{in}) R_{out}$$

$$A_v = \frac{v_{out,oc}}{v_{in}} = G_m R_{out}$$


□ S.C. Current Gain
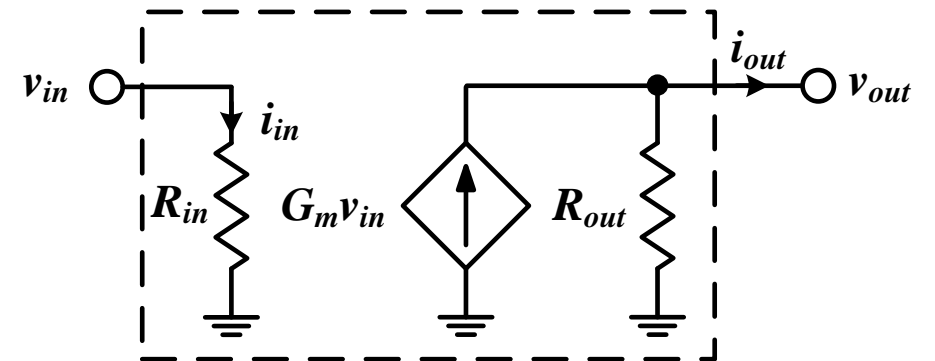
$$A_i = \frac{i_{out,sc}}{i_{in}} = \frac{i_{out,sc}}{v_{in}/R_{in}} = G_m R_{in}$$




Why GmRout?
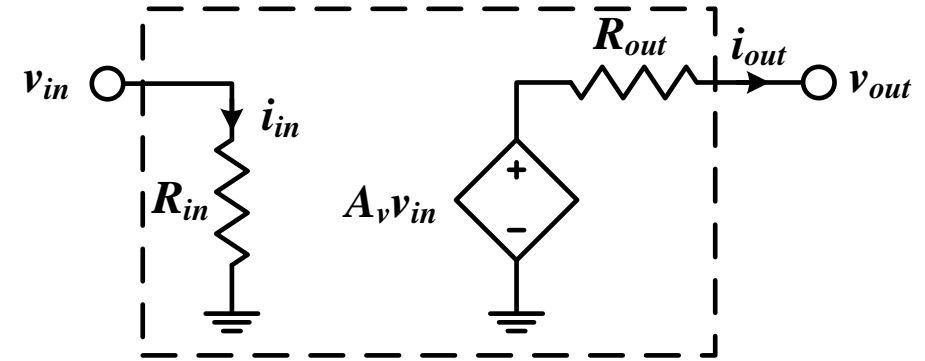
$$\begin{aligned}R_{in} &= v_{in}/i_{in} \\ R_{out} &= v_x/i_x @ v_{in} = 0 \\ G_m &= i_{out,sc}/v_{in} \\ A_v &= G_m R_{out} \\ A_i &= G_m R_{in}\end{aligned}$$



□ Divide and conquer



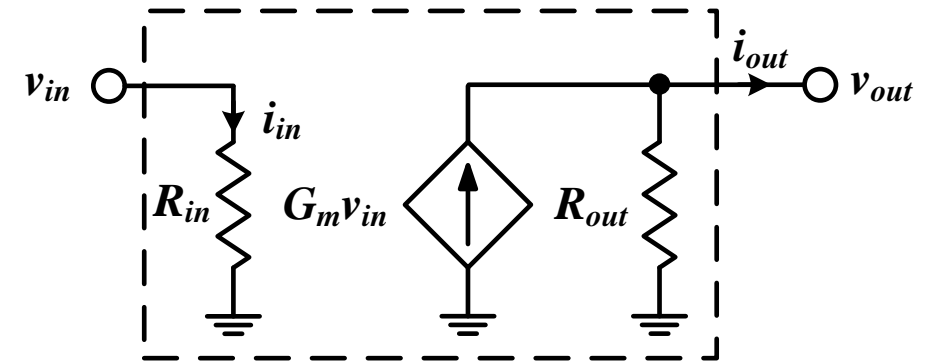
- Rout simplified: $v_{in} = 0$
- Gm simplified: $v_{out} = 0$
- We already need Rin/out and Gm
- We can quickly and easily get Rin/out from the shortcuts



Outline

- ❑ Recapping previous key results
- ❑ Why amplifiers?
- ❑ Basic amplifier operation
- ❑ Basic amplifier analysis
- ❑ R_{in}/R_{out} shortcuts
 - Looking from drain
 - Looking from source
- ❑ GmRout method
- ❑ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ❑ Large signal behavior

Basic Amplifier Topologies
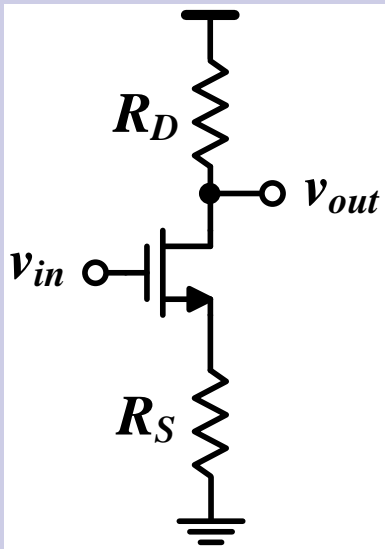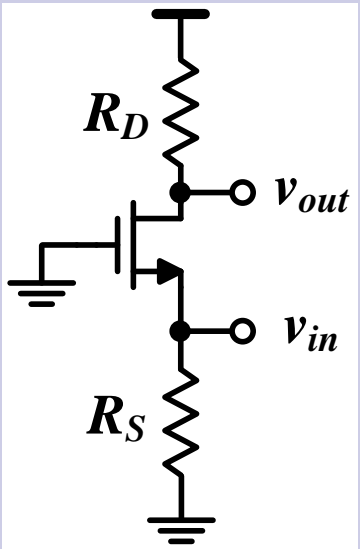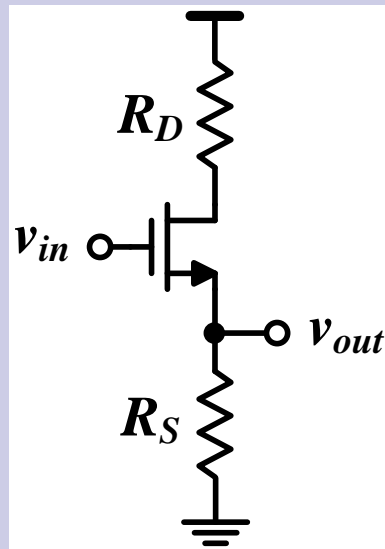
| | Common Source (CS) | Common Gate (CG) | Common Drain (CD) Source Follower (SF) |
|-----|---|---|---|
| |  |  |  |
| | Voltage & current amplifier | Voltage amplifier Current buffer | Voltage buffer Current amplifier |
| In | G | S | G |
| Out | D | D | S |

Common Source (CS)

- Apply KCL at S noting that $v_{gs} = v_{in} - (-i_{out,sc}R_S)$


$$i_{out,sc} + g_m(v_{in} + i_{out,sc}R_S) + g_{mb}(i_{out,sc}R_S) + \frac{i_{out,sc}R_S}{r_o} = 0$$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{-g_m}{1 + (g_m + g_{mb})R_S}$$

$$R_{out} \approx R_D || r_o [1 + (g_m + g_{mb})R_S]$$

$$A_v = G_m R_{out}$$

- If R_D is ac o.c.: $A_v = -g_m r_o$
- If $R_D \ll R_{LFD}$: $A_v \approx \frac{-g_m R_D}{1 + (g_m + g_{mb})R_S}$
- If $R_S = 0$: $A_v = -g_m (R_D || r_o)$

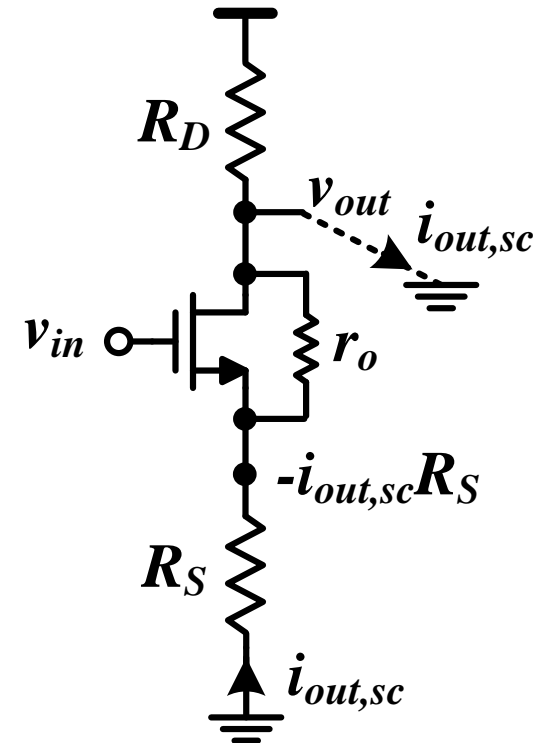

Common Source (CS)

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{-g_m}{1 + (g_m + g_{mb})R_S}$$

$$R_{out} \approx R_D || r_o [1 + (g_m + g_{mb})R_S]$$

$$A_v = G_m R_{out}$$


□ If S and B are ac connected (for PMOS):

$$A_v \approx \frac{-R_D || R_{LFD}}{\frac{1}{g_m} + R_S} = - \frac{\text{Drain Res.}}{\frac{1}{g_m} + \text{Source Res.}}$$

□ If $R_S \gg \frac{1}{g_m}$ & $R_D \ll R_{LFD}$: $A_v \approx \frac{-R_D}{R_S} \rightarrow$ Linear gain!

□ R_S reduces $G_m \rightarrow$ **Source degeneration**

▪ But improves linearity

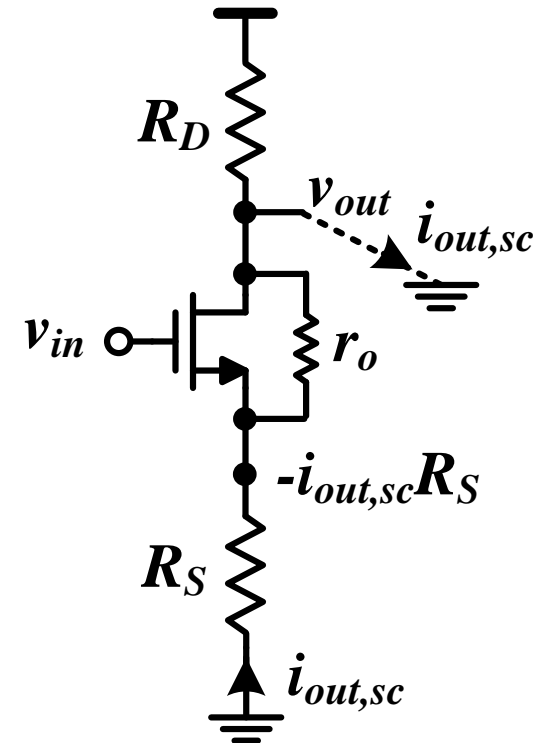

Common Gate (CG)

- Apply KCL at D noting that $v_{gs} = v_{bs} = 0 - v_{in}$


$$i_{out,sc} + (g_m + g_{mb})(-v_{in}) - \frac{v_{in}}{r_o} = 0$$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx g_m + g_{mb}$$

$$R_{out} \approx R_D || r_o \text{ (why?)}$$

$$A_v = G_m R_{out}$$

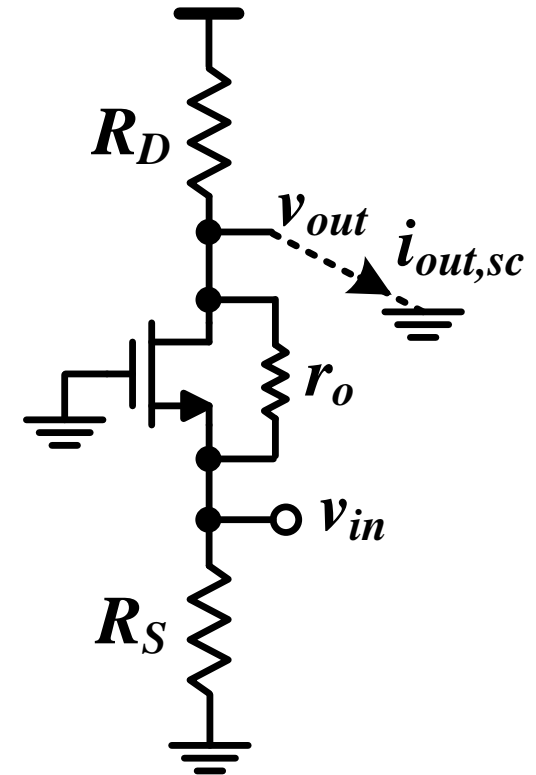- If R_D is ac o.c.: $A_v = (g_m + g_{mb})r_o$
- If $R_D \ll r_o$: $A_v \approx (g_m + g_{mb})R_D$
- If S and B are ac connected: $(g_m + g_{mb}) \rightarrow g_m$
- Note that $A_i = G_m R_{in} < \approx 1$ (**Current Buffer**)



Common Drain (CD) – Source Follower

- Apply KCL at D

$$i_{out,sc} - g_m v_{in} + \frac{i_{out,sc} R_D}{r_o} = 0$$

$$G_m = \frac{i_{out,sc}}{v_{in}} \approx \frac{g_m}{1 + R_D/r_o}$$


$$R_{out} \approx R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$$

$$A_v = G_m R_{out}$$




- If $R_S \gg R_{LFS}$: $A_v \approx \frac{g_m}{g_m + g_{mb}} < 1$

- If S and B are ac connected (for PMOS):
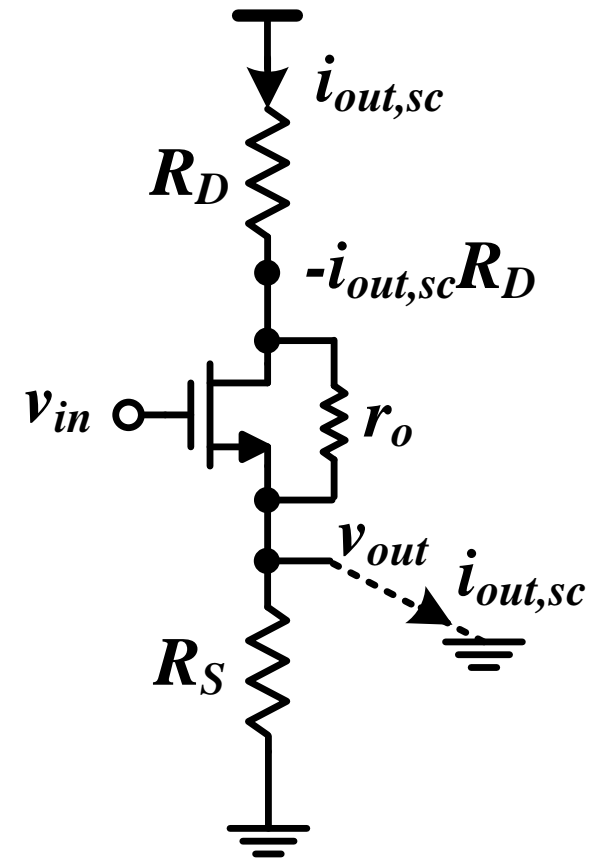
$$A_v \approx 1 \text{ (Voltage buffer)}$$




Summary of Basic Topologies
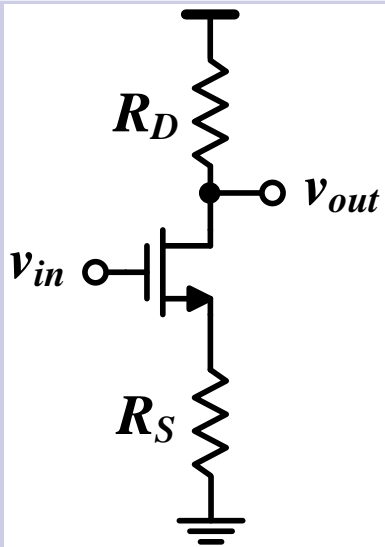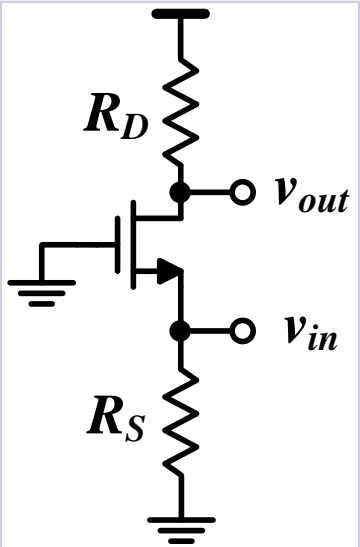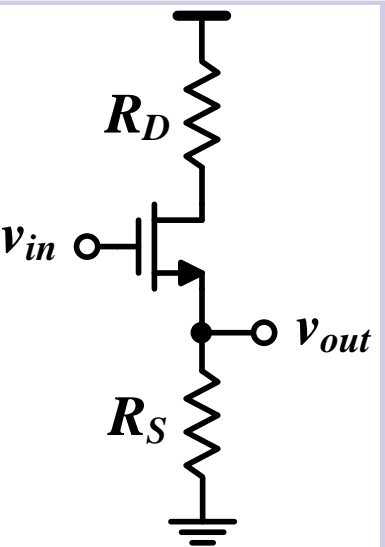
| | CS | CG | CD (SF) |
|------------------------|---|---|---|
| |  |  |  |
| | Voltage & current amplifier | Voltage amplifier Current buffer | Voltage buffer Current amplifier |
| R_{in} | ∞ | $R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$ | ∞ |
| R_{out} | $R_D \parallel r_o [1 + (g_m + g_{mb})R_S]$ | $R_D \parallel r_o$ | $R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$ |
| G_m | $\frac{-g_m}{1 + (g_m + g_{mb})R_S}$ | $g_m + g_{mb}$ | $\frac{g_m}{1 + R_D/r_o}$ |


Quiz

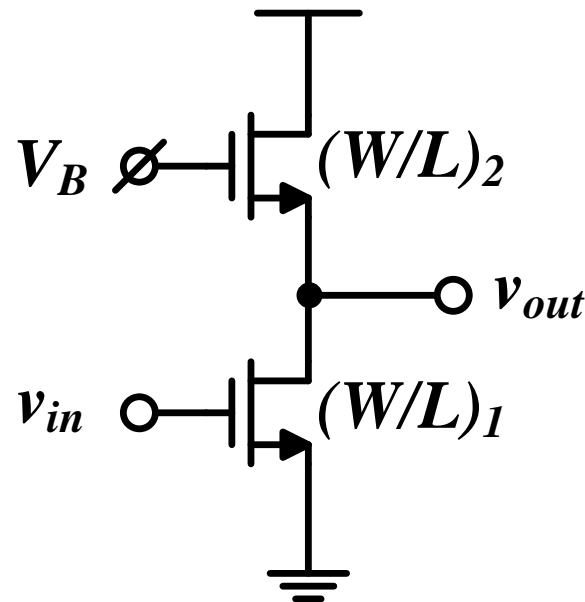- ☐ The circuit below shows a CS amplifier With diode-connected load
- ☐ Find the gain using GmRout (ignore body effect and CLM).
 - Express the gain in terms of $(W/L)_1$ and $(W/L)_2$.
- ☐ This is a “linear” CS amplifier.



Quiz

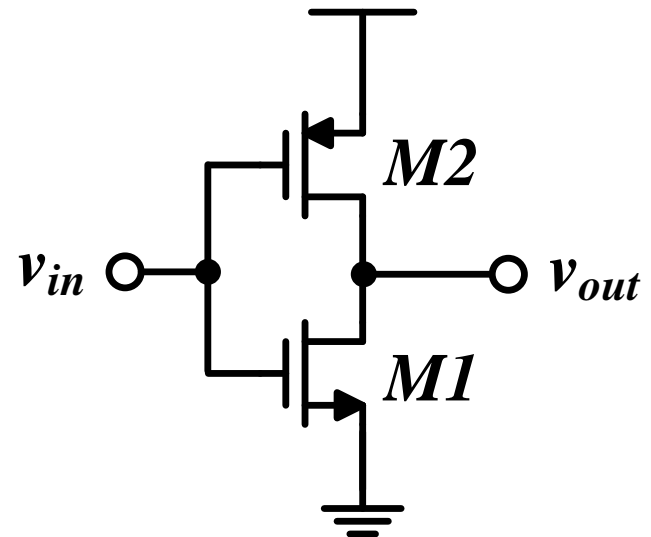
- ☐ The circuit below shows a complementary CS amplifier (inverter amp).
- ☐ Find the gain using GmRout.




Outline

- ❑ Recapping previous key results
- ❑ Why amplifiers?
- ❑ Basic amplifier operation
- ❑ Basic amplifier analysis
- ❑ R_{in}/R_{out} shortcuts
 - Looking from drain
 - Looking from source
- ❑ GmRout method
- ❑ Basic amplifier topologies
 - Common Source (CS)
 - Common Gate (CG)
 - Common Drain (CD) – Source Follower (SF)
- ❑ Large signal behavior

CS Amplifier Example




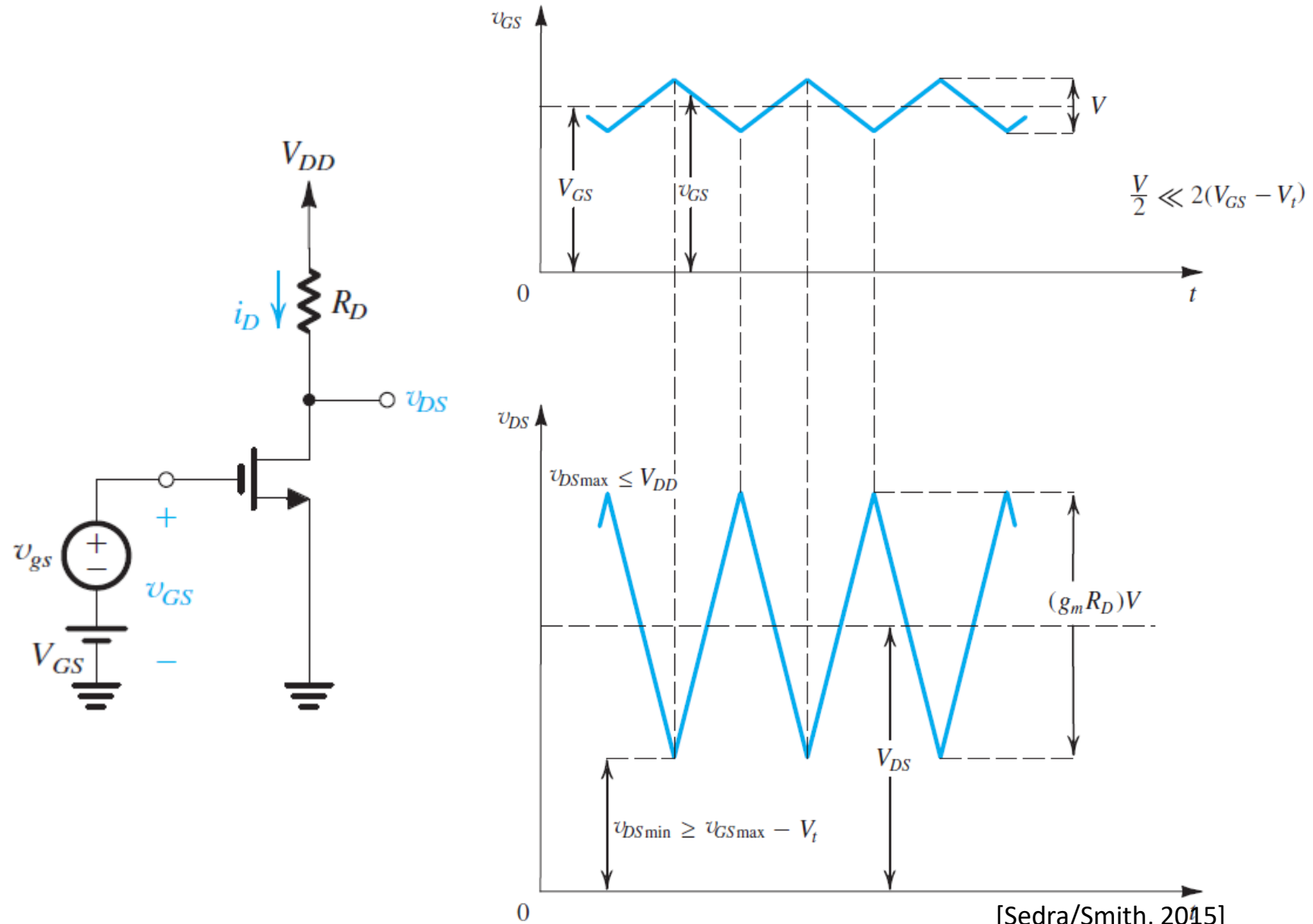


CS Large Signal Behavior

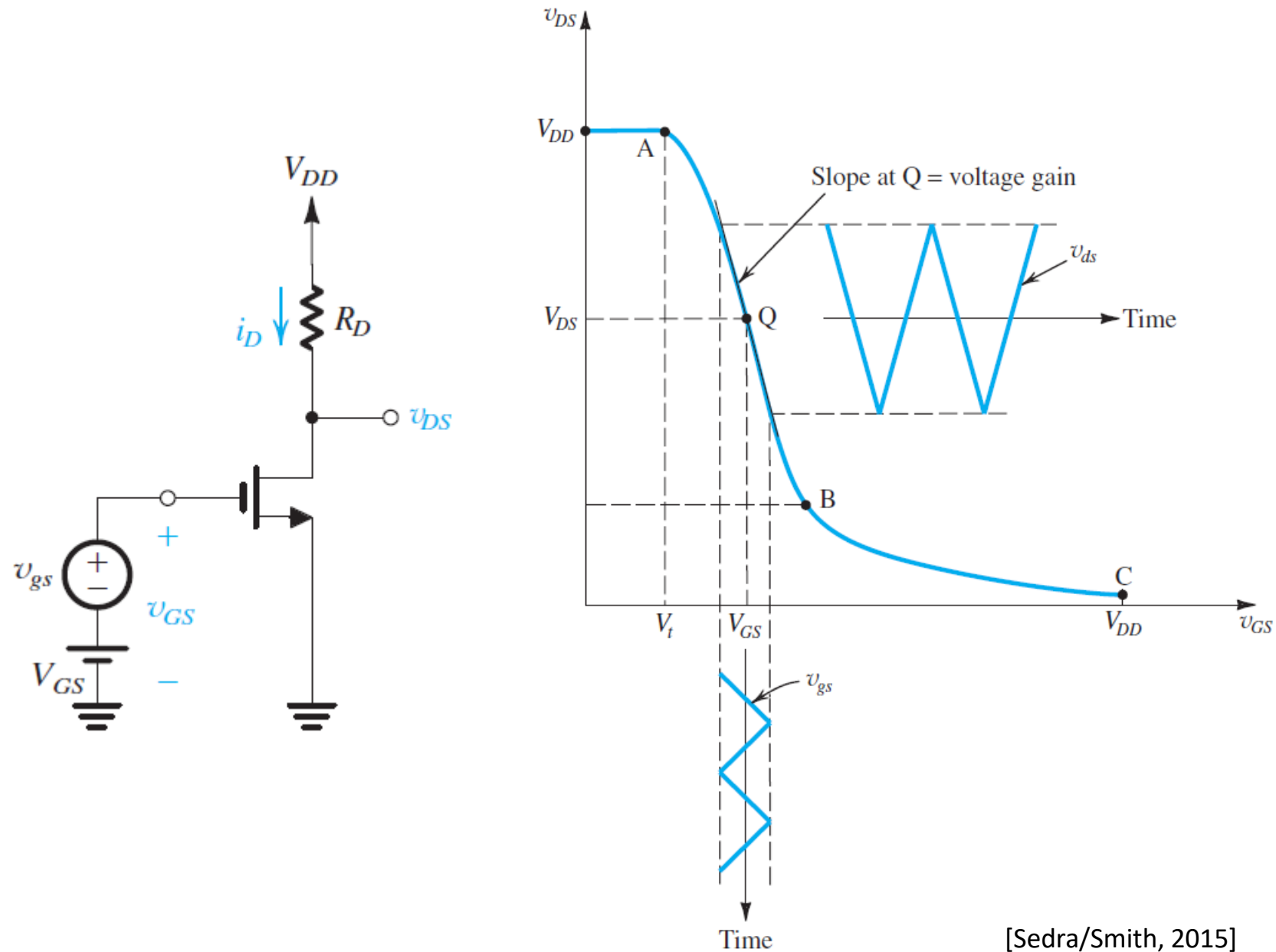

CS Large Signal Behavior

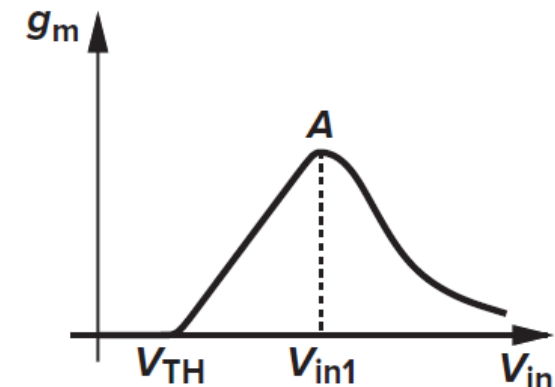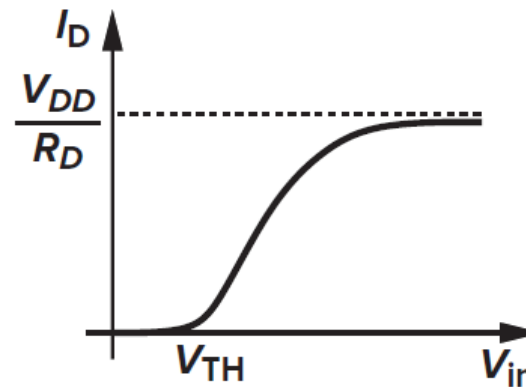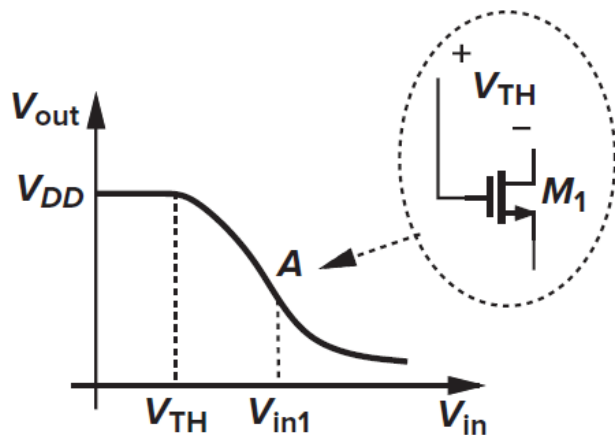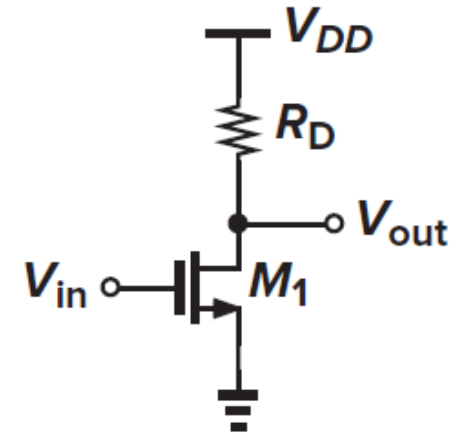- Gain is non-linear:
 - $A_v = f(V_{in})$
 - $g_m = f(V_{in})$
- For linear gain, A_v should NOT be $f(V_{in})$
- A_v and g_m are max at edge of triode
 - But they are highly non-linear
 - And the available signal swing vanishes




Output Signal Swing

$$V_{out,max} = V_{DD} - V_{ov2}$$



$$V_{out,min} = V_{ov1} = V_{in,max} - V_{TH}$$

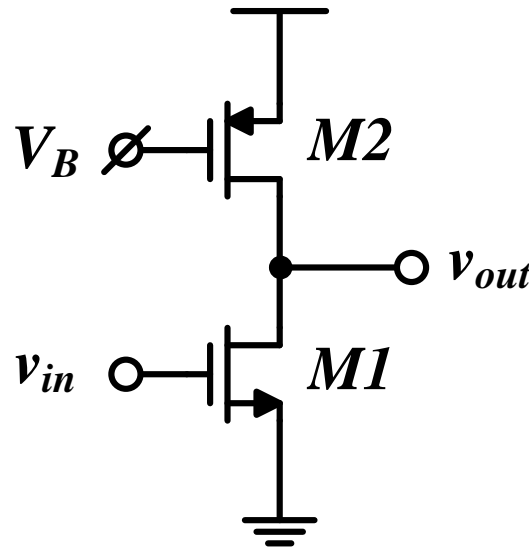□ Output swing $\approx V_{DD} - 2V_{ov}$



CD Large Signal Behavior

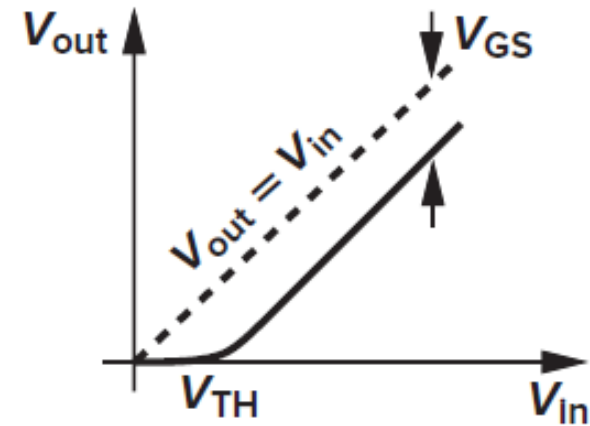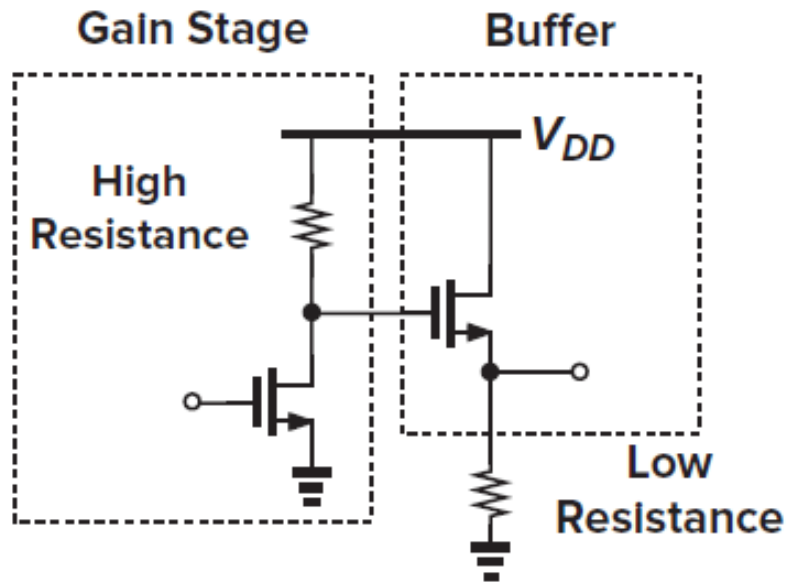- Why Source Follower?
 - Buffer
 - Level-shifter



Thank you!

References

- ❑ A. Sedra and K. Smith, “Microelectronic Circuits,” Oxford University Press, 7th ed., 2015
- ❑ B. Razavi, “Fundamentals of Microelectronics,” Wiley, 2nd ed., 2014
- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2nd ed., 2017