

Analog IC Design

Lecture 14 OTA Design Example

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Analog Design Trade-offs

- ❑ There are always tradeoffs between gain, speed, and energy efficiency.
- ❑ The design knobs that you use to control the tradeoffs are g_m/I_D and L .
- ❑ Choice of g_m/I_D
 - Large g_m/I_D : high efficiency (low power), large swing (low V^*), high gain (low V^*)
 - Small g_m/I_D : high speed, small area
- ❑ Choice of L
 - Long L : high gain, good matching, low flicker noise (more later)
 - Short L : high speed, small area
- ❑ Finding the best compromise for design tradeoffs given required specs is your job as a designer.

Outline

- ❑ OTA required specifications
- ❑ Topology selection
- ❑ Tradeoffs Matrix
- ❑ Design of input pair
- ❑ Design of current mirror load
- ❑ Design of tail current source
- ❑ Sizing and simulation results

Outline

- ❑ OTA required specifications
- ❑ Topology selection
- ❑ Tradeoffs Matrix
- ❑ Design of input pair
- ❑ Design of current mirror load
- ❑ Design of tail current source
- ❑ Sizing and simulation results

OTA Design Example

- Design a diff input SE output OTA that meets the following specs.

| | |
|---------------------------|-------------------|
| Technology | 180 nm CMOS |
| Supply voltage | 1.8 V |
| Load | 5 pF |
| Open loop DC voltage gain | ≥ 32 dB |
| Phase margin | $\geq 70^\circ$ |
| Reference Current | 10 μ A |
| OTA current consumption | ≤ 20 μ A |
| CM input range – low | ≤ 0.2 V |
| CM input range – high | ≥ 1.1 V |
| GBW | 5 MHz |
| CMRR @DC | 70 dB |

Outline


- ❑ OTA required specifications
- ❑ **Topology selection**
- ❑ Tradeoffs Matrix
- ❑ Design of input pair
- ❑ Design of current mirror load
- ❑ Design of tail current source
- ❑ Sizing and simulation results

Topology Selection

- ❑ The required gain is not high (only 32 dB = 40) so it can be achieved by a simple single stage OTA
 - If the gain is high, we must use cascode or two stage OTA
- ❑ Since the required CMIR is close to the ground rail, we need to use a PMOS input stage
- ❑ PMOS input stage has other advantages as well
 - PMOS input transistors can be placed in a separate well so they don't suffer from body effect
 - PMOS has lower flicker noise

Topology Selection

 - ❑ Single stage OTA has a single dominant pole, so we don't need to worry about phase margin
 - For two-stage you must use compensation network
- ❑ Use simple current mirror for biasing
 - The reference current is 10 μA
 - Doubled by the mirror such that 20 μA goes to the diff pair




Outline

- ☐ OTA required specifications
- ☐ Topology selection
- ☒ Tradeoffs Matrix
- ☐ Design of input pair
- ☐ Design of current mirror load
- ☐ Design of tail current source
- ☐ Sizing and simulation results

Trade-offs Matrix

| Spec | I_{SS} | L_{12} | $\left(\frac{g_m}{I_D}\right)_{12}$ | L_{34} | $\left(\frac{g_m}{I_D}\right)_{34}$ | L_5 | $\left(\frac{g_m}{I_D}\right)_5$ |
|-------------------------|----------|----------|-------------------------------------|----------|-------------------------------------|-------|----------------------------------|
| DC gain \uparrow | | | | | | | |
| CMIR – low \downarrow | | | | | | | |
| CMIR – high \uparrow | | | | | | | |
| GBW \uparrow | | | | | | | |
| CMRR @DC \uparrow | | | | | | | |

 

Outline

- ☐ OTA required specifications
- ☐ Topology selection
- ☐ Tradeoffs Matrix
- ☐ Design of input pair
- ☐ Design of current mirror load
- ☐ Design of tail current source
- ☐ Sizing and simulation results


PMOS Input Stage (1/3)

$$\square \quad GBW = \frac{g_m}{2\pi C_L}$$

$$\square \quad g_m = 2\pi \times 5 \text{ p} \times 5 \text{ M} \approx 160 \mu\text{S}$$

$$\blacksquare \quad I_D = \frac{20 \mu}{2} = 10 \mu A$$
 
$$\square \quad \frac{g_m}{I_D} = 16 \text{ S/A}$$





PMOS Input Stage (2/3)

- ❑ Next, we need to find the channel length to get the required gain
- ❑ For simplicity, assume PMOS and NMOS have same g_{ds}

$$A_v = \frac{g_m r_o}{2} > 40 \rightarrow \text{Let: } g_{ds2} = g_{ds4} < 2 \mu S$$

$$A_v = \frac{g_m r_o}{2} \rightarrow \frac{g_m}{g_{ds}} > 80$$

  
- ❑ From the design chart, we find that required length is **L = 0.8 μm**



PMOS Input Stage (3/3)

□ Going to the I_D/W chart
 
$$\frac{I_d}{W} = 0.44 \rightarrow W = \frac{10}{0.44} \approx 24 \mu m$$



Outline



- ☐ OTA required specifications
- ☐ Topology selection
- ☐ Tradeoffs Matrix
- ☐ Design of input pair
- ☐ Design of current mirror load
- ☐ Design of tail current source
- ☐ Sizing and simulation results

NMOS Current Mirror Load (1/6)

- From the DC gain spec select the length of the current mirror load

$$g_{ds4} = \frac{I_D}{V_A} < 2 \mu S \rightarrow V_A > 5 V$$

  - $V_A = I_D r_o$ slightly decreases with g_m/I_D (weak dependence)
- Assume an arbitrary but large g_m/I_D , e.g., $g_m/I_D = 15$



NMOS Current Mirror Load (1/6)



- From the DC gain spec select the length of the current mirror load

$$g_{ds4} = \frac{I_D}{V_A} < 2 \mu S \rightarrow V_A > 5 V$$

- $V_A = I_D r_o$ slightly decreases with g_m/I_D (weak dependence)

- Assume an arbitrary but large g_m/I_D , e.g., $g_m/I_D = 15$
  
$$\frac{g_m}{I_D} = 15 \rightarrow g_m = 150 \mu S \rightarrow \frac{g_m}{g_{ds}} = 75 \rightarrow L = 0.6 \mu m$$





NMOS Current Mirror Load (2/6)

- ❑ The design of the current mirror load is determined by CMIR, noise, and output swing specs

$$CMIR_{LOW} = -|V_{GS1}| + |V_{dsat1}| + V_{GS3} < 0.2 V$$

- ❑ Get V_{GS1} and V_{dsat1} (or use $V_1^* = 0.125 V$)

$$0.2 = -0.57 + |V_{dsat1}| + V_{GS3,max}$$

  



NMOS Current Mirror Load (3/6)

- ❑ The design of the current mirror load is determined by CMIR, noise, and output swing specs

$$CMIR_{LOW} = -|V_{GS1}| + |V_{dsat1}| + V_{GS3} < 0.2 V$$

- ❑ Get V_{GS1} and V_{dsat1} (or use $V_1^* = 0.125 V$)



$$0.2 = -0.57 + 0.1 + V_{GS3,max}$$

  

NMOS Current Mirror Load (4/6)

- ❑ The design of the current mirror load is determined by CMIR, noise, and output swing specs
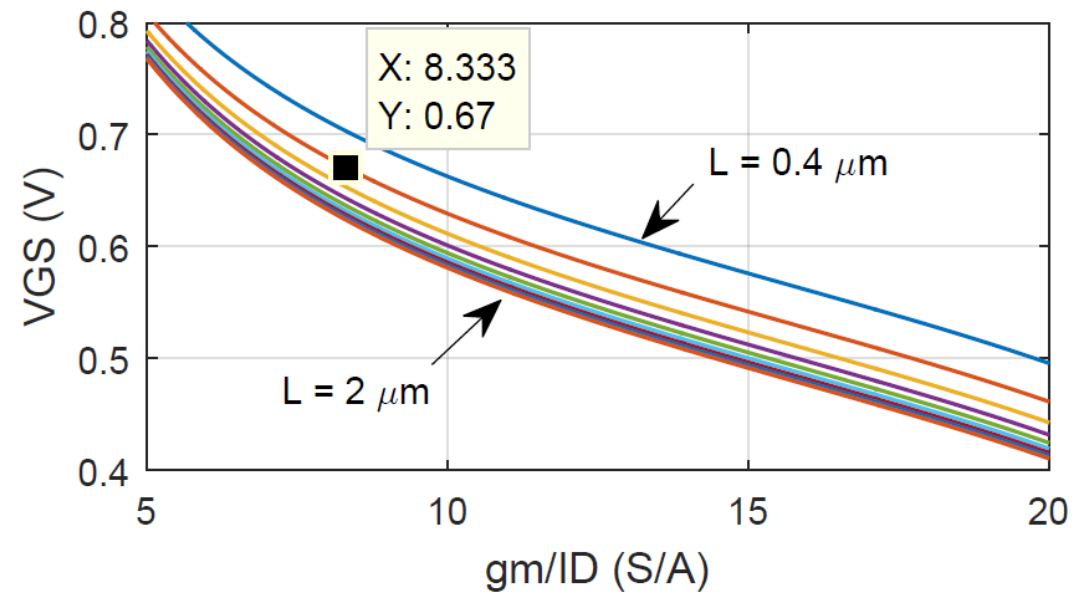 
$$V_{GS3,max} = 0.67 \text{ V}$$
$$\left(\frac{g_m}{I_D}\right)_{min} = 8.33$$



NMOS Current Mirror Load (5/6)

- ❑ The design of the current mirror load is determined by CMIR, noise, and output swing specs

$$V_{GS3,max} = 0.67 \text{ V}$$

$$\left(\frac{g_m}{I_D}\right)_{min} = 8.33$$


- ❑ Given no strict noise specification (to be discussed later), and to avoid placing M1,2 at edge of saturation, select a bit larger gm/ID

$$\frac{g_m}{I_D} = 10$$

NMOS Current Mirror Load (6/6)

- ❑ Assume minimum finger width is $2\ \mu\text{m}$
- ❑ Going to the I_D/W chart
 
$$\frac{I_d}{W} = 6.7 \rightarrow W = 2\ \mu\text{m}$$



Outline

- ☐ OTA required specifications
- ☐ Topology selection
- ☐ Tradeoffs Matrix
- ☐ Design of input pair
- ☐ Design of current mirror load
- ☐ Design of tail current source
- ☐ Sizing and simulation results

Tail Current Source (1/4)

$$A_{vCM} = \frac{V_{out}}{V_{iCM}} \approx -\frac{1}{2g_{m3,4}R_{SS}}$$

$$CMRR = \frac{A_v}{A_{vCM}} \approx g_{m1,2}(r_{o2} // r_{o4}) \cdot 2g_{m3,4}R_{SS}$$



- ❑ Long channel length means large output resistance: good CMRR @DC and good mirroring (less CLM)
 - But large area \rightarrow large parasitic cap: CMRR degrade at high frequencies
- ❑ Large g_m/I_D (small V^*): wide CMIR and wide swing
 - But large area \rightarrow large parasitic cap: ...
 - And more sensitivity to systematic V_{GS} errors (e.g., IR drops)

Tail Current Source (2/4)

$$|A_{vCM}| = \left| \frac{V_{out}}{V_{iCM}} \right| \approx \left| -\frac{1}{2g_{m3,4}R_{SS}} \right| = -38 \text{ dB} \rightarrow g_{ds5} < 2.6 \mu\text{S}$$

- $V_A = I_D r_o$ slightly decreases with g_m/I_D (weak dependence)
- Assume an arbitrary but large g_m/I_D , e.g., $g_m/I_D = 15$
  
$$\frac{g_m}{I_D} = 15 \rightarrow g_m = 300 \mu\text{S} \rightarrow \frac{g_m}{g_{ds}} > 115 \rightarrow L = 1.2 \mu\text{m}$$




Tail Current Source (3/4)

- The design is completed by CMIR spec (use V_{dsat5} or V_5^*)

$$CMIR_{HIGH} = V_{DD} - |V_{GS1}| - |V_{dsat5}| > 1.1 V$$

$$|V_{dsat5}| < 130 mV$$

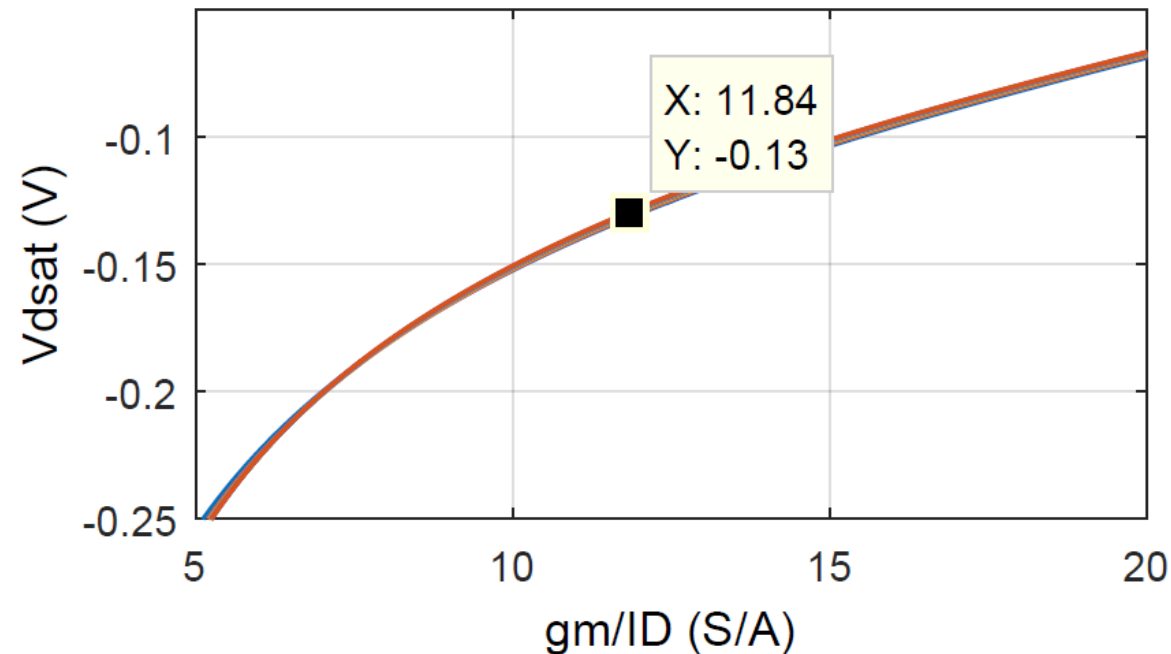
$$\frac{g_m}{I_D} > 11.8 \rightarrow \text{keep some margin and use } \frac{g_m}{I_D} = 14$$



Tail Current Source (4/4)

- Note that the tail current source has double the current
- Going to the I_D/W chart
 
$$\frac{I_d}{W} = 0.4 \rightarrow W \approx 52 \mu m$$




Outline


- ☐ OTA required specifications
- ☐ Topology selection
- ☐ Tradeoffs Matrix
- ☐ Design of input pair
- ☐ Design of current mirror load
- ☐ Design of tail current source
- ☐ Sizing and simulation results

Sizing Results


| Transistor | g_m/I_D | Length | Width | Function |
|------------|-----------|--------------|-----------------------------|---------------------|
| M1 and M2 | 16 | $0.8\ \mu m$ | $24\ \mu m$ | Input pair |
| M3 and M4 | 10 | $0.6\ \mu m$ | $2\ \mu m$ | Current mirror load |
| M5 and M6 | 14 | $1.2\ \mu m$ | $52\ \mu m$ and $26\ \mu m$ | Bias current mirror |

 

Simulation Results (1/4)


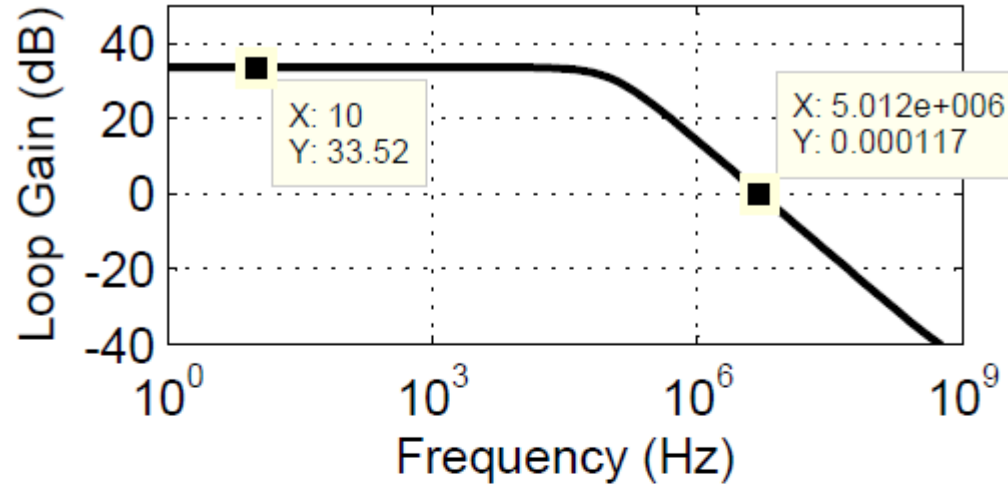


(a)

 


(b)

Simulation Results (2/4)

  


(a)

 

(b)

Simulation Results (3/4)

 

Simulation Results (4/4)

| Specification | Required | Achieved |
|--------------------------------|-------------------|---------------------|
| OTA Current Consumption | $20\ \mu A$ | $20\ \mu A$ |
| GBW | $5\ MHz$ | $5\ MHz$ |
| Phase Margin | 70° | 90° |
| Open Loop DC gain | $32\ dB$ | $33.5\ dB$ |
| Total Integrated Thermal Noise | $50\ \mu V_{rms}$ | $48.6\ \mu V_{rms}$ |
| Input Range | $0.2\ V - 1.1\ V$ | $0.14\ V - 1.12\ V$ |
| CMRR | $70\ dB$ | $73.6\ dB$ |


Notes

- ❑ The design charts (especially g_m/g_{ds}) depend on V_{DS}
 - We neglected this dependence for simplicity
- ❑ We neglected body effect (should be considered if input pair is NMOS)
- ❑ We did not consider OTA self-loading
- ❑ We did not consider process variations, mismatch, and noise
- ❑ Taking the above points into account (and even more)
 - The design procedure becomes a bit complicated iterative procedure
 - But it is still “systematic”
 - Thus can be automated using a computer program!

Thank you!


References (1/3)

 - ❑ P. Jespers and B. Murmann, Systematic Design of Analog CMOS Circuits Using Pre-Computed Lookup Tables, Cambridge University Press, 2017.



References (2/3)

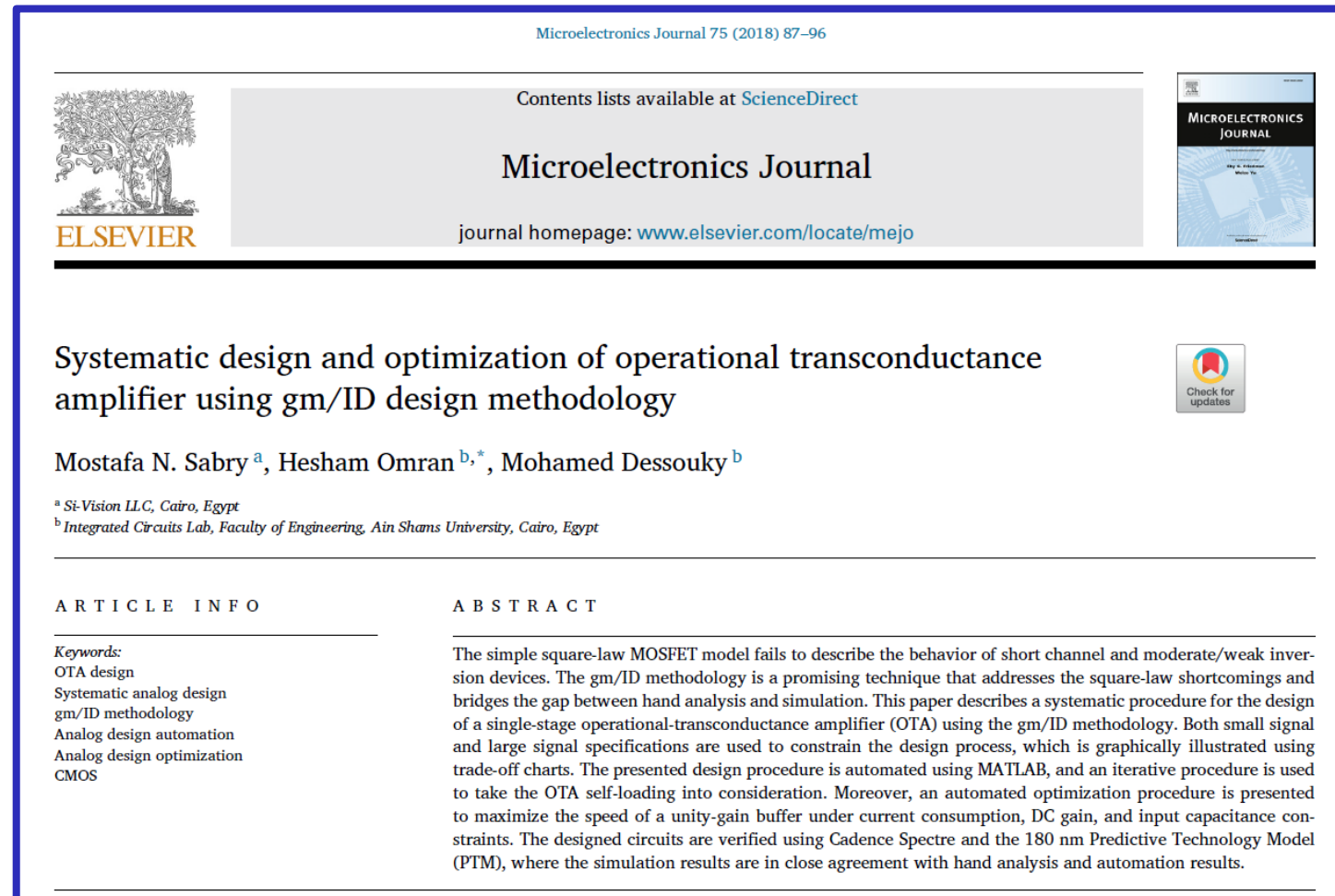- ❑ M. N. Sabry, H. Omran and M. Dessouky, "Systematic design and optimization of operational transconductance amplifier using gm/ID design methodology," *Microelectronics Journal*, vol. 75, pp. 87-96, May 2018.



References (3/3)

- ❑ B. Murmann, Gm/ID Starter Kit. [Online]. Available: <https://web.stanford.edu/~murmann/gmid>
- ❑ B. Murmann, EE214B Course Reader, Stanford University.
- ❑ B. Razavi, “Design Of Analog CMOS Integrated Circuit,” 2nd ed., McGraw-Hill, 2017.
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” 2nd ed., Wiley, 2012.