

Lab 6

Differential Amplifier

Part 1: Sizing Chart

Required Spec:

Parameter	
Supply (V_{DD})	1.8V
Bias current (I_{SS})	40 μ A
Differential gain	8
CM output level	$V_{DD}/3$
Load capacitance	1pF
Supply (V_{DD})	1.8V
Bias current (I_{SS})	40 μ A

Input Pair Sizing:

$$\text{Required } R_D: V_{RD} = 0.6 \rightarrow R_D = \frac{V_{RD}}{I_D} = \frac{0.6}{20\mu} = 30K\Omega$$

$$|A_v| \approx 0.91 \times gm R_D = 0.91 \times \frac{2ID}{V^*} \times R_D = \frac{1.82V_{RD}}{V^*} = 8$$

$$V^* = \frac{1.82V_{RD}}{|A_v|} \approx 136mV \quad (\text{Assuming } r_o = 10 * R_D)$$

From SA: $L = 350nm$, $W = 30.79\mu m$

8) The SA assumes V_{DS} at 0.9V

Thus $V_{CM} = V_{DD} - V_{GS_{4,3}} - V_{DS_1} = 0.56V$

The screenshot shows the Sizing Assistant interface for a PMOS transistor. The LUT is set to 'pmos_03v3'. The corner is 'TT' and the temperature is '27.0 °C'. The frequency is '1'. The input parameters are: ID = 20u, Vstar = 136m, ro = 300k, VDS = 0.9, VSB = 0.3, and Stack = 1. The results table shows the following values:

Name	TT-27.0
IG	N/A
L	350n
W	30.79u
VGS	939.3m
VDS	900m
VSB	300m
gm/ID	14.33
Vstar	139.5m
fT	1.094G
gm/gds	89.8

The Y-Expr is set to 'gm/ID*fT'.

Figure 1 Input Pair Dimensions from Sizing Assistant

Current Mirror Sizing:

Parameter	
Input current	$20\mu A$
Percent mismatch: $\sigma(I_{out})/I_{out}$	$\leq 2\%$
Compliance voltage	$\leq 200mV$
Area	Minimize

Using the equation supplied in the Lab manual for mismatch we can draw the following graphs

 


Figure 2 L vs Vstar

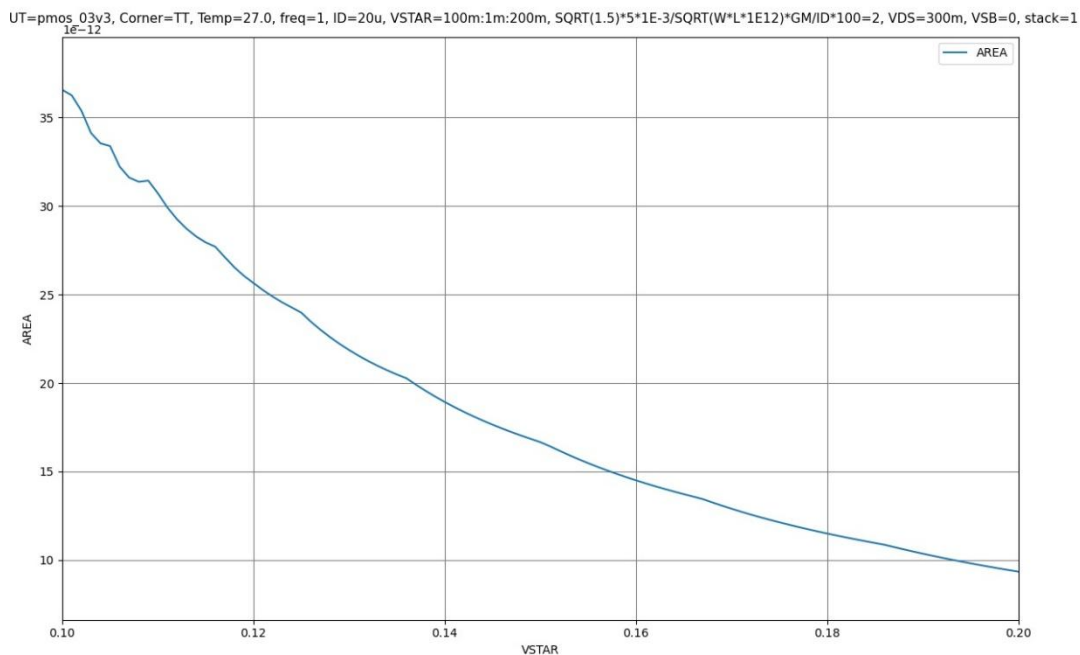


Figure 3 Area vs Vstar

 


Figure 4 W vs Vstar

Smallest area can be found at the largest acceptable value for V Compliance (200mV)

 


Figure 5 L at Required Vstar

 


Figure 6 W at Required Vstar

 


Figure 7 Area at Required Vstar

$$L = 517.8nm \quad , \quad W = 18.13\mu m$$

CM Input Level:

$$VICM_{MAX} = V_{DD} - V_{GS4} - V_1^* = 0.66V$$

$$VICM_{MIN} = 0.6 - V_{TH4} = -0.27V$$

The chosen VICM is a little close to the max input but has enough headroom, ideally though it should be at the average between the Max and Min

Part 2: Differential Amplifier

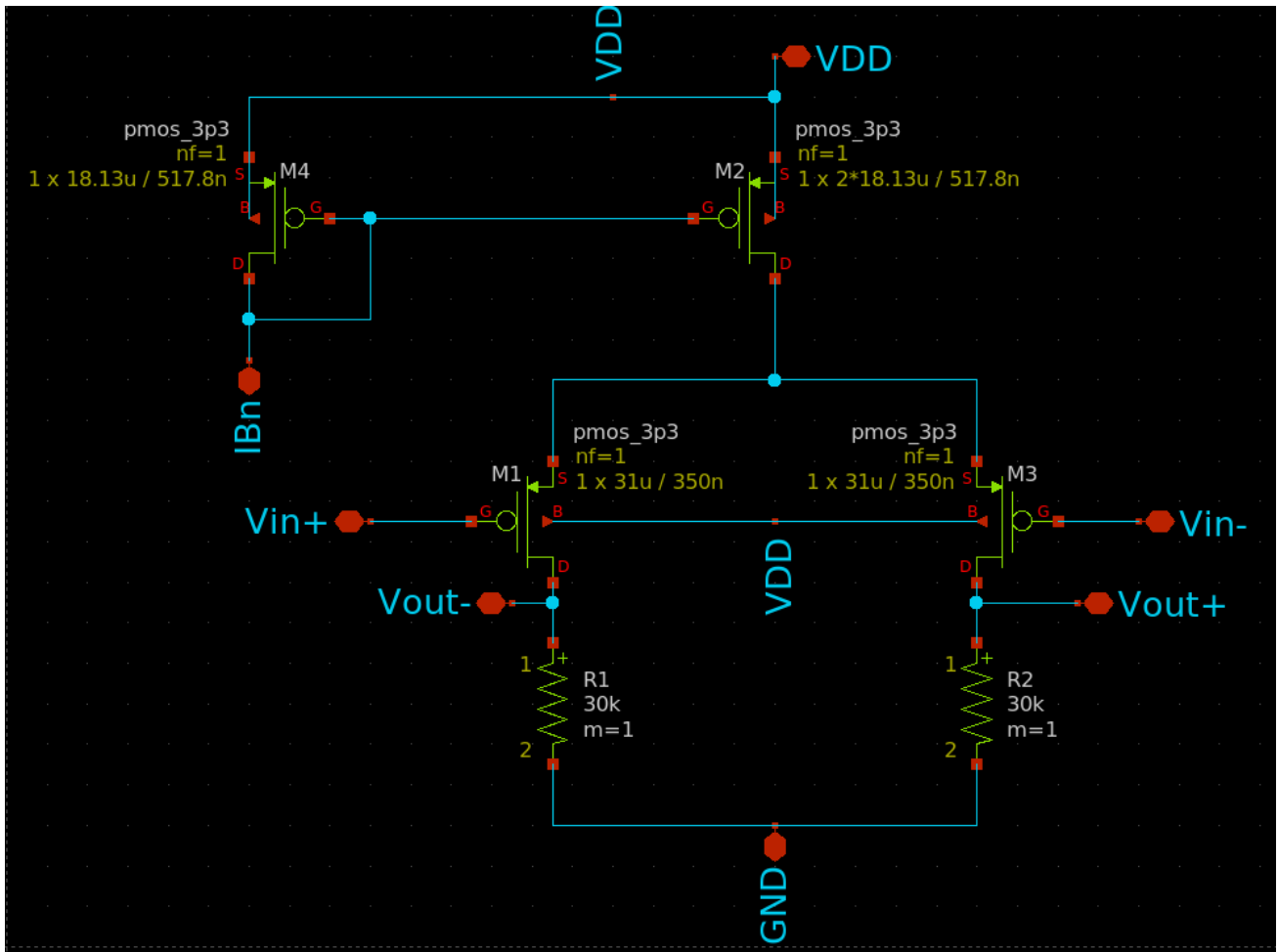


Figure 8 Differential Amplifier Schematic

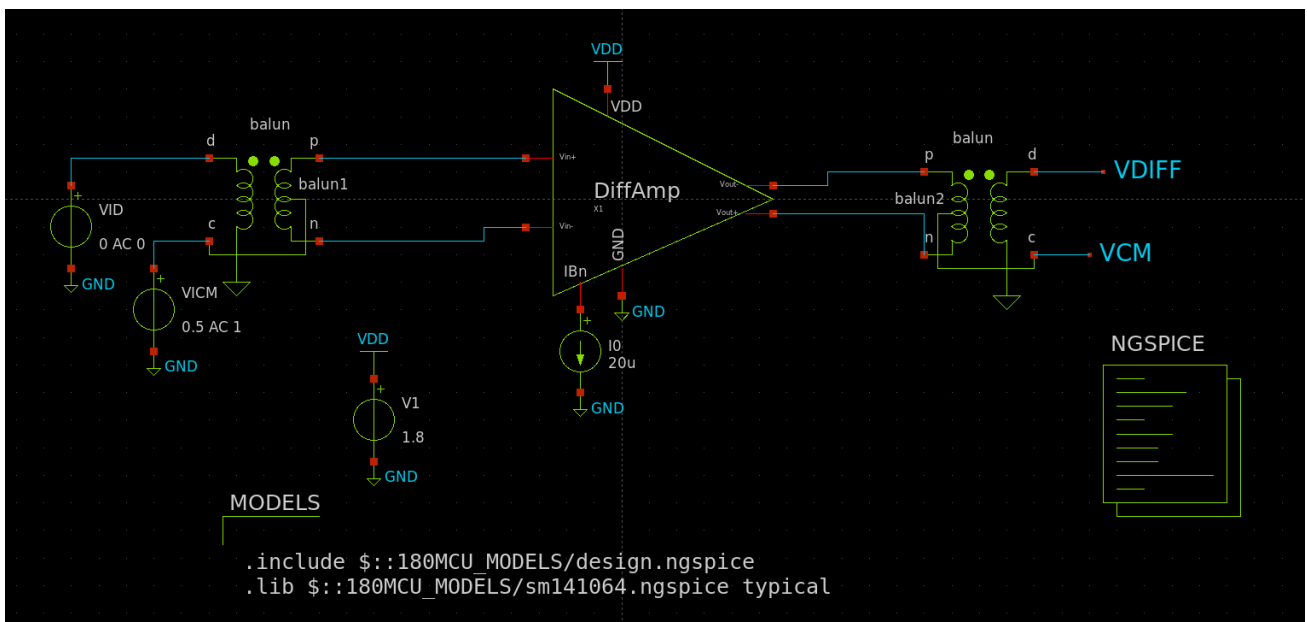


Figure 9 Testbench Schematic

OP Simulation:

```

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm2.m0      m.x1.xm1.m0      m.x1.xm3.m0
model       pmos_3p3.13      pmos_3p3.13      pmos_3p3.12
id          2e-05            3.84363e-05      1.92122e-05
gm          0.000205671      0.000392872      0.000284521
gds         1.0154e-06      5.81319e-06      3.09947e-06
vgs         0.940662        0.940662        0.937446
vth         0.790503        0.790148        0.87411
vds         0.940661        0.30255         0.921078
vdsat       0.165849        0.166111        0.11699

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m.x1.xm4.m0
model       pmos_3p3.12
id          1.92241e-05
gm          0.000284646
gds         3.10138e-06
vgs         0.937446
vth         0.874068
vds         0.920722
vdsat       0.117017

```

Figure 10 Operating Point of All Transistors

Note: xschem doesn't have support for the region variable.
All transistors appear to be in **Saturation!**

Diff Small Signal CCS:

 


Figure 11 Bode Plot of Diff Gain

```
gain = 7.742132e+00
bw = 5.669427e+06
```

Figure 12 Gain and BW from Simulation

Analytical Solution: $A_v = 0.91gmR_D = 7.769 \rightarrow 17.8 \text{ dB}$

$$BW = \frac{1}{\tau} = \frac{1}{2\pi R_D C_L} = 5.3 \text{ MHz}$$

	Analytical	Simulation
Diff Gain	7.769	7.742
Diff Gain (dB)	17.8 dB	17.78 dB
BW	5.3MHz	5.66MHz

CM Small Signal CCS:

 


Figure 13 AvCM Bode Plot

```
cmgain = 6.401523e-02
```

Figure 14 CM gain from Simulation

Analytical Solution:

$$A_{vCM} = \frac{gmR_D}{1 + 2(gm + gmb)R_{SS}} = 6.53 * 10^{-2}$$

	Analytical	Simulation
CM Gain	6.53e-2	6.4e-2
CM Gain (dB)	-23.69 dB	-23.87 dB

The common mode gain experiences a Pole then a Zero then another Pole at very high frequencies, the Pole caused by the high impedance node at the current source node causes it to fall till it reaches the zero also caused by the same node due to the parasitic capacitances seen at it (CP).

CMRR:

 


Figure 15 CMRR vs Frequency Bode Plot

```
cmgain      = 6.401523e-02
diffgain    = 7.767959e+00
cmrr_val    = 1.213455e+02
```

Figure 16 CMRR Value from Simulation

Analytical Solution:

$$CMRR = 1 + 2(gm + gmbs)_{1,2}R_{SS} = 130.5 \rightarrow 42.27dB$$

	Analytical	Simulation
CMRR	130.5	42.27
CMRR	121.3	41.68 dB

At high frequencies parasitic capacitances at the RSS node cause it to short significantly decreasing CMRR as we increase frequency.

Diff Large Signal CCS:

 


Figure 17 VODIFF vs VIDIFF

Analytical Solution:

At Extreme points current is steered completely into one of the two transistors while the other turns off thus $V_{odiff} = V_{pos}$ only or V_{neg} only

$$V_{ODIFF_{MAX}} = I_D R_D = 1.2V$$

	Analytical	Simulation
VODIFF Extreme	1.2	1.76

The simulation result is slightly less than the Analytical result due to current mirror errors, the current steered into the transistor is slightly less than 40uA as used in the calculations resulting in slightly less voltage.

CM Large Signal CCS:

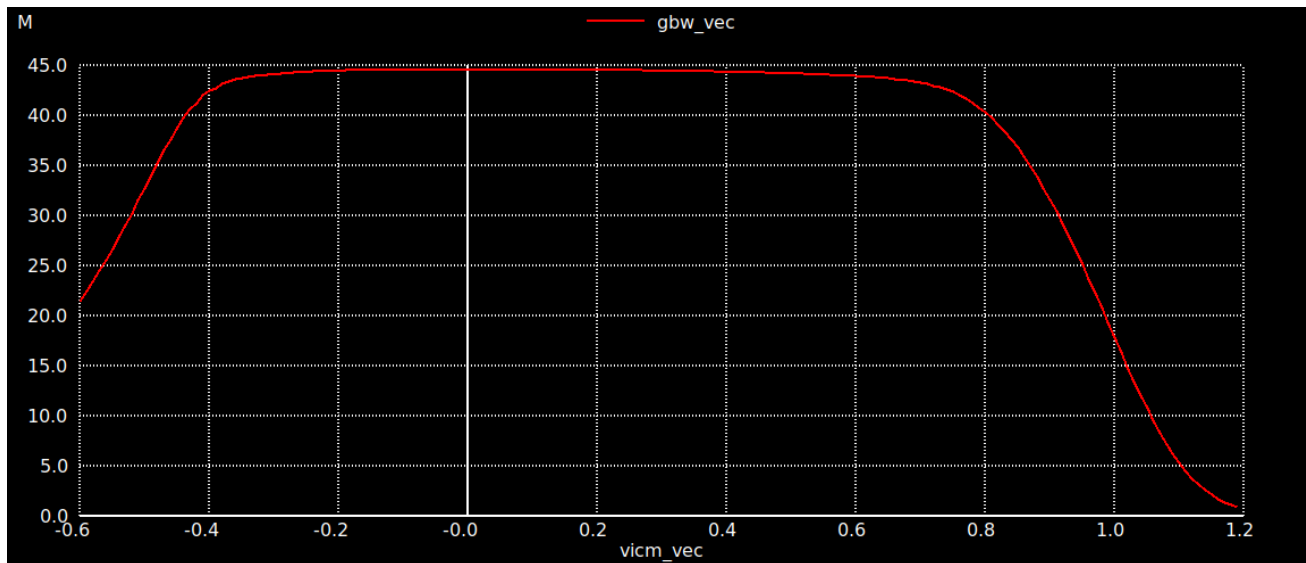


Figure 18 GBW vs VICM

```
vicmmax = 8.000000e-01
vicmmin = -4.400000e-01
```

Figure 19 VINCM Range from Simulation

Analytic Solution:

Using the same expressions derived during sizing we can find the the input range but using the results from the OP analysis

$$VICM_{MAX} = V_{DD} - V_{GS4} - V_{DSAT1} = 0.689V$$

$$VICM_{MIN} = ID_4 * R_D - V_{TH4} = -0.303V$$

	Analytical	Simulation
VINCM Minimum	-0.303	-0.44
VINCM Maximum	0.689	0.8