

Analog IC Design

Lecture 18 Noise in Amplifier Circuits

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Outline

- ❑ Recapping previous key results
- ❑ Noise in Amplifiers

Outline

- ❑ Recapping previous key results
- ❑ Noise in Amplifiers

MOSFET in Saturation




- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \quad \text{or} \quad V_{DS} \geq V_{ov}$$


- ❑ Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
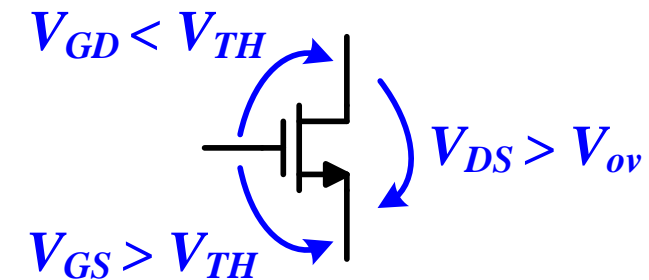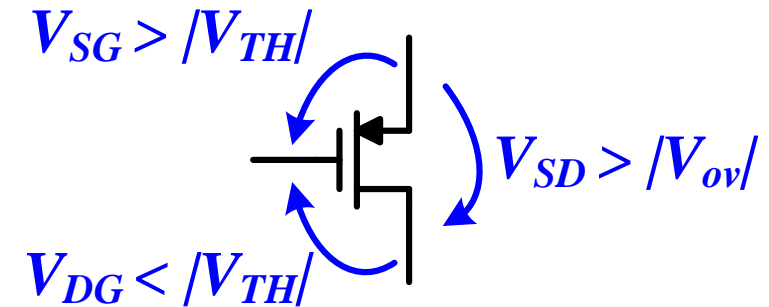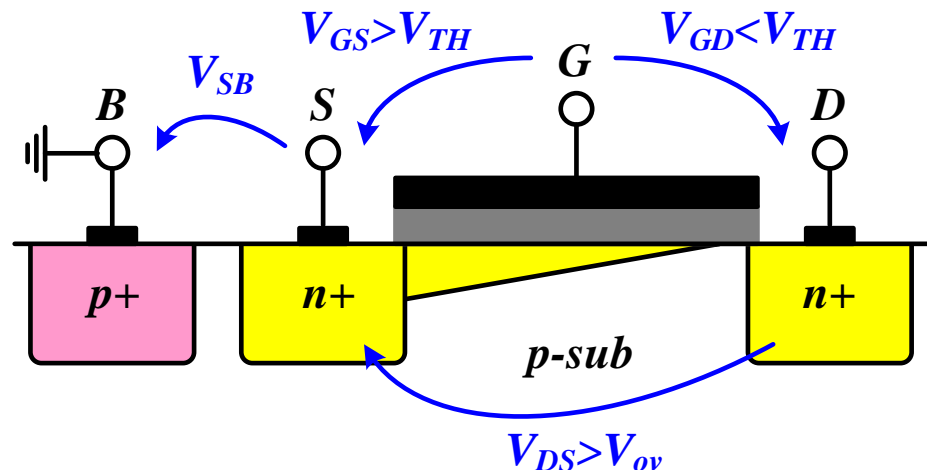
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$



Regions of Operation Summary

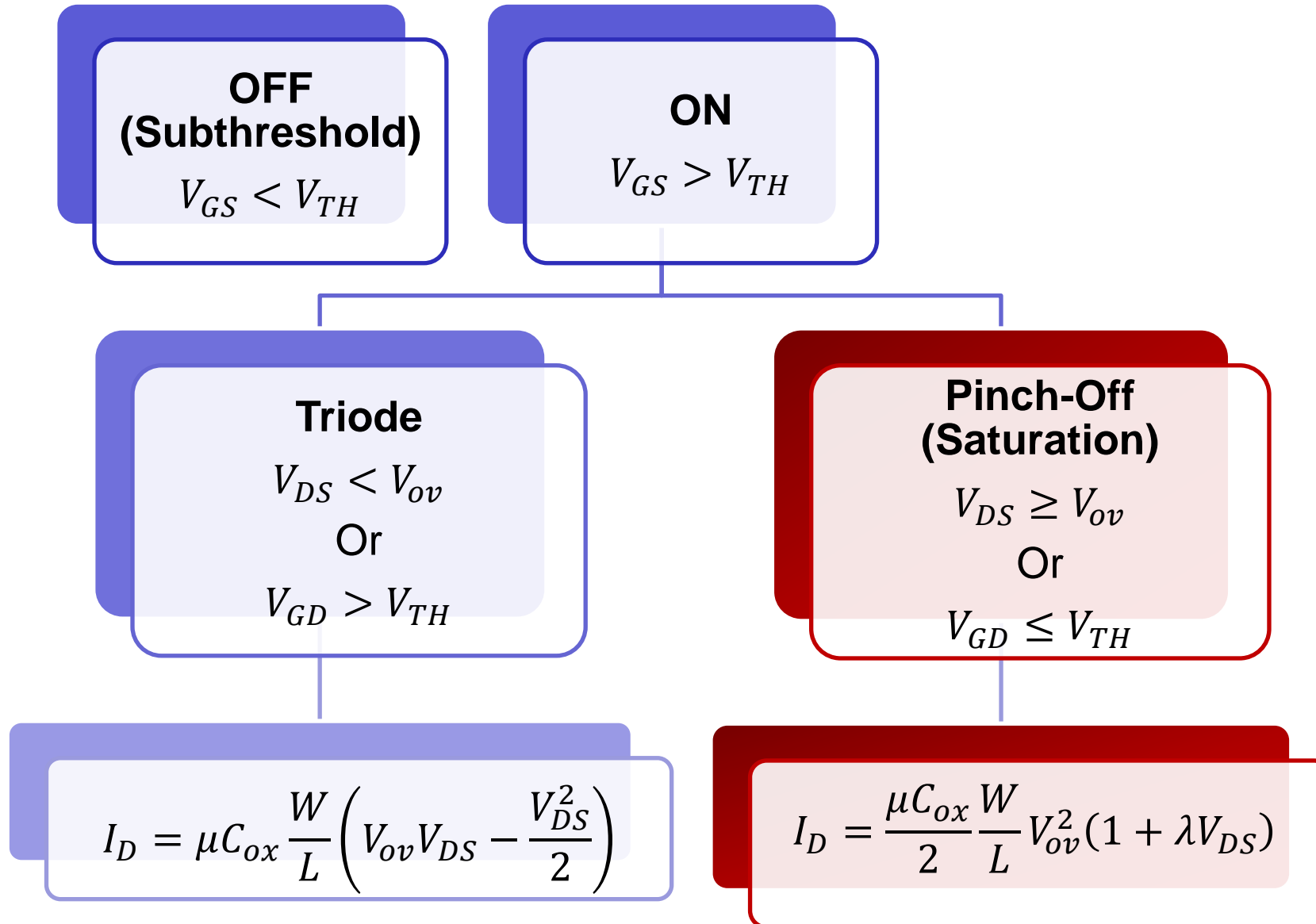

High Frequency Small Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$


$$g_{mb} = \eta g_m \quad \eta \approx 0.1 - 0.25$$

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D} \quad V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L} \quad V_{DS} \uparrow V_A \uparrow$$


$$C_{gb} \approx 0$$

$$C_{gs} \gg C_{gd}$$




$$C_{sb} > C_{db}$$

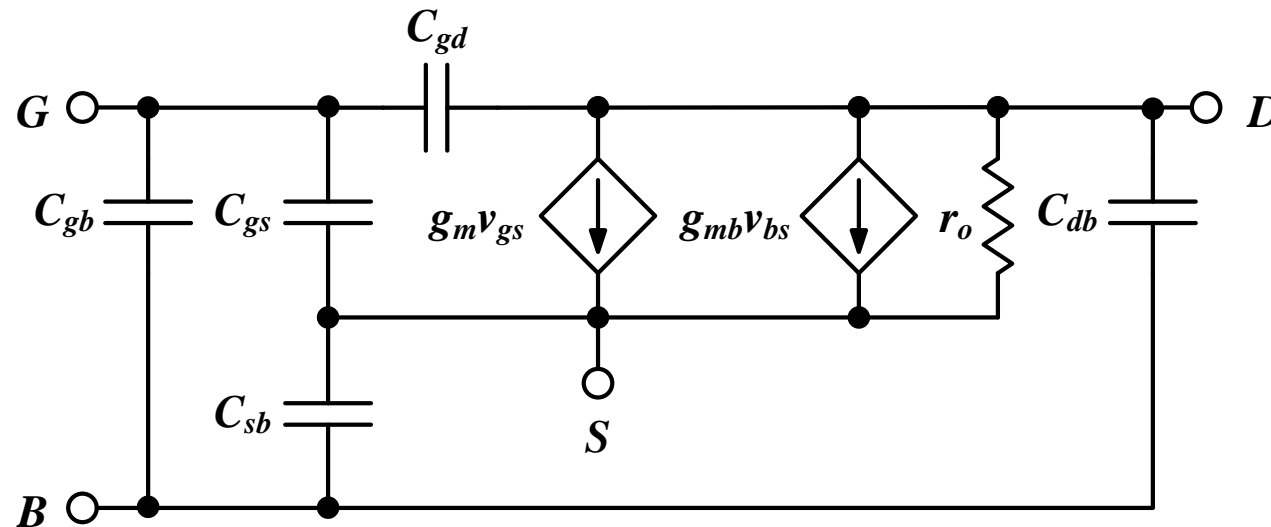

Rin/out Shortcuts Summary

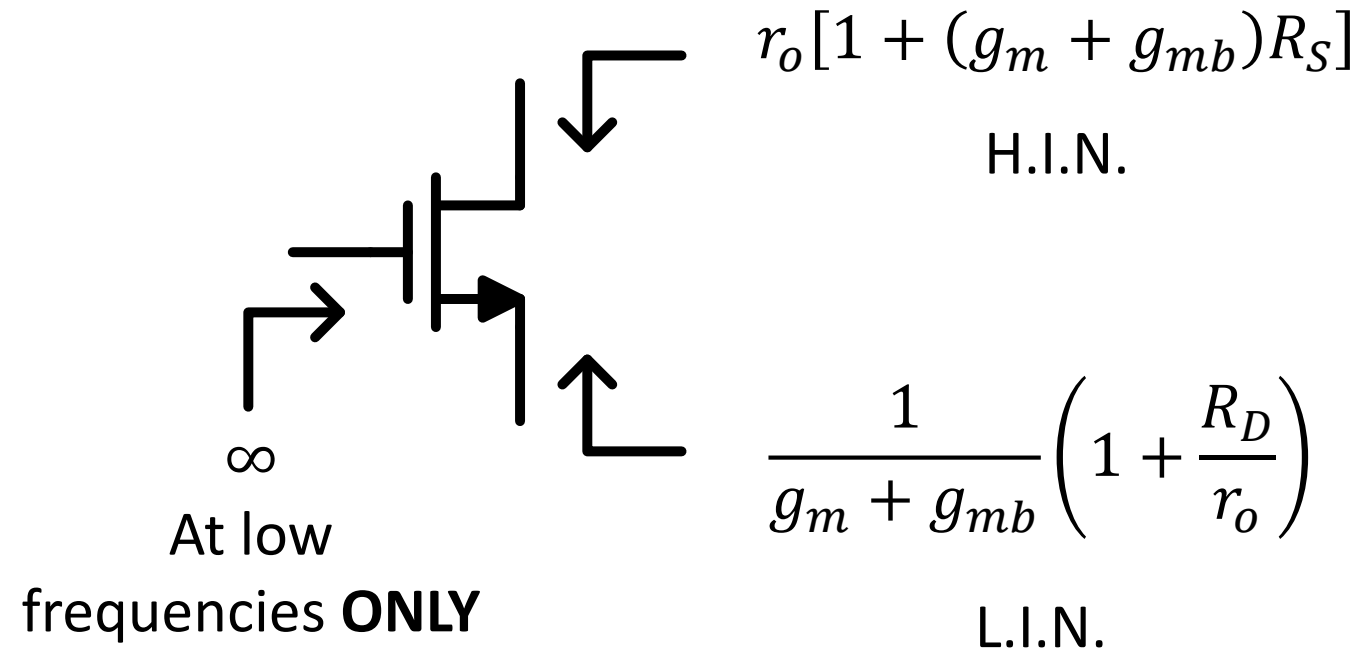

Summary of Basic Topologies

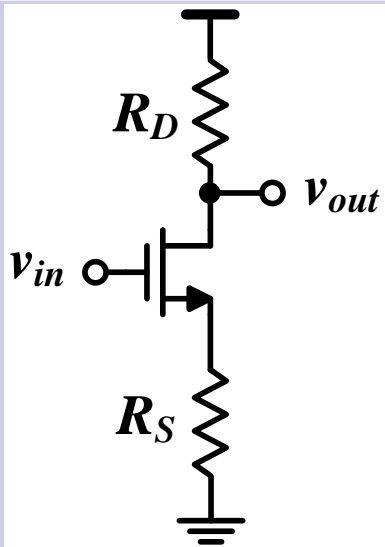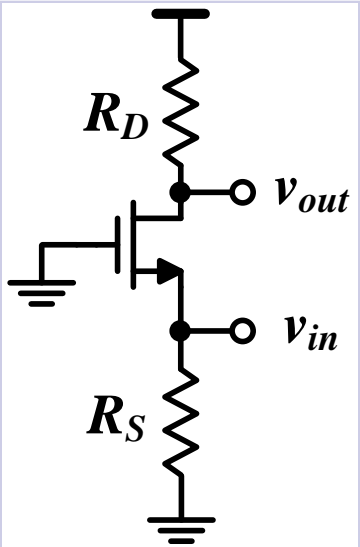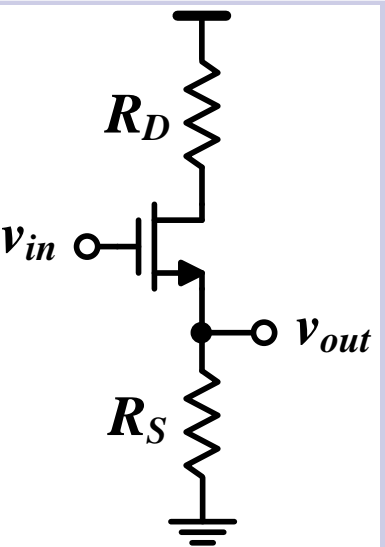	CS	CG	CD (SF)
			
	Voltage & current amplifier	Voltage amplifier Current buffer	Voltage buffer Current amplifier
R_{in}	∞	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$	∞
R_{out}	$R_D \parallel r_o [1 + (g_m + g_{mb})R_S]$	$R_D \parallel r_o$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$
G_m	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$

Differential Amplifier



	Pseudo Diff Amp	Diff Pair (w/ ideal CS)	Diff Pair (w/ R_{SS})
A_{vd}	$-g_m R_D$	$-g_m R_D$	$-g_m R_D$
A_{vCM}	$-g_m R_D$	0	$\frac{-g_m R_D}{1 + 2(g_m + g_{mb})R_{SS}}$
A_{vd}/A_{vCM}	1	∞	$2(g_m + g_{mb})R_{SS} \gg 1$

$$A_{vCM2d} = \frac{v_{od}}{v_{iCM}} \approx \frac{\Delta R_D}{2R_{SS}} + \frac{\Delta g_m R_D}{2g_{m1,2}R_{SS}}$$

$$CMRR = \frac{A_{vd}}{A_{vCM2d}}$$

Op-Amp

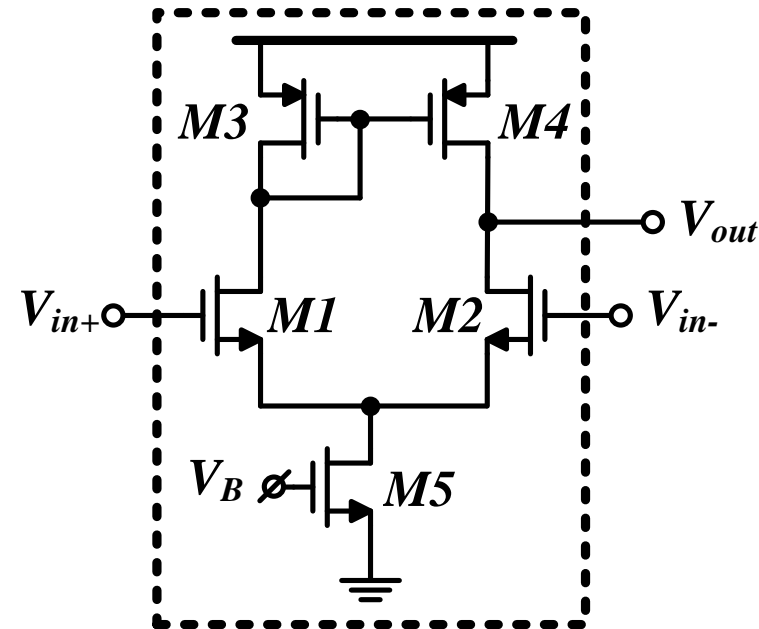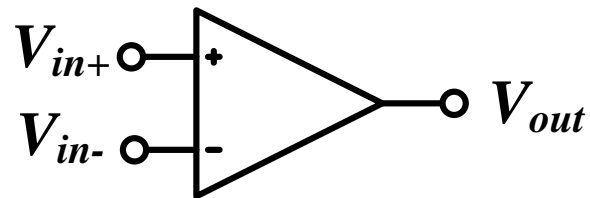- ❑ An op-amp is simply a high gain differential amplifier
 - The gain can be increased by using cascodes and multi-stage amplification
- ❑ The diff amp is a key block in many analog and RF circuits
 - DEEP understanding of diff amp is ESSENTIAL



Op-Amp vs OTA

- ❑ In short, an OTA is an op-amp without an output stage (buffer)
- ❑ Some designers just use op-amp name and symbol for both

	Op-amp	OTA
Rout	LOW	HIGH
Model		
Diff input, SE output		
Fully diff		

V-star (V^*)

- V-star (V^*) is inspired by V_{ov} but calculated from actual simulation data

$$g_m = \frac{2I_D}{V^*} \leftrightarrow V^* = \frac{2I_D}{g_m} = \frac{2}{g_m/I_D}$$

- Figures-of-merit in terms of V^*

$$g_m r_o = \frac{2I_D}{V^*} \cdot \frac{1}{\lambda I_D} = \frac{2}{\lambda V^*}$$

$$f_T = \frac{g_m}{2\pi C_{gg}} = \frac{1}{2\pi} \cdot \frac{2I_D}{V^*} \cdot \frac{1}{C_{gg}}$$

$$\frac{g_m}{I_D} = \frac{2}{V^*}$$

- The boundary between weak and strong inversion ($n = 1.2 \rightarrow 1.5$)



$$V_{ov}(SI) = V^*(WI) = 2nV_T \approx 60 \rightarrow 80mV$$

Negative Feedback

$$\beta = \frac{R_2}{R_1 + R_2}$$

$$A_{CL} = \frac{V_{out}}{V_{in}} = \frac{A_{OL}}{1 + \beta A_{OL}} = \frac{A_{OL}}{1 + \beta A_{OL}} \approx \frac{1}{\beta} = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$

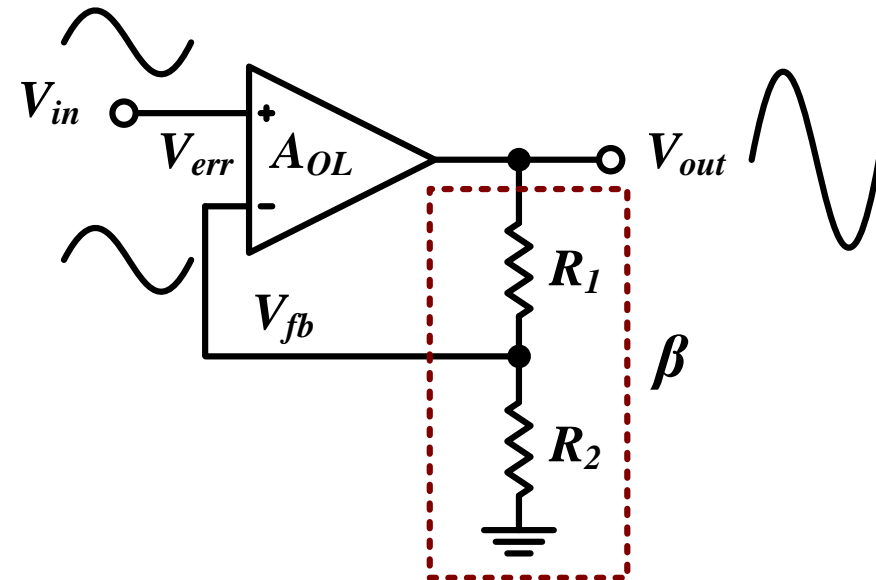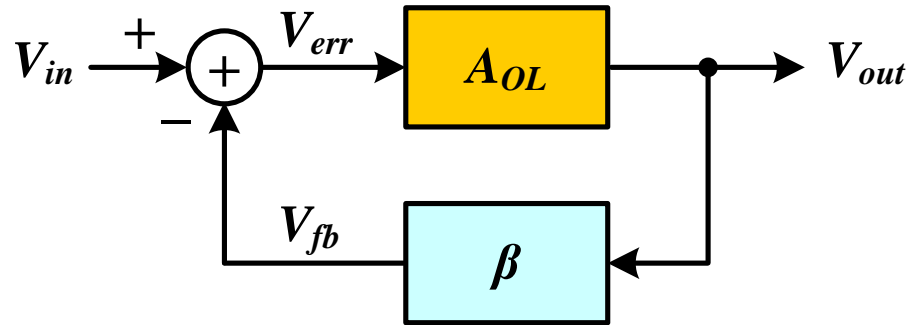
$$\omega_{p,CL} = (1 + \beta A_{OLo})\omega_{P,OL}$$



Phase Margin and the Ultimate GBW


- If $\omega_{p2} = \omega_u$: PM = 45°
 - Typically inadequate (peaking/ringing)
- Thus ω_{p2} should be $> \omega_u \rightarrow \omega_{p1} \ll \omega_u < \omega_{p2}$
 - ω_{p1} defines OL BW and ω_{p2} defines ultimate GBW (max CL BW)

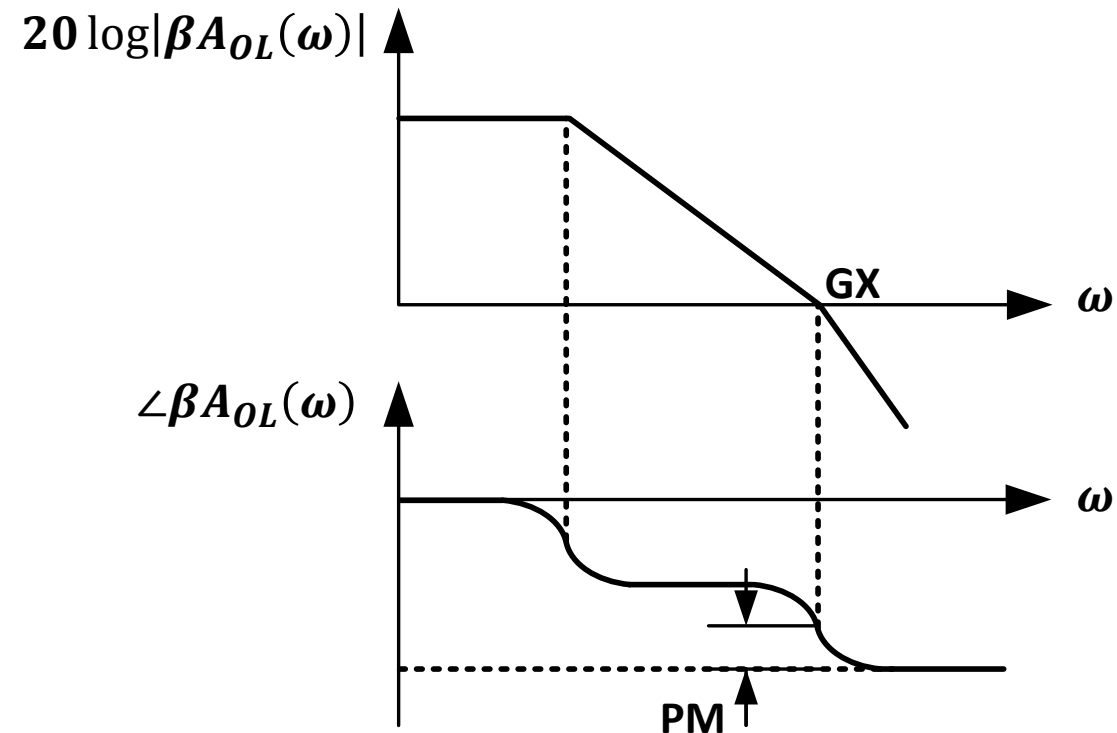Frequency domain peaking
→ noise amplification
Time domain ringing
→ poor settling time



Noise Models


Resistor thermal noise

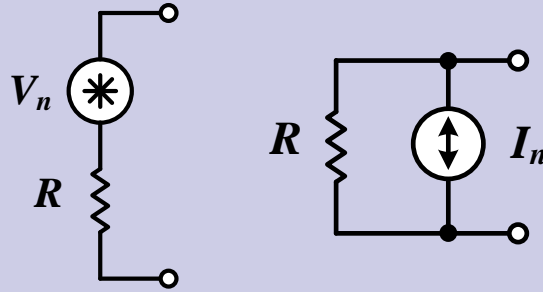

$$V_n(f) = \sqrt{4kTR} \approx \sqrt{\frac{R}{1\text{ k}}} \times 4 \frac{\text{nV}}{\sqrt{\text{Hz}}}$$

$$I_n(f) = \sqrt{\frac{4kT}{R}} \approx \sqrt{\frac{1\text{ k}}{R}} \times 4 \frac{\text{pA}}{\sqrt{\text{Hz}}}$$


MOSFET thermal and flicker noise

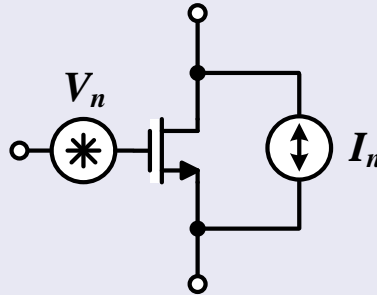

$$I_n^2(f) = 4kT\gamma g_m$$

$$V_n^2(f) = \frac{K}{C_{ox}WL} \frac{1}{f}$$

RMS noise

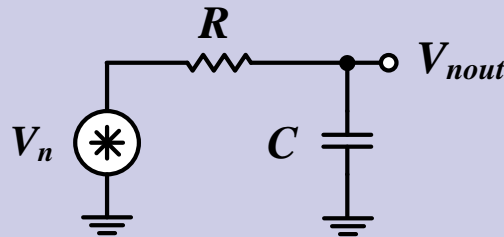

$$V_{n\text{outrms}}^2 = 4kTR \times B_N = \frac{kT}{C}$$

$$B_N = \frac{1}{4RC} = \frac{\pi}{2} f_p$$

$$V_{n\text{outrms}} \approx \sqrt{\frac{1\text{ p}}{C}} \times 64 \mu\text{Vrms}$$

Noise Analysis Procedure

- ❑ Deactivate the input signal
- ❑ Identify the **dominant** noise sources → Model as $V_n^2(f)$ or $I_n^2(f)$
- ❑ Find the output noise density for each source: $V_{nout,x}^2(f)$
- ❑ Calculate the rms output noise of each source

$$V_{nourms,x}^2 = V_{nout,x}^2(f) \times B_{N,x}$$

- ❑ Calculate total rms noise

$$V_{nourms,tot}^2 = V_{nrms,1}^2 + V_{nrms,2}^2 + \dots$$

- ❑ Calculate the input-referred rms noise voltage

$$V_{ninrms,tot}^2 = V_{nourms,tot}^2 / A_v^2$$

- ❑ For low Z_{in} , input referred noise current must be added

Outline

- ❑ Recapping previous key results
- ❑ Noise in Amplifiers

Noise in Amplifiers

- ☐ Common source amplifier
- ☐ Common gate amplifier
- ☐ Common drain amplifier
- ☐ Cascode amplifier
- ☐ Differential amplifier
- ☐ Common OTA topologies
 - 5T OTA
 - Telescopic cascode OTA
 - Folded cascode OTA
 - Two-stage OTA

CS Amplifier with Resistive Load


- Deactivate the input and find the noise spectral density at output

$$V_{nout}^2(f) = \left(4kT\gamma g_m + \frac{4kT}{R_D} \right) R_D^2 + \frac{K}{C_{ox}WL} \frac{1}{f} \cdot (g_m R_D)^2$$

- Divide by gain to get input-referred noise

$$V_{nin}^2(f) = \frac{V_{nout}^2(f)}{(g_m R_D)^2} = \frac{4kT}{g_m} \left(\gamma + \frac{1}{g_m R_D} \right) + \frac{K}{C_{ox}WL} \frac{1}{f}$$

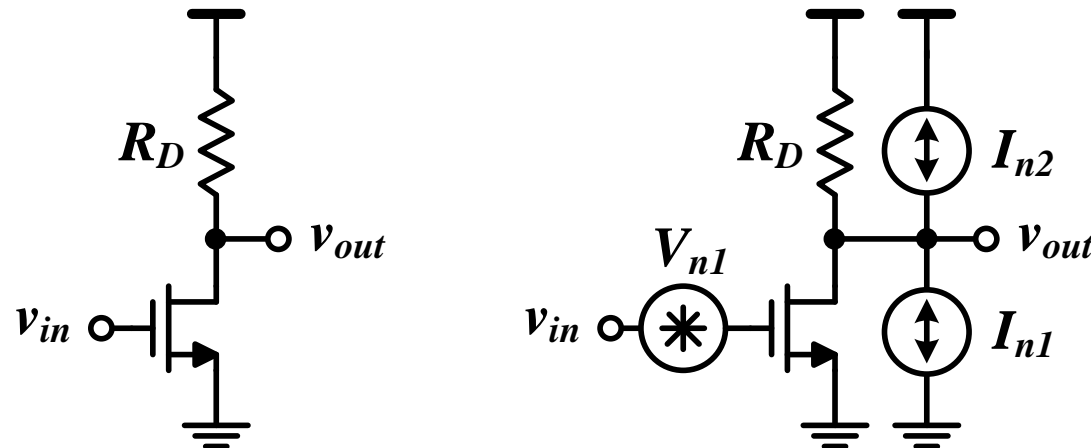- Maximize $g_m \rightarrow$ noise-power trade-off



CS Amplifier with Active Load



- Find the noise spectral density at output

$$V_{nout}^2(f) = (4kT\gamma g_{m1} + 4kT\gamma g_{m2})R_{out}^2$$

- Divide by gain to get input-referred noise

$$V_{nin}^2(f) = \frac{V_{nout}^2(f)}{(g_{m1}R_{out})^2} = \frac{4kT\gamma}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right) = \frac{4kT\gamma\alpha}{g_{m1}}$$

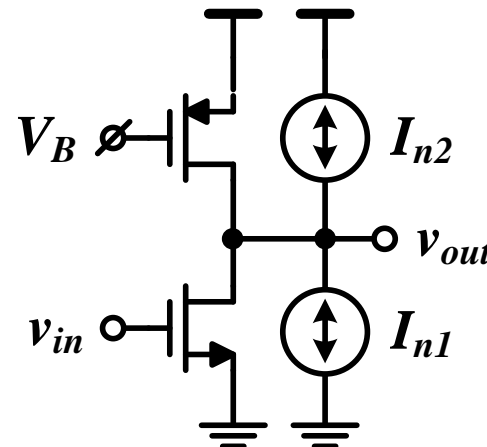
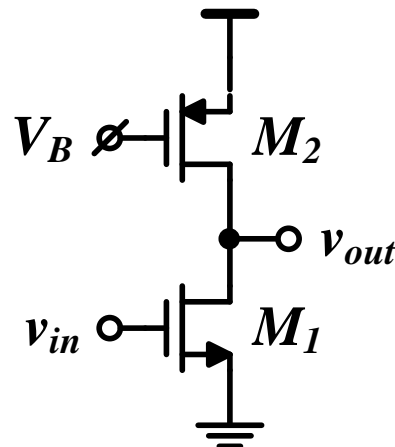
- Maximize g_{m1} (transconductor) and minimize g_{m2} (current source)



Small or Large g_m ?

$$V_{nin}^2(f) = \frac{4kT\gamma}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right) = \frac{4kT\gamma\alpha}{g_{m1}}$$

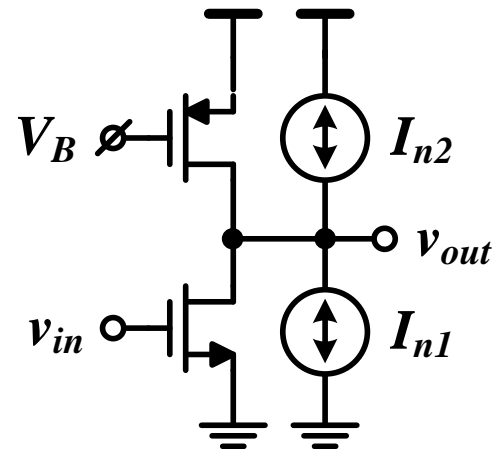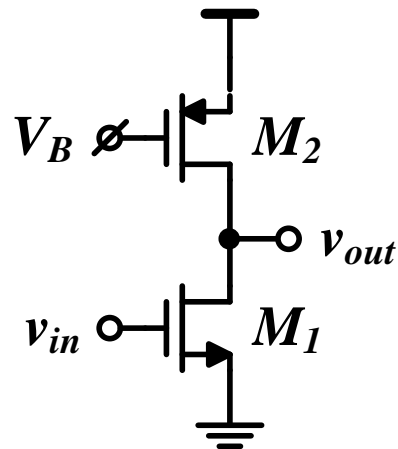- ❑ From noise perspective, do we want small or large g_m ?
- ❑ Large g_m for amplifier/transconductor (g_{m1}) \rightarrow Large gm/ID
 - Noise power $\propto g_{m1}$ but signal power $\propto g_{m1}^2$
- ❑ Small g_m for constant current source (g_{m2}) \rightarrow Small gm/ID
 - Noise power $\propto g_{m2}$ but signal power independent of g_{m2}



Design for Low Noise: Thermal Noise


$$V_{nin}^2(f) = \frac{4kT\gamma}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right)$$

□ Maximize g_{m1}

- $I_D \uparrow \rightarrow \text{power consumption} \uparrow$
- Or $(g_m/I_D)_1 \uparrow \rightarrow V_1^* \downarrow \rightarrow f_T \downarrow$ (area and capacitance \uparrow)

□ Minimize g_{m2}

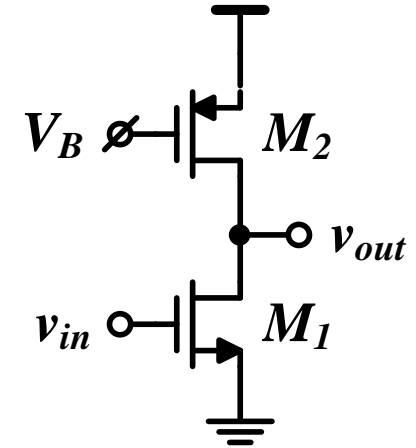- $(g_m/I_D)_2 \downarrow \rightarrow V_2^* \uparrow \rightarrow \text{headroom} \downarrow$



Design for Low Noise: Flicker Noise


$$V_{nin}^2(f) = \frac{K_N}{C_{ox}(WL)_1} \frac{1}{f} + \frac{K_P}{C_{ox}(WL)_2} \frac{1}{f} \left(\frac{g_{m2}}{g_{m1}} \right)^2$$

□ If $L_1 = L_2$: NMOS dominates

▪ Because $K_N > K_P$ and $\mu_N > \mu_P$

□ Increase $W_1 \rightarrow I_D \uparrow$ (if V^* is constant) \rightarrow power consumption \uparrow

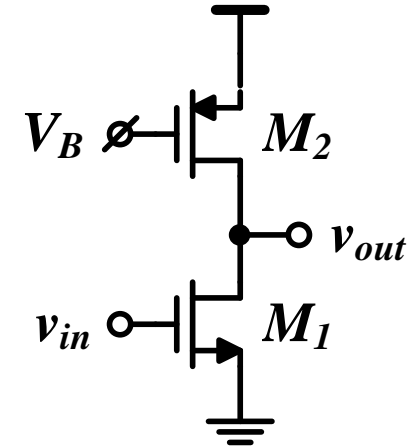□ Increase $L_1 \rightarrow f_T \downarrow \rightarrow$ area and capacitance \uparrow



CS Amplifier SNR

- Assume BW is limited by a load capacitance C_L

$$V_{n_{out}rms}^2 = V_{n_{out}}^2(f) \cdot \frac{1}{4R_{out}C_L} \approx \frac{kT\gamma\alpha g_{m1}R_{out}}{C_L}$$

- Assume input signal is a sinusoid with amplitude = V_p

$$\begin{aligned} SNR &= \frac{V_{outrms}^2}{V_{n_{out}rms}^2} \approx \left(\frac{V_p}{\sqrt{2}} \cdot g_{m1}R_{out} \right)^2 \cdot \frac{C_L}{kT\gamma\alpha g_{m1}R_{out}} \\ &= \frac{V_p^2}{2} \frac{g_{m1}R_{out}C_L}{kT\gamma\alpha} = \frac{V_p^2}{2} \frac{g_{m1}R_{out}C_L}{kT\gamma \left(1 + \frac{g_{m2}}{g_{m1}} \right)} \end{aligned}$$

- Maximize g_{m1} (transconductor) and minimize g_{m2} (current source)
 - Large gm/ID for transconductor and small gm/ID for load

CS Amplifier SNR


- Assume a maximum rms output amplitude = κV_{DD}

$$\begin{aligned} SNR &= \frac{V_{outrms}^2}{V_{nourms}^2} \approx (\kappa V_{DD})^2 \cdot \frac{C_L}{kT\gamma\alpha g_{m1}R_{out}} \\ &= \frac{(\kappa V_{DD})^2 C_L}{kT\gamma \left(1 + \frac{g_{m2}}{g_{m1}}\right) |A_v|} \end{aligned}$$

- Maximize g_{m1} (transconductor) and minimize g_{m2} (current source)
 - Large gm/ID for transconductor and small gm/ID for load

Dominant Noise Contributors By Inspection

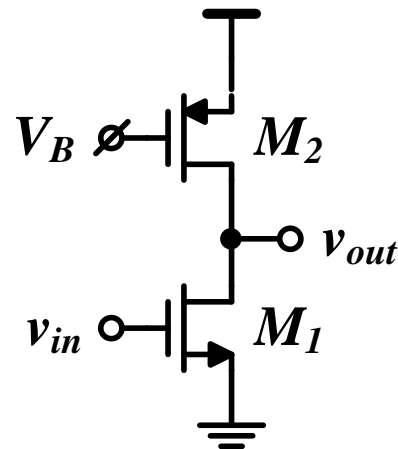
- ❑ At least two devices contribute to the amplifier noise
 - One input transistors and one load transistors
- ❑ Determine dominant noise contributors by inspection
 - Estimate the gain from the gate of the transistor to the output
 - Is it comparable to the gain from the input to output?



Cascode Amplifier

- Identify dominant noise contributors
 - Noise signals with high gain paths $\rightarrow V_{n1}$ and V_{n4} only (why?)
 - But $V_{n2,3}$ contribution may be large at high frequencies (why?)
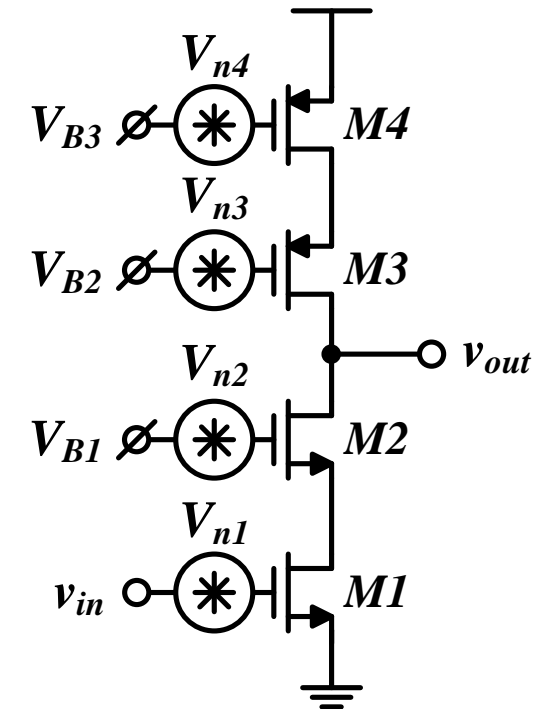
$$V_{nout}^2(f) \approx (4kT\gamma g_{m1} + 4kT\gamma g_{m4})R_{out}^2$$
$$V_{nin}^2(f) \approx \frac{V_{nout}^2(f)}{(g_{m1}R_{out})^2} = \frac{4kT\gamma}{g_{m1}} \left(1 + \frac{g_{m4}}{g_{m1}} \right)$$
$$= \frac{4kT\gamma\alpha}{g_{m1}}$$




Differential Pair with Resistive Load

- ❑ Use half-circuit principle
- ❑ Twice the noise of CS amplifier (variances add)

$$V_{nin}^2(f) = 2 \times \frac{4kT}{g_m} \left(\gamma + \frac{1}{g_m R_D} \right) + 2 \times \frac{K}{C_{ox} W L} \frac{1}{f}$$

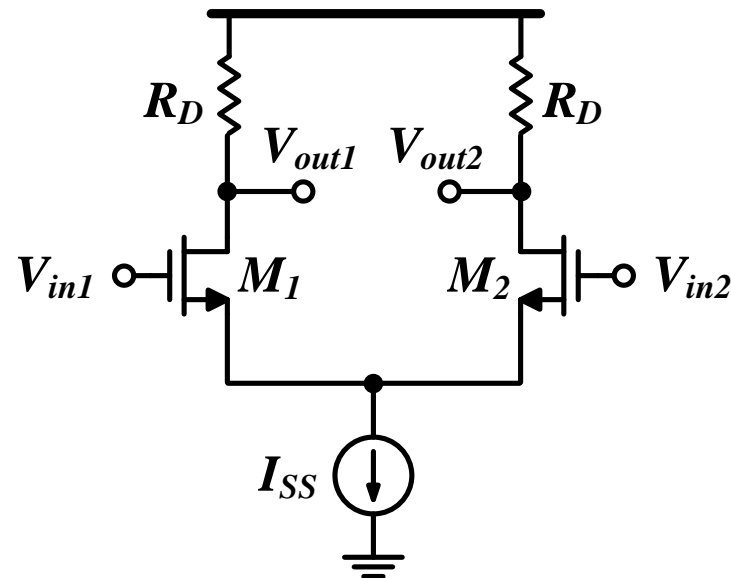- ❑ But SNR is improved by a factor of two = 3 dB compared to CS (why?)




Differential Pair with Active Load

- ❑ Use half-circuit principle
- ❑ Twice the noise of CS amplifier (variances add)

$$V_{nin}^2(f) = \frac{8kT\gamma}{g_{m1,2}} \left(1 + \frac{g_{m3,4}}{g_{m1,2}} \right) + \frac{2K_N}{C_{ox}(WL)_{1,2}} \frac{1}{f} + \frac{2K_P}{C_{ox}(WL)_{3,4}} \frac{1}{f} \left(\frac{g_{m3,4}}{g_{m1,2}} \right)^2$$


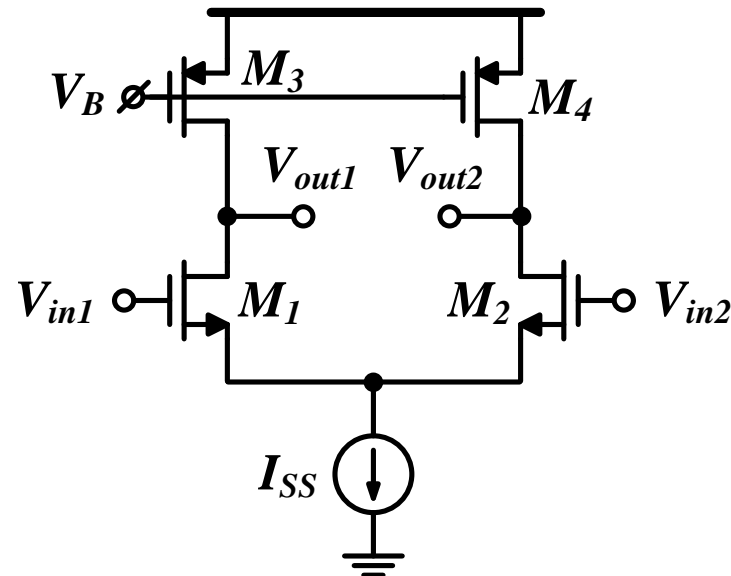
- ❑ But SNR is improved by a factor of two = 3 dB compared to CS (why?)



Differential Pair with CM Load (5T OTA)

- ❑ Noise sources of M1 and M2 are already input referred
- ❑ M3 is diode connected and drain of M1 is H.I.N.: $V_{gs4} \approx V_{n3}$
- ❑ Same as differential pair noise:

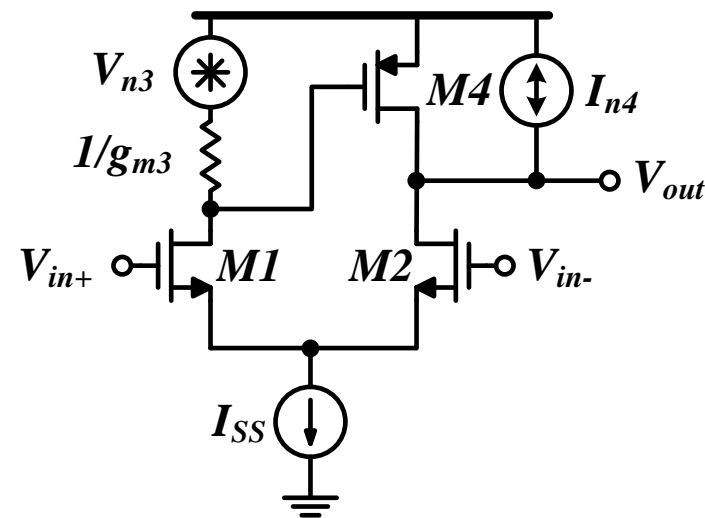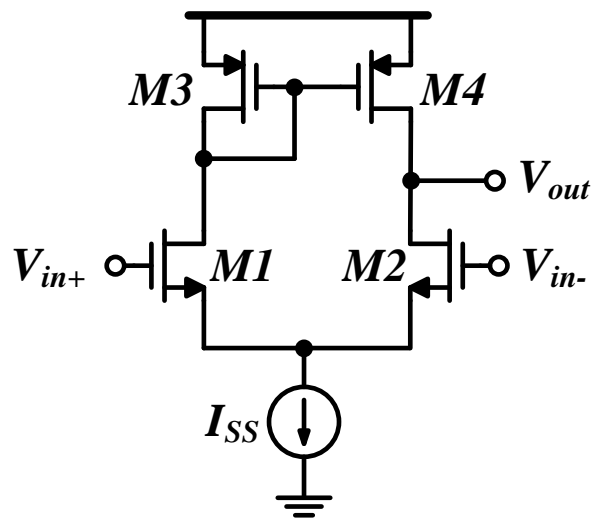
$$V_{nin}^2(f) = \frac{8kT\gamma}{g_{m1,2}} \left(1 + \frac{g_{m3,4}}{g_{m1,2}} \right) + \frac{2K_N}{C_{ox}(WL)_{1,2}} \frac{1}{f} + \frac{2K_P}{C_{ox}(WL)_{3,4}} \frac{1}{f} \left(\frac{g_{m3,4}}{g_{m1,2}} \right)^2$$



Differential Pair with CM Load (5T OTA)

- ❑ Noise of tail current source appears at output, even if we assume perfect matching
 - Noise of tail current source split equally between M1 and M2
 - V_{out} follow $V_D \rightarrow R_{out} = 1/g_{m3} \rightarrow$ negligible contribution


$$V_{nin,M5}^2(f) = \left(\frac{I_{n5}}{2}\right)^2 \cdot \frac{1}{g_{m3}^2} \cdot \frac{1}{g_{m1}^2 (r_{o2} || r_{o4})^2}$$

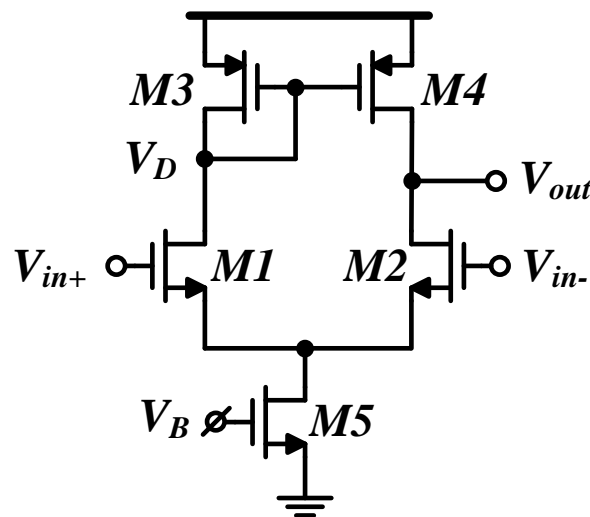

Telescopic Cascode

- ❑ The noise of the cascode devices is negligible at low frequencies
- ❑ M1,2 and M7,8 are the primary noise sources

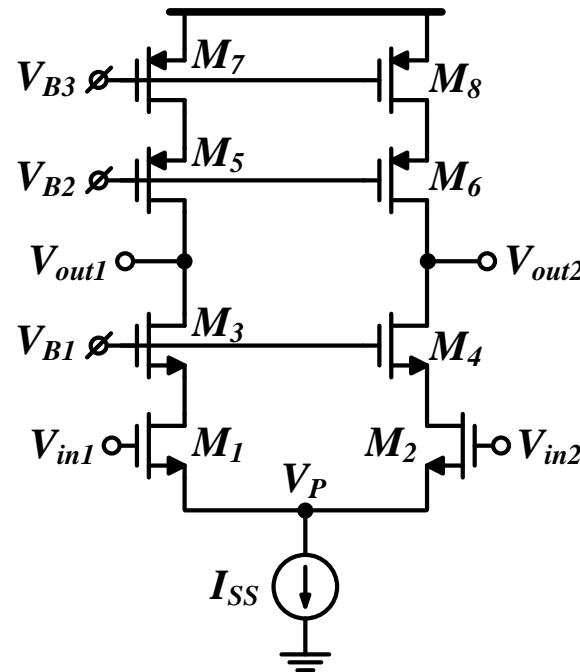
$$V_{nin}^2(f) = \frac{8kT\gamma}{g_{m1,2}} \left(1 + \frac{g_{m7,8}}{g_{m1,2}} \right) + \frac{2K_N}{C_{ox}(WL)_{1,2}} \frac{1}{f} + \frac{2K_P}{C_{ox}(WL)_{7,8}} \frac{1}{f} \left(\frac{g_{m7,8}}{g_{m1,2}} \right)^2$$



Folded Cascode


- ❑ The noise of the cascode devices is negligible at low frequencies
- ❑ M1, M2, and M5 are the primary noise sources
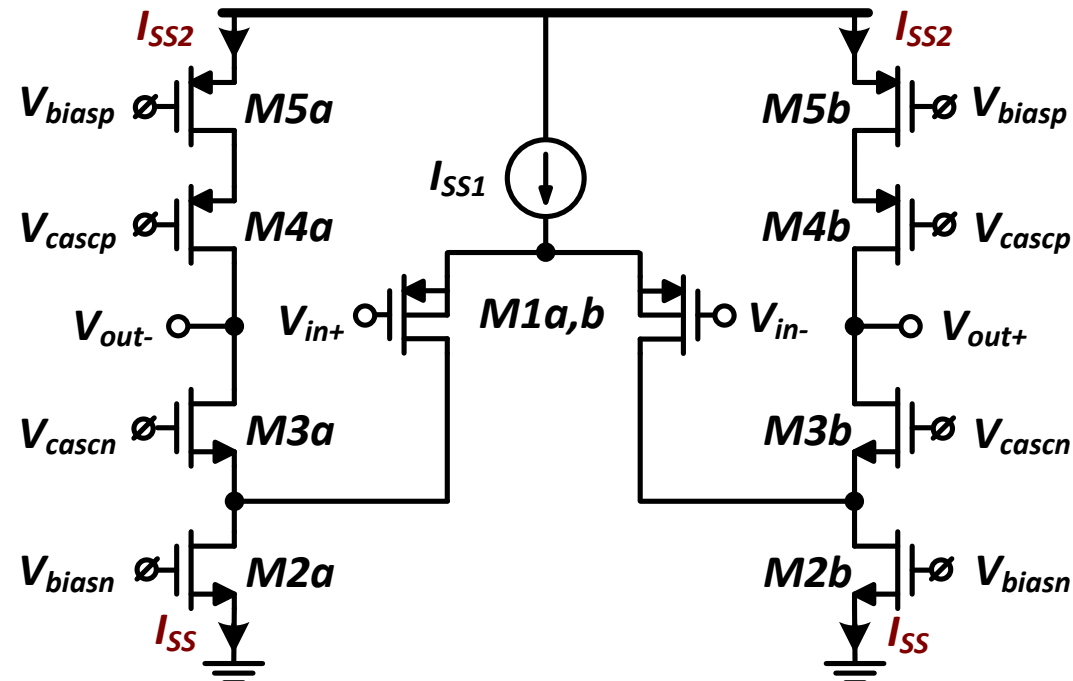
$$V_{nin}^2(f) = \frac{8kT\gamma}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} + \frac{g_{m5}}{g_{m1}} \right) = \frac{8kT\gamma\alpha}{g_{m1}}$$



Two-Stage OTA

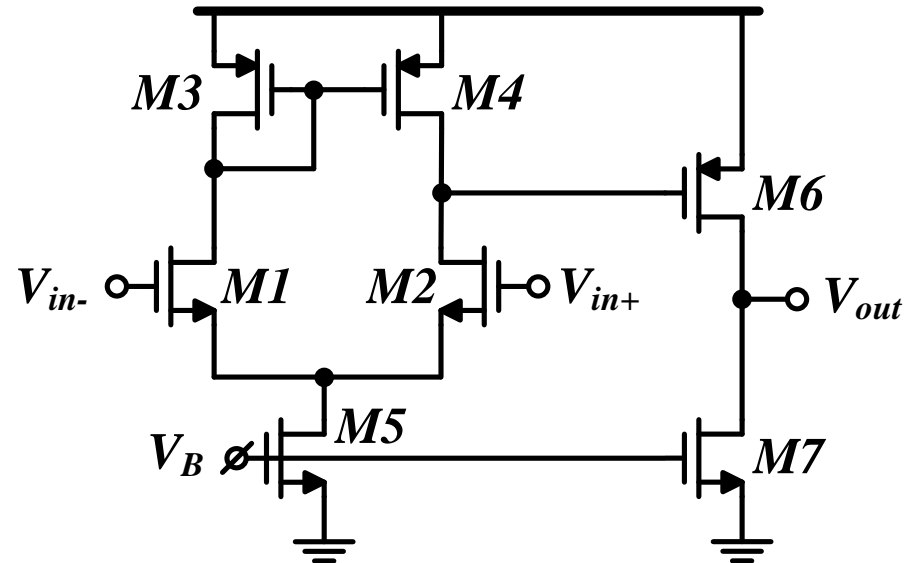- ❑ The noise of the second stage is divided by the gain of the first stage when referred to the input
 - Usually noise of first stage is dominant
 - A general result for multi-stage amplifiers
- ❑ More accurate result for Miller compensated OTA shortly





Single-Stage Noise in Closed-loop

$$\omega_u = \frac{g_m}{C_L} \quad A_{CL} \approx \frac{1}{\beta} \quad BW_{CL} \approx \frac{1}{2\pi} \frac{\omega_u}{A_{CL}} = \frac{1}{2\pi} \beta \omega_u \quad V_{nin}^2(f) = \frac{8kT\gamma\alpha}{g_m}$$

$$V_{noutrms}^2 = \overline{V_{nout}^2} = V_{nin}^2(f) \cdot A_{CL}^2 \cdot \frac{\pi}{2} BW_{CL} = \frac{8kT\gamma\alpha}{g_m} \cdot \frac{1}{\beta^2} \cdot \frac{\beta g_m}{4C_L}$$

$$= \frac{2kT\gamma\alpha}{\beta C_L}$$

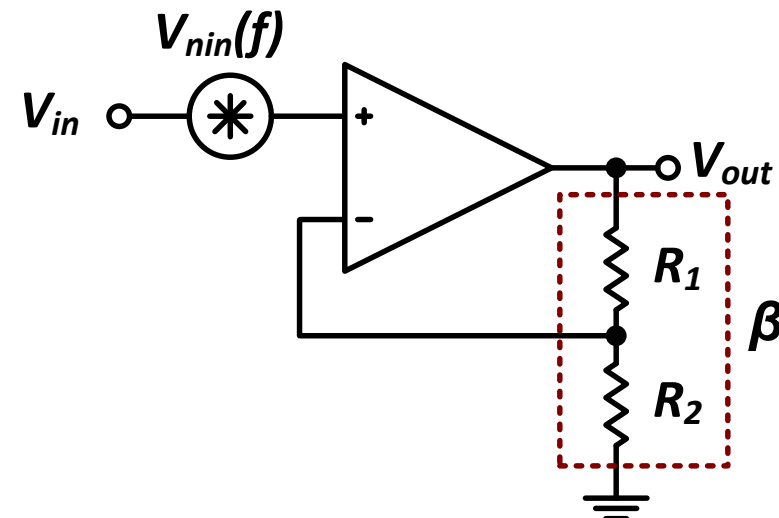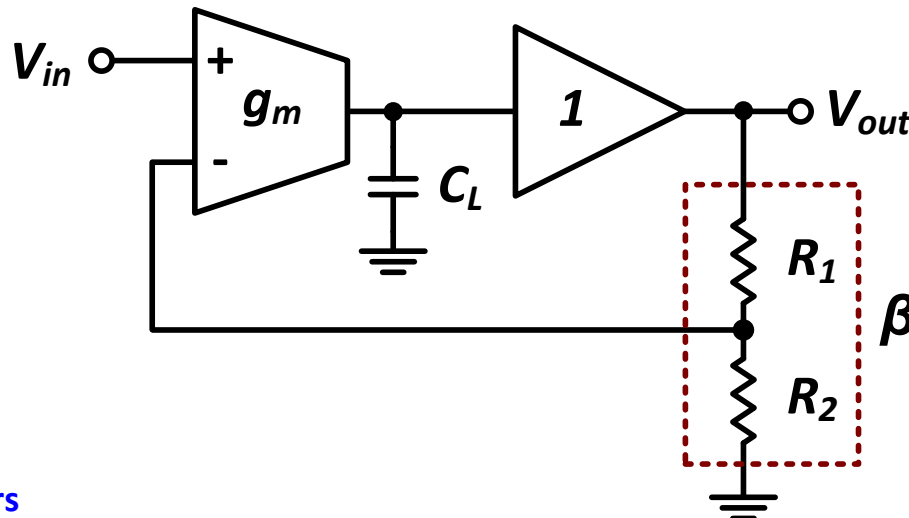


Two-Stage Noise in Closed-loop

$$\overline{V_{nout1}^2} \approx V_{nin1}^2(f) \cdot A_{CL}^2 \cdot \frac{\pi}{2} BW_{CL} = \frac{2kT\gamma\alpha_1}{\beta C_C}$$


$$\overline{V_{nout2}^2} \approx 4kT\gamma g_{m2}\alpha_2 \cdot \frac{1}{g_{m2}^2} \cdot \frac{g_{m2}}{4C_2} = \frac{kT\gamma\alpha_2}{C_2}$$
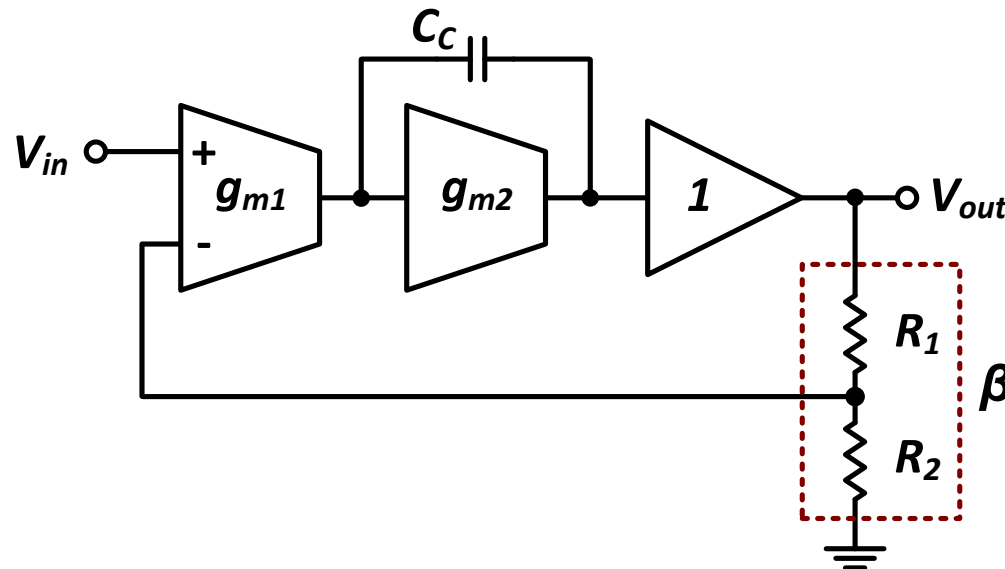
$$\overline{V_{nout}^2} = \overline{V_{nout1}^2} + \overline{V_{nout2}^2} \approx \frac{2kT\gamma\alpha_1}{\beta C_C} \left(1 + \frac{\beta\alpha_2 C_C}{2\alpha_1 C_2} \right)$$



Noise Analysis Example

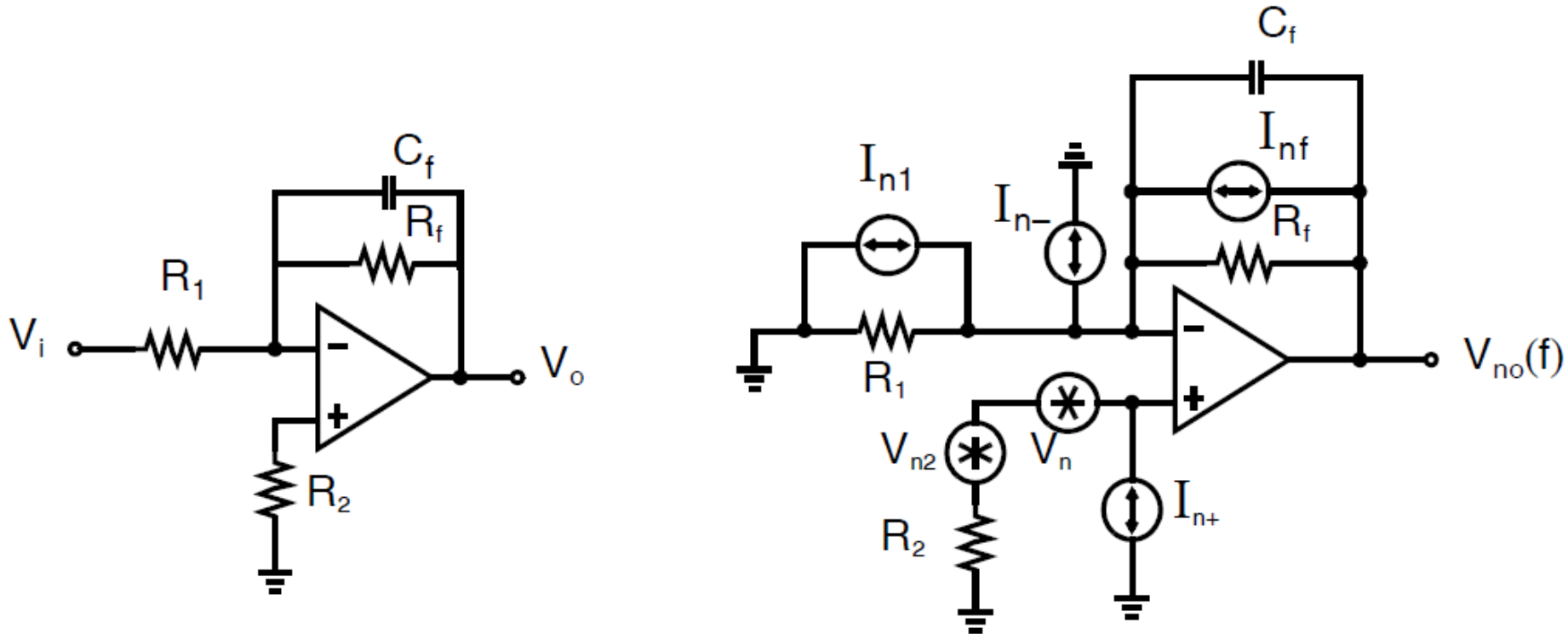- ❑ HW: Read Section 9.4.1 and solve Example 9.10 in [Johns and Martin, 2015]
- ❑ Inverting amplifier (R_f and R_1) and LPF (R_f and C_f)
- ❑ V_n , I_{n-} , and I_{n+} model the op-amp equivalent input noise



References

- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2nd ed., 2017.
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” 2nd ed., Wiley, 2012.
- ❑ B. Murmann, EE214 Course Reader, Stanford University.

Thank you!