

Analog IC Design

Lecture 09 Frequency Response (2)

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Electrical Communication Eng. Dept.
Faculty of Engineering
Ain Shams University

Outline

- ❑ Recapping previous key results
- ❑ Frequency response of CS: Midband, LFR, and HFR (Miller's effect)
- ❑ Frequency response of CG: HFR
- ❑ Frequency response of cascode: HFR
 - Cascode for gain and cascode for BW
- ❑ Frequency response of CD: HFR
 - Frequency domain peaking and time domain ringing
 - Z_{in} : negative resistance and Z_{out} : inductive rise

Outline

❑ Recapping previous key results

- ❑ Frequency response of CS: Midband, LFR, and HFR (Miller's effect)
- ❑ Frequency response of CG: HFR
- ❑ Frequency response of cascode: HFR
 - Cascode for gain and cascode for BW
- ❑ Frequency response of CD: HFR
 - Frequency domain peaking and time domain ringing
 - Z_{in} : negative resistance and Z_{out} : inductive rise

MOSFET in Saturation




- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \quad \text{OR} \quad V_{DS} \geq V_{ov}$$


- ❑ Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
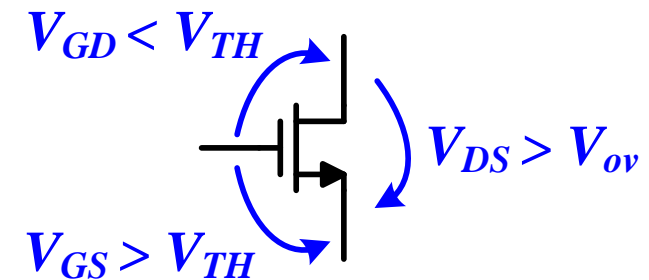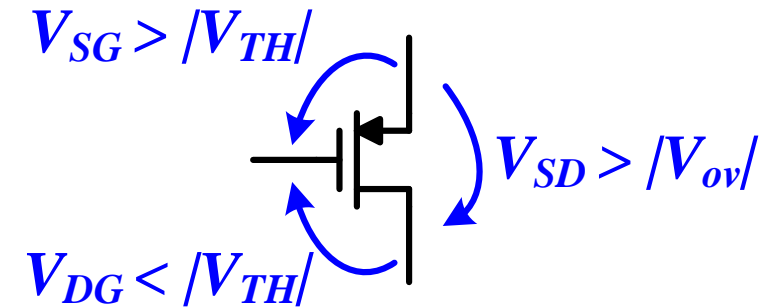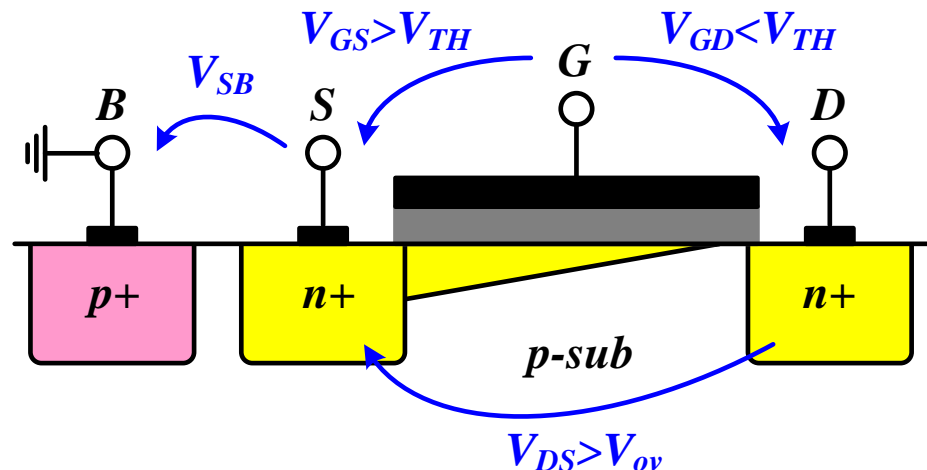
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$



Regions of Operation Summary

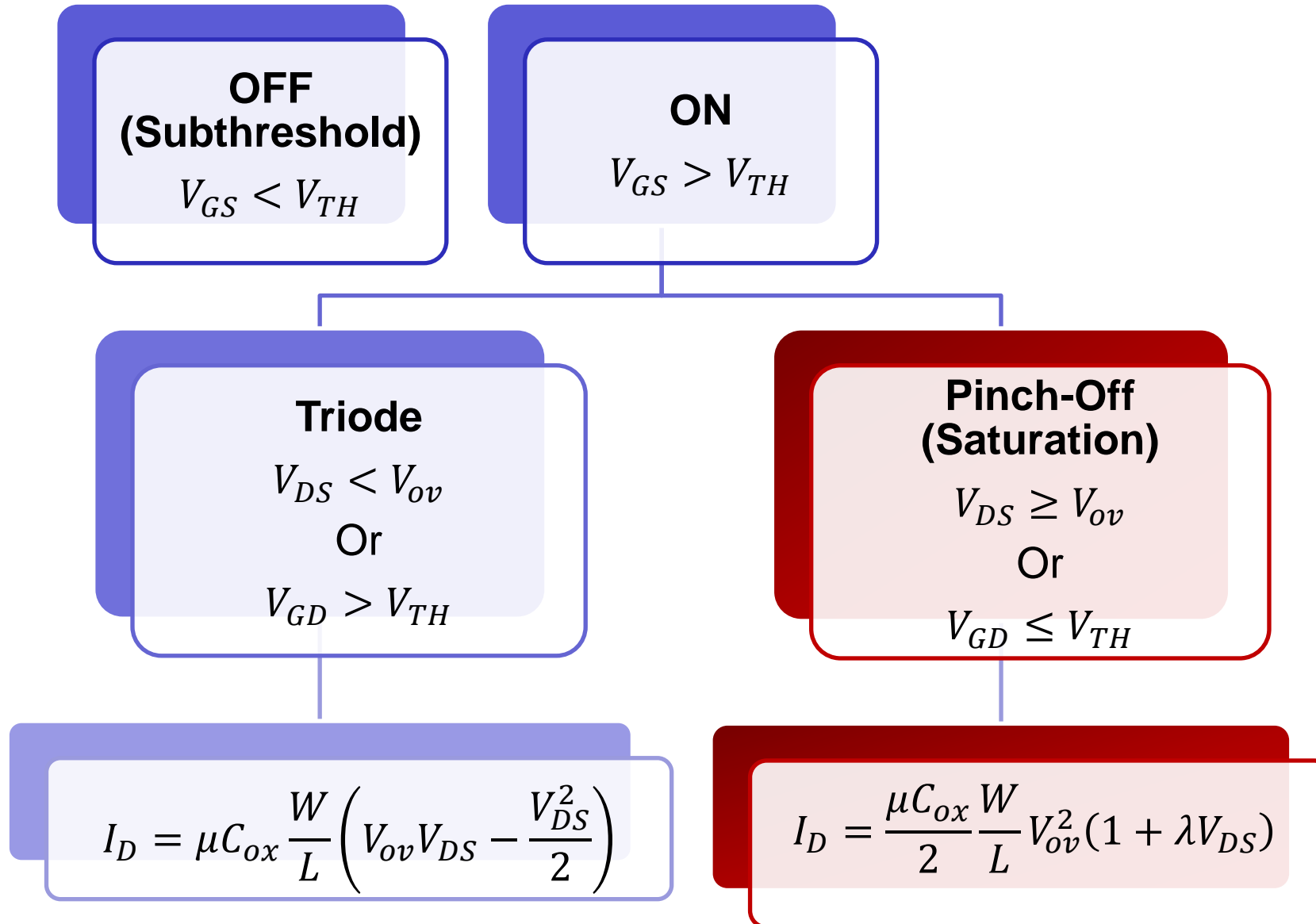

High Frequency Small Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$


$$g_{mb} = \eta g_m \quad \eta \approx 0.1 - 0.25$$

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D} \quad V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L} \quad V_{DS} \uparrow V_A \uparrow$$


$$C_{gb} \approx 0$$

$$C_{gs} \gg C_{gd}$$




$$C_{sb} > C_{db}$$

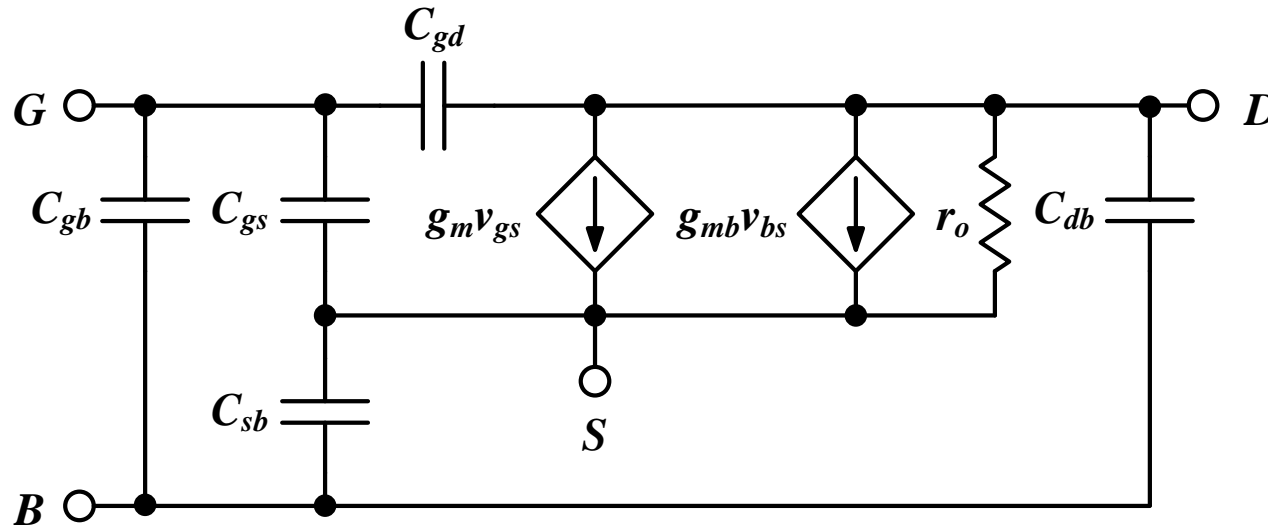

Rin/out Shortcuts Summary

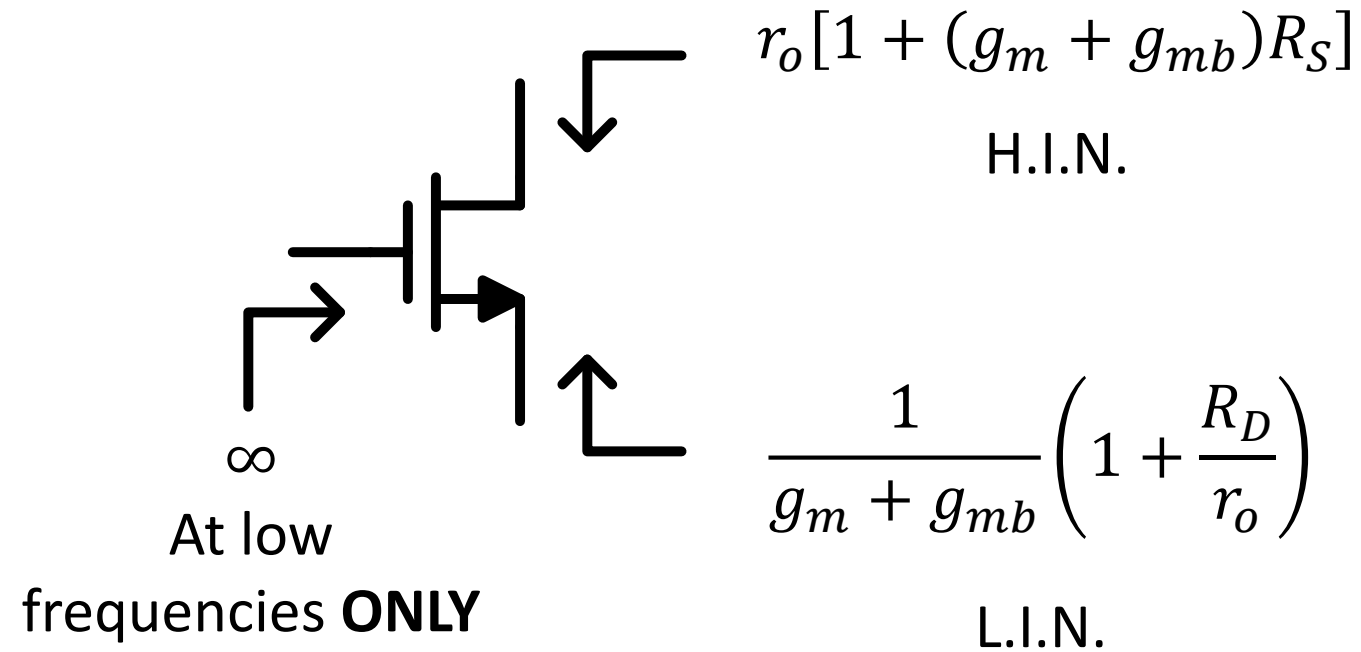

Summary of Basic Topologies

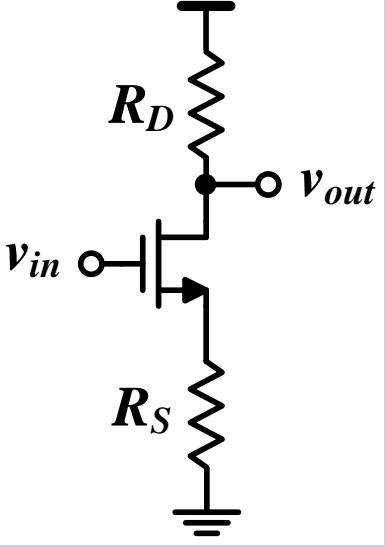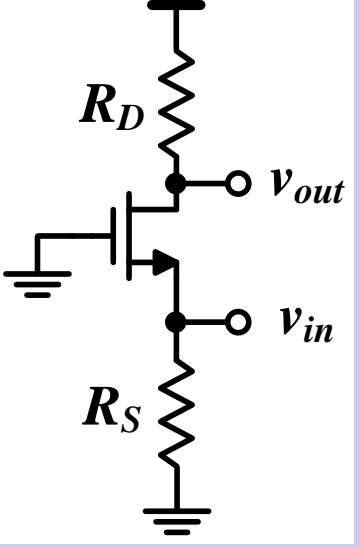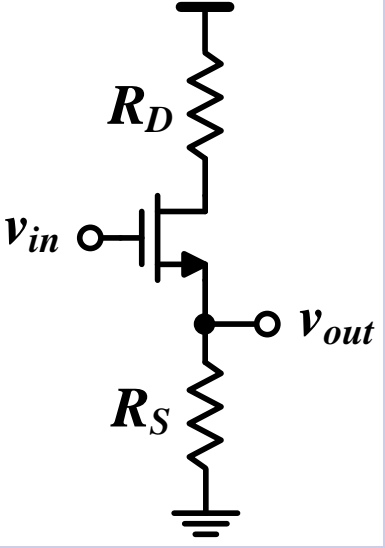	CS	CG	CD (SF)
			
	Voltage & current amplifier	Voltage amplifier Current buffer	Voltage buffer Current amplifier
R_{in}	∞	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$	∞
R_{out}	$R_D \parallel r_o [1 + (g_m + g_{mb})R_S]$	$R_D \parallel r_o$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$
G_m	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$

Outline


- ❑ Recapping previous key results
- ❑ Frequency response of CS: Midband, LFR, and HFR (Miller's effect)
- ❑ Frequency response of CG: HFR
- ❑ Frequency response of cascode: HFR
 - Cascode for gain and cascode for BW
- ❑ Frequency response of CD: HFR
 - Frequency domain peaking and time domain ringing
 - Z_{in} : negative resistance and Z_{out} : inductive rise

Frequency Response of CS: Midband

$$A_v = \frac{v_{in}}{v_{sig}} \cdot \frac{v_{out}}{v_{in}}$$


$$\frac{v_{out}}{v_{in}} = G_m R_{out} = -g_m (R_D || R_L || r_o)$$

$$\frac{v_{in}}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}}, R_{in} = R_G = R_{G1} || R_{G2}$$

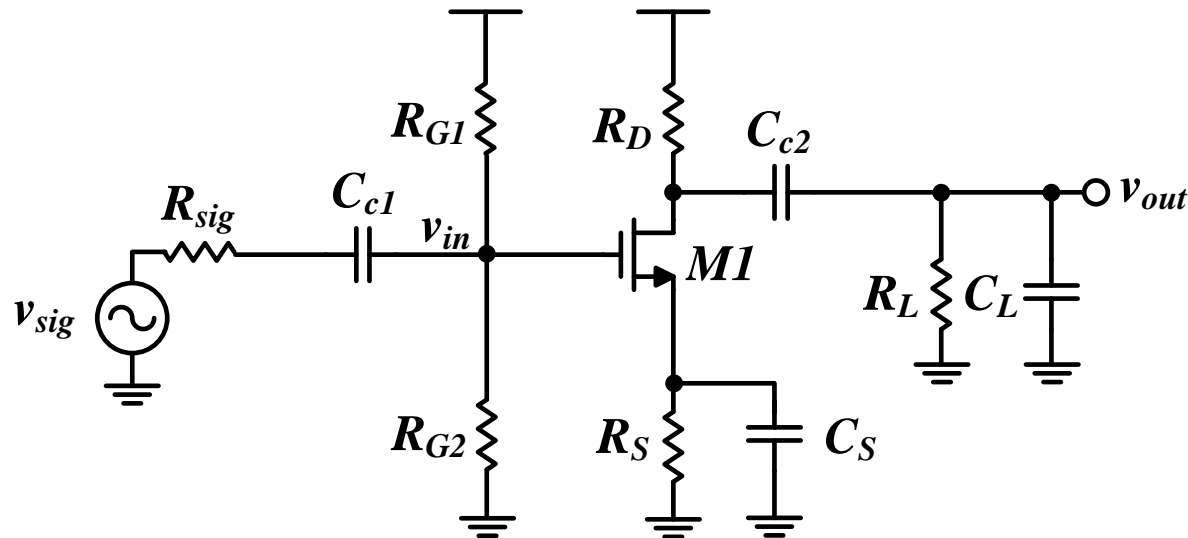

Frequency Response of CS: LFR


- C_{C1} : $R_{th} = R_{sig} + R_G \rightarrow \omega_{p,C_{C1}} = \frac{1}{(R_{sig} + R_G)C_{C1}}$ & $\omega_{z,C_{C1}} = 0$
- C_{C2} : $R_{th} = R_L + R_D || r_o \rightarrow \omega_{p,C_{C2}} = \frac{1}{(R_L + R_D || r_o)C_{C2}}$ & $\omega_{z,C_{C2}} = 0$
- C_S : $R_{th} = R_S || R_{LFS} \rightarrow \omega_{p,C_S} = \frac{1}{(R_S || R_{LFS})C_S}$ & $\omega_{z,C_S} = \frac{1}{R_S C_S}$
- Usually ω_{p,C_S} is dominant: $\omega_L \approx \omega_{p,C_S}$ (why?)
- Note that for IC amplifiers we usually use direct coupling (no LFR)

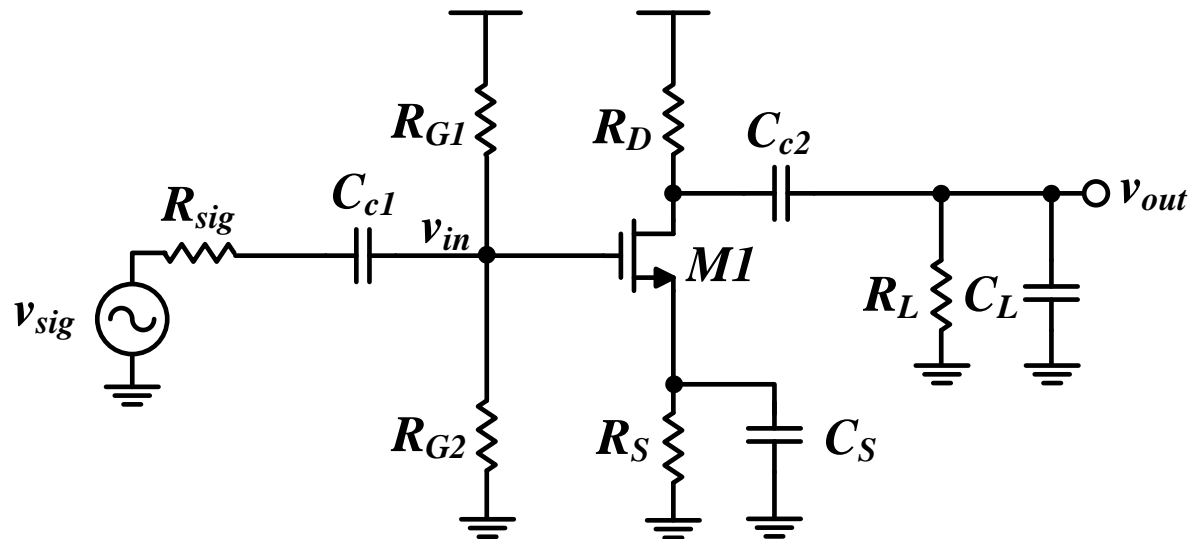

CS HFR: (1) Miller's Approx + OCTC

- ❑ Break the feedback capacitance (C_{gd}) using Miller's approx
- ❑ Each node is associated with a pole
 - v_{in} node \rightarrow i/p pole ($\omega_{p,in}$)
 - v_{out} node \rightarrow o/p pole ($\omega_{p,out}$)
- ❑ Don't forget the RHP feedforward zero
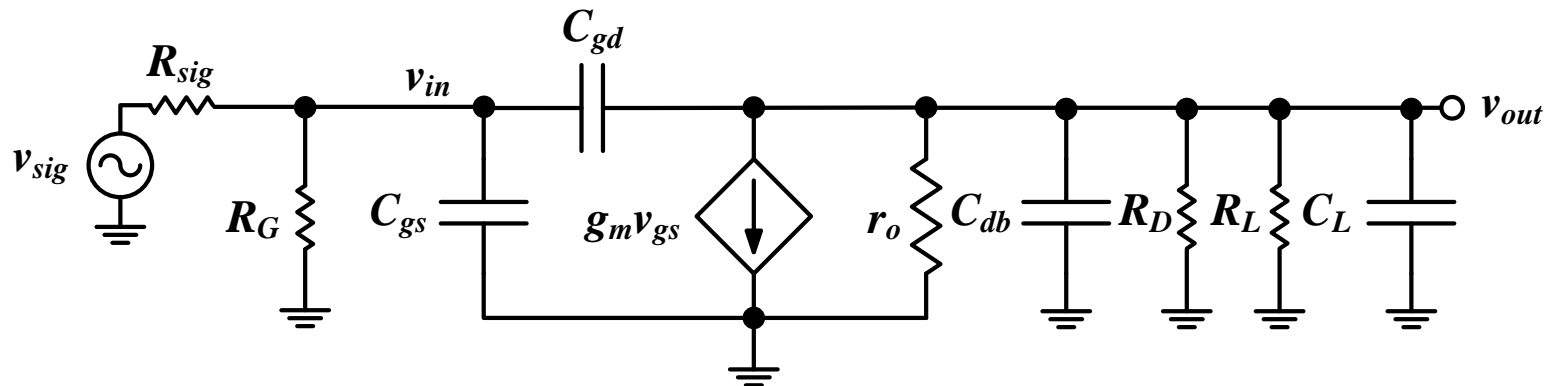
$$\omega_{z,C_{gd}} = \frac{g_m}{C_{gd}} \rightarrow \text{Usually } \omega_{z,C_{gd}} \text{ is very high (why?)}$$



CS HFR: (1) Miller's Approx + OCTC

- i/p pole: suffers from Miller effect (capacitance multiplication)


$$R_{th,in} = R_{sig} || R_G = R'_{sig} \rightarrow \omega_{p,in} \approx \frac{1}{R'_{sig} [C_{gs} + \textcolor{red}{C_{gd}}(1 + A_o)]}$$

$$A_o = \left| \frac{v_{out}}{v_{in}} \right| = g_m R_{out}$$

- o/p pole: $R_{th,out} = R_L || R_D || r_o$

$$\rightarrow \omega_{p,out} \approx \frac{1}{R_{out} \left(C_L + C_{db} + C_{gd} \left(1 + \frac{1}{A_o} \right) \right)} \approx \frac{1}{R_{out} (C_{out} + C_{gd})}$$

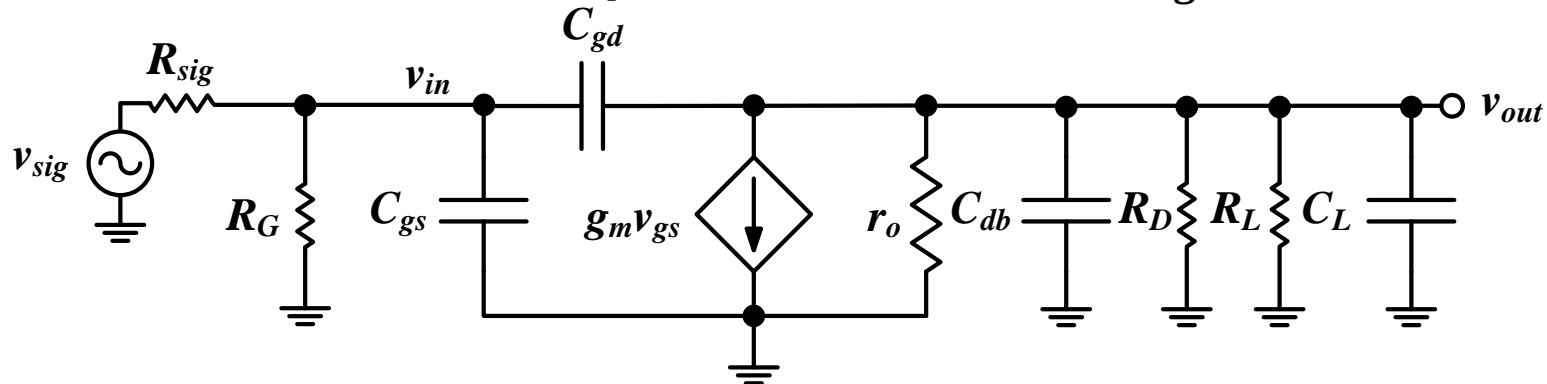- Usually i/p pole is dominant: $\omega_H \approx \omega_{p,in}$ (why?), unless $R'_{sig} \downarrow \downarrow$



CS HFR: (1) Miller's Approx + OCTC

$$\omega_H \approx \frac{1}{\frac{1}{\omega_{p,in}} + \frac{1}{\omega_{p,out}}} = \frac{1}{R'_{sig}[C_{gs} + C_{gd}(1 + g_m R_{out})] + R_{out}(C_{out} + C_{gd})}$$

- If input pole is dominant (e.g., if $R'_{sig} \uparrow\uparrow$ or $C_L \downarrow\downarrow$)

$$\omega_H \approx \frac{1}{R'_{sig}[C_{gs} + C_{gd}(1 + g_m R_{out})]} \approx \omega_{p,in}$$

- If output pole is dominant (e.g., if $R'_{sig} \downarrow\downarrow$ or $C_L \uparrow\uparrow$)

$$\omega_H \approx \frac{1}{R_{out}(C_{out} + C_{gd})} \approx \omega_{p,out}$$

$$GBW = A_v \omega_H = G_m R_{out} \cdot \frac{1}{R_{out}(C_{out} + C_{gd})} = \frac{G_m}{C_{out} + C_{gd}}$$

→ independent of R_{out} !


CS HFR: (2) Just OCTC Technique

$$\square C_{gs}: R_{th,in} = R_{sig} || R_G = R'_{sig} \rightarrow \omega_{p,C_{gs}} = \frac{1}{R'_{sig} C_{gs}}$$

$$\square C_{out} = C_L + C_{db}: R_{th} = R_L || R_D || r_o = R_{out} \rightarrow \omega_{p,C_{out}} = \frac{1}{R_{out} C_{out}}$$

$$\square C_{gd}: R_{th} = \frac{v_x}{i_x} = R'_{sig}(1 + g_m R_{out}) + R_{out} \rightarrow \omega_{p,C_{gd}} = \frac{1}{[R'_{sig}(1 + g_m R_{out}) + R_{out}] C_{gd}}$$
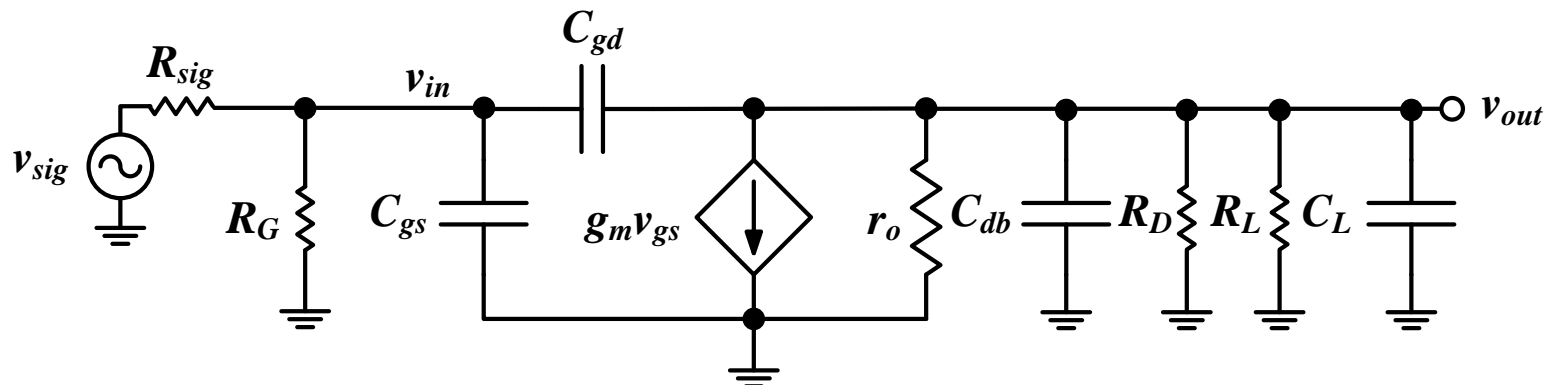
$$\omega_H \approx \frac{1}{\frac{1}{\omega_{p,C_{gs}}} + \frac{1}{\omega_{p,C_{out}}} + \frac{1}{\omega_{p,C_{gd}}}} = \frac{1}{R'_{sig} C_{gs} + R_{out} C_{out} + [R'_{sig}(1 + g_m R_{out}) + R_{out}] C_{gd}}$$



CS HFR: (2) Just OCTC Technique

$$\omega_H \approx \frac{1}{R'_{sig}[C_{gs} + C_{gd}(1 + g_m R_{out})] + R_{out}(C_{out} + C_{gd})}$$

- If input pole is dominant (e.g., if $R'_{sig} \uparrow\uparrow$ or $C_L \downarrow\downarrow$)

$$\omega_H \approx \frac{1}{R'_{sig}[C_{gs} + C_{gd}(1 + g_m R_{out})]} \approx \omega_{p,in}$$

- If output pole is dominant (e.g., if $R'_{sig} \downarrow\downarrow$ or $C_L \uparrow\uparrow$)

$$\omega_H \approx \frac{1}{R_{out}(C_{out} + C_{gd})} \approx \omega_{p,out}$$

- Same as the expressions obtained from Miller approx

CS HFR: (3) Exact Analysis + Dominant Pole Approx

- ❑ Surprisingly, exact analysis gives a quite complex expression

- See [Johns & Martin 2012] or [Razavi 2017]

- ❑ If dominant pole approximation is applied

$$\omega_{pd} \approx \frac{1}{b_1} = \frac{1}{R'_{sig} [C_{gs} + C_{gd}(1 + g_m R_{out})] + R_{out}(C_{out} + C_{gd})}$$

- Same result as OCTC (both based on same approximation)

- ❑ Additionally, dominant pole approx gives an expression for ω_{pnd}

$$\omega_{pnd} \approx \frac{1}{b_2 \omega_{p1}} = \frac{b_1}{b_2} = \frac{g_m C_{gd}}{C_{gd}(C_{gs} + C_{out}) + C_{gs} C_{out}}$$

- If a large cap is connected parallel to C_{gd} : $\omega_{pnd} \approx \frac{g_m}{C_{gs} + C_{out}}$

- Can be derived intuitively without analysis (how?)

- **We will need this case when we study two-stage OTA**

Frequency Response of CS: Z_{in}



- With Miller approx.

$$Z_{in} = \frac{1}{s[C_{gs} + (1 + g_m R_D)C_{gd}]}$$

- Exact Analysis (C_{gs} adds in parallel)

$$Z_{in} = \frac{V_X}{I_X} = \frac{1 + sR_D(C_{gd} + C_{db})}{sC_{gd}(1 + g_m R_D + sR_D C_{db})}$$

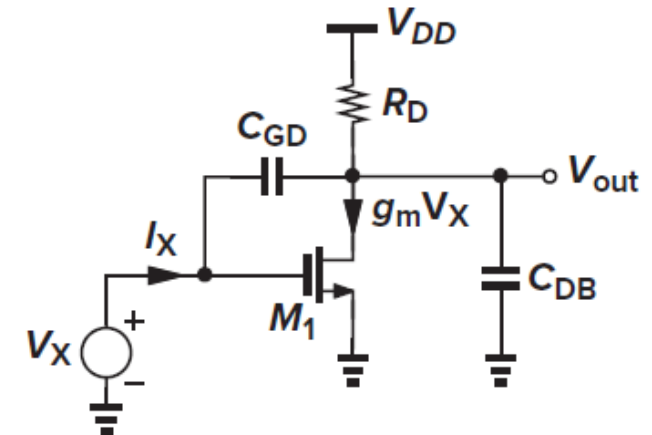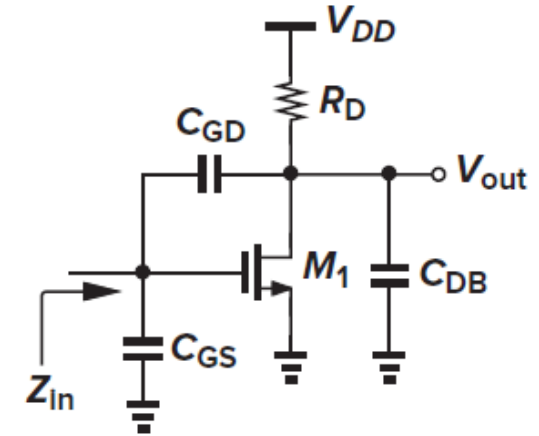- Extra pole and zero at high frequency ($\omega_p > \omega_z$)
- At relatively low frequency the exact solution reduces to Miller approx.



Frequency Response of CS: Z_{out}

□ Can we use Miller?

$$i_x = f(v_{gs}) = g_m v_{gs} + \frac{v_{gs}(1 + sR_{sig}C_{gs})}{R_{sig}}$$



$$v_x = f(v_{gs}) = v_{gs} + \frac{v_{gs}(1 + sR_{sig}C_{gs})}{sR_{sig}C_{gd}}$$

$$Z_{out} = \frac{v_x}{i_x} \approx \frac{1 + sR_{sig}(C_{gs} + C_{gd})}{sC_{gd}g_mR_{sig}\left(1 + s\frac{C_{gs}}{g_m}\right)}$$

□ r_o and C_{db} add in parallel

□ Important special case: If we have a large capacitor parallel to C_{gd}

- $|Z_m| \approx 1/g_m \rightarrow$ We will need this case when we study Miller OTA

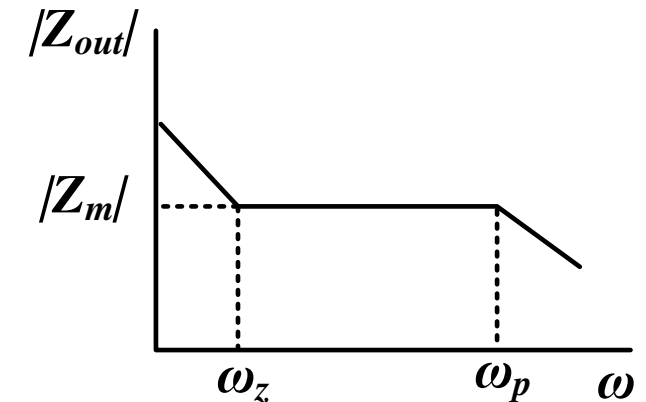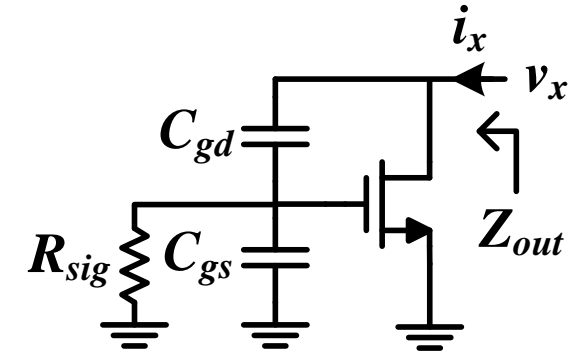


Outline

- ❑ Recapping previous key results
- ❑ Frequency response of CS: Midband, LFR, and HFR (Miller's effect)
- ❑ Frequency response of CG: HFR
- ❑ Frequency response of cascode: HFR
 - Cascode for gain and cascode for BW
- ❑ Frequency response of CD: HFR
 - Frequency domain peaking and time domain ringing
 - Z_{in} : negative resistance and Z_{out} : inductive rise

Frequency Response of CG: HFR

- i/p pole: $\omega_{p,in} = \frac{1}{(R_{sig} || R_S || R_{LFS})(C_{gs} + C_{sb})}$
- o/p pole: $\omega_{p,out} = \frac{1}{(R_D || R_{LFD})(C_L + C_{db} + C_{gd})}$
- Usually o/p pole is dominant: $\omega_H \approx \omega_{p,out}$ (why?)
- No FB cap \rightarrow No Miller effect \rightarrow **$BW_{CG} \gg BW_{CS}$**

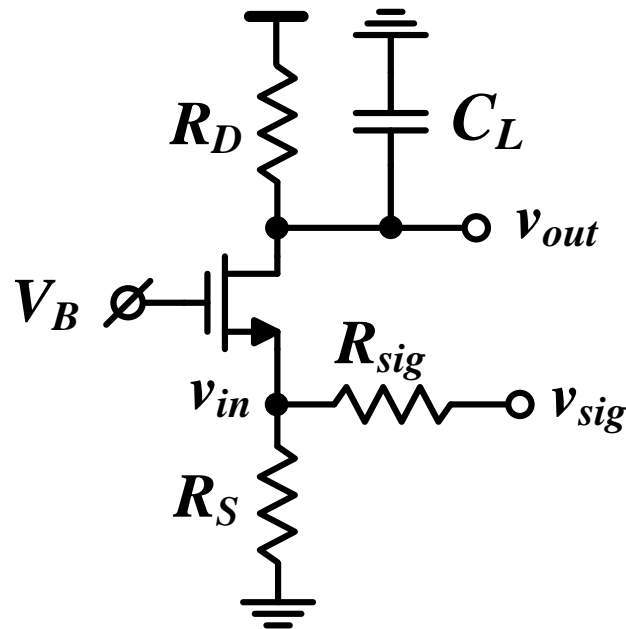

Outline

- ❑ Recapping previous key results
- ❑ Frequency response of CS: Midband, LFR, and HFR (Miller's effect)
- ❑ Frequency response of CG: HFR
- ❑ Frequency response of cascode: HFR
 - Cascode for gain and cascode for BW
- ❑ Frequency response of CD: HFR
 - Frequency domain peaking and time domain ringing
 - Z_{in} : negative resistance and Z_{out} : inductive rise

Frequency Response of Cascode: HFR

Case 1: BW limited by o/p pole ($R_D \uparrow\uparrow R_{sig} \downarrow\downarrow$) (cascode for gain)

$$\square A_v = \frac{v_{out}}{v_{sig}} \approx (g_{m1}r_{o1})(g_{m2}r_{o2}) = A_{v,CS} \cdot (g_{m2}r_{o2})$$

$$\square \omega_{p,out} \approx \frac{1}{r_{o1}(g_{m2}r_{o2})(C_L + C_{db2} + C_{gd2})} = \frac{\omega_{p,out,CS}}{g_{m2}r_{o2}} \rightarrow \text{Dominant}$$

$$\square GBW = A_v \omega_{p,out} = A_{v,CS} \omega_{p,out,CS}$$


$$= \frac{G_m}{C_{out} + C_{gd2}} \rightarrow \text{Same as CS!}$$

$$\square A_{o1} = \left| \frac{v_x}{v_{in}} \right| = g_{m1}(r_{o1} || R_{LFS2}), R_{LFS2} = ?$$

▪ $A_{o1} \ll g_{m1}r_{o1}$ Miller effect reduced

$$\square \omega_{p,in} = \frac{1}{R_{sig}(C_{gs1} + C_{gd1}(1 + A_{o1}))} = \omega_{p,in,CS}$$

$$\square \omega_{p,x} = \frac{1}{(r_{o1} || R_{LFS2})(C_{gs2} + C_{sb2} + C_{db1} + C_{gd1}(1 + 1/A_{o1}))}$$

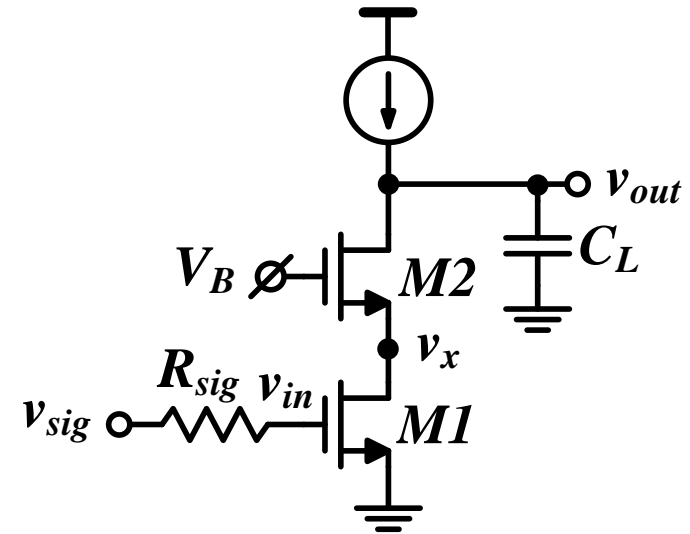

Frequency Response of Cascode: HFR

Case 2: BW limited by i/p pole ($R_D \downarrow \downarrow R_{sig} \uparrow \uparrow$) (cascode for BW)

□ $A_v = \frac{v_{out}}{v_{sig}} \approx g_{m1} R_D \approx A_{v,CS} \rightarrow$ Similar to CS!

□ $A_{o1} = \left| \frac{v_x}{v_{in}} \right| = g_{m1} (r_{o1} \parallel \frac{1}{g_{m2}}) \approx 1$


□ $\omega_{p,in} \approx \frac{1}{R_{sig}(C_{gs1} + 2C_{gd1})} > \omega_{p,in,CS}$

- **Miller effect significantly reduced**
- **\rightarrow BW extension!**

□ $\omega_{p,x} \approx \frac{1}{(r_{o1} \parallel \frac{1}{g_{m2}})(C_{gs2} + C_{sb2} + C_{db1} + 2C_{gd1})}$

□ $\omega_{p,out} \approx \frac{1}{R_D(C_L + C_{db2} + C_{gd2})}$

□ $GBW = A_v \omega_{p,in} > GBW$ of CS

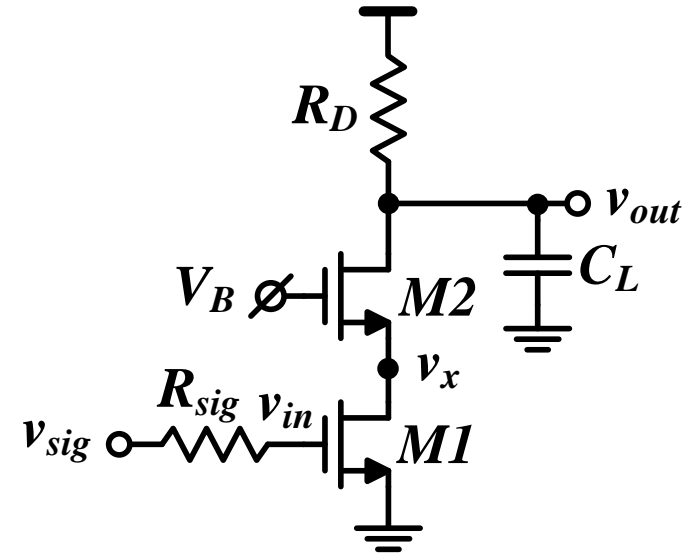

Cascode HFR: Recapping


□ If BW is limited by o/p pole

- $GBW = A_v \omega_{p,out} = G_m R_{out} \cdot \frac{1}{R_{out} C_{out}} = \frac{G_m}{C_{out}}$
- Cascode can be used **to trade gain for bandwidth** by modifying R_{out}
- But $GBW = A_v \omega_{p,out}$ remain unchanged

□ If BW is limited by i/p pole

- Cascode can provide higher BW (Miller ↓)
- The gain may be higher as well
- $GBW = A_v \omega_{p,in}$ increases
- Also improves reverse isolation (RF LNAs)

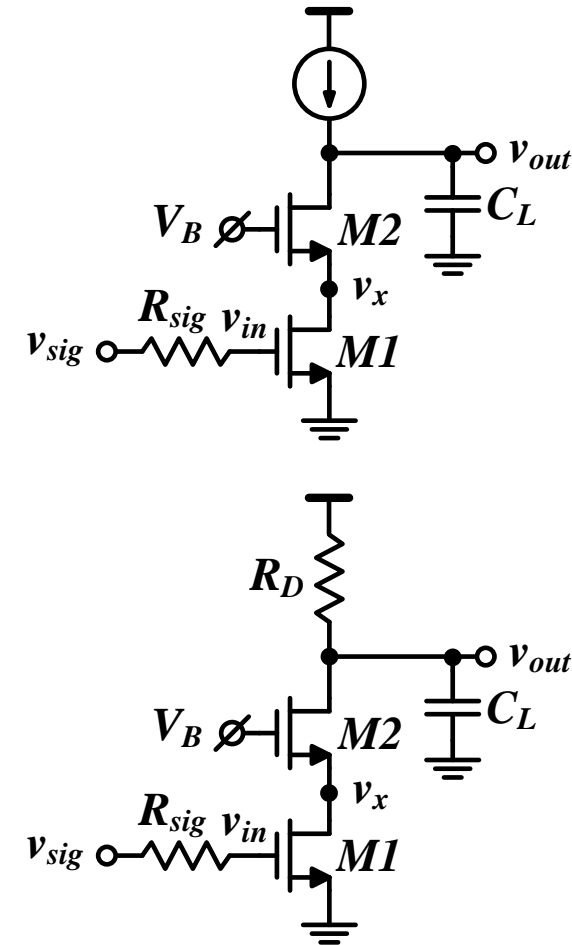□ See Example 10.10 in Sedra/Smith 7th ed.




Outline

- ❑ Recapping previous key results
- ❑ Frequency response of CS: Midband, LFR, and HFR (Miller's effect)
- ❑ Frequency response of CG: HFR
- ❑ Frequency response of cascode: HFR
 - Cascode for gain and cascode for BW
- ❑ Frequency response of CD: HFR
 - Frequency domain peaking and time domain ringing
 - Z_{in} : negative resistance and Z_{out} : inductive rise


Frequency Response of CD: HFR

- ❑ Assume real and widely spaced poles (revisited next slide)
- ❑ Apply Miller: Ideally $A_o = v_{out}/v_{in} \approx 1 \rightarrow C_{gs}$ is **bootstrapped**
- ❑ i/p pole: $\omega_{p,in} = \frac{1}{R_{sig}(C_{gd} + C_{gs}(1 - A_o))}$
- ❑ o/p pole: $\omega_{p,out} = \frac{1}{(R_S || R_{LFS})(C_L + C_{sb} + C_{gs}(1 - 1/A_o))}$
- ❑ Both poles are at high frequency (why?) \rightarrow Large BW
- ❑ Don't forget the LHP feedforward zero: $\omega_z = \frac{g_m}{C_{gs}} \uparrow\uparrow$

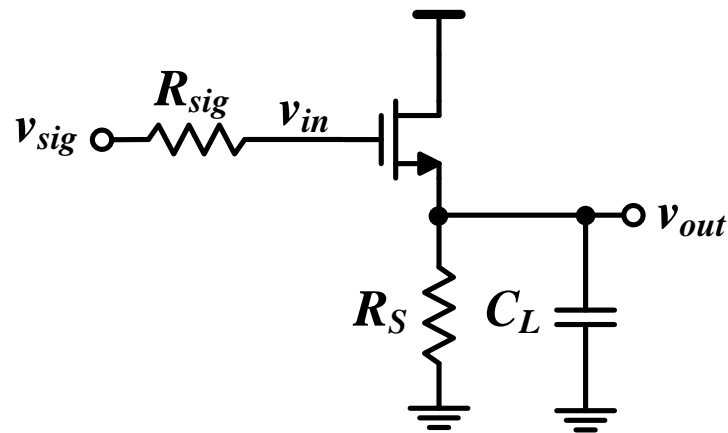

CD HFR: Why Approximations Fail?

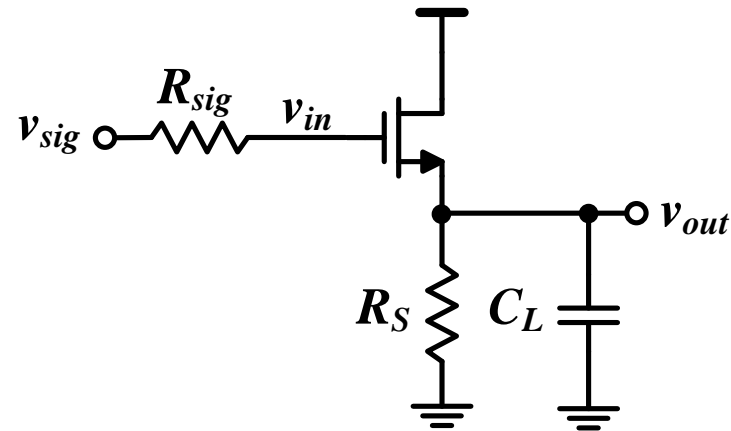- ❑ The two poles are nearby and possibly complex conjugate
- ❑ OCTC technique and Miller approx cannot be used 😞




CD HFR: Exact Analysis

- Simple circuit, but exact analysis gives a complex expression!

$$\begin{aligned}\frac{v_{out}}{v_{sig}} &= A_M \frac{1 + s/\omega_z}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)} = A_M \frac{1 + s/\omega_z}{1 + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + \frac{s^2}{\omega_{p1}\omega_{p2}}} \\ &= A_M \frac{1 + s/\omega_z}{1 + b_1s + b_2s^2} = A_M \frac{1 + s/\omega_z}{1 + \frac{1}{Q}\frac{s}{\omega_o} + \frac{s^2}{\omega_o^2}} = A_M \frac{1 + s/\omega_z}{1 + 2\zeta\frac{s}{\omega_o} + \frac{s^2}{\omega_o^2}}\end{aligned}$$

- Special case: $R_S \uparrow\uparrow$ (IDC) + CLM and body effect neglected
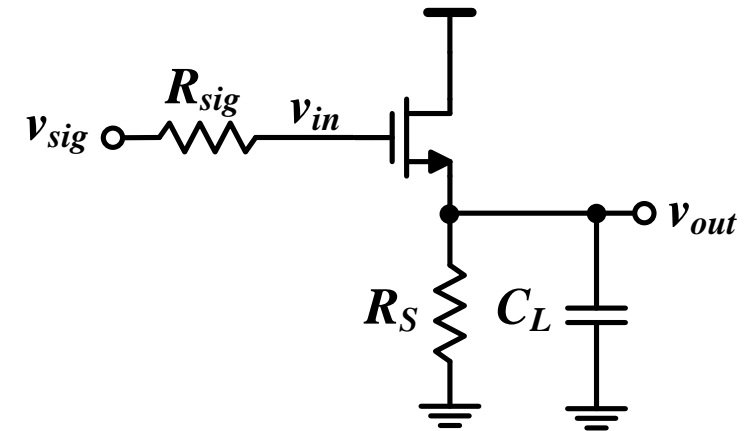
$$\begin{aligned}b_1 &= C_{gd}R_{sig} + \frac{C_{gs} + C_L}{g_m} \\ b_2 &= \left(\frac{(C_{gs} + C_{gd})C_L + C_{gs}C_{gd}}{g_m}\right)R_{sig} \\ \omega_z &= \frac{g_m}{C_{gs}}, \omega_o = \frac{1}{\sqrt{b_2}}, \mathbf{Q} = \frac{\sqrt{\mathbf{b_2}}}{\mathbf{b_1}}\end{aligned}$$




Peaking and Ringing

- ❑ $\omega_z \uparrow\uparrow$ is ignored
- ❑ $Q > 0.5$ ($\zeta < 1$): Underdamped system (complex conj. poles)
 - Ringing (overshoot) in step response (time domain)

$$\% \text{ overshoot} = 100 e^{\frac{-\pi}{\sqrt{4Q^2 - 1}}}$$

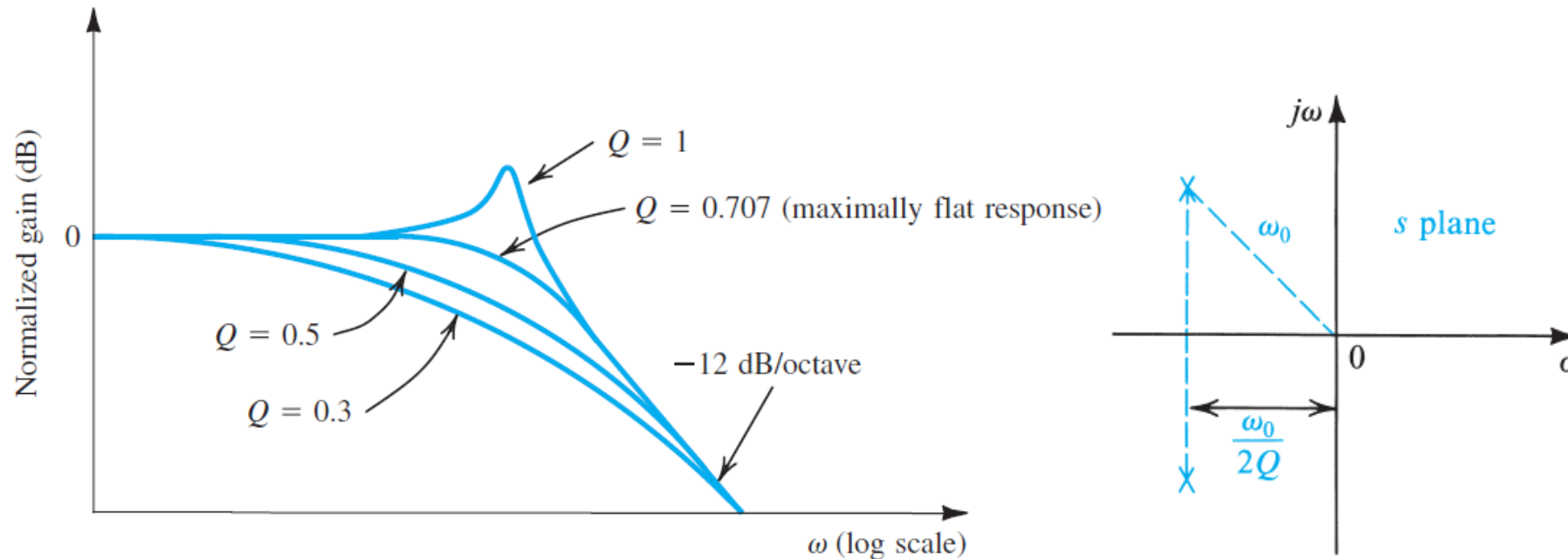- ❑ $Q > \frac{1}{\sqrt{2}} = 0.707$ ($\zeta < 0.707$): Peaking in frequency response



Driving Large Capacitive Load

- Special case: $R_S \uparrow\uparrow$ (IDC) + CLM and body effect neglected + $C_L \uparrow\uparrow$


$$b_1 = C_{gd}R_{sig} + \frac{C_{gs} + C_L}{g_m} \approx \frac{C_L}{g_m}$$

$$b_2 = \left(\frac{(C_{gs} + C_{gd})C_L + C_{gs}C_{gd}}{g_m} \right) R_{sig} \approx \frac{(C_{gs} + C_{gd})C_L R_{sig}}{g_m}$$

$$\omega_z = \frac{g_m}{C_{gs}}$$

$$\omega_o = \frac{1}{\sqrt{b_2}} \approx \sqrt{\frac{g_m}{(C_{gs} + C_{gd})C_L R_{sig}}}$$


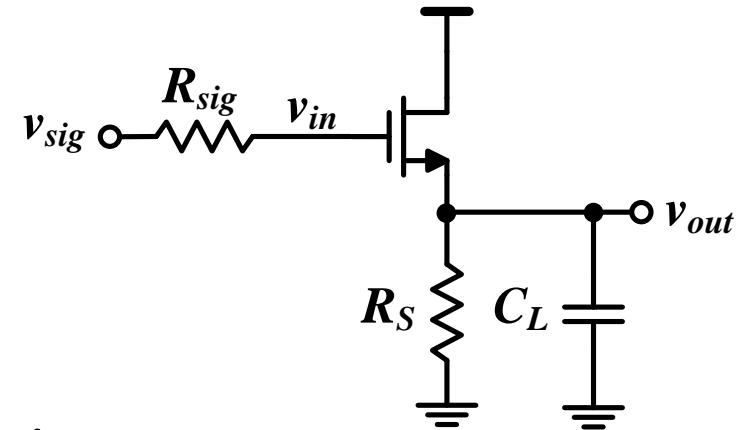
$$Q = \frac{\sqrt{b_2}}{b_1} \approx \sqrt{\frac{g_m(C_{gs} + C_{gd})R_{sig}}{C_L}}$$



- Increasing C_L eventually decreases $Q \rightarrow \omega_{p,out}$ becomes dominant

Suppressing the Overshoot

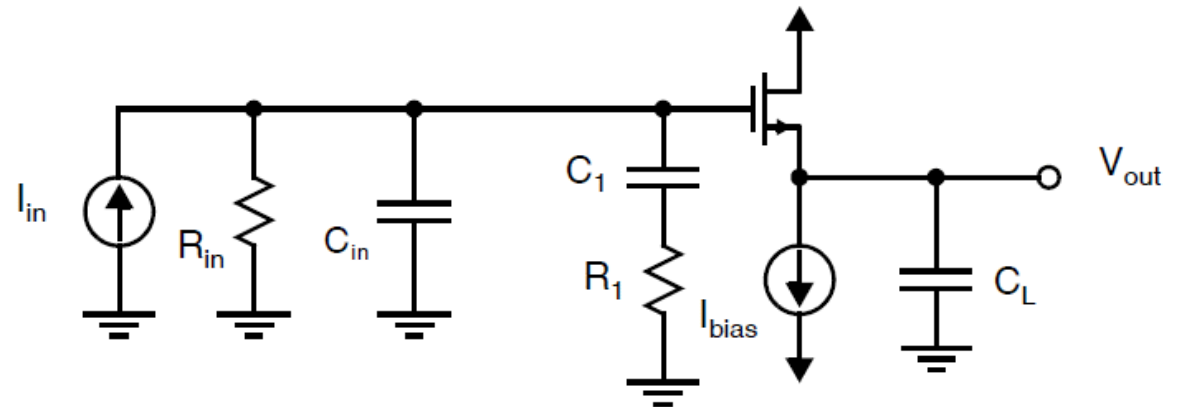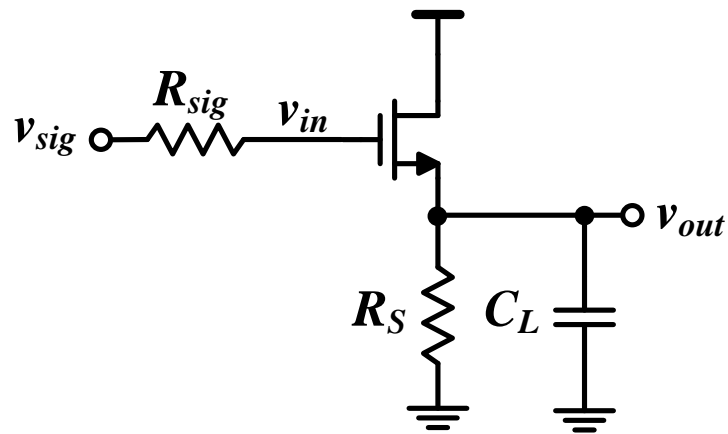- ❑ Space the two poles far apart \rightarrow single dominant pole
 - Increase C_L (till $Q < 0.5$)
 - Or increase C_{in} (adds to C_{gd}) \rightarrow but buffer becomes less useful!
- ❑ More clever solution
 - A compensation network (R_1 and C_1) can be used to compensate for the negative input impedance and prevent overshoots
 - See [Johns and Martin, 2012] Section 4.4 for more details



Z_{in} of CD

□ $v_{gs} = i_{in}/sC_{gs}$

□ $v_{in} = i_{in}/sC_{gs} + (i_{in} + g_m i_{in}/sC_{gs})(r_o || 1/g_{mb} || 1/sC_L)$



$$Z_{in} = \frac{v_{in}}{i_{in}} = 1/sC_{gs} + (1 + g_m/sC_{gs})(r_o || 1/g_{mb} || 1/sC_L)$$

□ If $1/sC_L$ is dominant (e.g., driving large cap load, or @ high freq)

$$Z_{in} \approx \frac{1}{sC_{gs}} + \frac{1}{sC_L} + \frac{g_m}{s^2 C_{gs} C_L} = \frac{1}{j\omega C_{gs}} + \frac{1}{j\omega C_L} - \frac{g_m}{\omega^2 C_{gs} C_L} \rightarrow \text{-ve res!}$$

□ Can be used in oscillators, and may make amplifiers unstable!

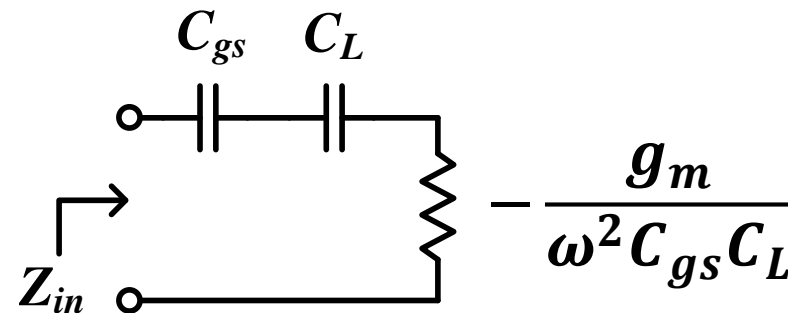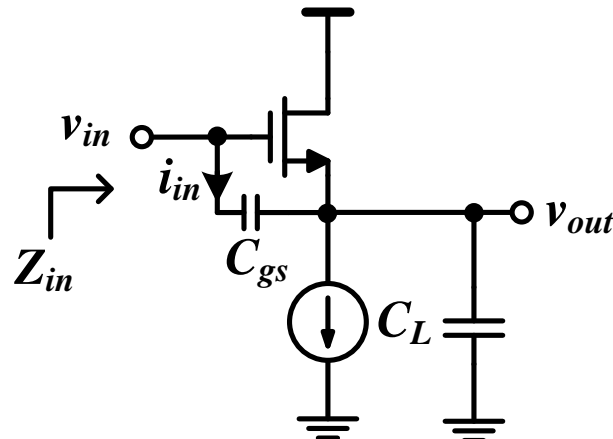□ Note that C_{gd} shunts Z_{in} at high frequency





Z_{out} of CD

$$\square \quad i_x = \frac{v_x}{1/sC_{gs} + R_{sig}} + g_m \cdot \frac{v_x}{1/sC_{gs} + R_{sig}} \cdot \frac{1}{sC_{gs}}$$

$$Z_{out} = \frac{v_x}{i_x} = \frac{1}{g_m} \left(\frac{1 + sR_{sig}C_{gs}}{1 + s\frac{C_{gs}}{g_m}} \right)$$

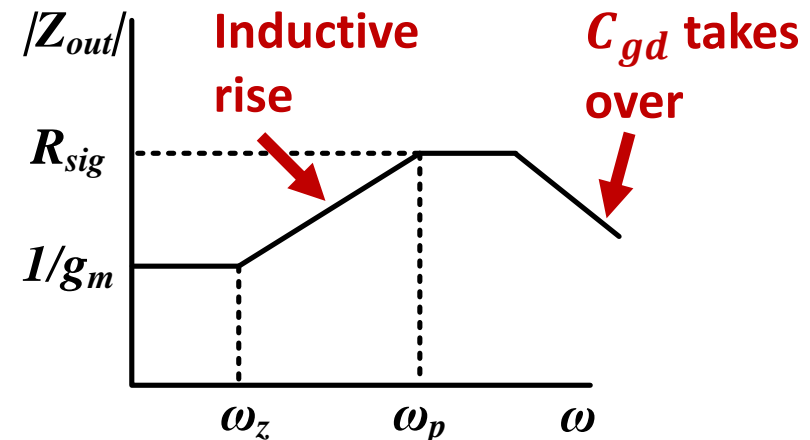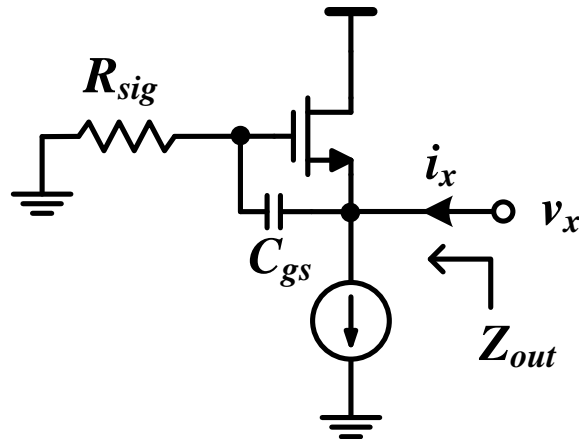- \square By intuition: $\omega \downarrow\downarrow$: $Z_{out} \approx 1/g_m$ and $\omega \uparrow\uparrow$: $Z_{out} \approx R_{sig}$
- \square Usually $R_{sig} > 1/g_m$ (buffer) \rightarrow inductive rise
- \square Note that C_{gd} shunts R_{sig} at high frequency ($\approx 1/R_{sig}C_{gd}$)
- \square Body resistance ($1/g_{mb}$) and r_o add to Z_{out} in parallel



Thank you!

References

- ❑ A. Sedra and K. Smith, “Microelectronic Circuits,” Oxford University Press, 7th ed., 2015
- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2nd ed., 2017
- ❑ T. C. Carusone, D. Johns, and K. W. Martin. “Analog Integrated Circuit Design,” Wiley, 2nd ed., 2012

Quiz

- ☐ $L_D = 100 \text{ nH}$, $C_{gd} = 10 \text{ fF}$, $g_m = 10 \text{ mS}$, $w = 10 \text{ Gr/s}$
- ☐ Ignore V_A and other caps
- ☐ Assume $A_v \gg 1$
- ☐ $R_{in} = ?$

