

Analog IC Design

Lecture 08 Frequency Response (1)

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Outline

- ❑ Recapping previous key results
- ❑ Bode plot review
- ❑ Where are the capacitors?
- ❑ Approximate analysis techniques
 - Short-circuit time constant (SCTC) and open-circuit time constant (OCTC) techniques
 - Dominant pole approximation
- ❑ IC amplifier frequency response
 - Unity gain frequency (UGF) and gain-bandwidth product (GBW)
- ❑ Calculating zeros and poles by inspection
 - Associating poles with nodes
- ❑ Miller's theorem

Outline

- ❑ Recapping previous key results
- ❑ Bode plot review
- ❑ Where are the capacitors?
- ❑ Approximate analysis techniques
 - Short-circuit time constant (SCTC) and open-circuit time constant (OCTC) techniques
 - Dominant pole approximation
- ❑ IC amplifier frequency response
 - Unity gain frequency (UGF) and gain-bandwidth product (GBW)
- ❑ Calculating zeros and poles by inspection
 - Associating poles with nodes
- ❑ Miller's theorem

MOSFET in Saturation




- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \quad OR \quad V_{DS} \geq V_{ov}$$


- ❑ Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
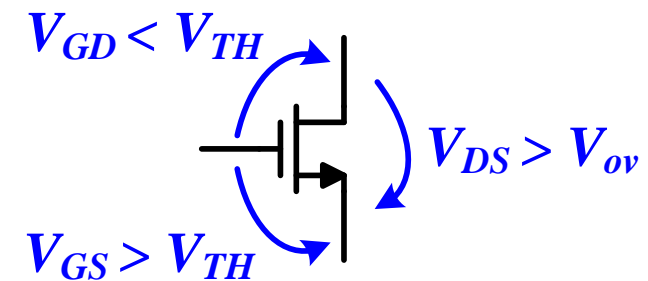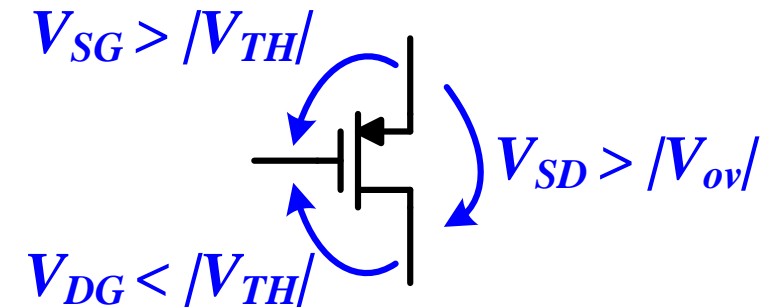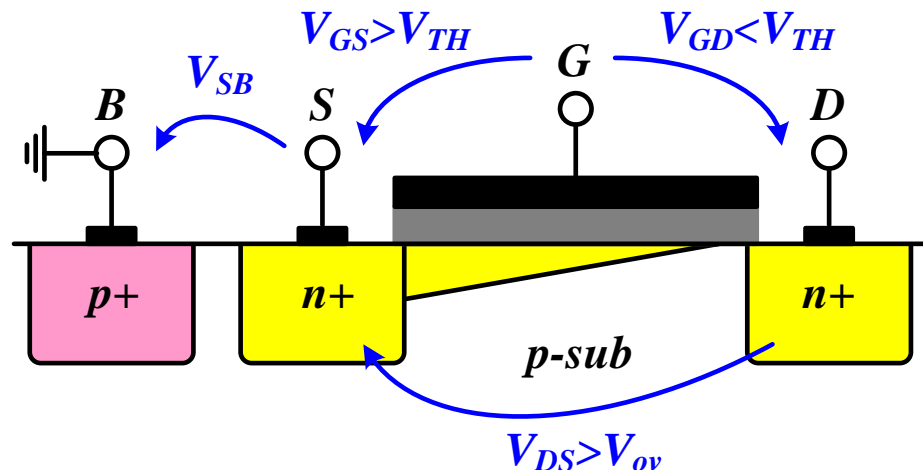
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$



Regions of Operation Summary

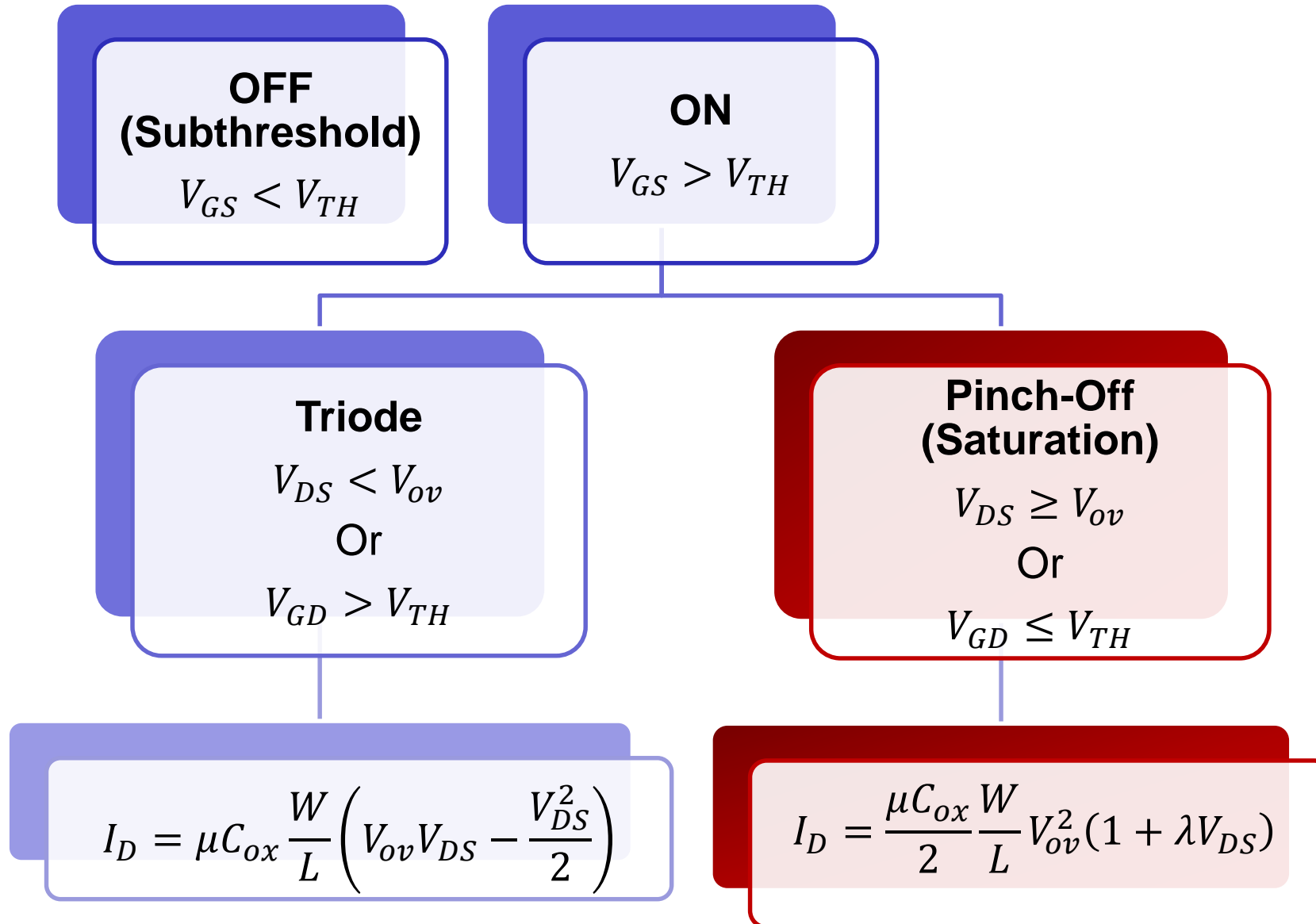


Low-Frequency Small-Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$
$$g_{mb} = \eta g_m \quad \eta \approx 0.1 - 0.25$$


$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D}$$

$$V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L}$$


$$V_{DS} \uparrow \quad V_A \uparrow$$

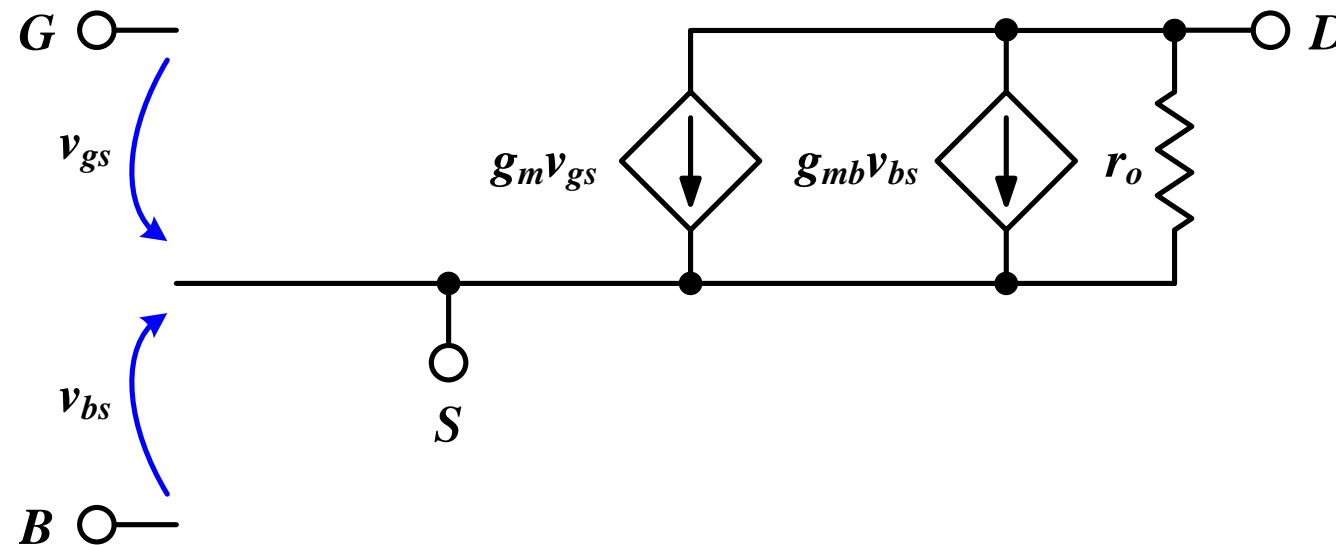

Rin/out Shortcuts Summary




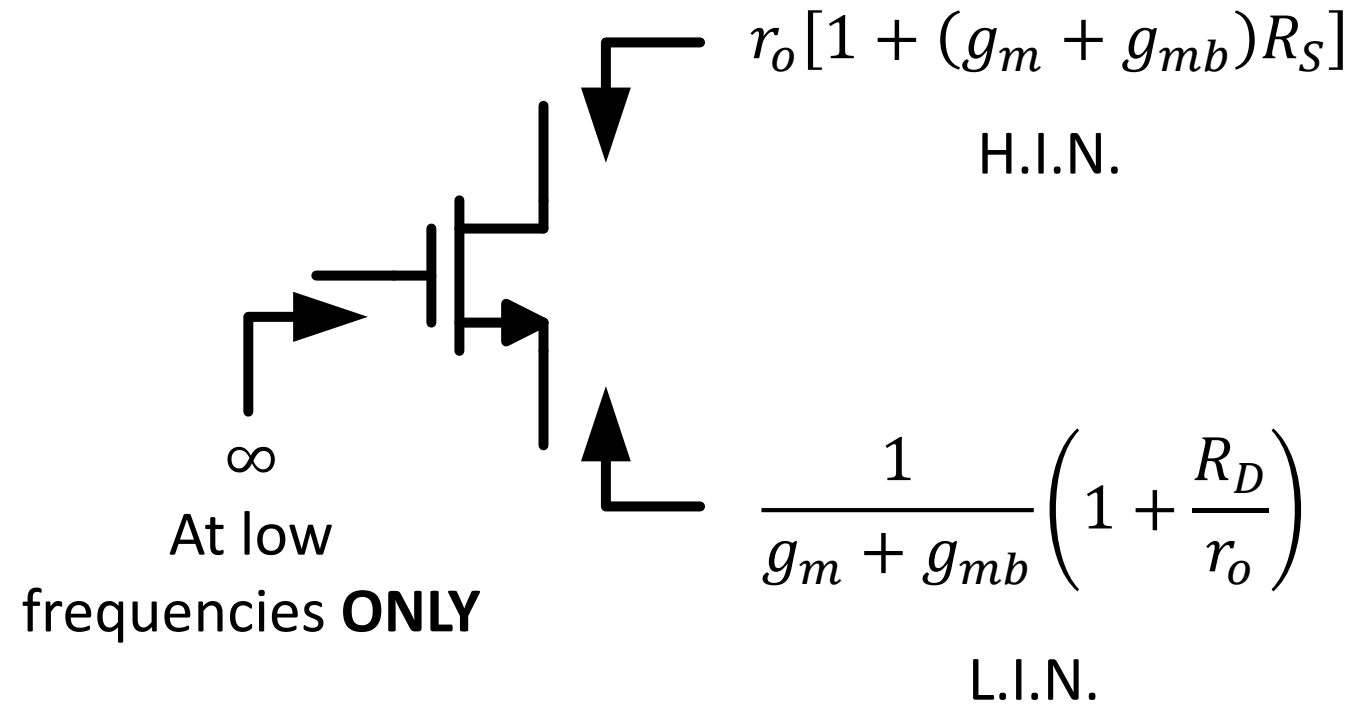


Active Load (Source OFF)

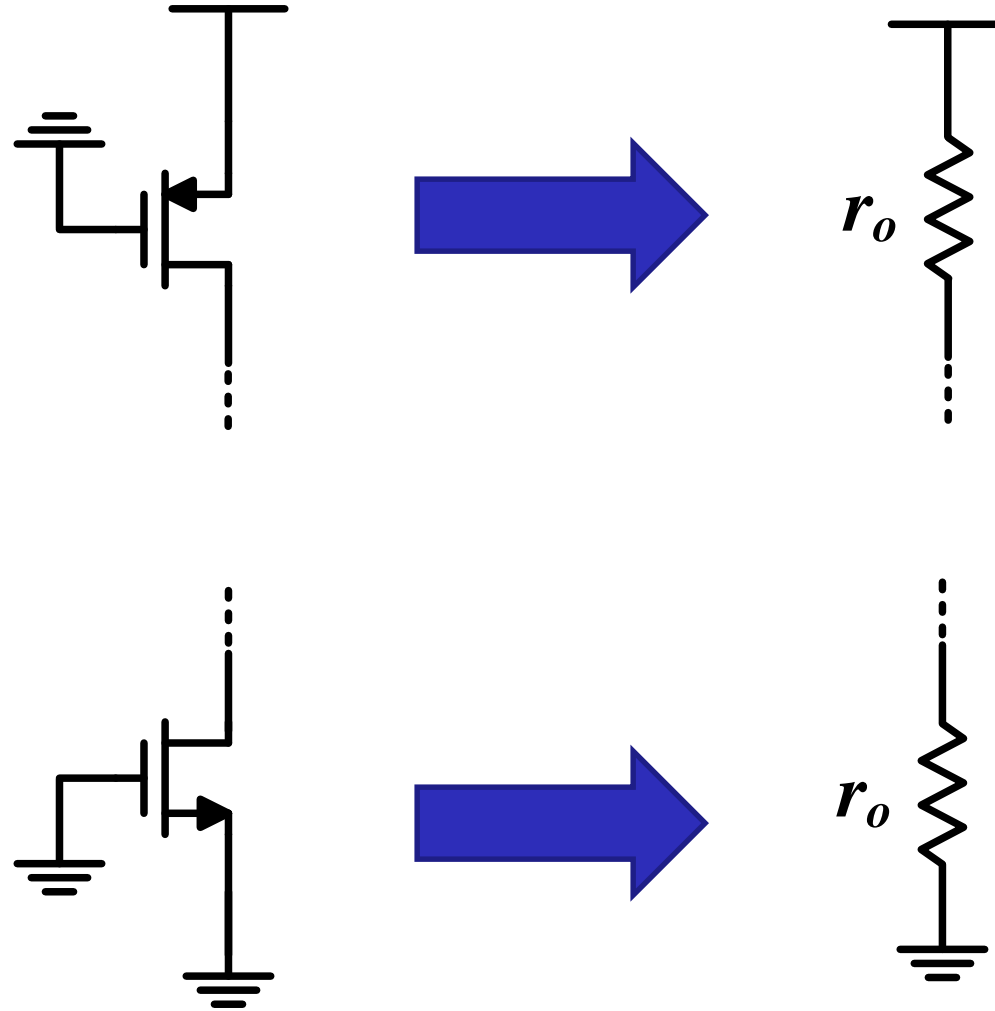

Diode Connected (Source Absorption)

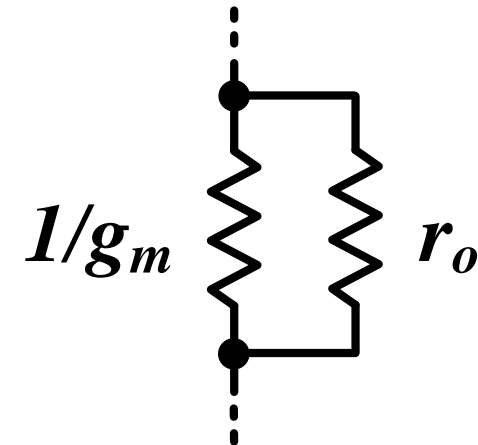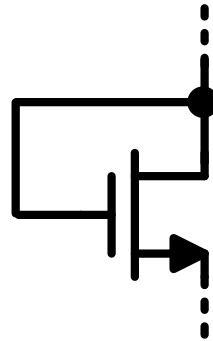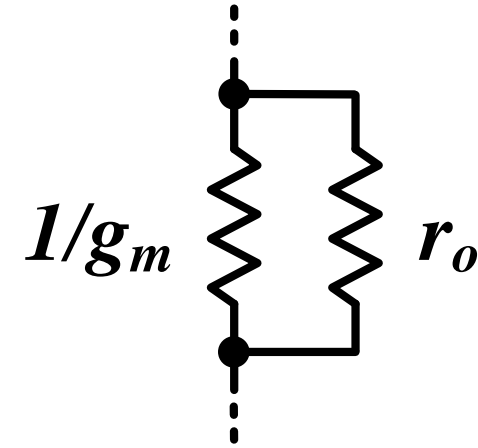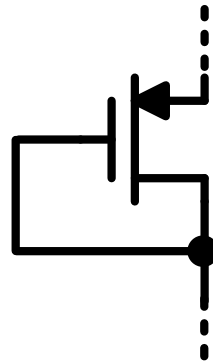- ❑ Always in saturation ($V_{DS} = V_{GS} > V_{ov}$)
- ❑ Body effect: $g_m \rightarrow g_m + g_{mb}$ (if G is ac gnd)



Why GmRout?


$$R_{in} = v_{in}/i_{in}$$

$$R_{out} = v_x/i_x @ v_{in} = 0$$

$$G_m = i_{out,sc}/v_{in}$$


$$A_v = G_m R_{out}$$

$$A_i = G_m R_{in}$$



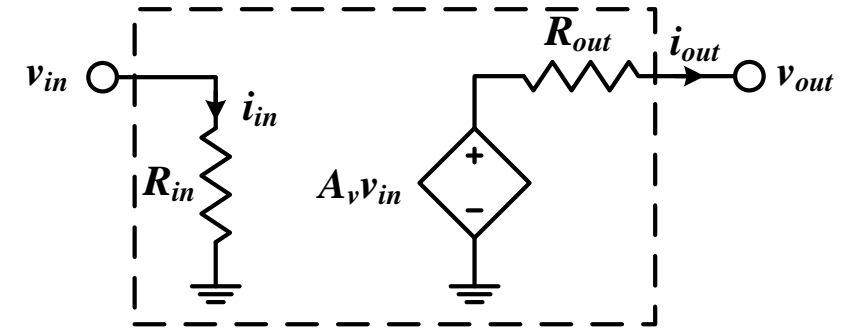


□ Divide and conquer

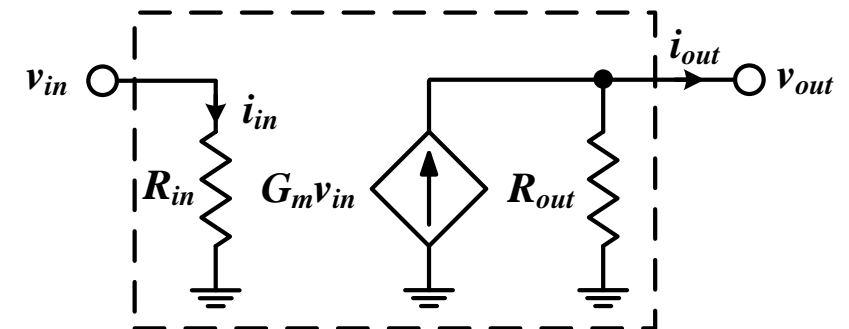- Rout simplified: $v_{in}=0$
- Gm simplified: $v_{out}=0$
- We already need R_{in}/out and Gm
- We can quickly and easily get R_{in}/out from the shortcuts



Summary of Basic Topologies

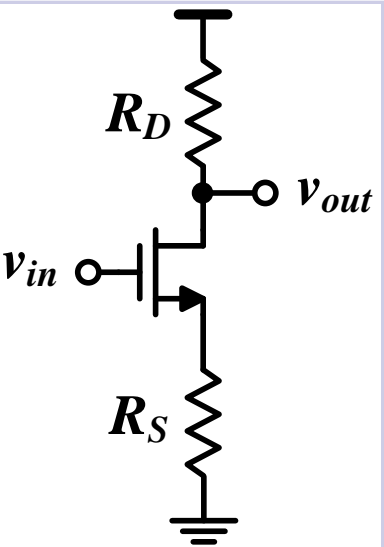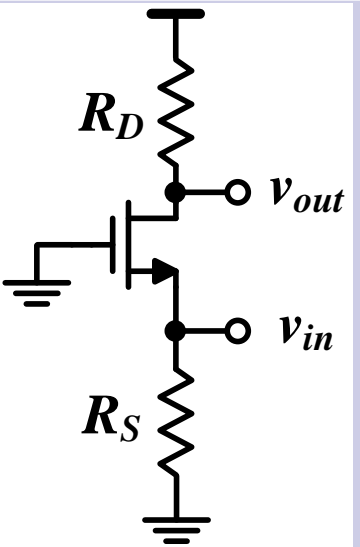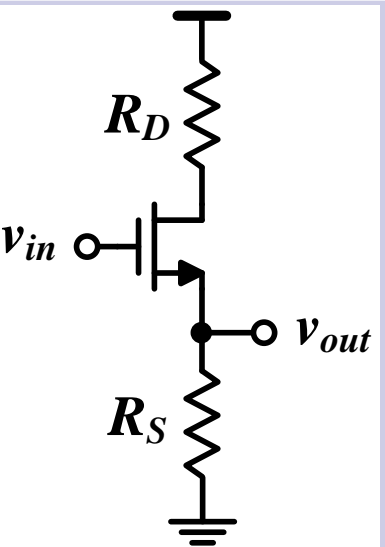	CS	CG	CD (SF)
			
	Voltage & current amplifier	Voltage amplifier Current buffer	Voltage buffer Current amplifier
R_{in}	∞	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$	∞
R_{out}	$R_D \parallel r_o [1 + (g_m + g_{mb})R_S]$	$R_D \parallel r_o$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$
G_m	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$



Outline

- ❑ Recapping previous key results
- ❑ **Bode plot review**
- ❑ Where are the capacitors?
- ❑ Approximate analysis techniques
 - Short-circuit time constant (SCTC) and open-circuit time constant (OCTC) techniques
 - Dominant pole approximation
- ❑ IC amplifier frequency response
 - Unity gain frequency (UGF) and gain-bandwidth product (GBW)
- ❑ Calculating zeros and poles by inspection
 - Associating poles with nodes
- ❑ Miller's theorem



Frequency Response

□ Y-axis: magnitude of frequency response, x-axis: frequency



LPF

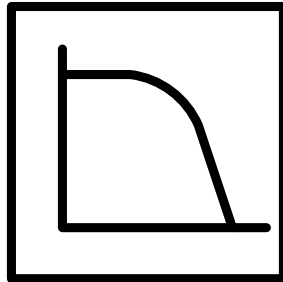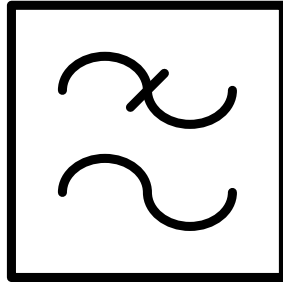

BPF

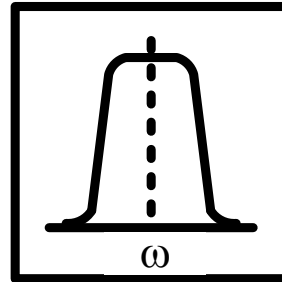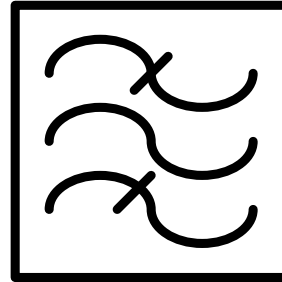

HPF

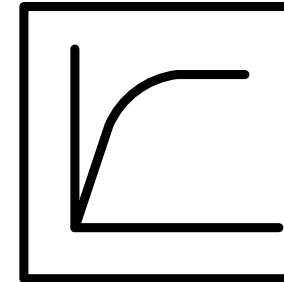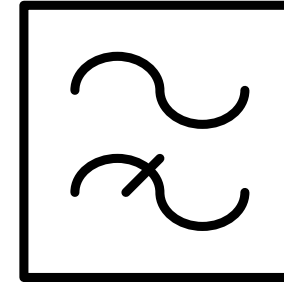

Poles and Zeros

❑ Transfer function

$$H(s) = \frac{N(s)}{D(s)}$$

❑ Zeros: roots of numerator $\Rightarrow N(s)$


❑ Poles: roots of denominator $\Rightarrow D(s)$

❑ Frequency response: $s \Rightarrow j\omega$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = |H(j\omega)|e^{j\phi}$$

❑ Magnitude($a + jb$) = $r = \sqrt{a^2 + b^2}$

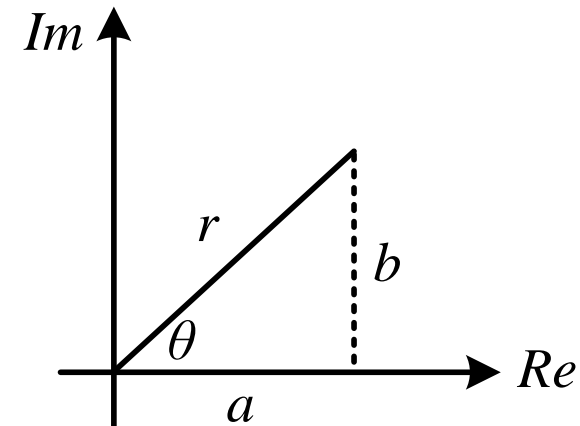❑ Phase($a + jb$) = $\theta = \tan^{-1} \frac{b}{a}$



1st Order LPF

$$H(s) = \frac{v_{out}}{v_{in}} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{1}{1 + s\tau}$$

$$H(j\omega) = \frac{v_{out}}{v_{in}} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + \frac{j\omega}{\omega_c}}$$



□ $\tau = RC$: time constant

□ $\omega_c = \frac{1}{\tau} = \frac{1}{RC}$: cutoff/corner frequency

□ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$, Zeros: ?

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$
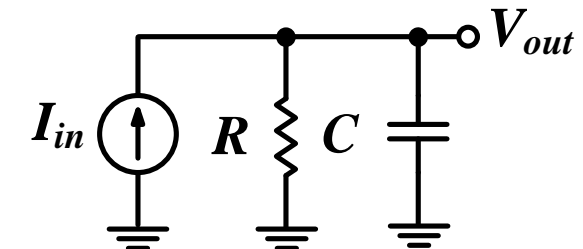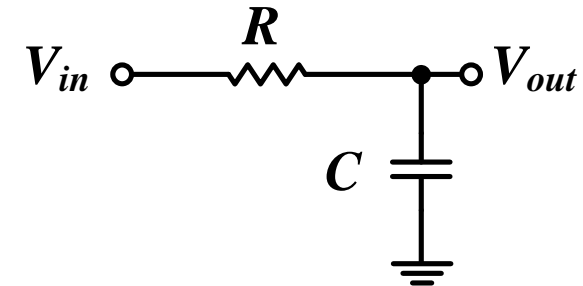
$$P(H(j\omega)) = -\tan^{-1} \frac{\omega}{\omega_c}$$




Bode Plot Rules

	Pole	Zero
Magnitude	-20 dB/decade Actual Mag @ pole: -3 dB	+20 dB/decade Actual Mag @ zero: +3 dB
Phase	-90° Actual Phase @ pole: -45°	LHP zero: +90° Actual Phase @ zero: +45°
		RHP zero: -90° Actual Phase @ zero: -45°

- RHP: Right-half plane ($\text{Re}\{s\} > 0$)
- LPH: Left-half plane ($\text{Re}\{s\} < 0$)


1st Order LPF Bode Plot

$20 \log|H(j\omega)|$ (dB)

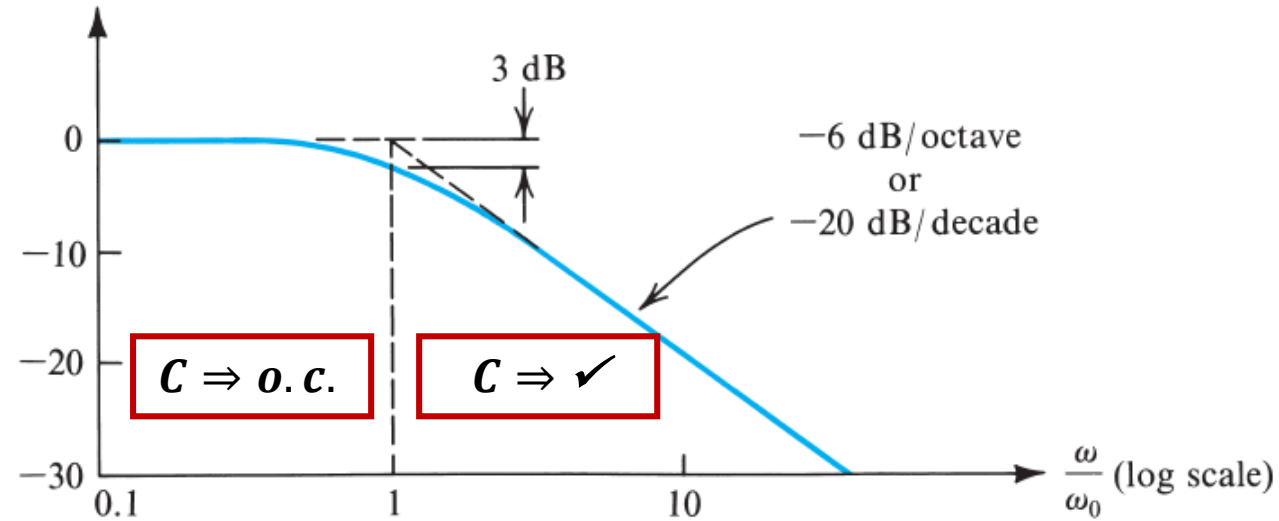

(a)

$P(H(j\omega))$

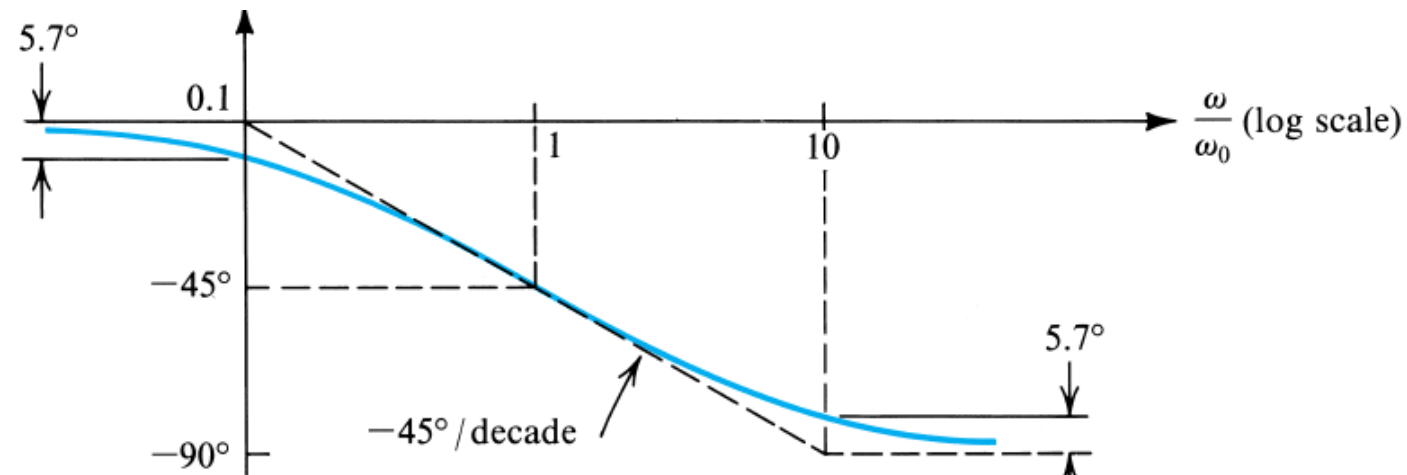

(b)

1st Order HPF

$$H(s) = \frac{v_{out}}{v_{in}} = \frac{R}{R + 1/sC} = \frac{sRC}{1 + sRC} = \frac{s\tau}{1 + s\tau}$$


$$H(j\omega) = \frac{v_{out}}{v_{in}} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} = \frac{\frac{j\omega}{\omega_c}}{1 + \frac{j\omega}{\omega_c}}$$

❑ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$

❑ Zeros: $s_z = 0$

❑ $|H(j\omega)| = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$

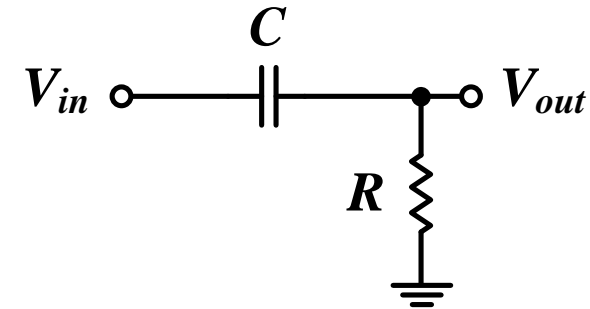❑ $P(H(j\omega)) = 90^\circ - \tan^{-1} \frac{\omega}{\omega_c}$




Bode Plot Rules

	Pole	Zero
Magnitude	-20 dB/decade Actual Mag @ pole: -3 dB	+20 dB/decade Actual Mag @ zero: +3 dB
Phase	-90° Actual Phase @ pole: -45°	LHP zero: +90° Actual Phase @ zero: +45°
		RHP zero: -90° Actual Phase @ zero: -45°

- RHP: Right-half plane ($\text{Re}\{s\} > 0$)
- LPH: Left-half plane ($\text{Re}\{s\} < 0$)


1st Order HPF Bode Plot

$20 \log|H(j\omega)|$ (dB)

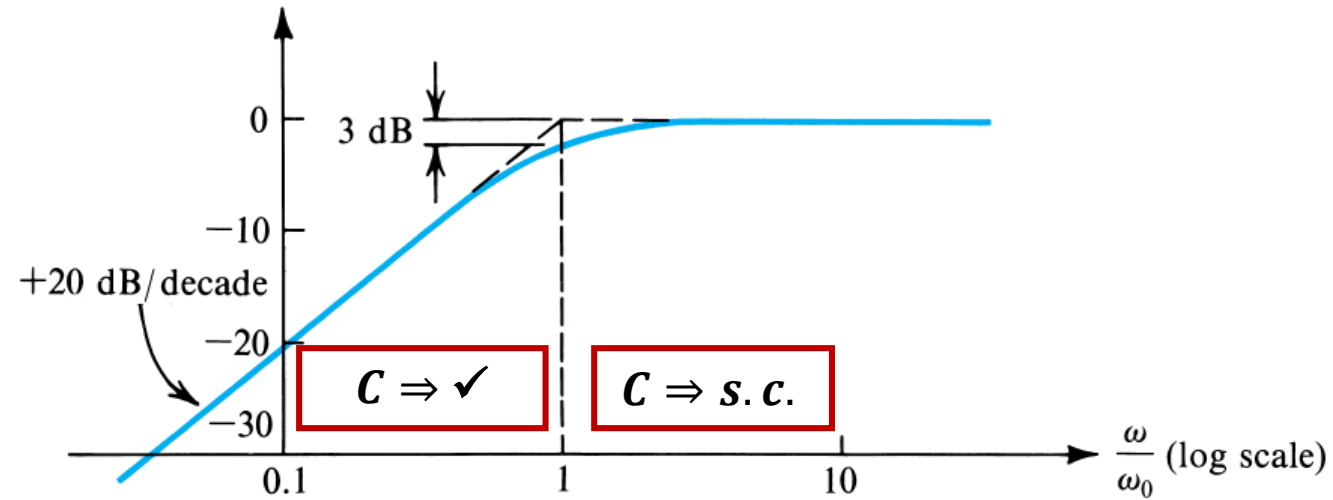

(a)

$P(H(j\omega))$

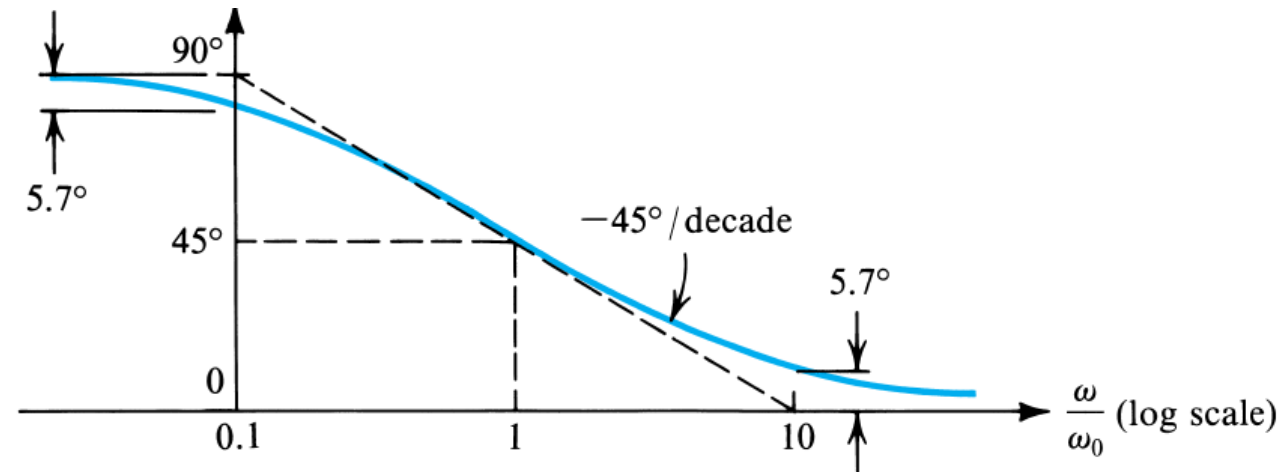


(b)

Outline

- ❑ Recapping previous key results
- ❑ Bode plot review
- ❑ Where are the capacitors?
- ❑ Approximate analysis techniques
 - Short-circuit time constant (SCTC) and open-circuit time constant (OCTC) techniques
 - Dominant pole approximation
- ❑ IC amplifier frequency response
 - Unity gain frequency (UGF) and gain-bandwidth product (GBW)
- ❑ Calculating zeros and poles by inspection
 - Associating poles with nodes
- ❑ Miller's theorem

Where are the Capacitors?

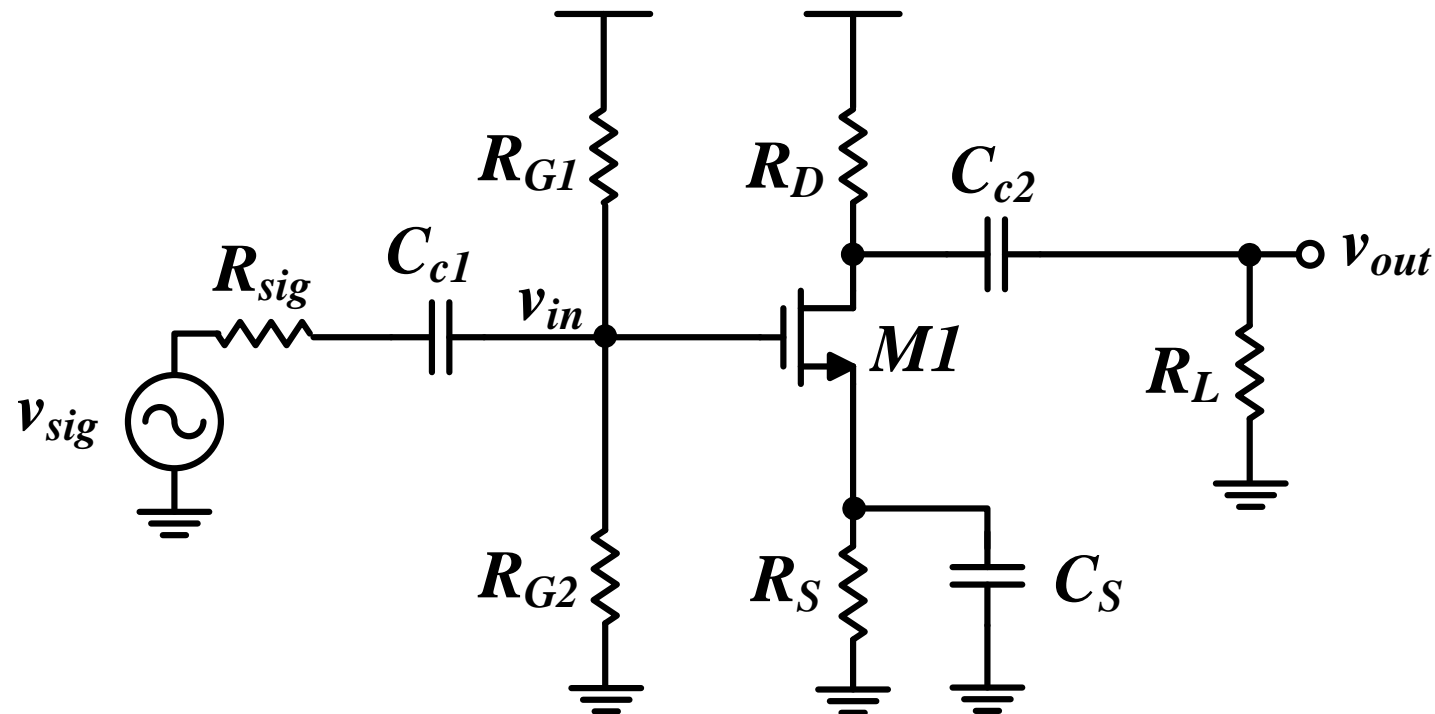- ❑ Coupling capacitors: C_{c1} and C_{c2} \rightarrow act as HPF (affect LFR)
- ❑ Bypass capacitor: C_S
- ❑ Usually quite large $\sim \mu F$



Effect of Bypass Capacitor


□ Does C_S act as a LPF or a HPF?

- By intuition, at high frequency C_S will increase the gain \rightarrow HPF

$$G_m(s) = \frac{g_m}{1+g_m Z_S} \quad Z_S = \frac{1}{1/R_S + sC_S} = \frac{R_S}{1+sR_SC_S}$$


$$G_m(s) = \frac{g_m(1+sR_SC_S)}{(1+g_mR_S)\left(1+\frac{sR_SC_S}{1+g_mR_S}\right)}$$
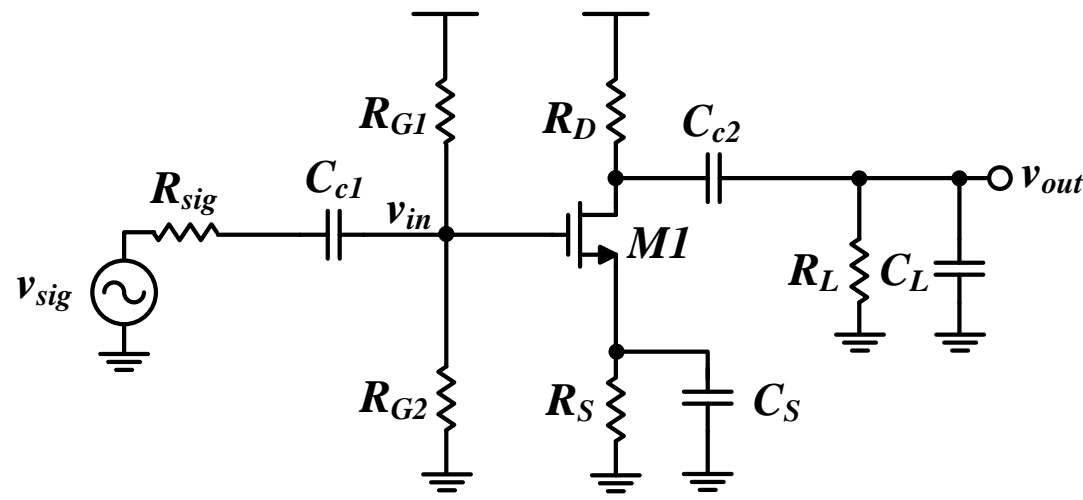
$$s_z = -\frac{1}{R_SC_S} \text{ and } s_p = -\frac{1+g_mR_S}{R_SC_S} \Rightarrow \omega_p > \omega_z \Rightarrow \text{HPF}$$



Where are the Capacitors?

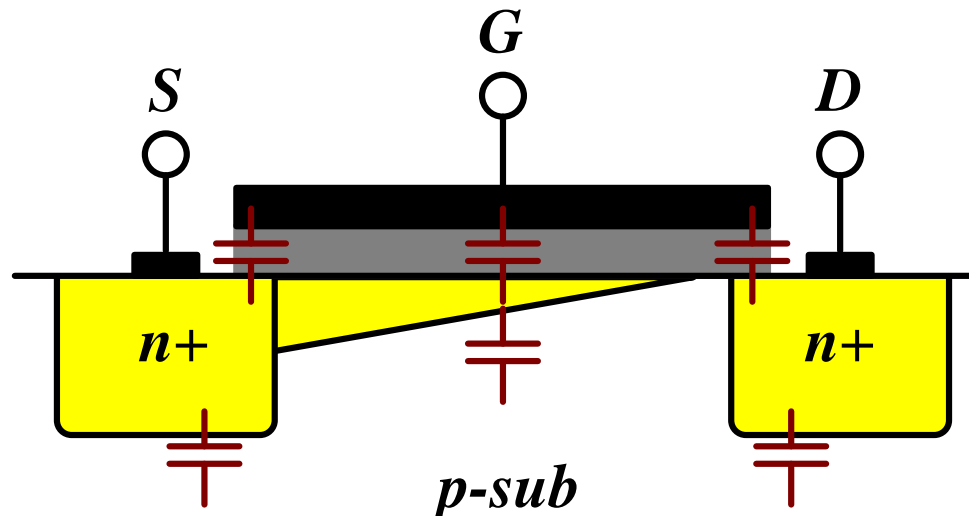
- ❑ Gate capacitance ($C_{gg} = C_{gb} + C_{gs} + C_{gd}$)
 - Intrinsic part fundamental to MOSFET operation
 - Parasitic part due to the overlap between gate and S/D (C_{ov})
- ❑ S/D capacitance (C_{sb} and C_{db})
 - Parasitic capacitances due to reverse biased pn-junctions
 - Bottom-plate (C_j) and side-wall components (C_{jsw})
- ❑ Usually quite small $\sim fF$



MOSFET Capacitance


- C_{ov} per unit width, C_j per unit area, and C_{jsw} per unit perimeter

	Cutoff	Triode	Saturation
C_{gb}	$< WLC_{ox}$	0	0
C_{gs}	WC_{ov}	$\frac{1}{2}WLC_{ox} + WC_{ov}$	$\frac{2}{3}WLC_{ox} + WC_{ov}$
C_{gd}	WC_{ov}	$\frac{1}{2}WLC_{ox} + WC_{ov}$	WC_{ov}
C_{sb}	$A_S C_j + P_S C_{jsw}$	$\left(A_S + \frac{WL}{2}\right) C_j + P_S C_{jsw}$	$(A_S + WL) C_j + P_S C_{jsw}$
C_{db}	$A_D C_j + P_D C_{jsw}$	$\left(A_D + \frac{WL}{2}\right) C_j + P_D C_{jsw}$	$A_D C_j + P_D C_{jsw}$

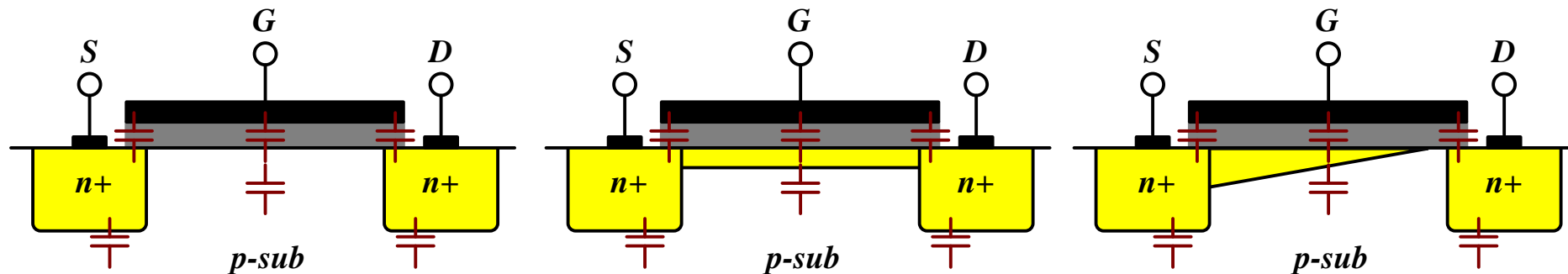


High Frequency Small Signal Model

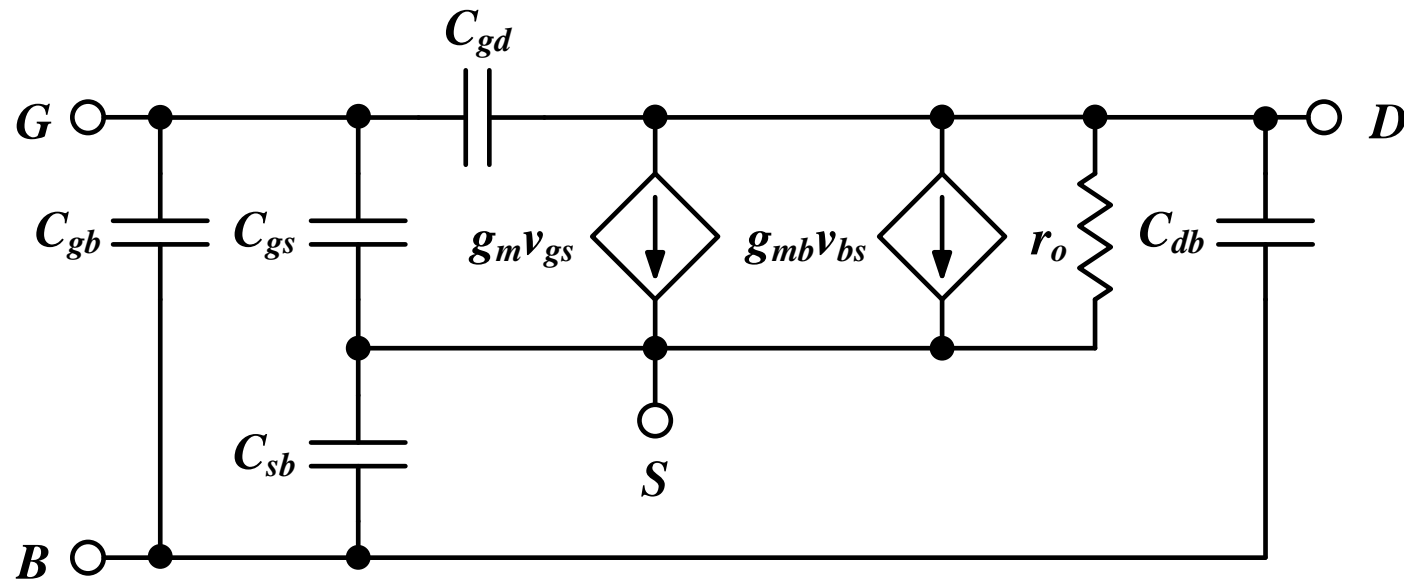- ❑ MOSFET capacitances act as LPF (affect HFR)
- ❑ In pinch-off saturation
 - $C_{gb} \approx 0$ (for SI only)
 - $C_{gs} \gg C_{gd}$ (not valid for $L \downarrow\downarrow$, why?)
 - $C_{sb} > C_{db}$



N-Well Capacitance

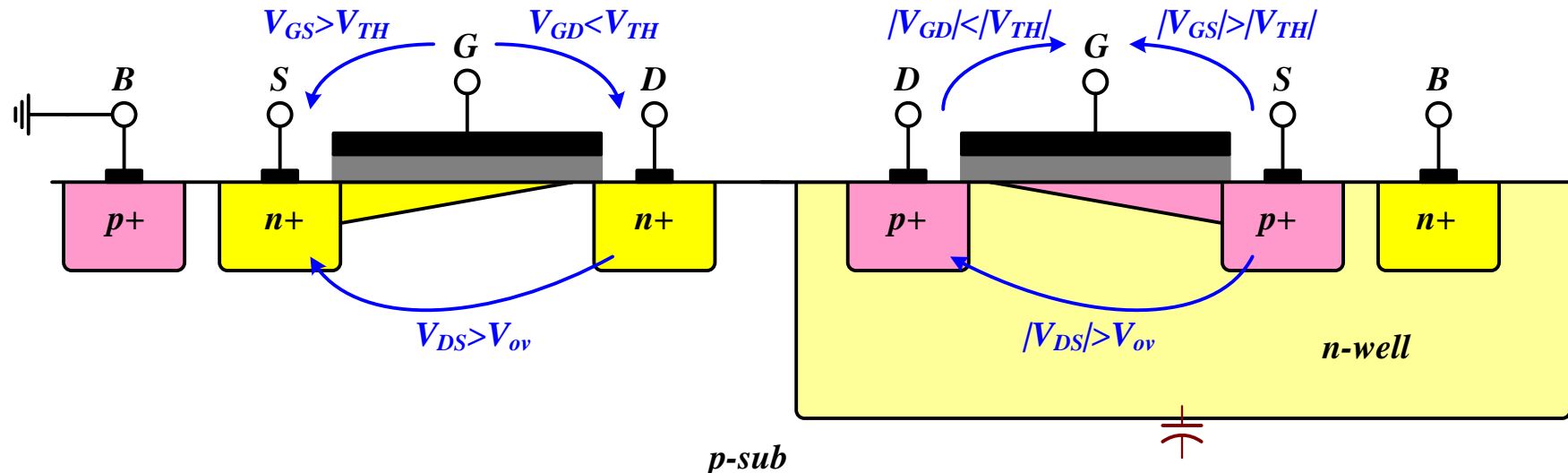
- ❑ There is an additional junction cap between n-well and p-sub
- ❑ If the n-well is tied to VDD this cap is ac shorted (why?)
- ❑ But if n-well is floating (e.g., PMOS S and B connected) this cap is not ac shorted
 - Usually not modeled in SPICE
 - Must be added manually $\sim 0.05fF/\mu m^2$



Outline

- ❑ Recapping previous key results
- ❑ Bode plot review
- ❑ Where are the capacitors?
- ❑ **Approximate analysis techniques**
 - Short-circuit time constant (SCTC) and open-circuit time constant (OCTC) techniques
 - Dominant pole approximation
- ❑ IC amplifier frequency response
 - Unity gain frequency (UGF) and gain-bandwidth product (GBW)
- ❑ Calculating zeros and poles by inspection
 - Associating poles with nodes
- ❑ Miller's theorem

Frequency Response

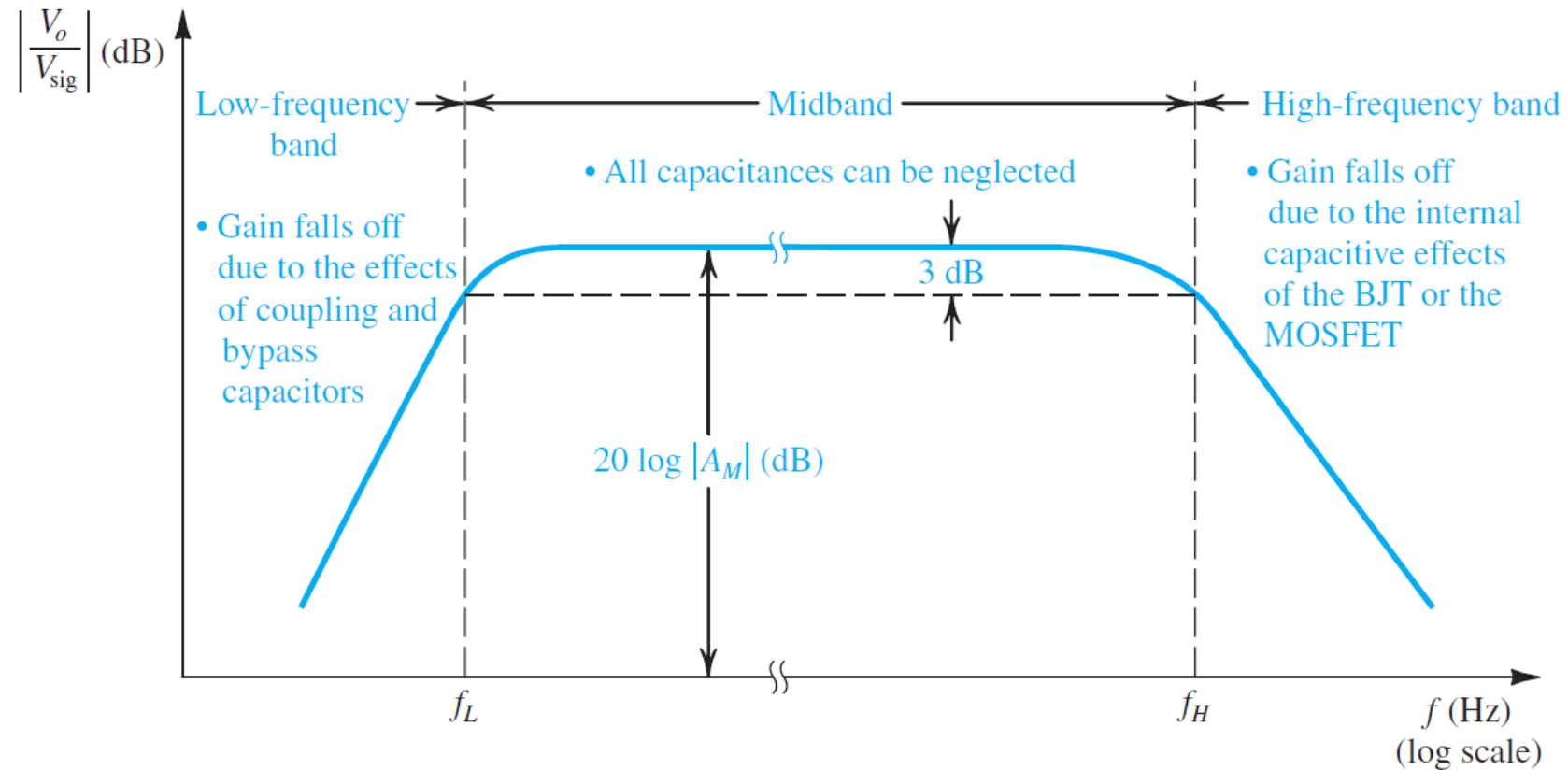

Coupling and bypass cap	✓	S.C.	S.C.
MOSFET and load cap	O.C.	O.C.	✓

SCTC and OCTC Techniques

- ❑ Low-frequency range (LFR) => Not common in Analog IC design
 - Only consider one cap at a time → Assume other caps are s.c. → s.c. time constant (SCTC) technique
 - $\omega_{L,3dB} \approx \omega_{L1} + \omega_{L2} + \dots$
 - Highest pole dominates (L.I.N. dominates)
- ❑ **High-frequency range (HFR) => More important in Analog ICs**
 - Only consider one cap at a time → Assume other caps are o.c. → o.c. time constant (OCTC) technique
 - $\omega_{H,3dB} \approx \omega_{H1} // \omega_{H2} // \dots$
 - Lowest pole dominates (H.I.N. dominates)
- ❑ Both SCTC and OCTC provide good approx if one pole is dominant and poles are real

Dominant Pole Approximation

- Assume the poles are real and widely separated: $\omega_{p1} \ll \omega_{p2}$

$$\begin{aligned} A_v(s) &\approx \frac{A_o}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)} = \frac{A_o}{1 + \left(\frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}}\right)s + \frac{1}{\omega_{p1}\omega_{p2}}s^2} \\ &\approx \frac{A_o}{1 + \left(\frac{1}{\omega_{p1}}\right)s + \frac{1}{\omega_{p1}\omega_{p2}}s^2} = \frac{A_o}{1 + b_1s + b_2s^2} \\ \omega_{p1} &\approx \frac{1}{b_1} \quad \text{and} \quad \omega_{p2} \approx \frac{1}{b_2\omega_{p1}} = \frac{b_1}{b_2} \end{aligned}$$

- OCTC provides an approx value for dominant pole only
- Dominant pole approx provides an approx value for both dominant and non-dominant poles


Outline

- ❑ Recapping previous key results
- ❑ Bode plot review
- ❑ Where are the capacitors?
- ❑ Approximate analysis techniques
 - Short-circuit time constant (SCTC) and open-circuit time constant (OCTC) techniques
 - Dominant pole approximation
- ❑ IC amplifier frequency response
 - Unity gain frequency (UGF) and gain-bandwidth product (GBW)
- ❑ Calculating zeros and poles by inspection
 - Associating poles with nodes
- ❑ Miller's theorem

IC Amplifier Frequency Response

- ❑ A_o is the low-frequency gain (or DC gain) of the amplifier
- ❑ ω_{p1} is the dominant pole (ω_{pd}) \approx 3dB bandwidth = $BW = \omega_{3dB}$
- ❑ ω_{p2} is the non-dominant pole (ω_{pnd})
- ❑ Unity gain frequency (UGF, ω_u) is the frequency at which gain is unity (1 = 0dB)
- ❑ Gain-Bandwidth Product (GBW) = $Gain \times BW \approx A_o \omega_{p1}$
- ❑ Usually, we design the amplifier such that ω_{p2} and $\omega_z > \omega_u$
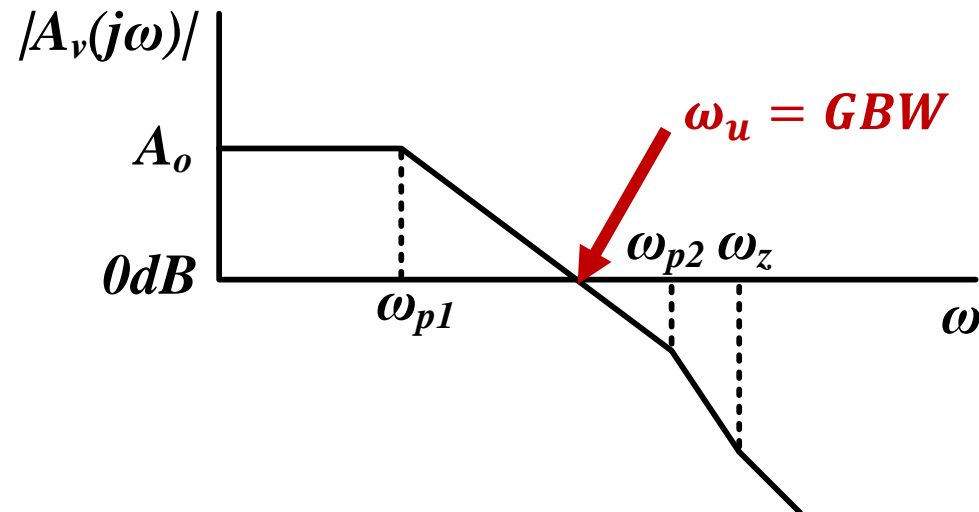
$$A_v(s) = \frac{A_o \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$




UGF and GBW

□ At UGF $\omega = \omega_u$: $\omega \gg \omega_{p1}$ and $\omega \ll \omega_{p2}, \omega_z$

$$|A_v(\omega_u)| = \left| \frac{A_o \left(1 + \frac{j\omega_u}{\omega_z}\right)}{\left(1 + \frac{j\omega_u}{\omega_{p1}}\right) \left(1 + \frac{j\omega_u}{\omega_{p2}}\right)} \right| \approx \left| \frac{A_o}{j\omega_u/\omega_{p1}} \right| = 1 = 0 \text{ dB}$$

$$UGF = \omega_u \approx A_o \omega_{p1} \approx \text{Gain} \times BW = GBW$$
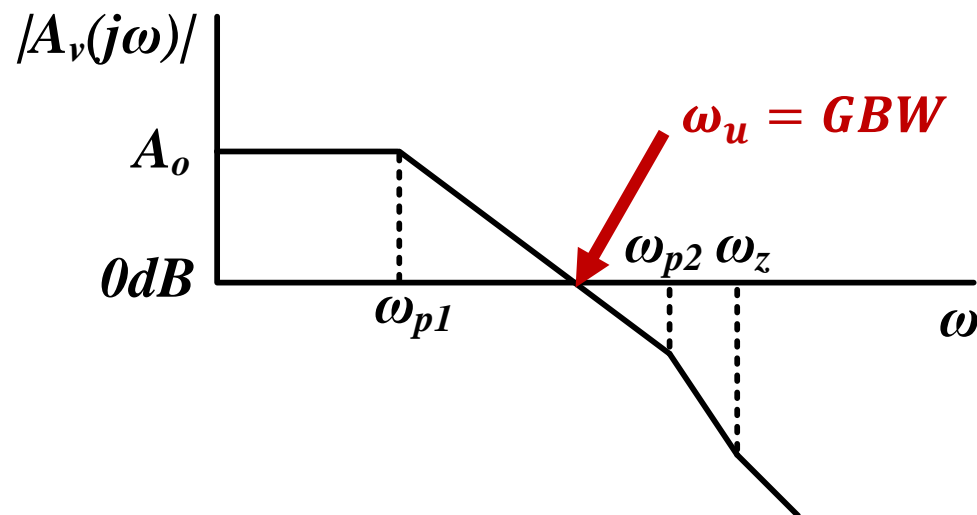
$$A_v(s) = \frac{A_o \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$



Outline


- ❑ Recapping previous key results
- ❑ Bode plot review
- ❑ Where are the capacitors?
- ❑ Approximate analysis techniques
 - Short-circuit time constant (SCTC) and open-circuit time constant (OCTC) techniques
 - Dominant pole approximation
- ❑ IC amplifier frequency response
 - Unity gain frequency (UGF) and gain-bandwidth product (GBW)
- ❑ Calculating zeros and poles by inspection
 - Associating poles with nodes
- ❑ Miller's theorem

Calculating Zeros by Inspection

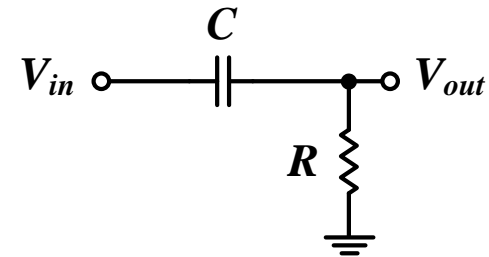1. Find the value $s = s_z$ that makes $H(s) = 0 \Rightarrow v_{out} = 0$

□ Ex1: C : $v_o = 0$ if $Z_C = \infty$

- $Z_C = \frac{1}{sC}$
- $\Rightarrow s_z = 0$




□ Ex2: C_{c1} : $v_o = 0$ if $Z_{C_1} = \infty$

- $Z_{C_1} = \frac{1}{sC_1}$
- $\Rightarrow s_{z1} = 0$

□ Ex3: C_S : $v_o = 0$ if $Z_S = \infty$

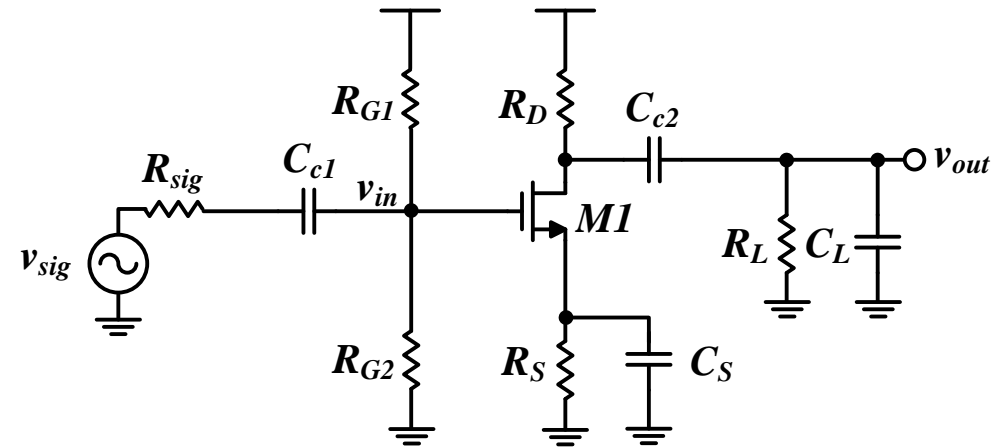- $Z_S = \frac{R_S}{1+sR_SC_S}$
- $\Rightarrow s_{z2} = -\frac{1}{R_SC_S}$



Calculating Poles by Inspection

1. Set $v_{sig} = 0$ (deactivate independent sources)
2. Calculate Thevenin resistance ($R_{th,i}$) seen by each cap (C_i)

$$3. s_{p,i} = -\frac{1}{R_{th,i}C_i}$$

□ Ex1: $C: R_{th} = R$



■ $\Rightarrow s_p = -\frac{1}{RC}$

□ Ex2: $C_{c1}: R_{th} = R_{sig} + R_G$

■ $\Rightarrow s_{p1} = -\frac{1}{(R_{sig} + R_G)C_{c1}}$

□ Ex3: $C_S: R_{th} \approx R_S // \frac{1}{g_m}$

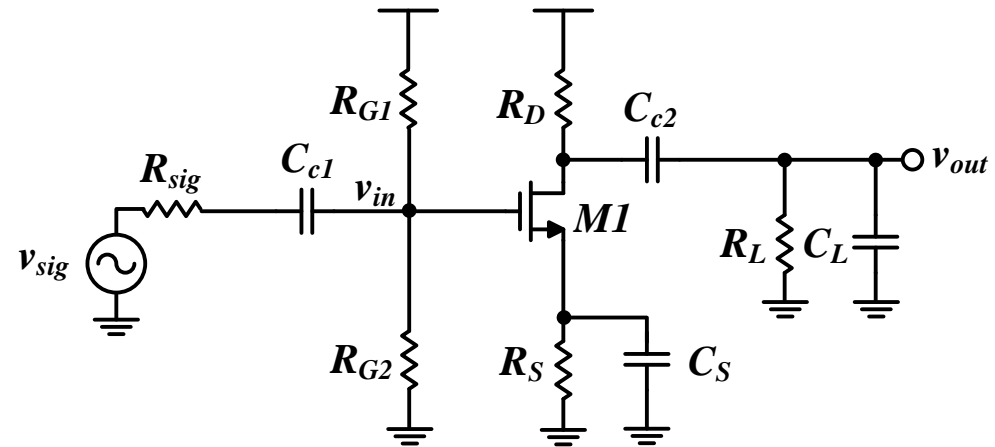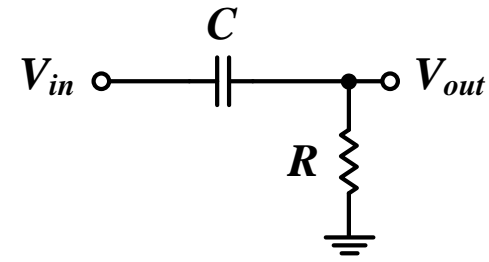■ $\Rightarrow s_{p2} = -\frac{1}{\left(R_S // \frac{1}{g_m}\right)C_S}$



Associating Poles with Nodes


1. Set $v_{sig} = 0$ (deactivate independent sources)
2. Calculate Thevenin resistance ($R_{th,i}$) seen by each cap (C_i)

3. $s_{p,i} = -\frac{1}{R_{th,i}C_i}$

□ Example: Ignore MOSFET r_o and capacitance

- Each node is associated with a pole
- H.I.N. dominates
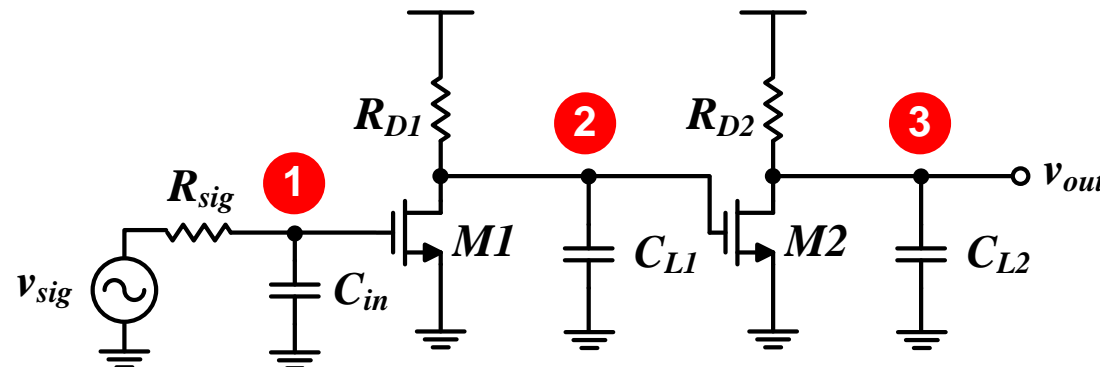
$$H(s) = \frac{(g_{m1}R_{D1})(g_{m2}R_{D2})}{(1 + sR_{sig}C_{in})(1 + sR_{D1}C_{L1})(1 + sR_{D2}C_{L2})}$$





Outline

- ❑ Recapping previous key results
- ❑ Bode plot review
- ❑ Where are the capacitors?
- ❑ Approximate analysis techniques
 - Short-circuit time constant (SCTC) and open-circuit time constant (OCTC) techniques
 - Dominant pole approximation
- ❑ IC amplifier frequency response
 - Unity gain frequency (UGF) and gain-bandwidth product (GBW)
- ❑ Calculating zeros and poles by inspection
 - Associating poles with nodes
- ❑ Miller's theorem

Miller's Theorem
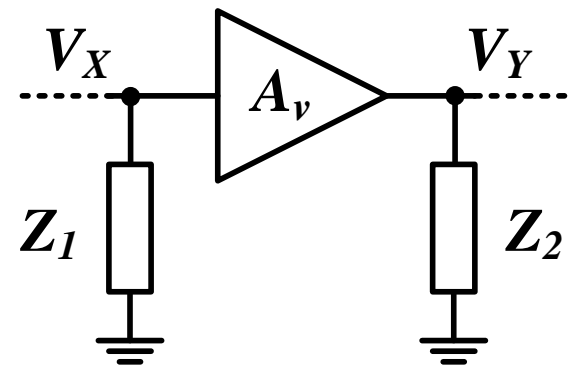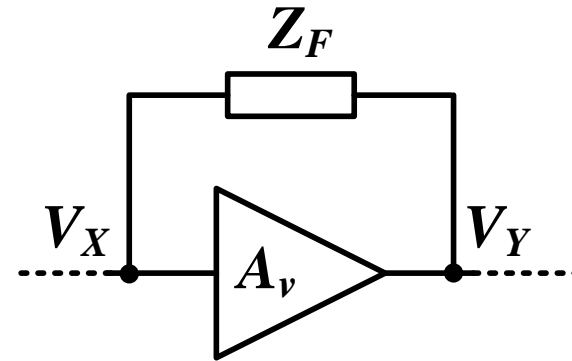
$$A_v = \frac{V_Y}{V_X}$$
$$\frac{V_X - V_Y}{Z_F} = \frac{V_X}{Z_1}$$
$$Z_1 = \frac{Z_F}{1 - \frac{V_Y}{V_X}} = \frac{Z_F}{1 - A_v}$$
$$\frac{V_Y - V_X}{Z_F} = \frac{V_Y}{Z_2}$$
$$Z_2 = \frac{Z_F}{1 - \frac{V_X}{V_Y}} = \frac{Z_F}{1 - \frac{1}{A_v}}$$





❑ Note: Miller's Theorem cannot be used for Z_{out} calculation (why?)

Miller Effect

□ Miller Effect: Capacitance multiplication if $Z_F = 1/sC_F$

$$Z_1 = \frac{Z_F}{1 + A_v} \approx \frac{Z_F}{A_v} = \frac{1}{sA_vC_F} \Rightarrow \mathbf{C_{in} = A_vC_F}$$

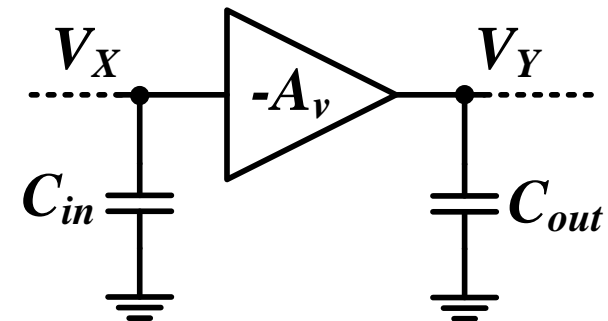
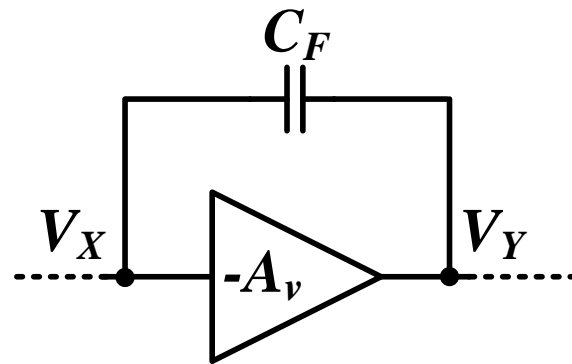
$$Z_2 = \frac{Z_F}{1 + \frac{1}{A_v}} \approx Z_F = \frac{1}{sC_F} \Rightarrow C_{out} \approx C_F$$



Miller's Approximation

$$Z_1 = \frac{Z_F}{1 - A_v} \quad \& \quad Z_2 = \frac{Z_F}{1 - \frac{1}{A_v}}$$

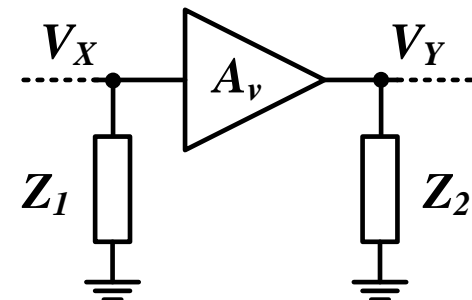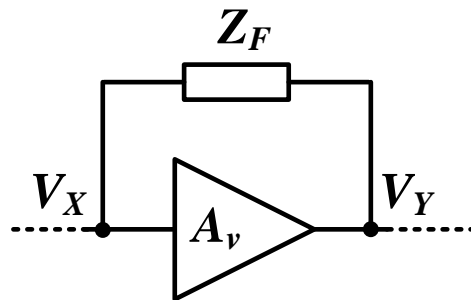- ❑ But A_v is a function of frequency!
- ❑ Miller's Approximation: Substitute with the low frequency gain
 - $A_v(s) \approx A_o$
 - **Gives good approx for the dominant pole ONLY (why?)**
 - It does not tell about the feedforward zero (next slide)



The Feedforward Zero

□ $v_{out} = 0 \rightarrow i_{out} = 0$



□ $v_{in} s C_F = -G_m v_{in}$

$$s_z = -\frac{G_m}{C_F}$$

□ LHP zero if G_m is +ve (e.g. CD)

□ **RHP zero if G_m is -ve (e.g. CS)**

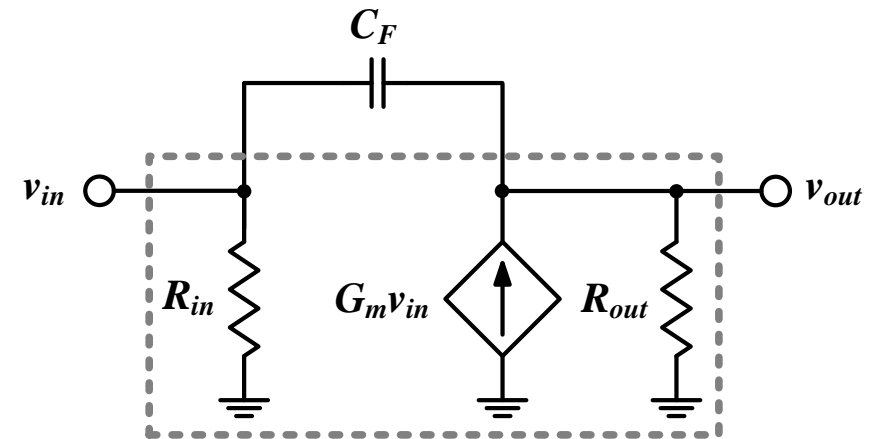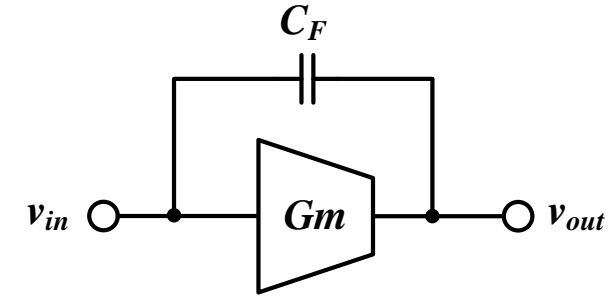- Mag inc and phase drops
- Very bad for FB loop stability
- More on this when we study op-amp design



Thank you!

References

- ❑ A. Sedra and K. Smith, “Microelectronic Circuits,” 7th ed., Oxford University Press, 2015
- ❑ B. Razavi, “Fundamentals of Microelectronics,” 2nd ed., Wiley, 2014
- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2nd ed., 2017
- ❑ N. Weste and D. Harris, “CMOS VLSI Design,” 4th ed., Pearson, 2010
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” 2nd ed., Wiley, 2012
- ❑ R. J. Baker, “CMOS circuit design,” 3rd ed., Wiley, 2010
- ❑ B. Murmann, EE214 Course Reader, Stanford University