

Lab 3

Cascode Amplifier

Part 1: Sizing Chart

Required Spec:

L	0.5um
V*	160mV
Supply	3v
Current Consumption	10uA

Analytic Calculations:

$$|A_v| \approx g_m r_o = \frac{2I_D}{V_{ov}} \times \frac{V_A}{I_D} = \frac{2V_A}{V_{ov}}$$

In Simulation $V_{ov} \neq \frac{2I_D}{g_m}$ all the time, Instead use $V^ = \frac{2I_D}{g_m}$*

$$|A_v| = \frac{2V_A}{V^*}$$

All we need to calculate now is W, which we will do using sizing charts.

Testbench Schematic:

Using **W/L = 10u/0.5u** and **V_{DS} = 1.5 V** NMOS only since we aren't using PMOS in this Lab

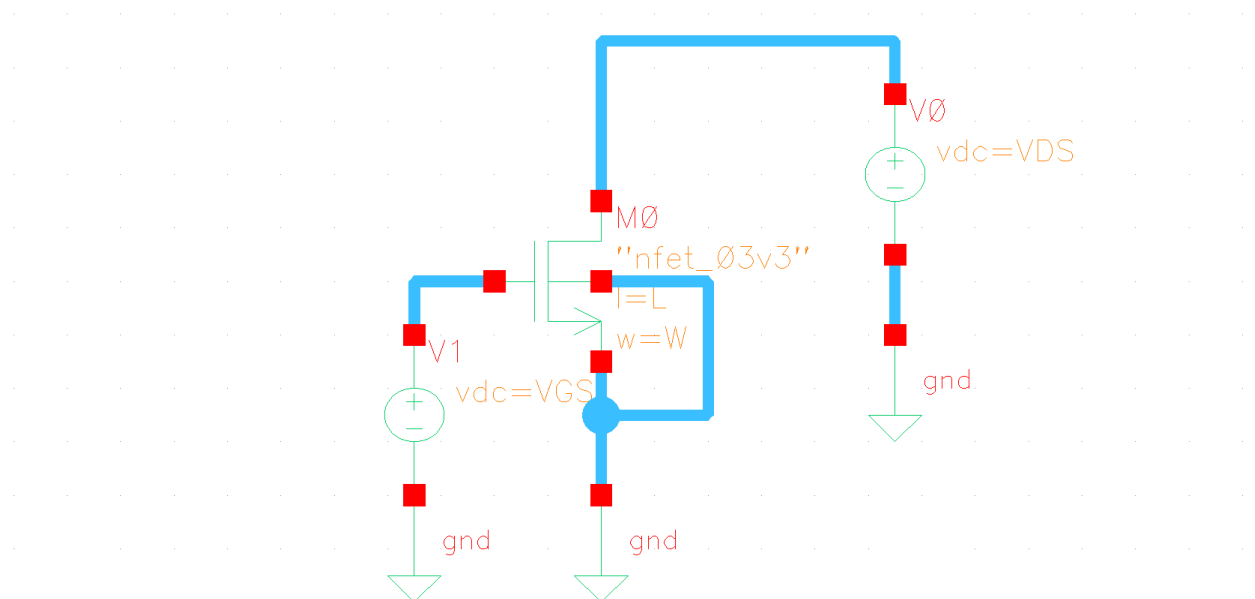


Figure 1 Sizing Testbench Schematic

Sweeping VGS from 0:10mV:(Vth + 0.4):

I ran a simple DC Op once to determine the value of V_{th}

$$V_{th} = 712.3m$$

$$\text{Sweep Range} \rightarrow 0: 10mV: 1.1123V$$

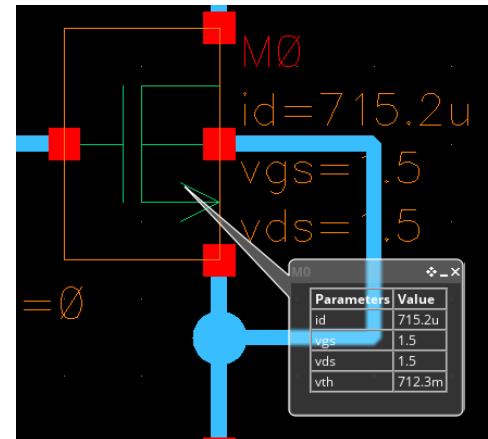


Figure 2 Value of V_{th} from simulation

V^* and V_{ov} Overlaid vs V_{GS} :

V_{ov}	expr	$(v("M0:vgs" ?result "dc") - v("M0:vth" ?result "dc"))$
V^*	expr	$((2 * \text{getData}("M0:id" ?result "dc")) / \text{getData}("M0:gm" ?result "dc"))$

Figure 3 Output Setup and Expressions for V_{ov} and V^*

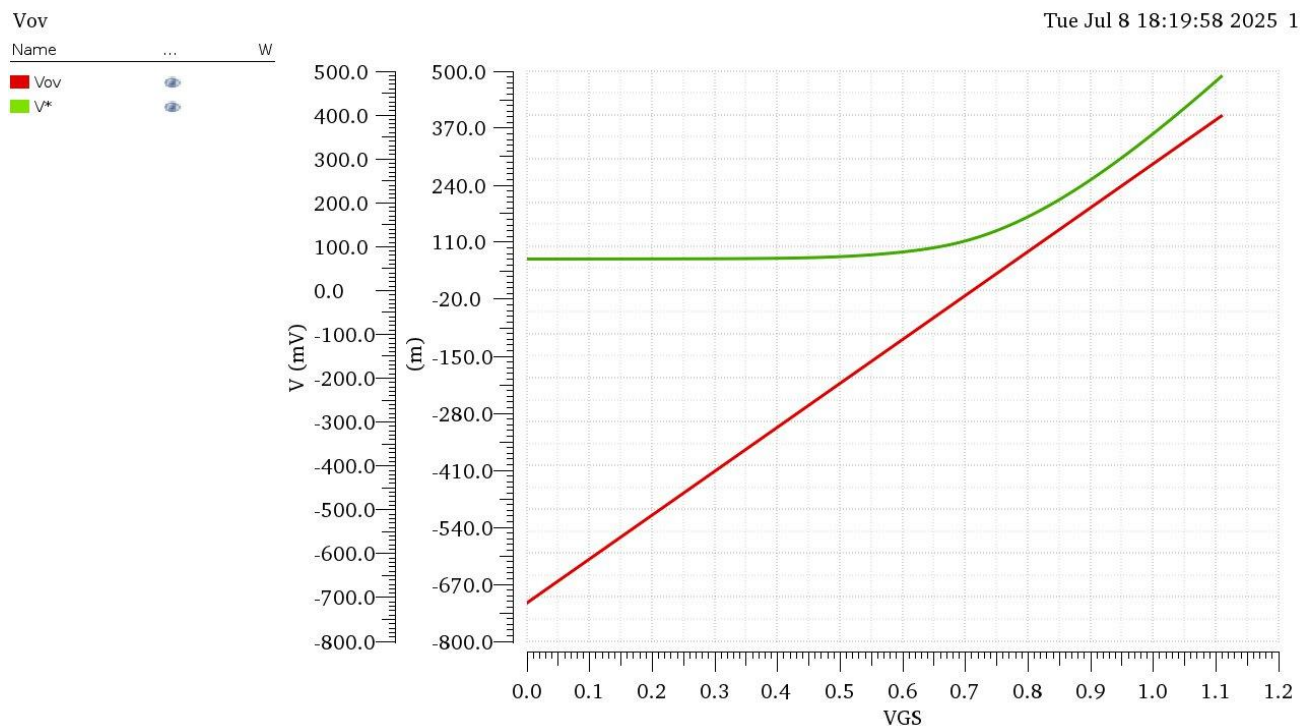



Figure 4 V_{ov} and V^* vs V_{GS} NMOS

Comment: V_{ov} and V^* are relatively close in value to each other at the region of moderate inversion meaning the square law is relatively valid there. But for Deep Strong inversion (Large V_{ov}) or weak inversion, the behavior is quite far from the square law.

Locating V_Q^* and V_{GSQ} , V_{ovQ} :

Vov

Tue Jul 8 18:19:58 2025 1

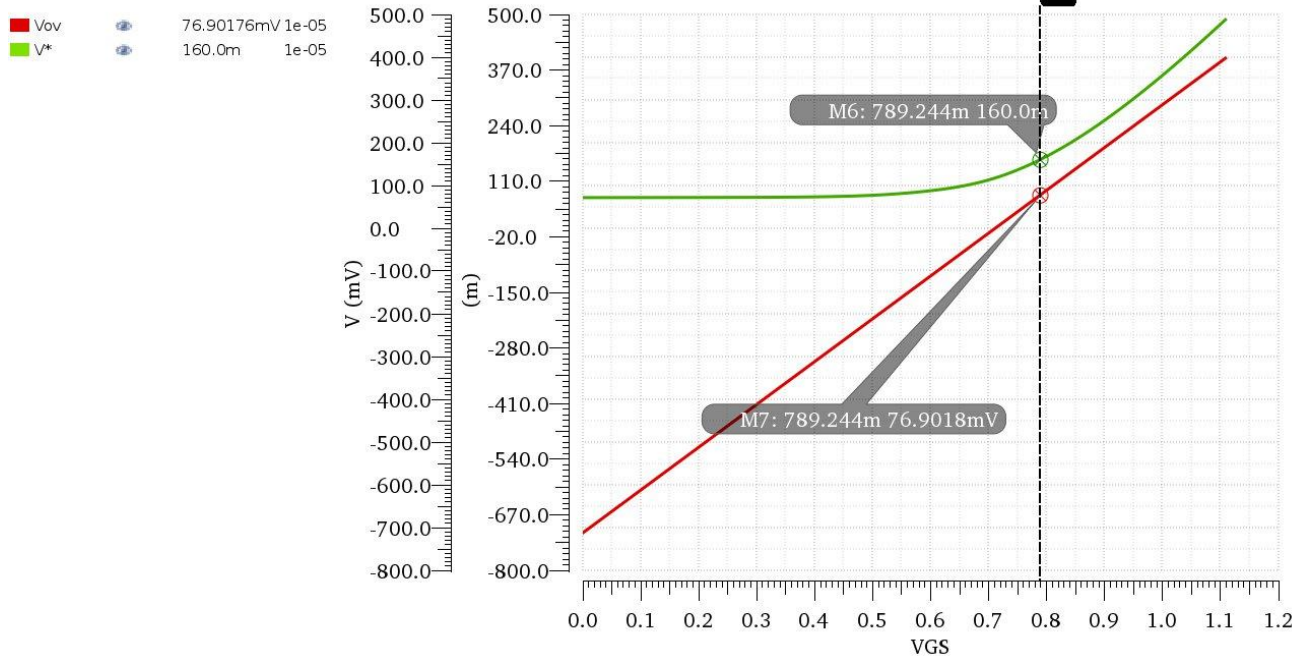
Figure 5 V_Q^* , V_{ovQ} and V_{GSQ} NMOS

$$@V_Q^* = 160mV, \quad V_{ovQ} = 76.902mV, \quad V_{GSQ} = 789.244mV$$

Plotting I_D , g_m , g_{ds} vs V_{GS} :

DC Analysis `dc`: VGS = (0 -> 1.11234)

Tue Jul 8 19:08:13 2025 1

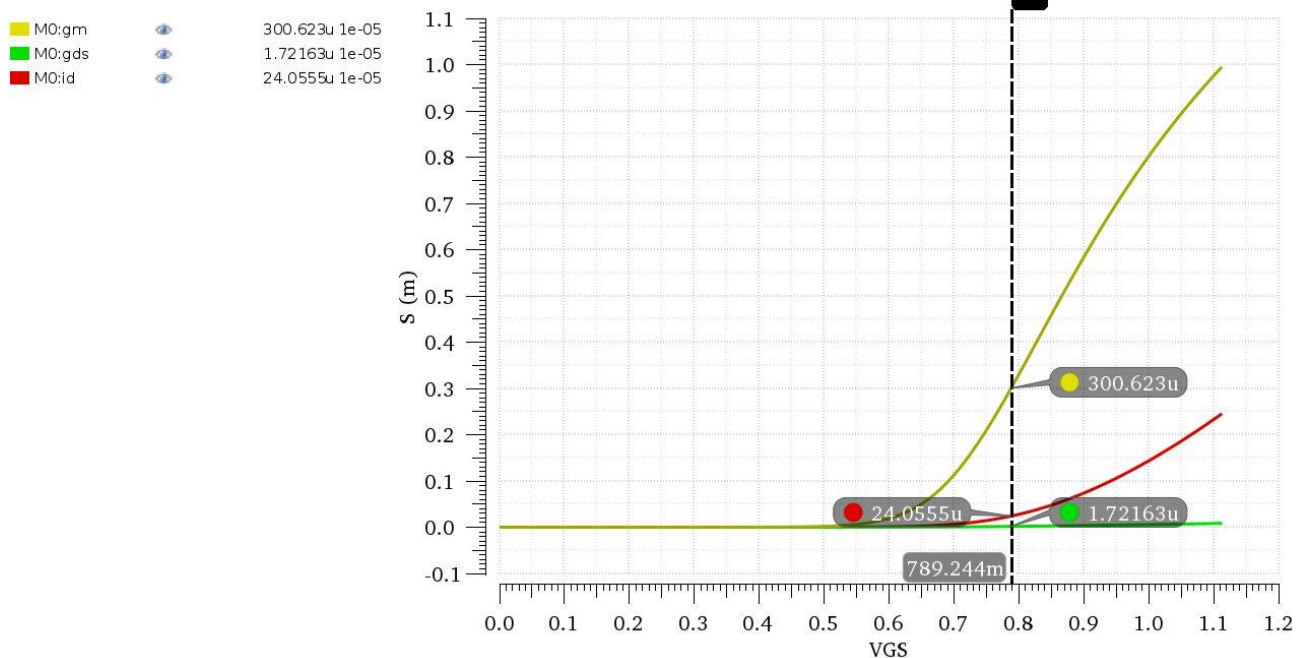Figure 6 I_D , g_m , g_{ds} vs V_{GS} and their corresponding values at V_{GSQ}

IDx	24.0555 uA
gmX	300.523 uS
gdsx	1.72163 uS

Getting the Value of W:

These Values were Calculated at $W = 10\mu\text{m}$, to get the actual value of W for the design we can simply do cross multiplication since I_d is directly proportional to W regardless square law is valid or no.

W	ID
$10\mu\text{m}$	$I_{DX} @ V_{Q*}$ (from the chart)
?	$I_{DQ} = 10\mu\text{A}$ (from the specs)

$$W = W * \frac{I_{DQ}}{I_{DX}} = \frac{10\mu * 10\mu}{24.0555\mu} = \mathbf{4.157\mu\text{m}}$$

Calculating the remaining Design parameters:

Using cross-multiplication we can get the values of gm_Q and gds_Q as follows...

W	gm	gds
$10\mu\text{m}$	$gm_X = 300.523 \text{ uS}$	$gds_X = 1.72163 \text{ uS}$
$4.157\mu\text{m}$	gm_Q	gds_Q

$$gm_Q = \frac{4.157\mu * 300.523\mu}{10\mu} \approx \mathbf{124.93 \text{ uS}} \quad , \quad gds_Q = \frac{4.157\mu * 1.72163\mu}{10\mu} = \mathbf{0.7157\mu\text{S}}$$

$$r_o = \frac{1}{gds} = \frac{1}{0.7157\mu\text{S}} = \mathbf{1.397\text{M}\Omega}$$

Final Parameter List:

Supply	3 V
V*	160 mV
ID	10 uA
W	4.157 um
L	0.5 um
gm	124.93 mS
gds	0.7157 uS
ro	1.397 MΩ
Vgs	789.244 mV

Part 2: Cascode for Gain

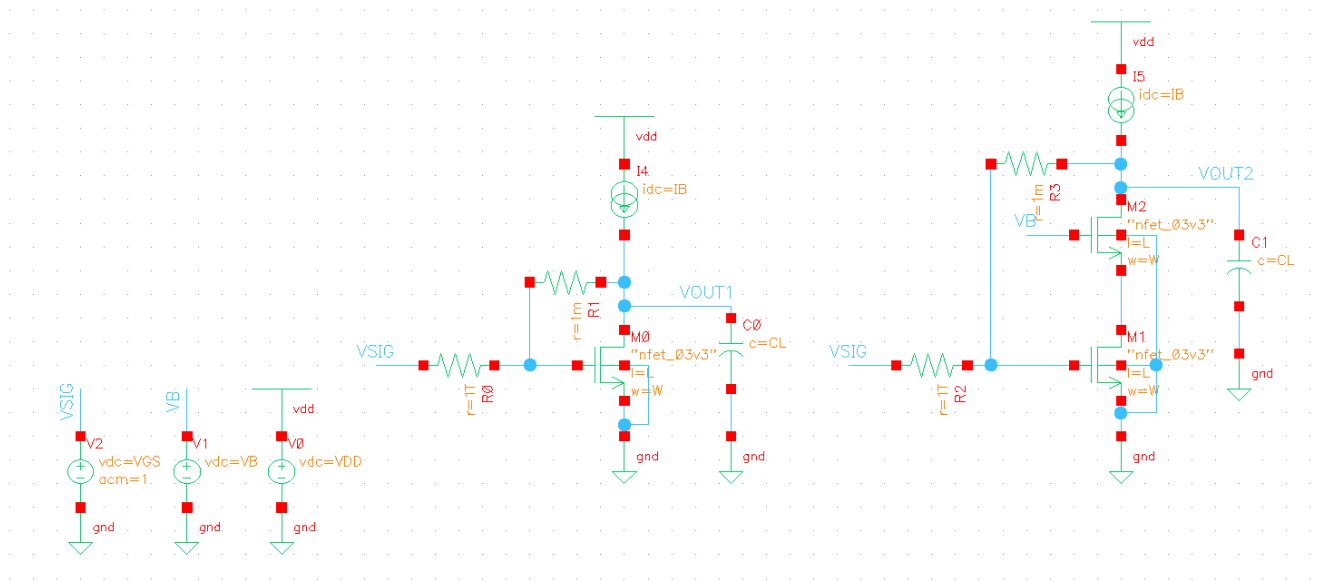


Figure 7 CS Amplifier and Cascode Amplifier

Finding V_B :

V_{ds} of should be $V_{DS} \approx V^* + 100mV \approx \mathbf{260mV}$

DC Analysis `dc`: $VB = (0 \rightarrow 3)$

Name	...	IB
M1: vds		1e-05

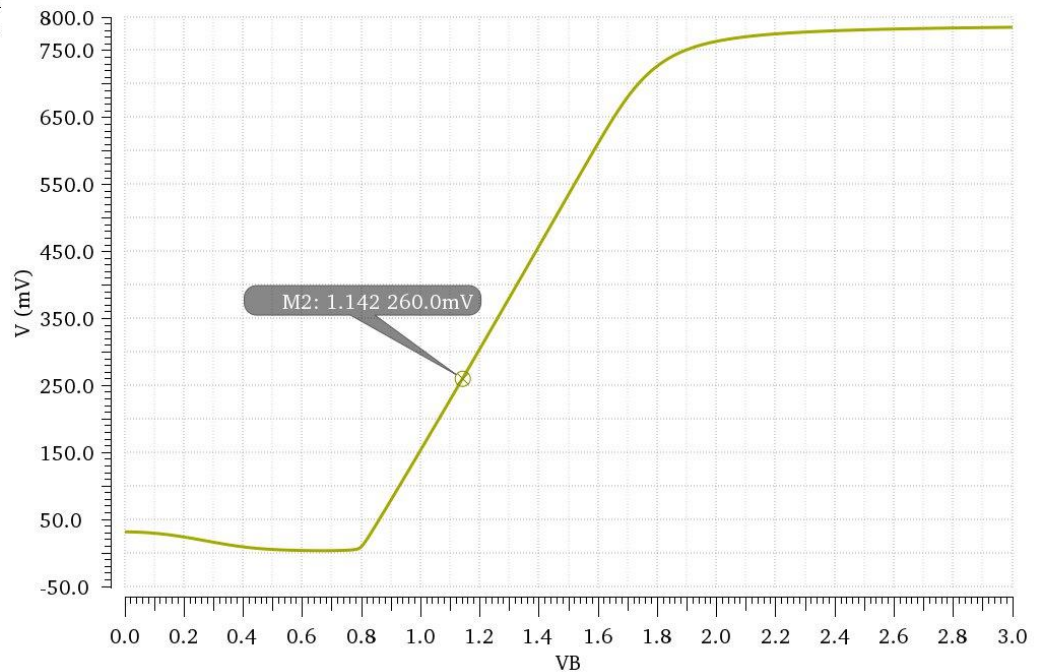


Figure 8 V_{DS} of $M1$ vs V_B

Ideal value of $V_B = \mathbf{1.142V}$

DC Operating Point:

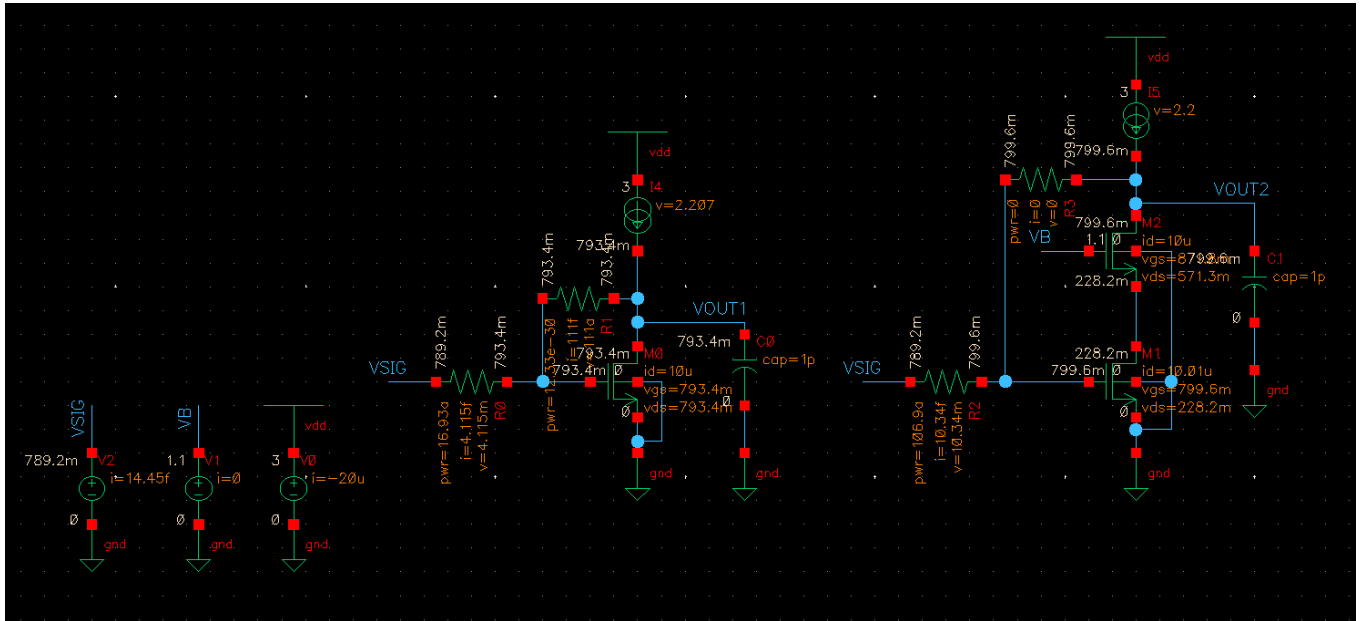


Figure 9 DC Voltages Annotated on Schematic

The following table holds the required DC Operating Point parameters for each transistor where: M0 is the CS Amplifier, M1 is Cascode Bottom Transistor, M2 Cascode Top Transistor.

	M0	M1	M2
ID	10.0 uA	10.0 uA	10.01 uA
VGS	793.4 mV	798.8 mV	881.6 mV
VDS	793.4 mV	258.4 mV	540.3 mV
VTH	710.1 mV	710.8 mV	795.4 mV
VDSAT	135 mV	138.1 mV	138.6 mV
gm	124.8 uS	122.3 uS	124.2 uS
gds	886.7 nS	2.61 uS	1.09 uS
gmb	44.68 uS	43.81 uS	38.68 uS
Cdb	544.6 aF	565.3 aF	477.9 aF
Cgd	776.7 aF	847.1 aF	823.9 aF
Cgs	4.33 fF	4.42 fF	4.4 fF
Csb	815.8 aF	834.1 aF	714.8 aF
Region	2	2	2

- **Check that all transistors operate in saturation.**

They all operate in saturation.

- **Do all transistors have the same v_{th} ? Why?**

M0 and M1 have the same V_{TH} as they have the same V_{SB} , but M2 has a higher V_{TH} due to the higher voltage seen at its source.

- **What is the relation (\ll , $<$, $=$, $>$, \gg) between g_m and g_{ds} ?**

$g_m \gg$ (Much Greater Than) g_{ds}

- **What is the relation (\ll , $<$, $=$, $>$, \gg) between g_m and g_{mb} ?**

$g_m >$ (Greater Than) g_{mb}

- **What is the relation (\ll , $<$, $=$, $>$, \gg) between c_{gs} and c_{gd} ?**

$C_{gs} \gg$ (Much Greater Than) C_{gd}

- **What is the relation (\ll , $<$, $=$, $>$, \gg) between c_{sb} and c_{db} ?**

$C_{sb} >$ (Greater Than) c_{db}

AC Analysis:

CS Bode Plot	expr	dB20(VF("/VOUT1"))
CS Gain dB	expr	ymax(dB20(VF("/VOUT1")))
CS Gain	expr	ymax(mag(VF("/VOUT1")))
CS BW	expr	bandwidth(VF("/VOUT1") 3 "low")
CS GBW	expr	gainBwProd(VF("/VOUT1"))
Cascode Bode Plot	expr	dB20(VF("/VOUT2"))
Cascode Gain dB	expr	ymax(dB20(VF("/VOUT2")))
Cascode Gain	expr	ymax(mag(VF("/VOUT2")))
Cascode BW	expr	bandwidth(VF("/VOUT2") 3 "low")
Cascode GBW	expr	gainBwProd(VF("/VOUT2"))

Figure 10 AC Output Setup

Outputs:

Cascode Bode Plot

Wed Jul 9 08:50:09 2025 1

Name	...	IB
Cascode Bode Plot		1e-05
CS Bode Plot		1e-05

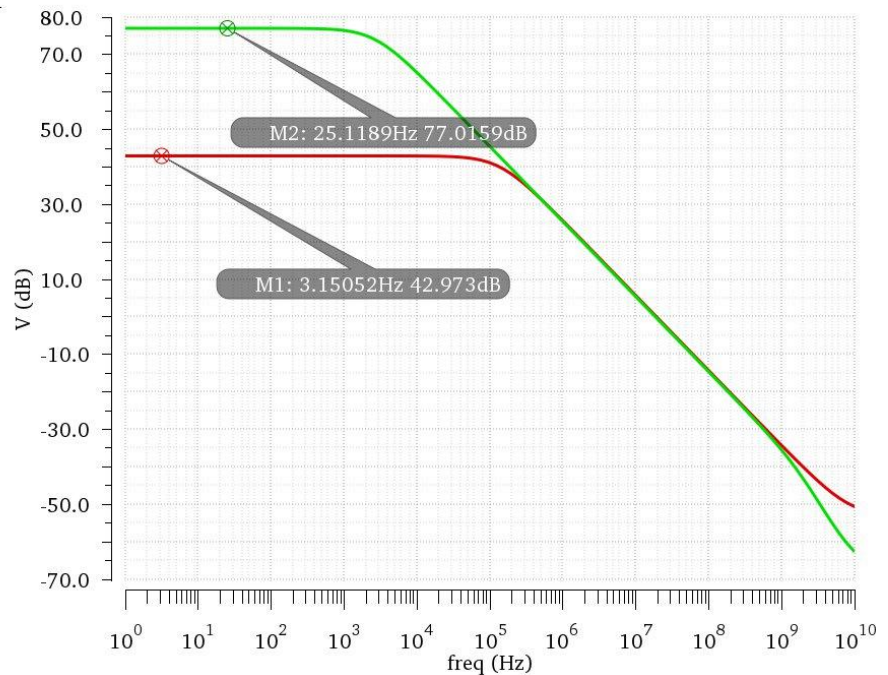


Figure 11 Bode Plots of both CS and Cascode Amplifiers

Cascode Bode Plot

Wed Jul 9 08:50:09 2025 1

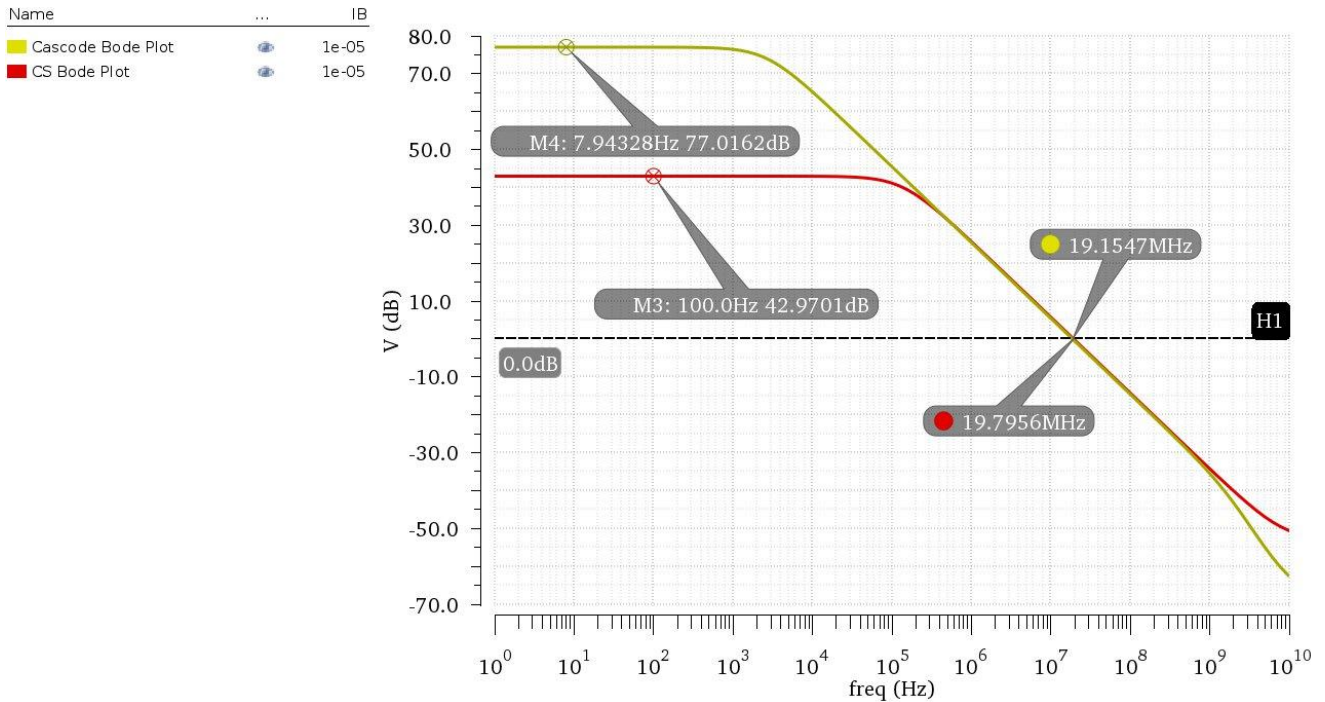


Figure 12 Gain and UGF Highlighted on Bode Plot

All Results:

	CS	Cascode
Gain (dB)	42.97	77.02
Gain	140.8	7.09 K
BW	140.6 KHz	2.69 KHz
GBW	19.84 MHz	19.14 MHz
UGF	19.7956 MHz	19.1547 MHz

Hand Analysis:

CS Amplifier:

$$DC\ Gain = |A_v| = gm * ro = \frac{gm}{g_{ds}} = \frac{124.8\mu}{886.7n} \approx \mathbf{140.75}$$

$$Gain\ in\ dB = 20\text{Log}(A_v) = 20\text{Log}(140.75) = \mathbf{42.97dB}$$

Bandwidth (Neglecting Parasitic Capacitances and current source resistance):

$$F_P = \frac{1}{\tau * 2\pi} = \frac{1}{2\pi * ro * C_L} = \frac{g_{ds}}{2\pi * C_L} = \frac{886.7n}{2\pi * 1p} = \mathbf{141.122\ KHz}$$

$$GBW = Gain * BW = 140.75 * 141.122K = \mathbf{19.863MHz}$$

$$Since\ this\ is\ a\ Single\ Pole\ System: \quad UGF = GBW = \mathbf{19.863MHz}$$

Cascode Amplifier:

$$R_{out} \approx r_{o2}(g_{m2} + g_{mb2})r_{o1} = \frac{g_{m2} + g_{mb2}}{g_{ds1} * g_{ds2}} = \frac{124.2\mu + 38.68\mu}{2.61\mu * 1.09\mu} = \mathbf{57.253M\Omega}$$

$$DC\ Gain = |A_v| = G_m * R_{out} = g_{m1} * R_{out} = 122.3\mu * 57.253M \approx \mathbf{7K}$$

$$Gain\ in\ dB = 20Log(A_v) = 20Log(7K) = \mathbf{76.9\ dB}$$

Bandwidth (Neglecting Parasitic Capacitances and current source resistance):

$$F_p = \frac{1}{\tau * 2\pi} = \frac{1}{2\pi * R_{out} * C_L} = \frac{1}{2\pi * 1p * 57.253M} = \mathbf{2.78\ KHz}$$

$$GBW = Gain * BW = 7K * 2.78K = \mathbf{19.46\ MHz}$$

Since this is a Single Pole System: $UGF = GBW = \mathbf{19.46MHz}$

Comparison of Results:

	CS		Cascode	
	Simulation	Analytic	Simulation	Analytic
Gain (dB)	42.97	42.97	77.02	76.9
Gain	140.8	140.75	7.09 K	7 K
BW	140.6 KHz	141.122 KHz	2.69 KHz	2.78 KHz
GBW	19.84 MHz	19.863 MHz	19.14 MHz	19.46 MHz
UGF	19.7956 MHz	19.863 MHz	19.1547 MHz	19.46 MHz

Comments:

- Simulation and Analytic Results are nearly identical!
- Cascode amplifier has a much greater gain than the CS Amplifier. Due to the higher output resistance
- The Bandwidth of the Cascode Amplifier is much lesser than the CS Amplifier also due to the higher output resistance.
- This results in both amplifiers having nearly identical Gain-Bandwidth-Product as well as Unity Gain Frequency.