

LAB 2

Part 1: Sizing Chart

$$V_{rd} \text{ required} = V_{DD}/2 = 1.8/2 = \mathbf{0.9v}$$

$$V^* \text{ required} = 2 \cdot V_{rd}/A_v = 2 \cdot 0.9/8 = \mathbf{0.225v}$$

$$R_d = V_{rd}/I_{dq} = 0.9/100\mu = \mathbf{9k \text{ ohm}}$$

V^* and V_{ov} overlaid vs V_{GS} :

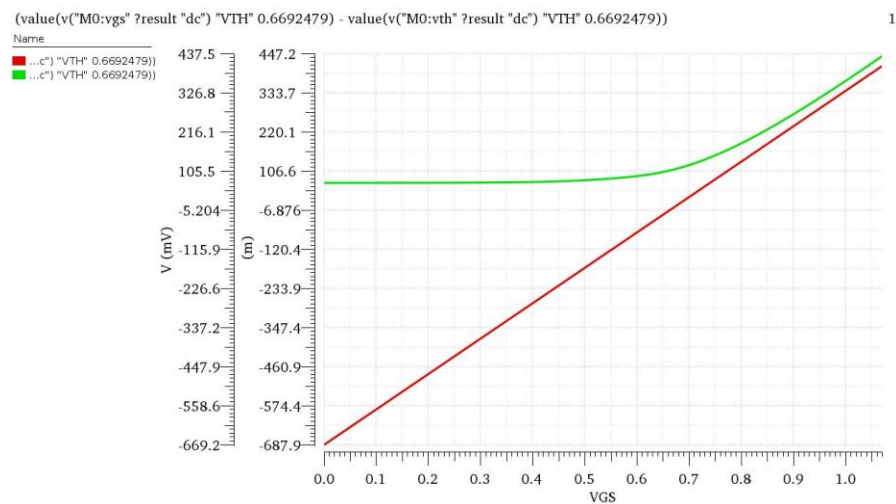


Figure 1 NMOS

(value(v("M0:vgS" ?result "dc") "VTH" 0.6692479) - value(v("M0:vth" ?result "dc") "VTH" 0.6692479))

1


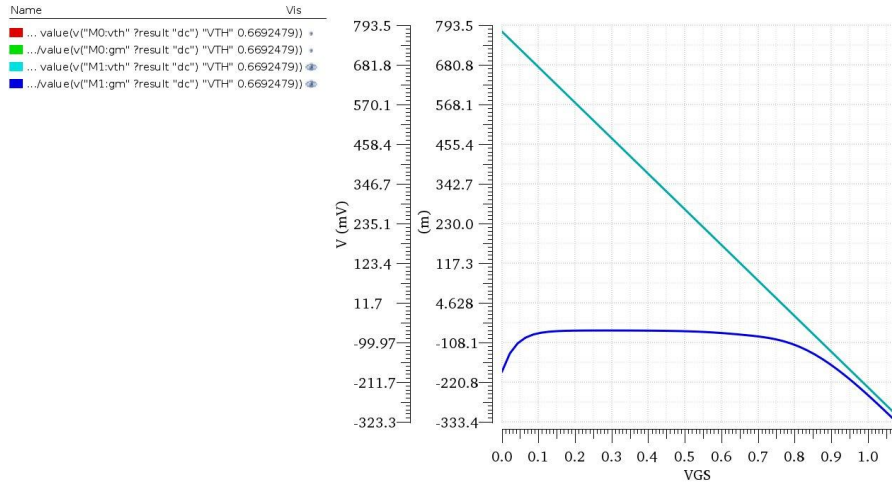


Figure 2 PMOS

V*

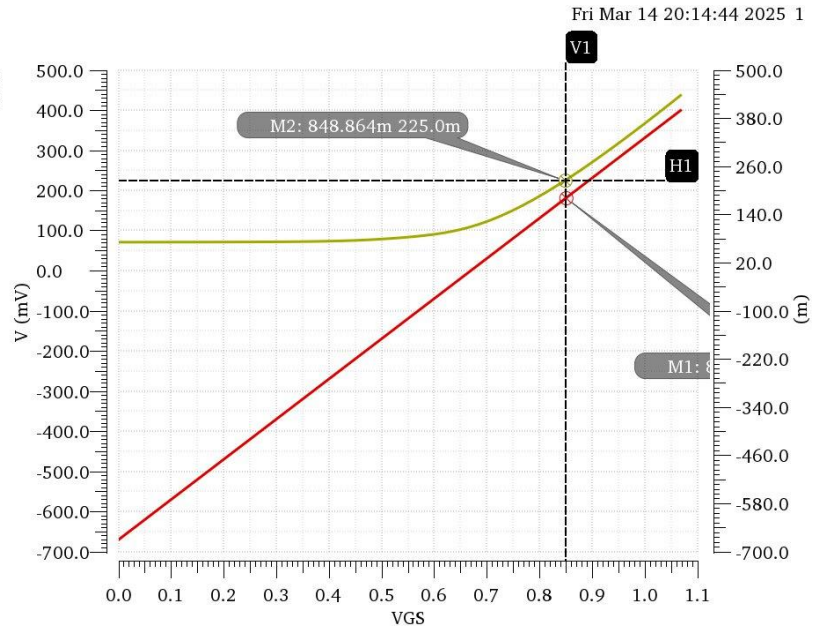Vov 180.75209mV ...92479
V* 225.9522m ...92479




Required Vgs = 848.864mV

IdX	14.0456 μ A
gmX	124.6185 μ A/V
gdsX	258.8859 nA/V

gds

Sun Mar 16 09:27:09 2025 1

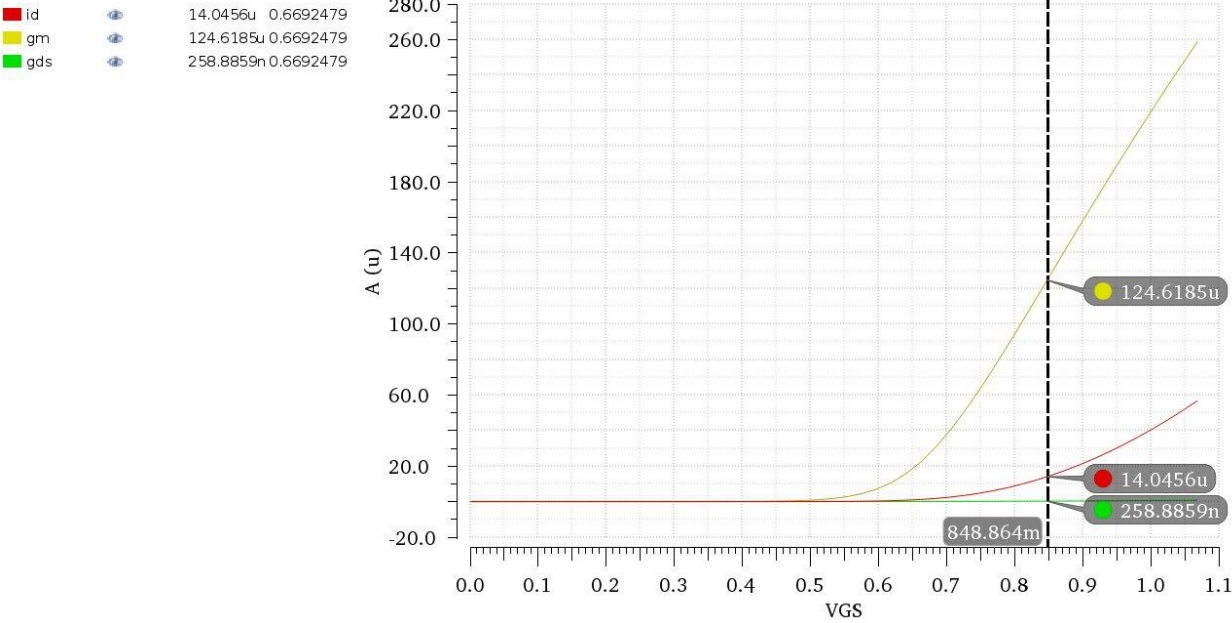

Using cross multiplication to get Wq from Idq, as well as gmq and gdsq:

Wq	71.1966um
Gmq	887.2413 μ A/v
gdsq	1843.17 nA/v

Part 2: CS Amplifier

2- DC Operating Point:

Output	Nominal
Ids	99.95e-6
Vgs	848.9e-3
Vds	900.4e-3
gm	888.8e-6
ro	542.3e3
region	2

Simulated results agree with the calculated results from the previous part.


3- r_o is significantly larger than R_d , neglecting it would be valid and won't change the results significantly.

4- Intrinsic Gain = $-g_m \cdot r_o = -888.8e-6 \cdot 542.3e3 = -482.0287$


5- Amplifier Gain = $-g_m \cdot (r_o \parallel R_d) = 7.868 < \text{intrinsic gain}$

Intrinsic gain is the highest attainable gain by the amplifier.

6-

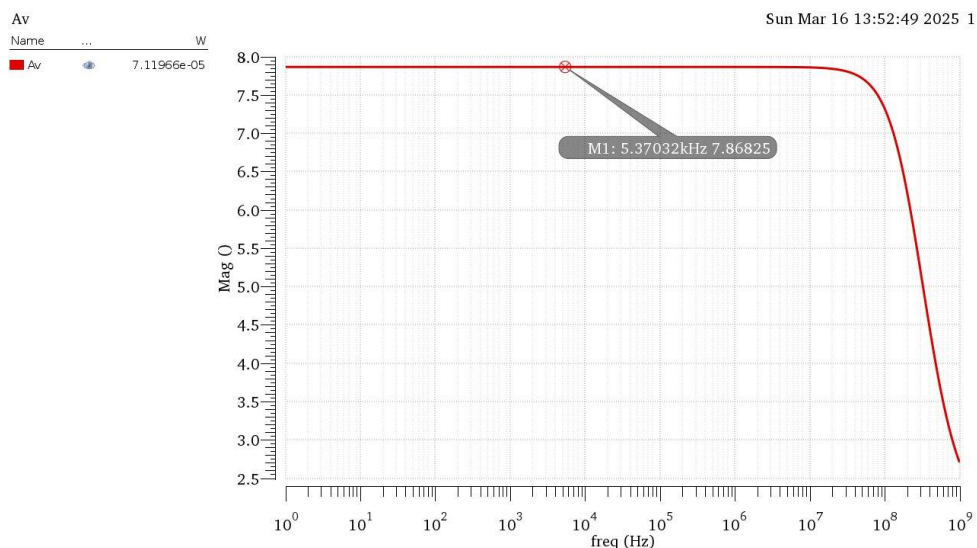


2- VOUT vs VIN:

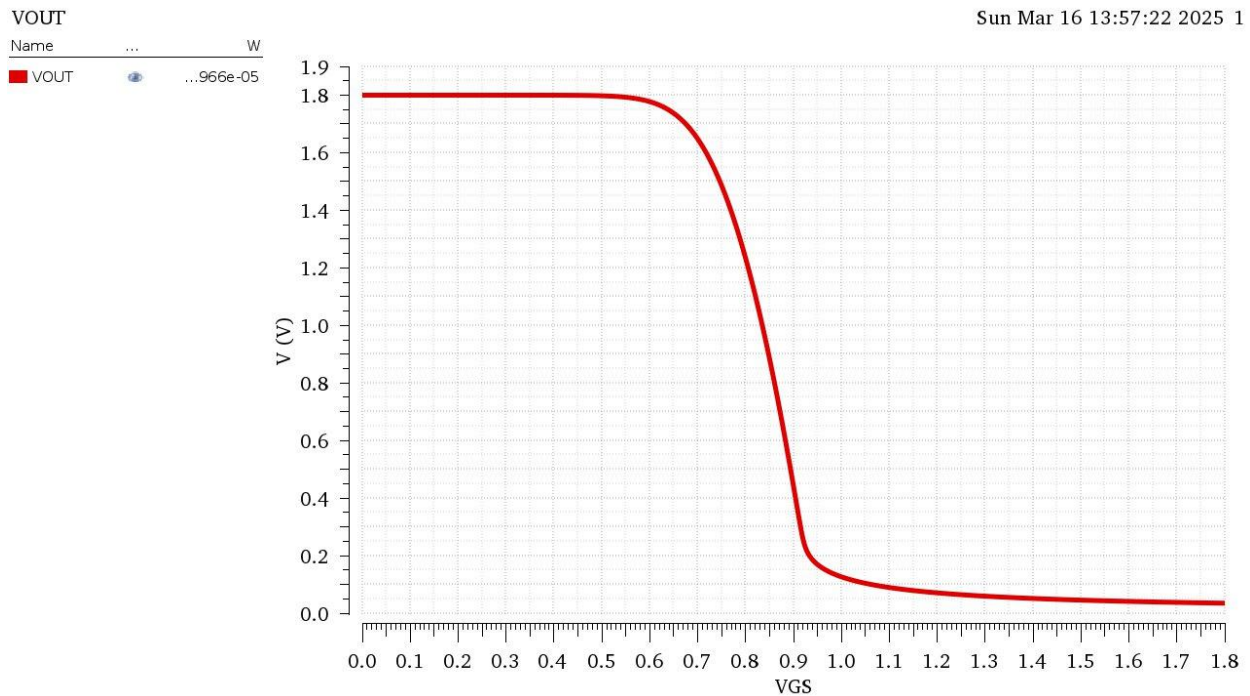

The relation is not linear as it depends on the square law, although towards the middle it seems more linear which is the best region to operate the amplifier in to get steady gain.

3-

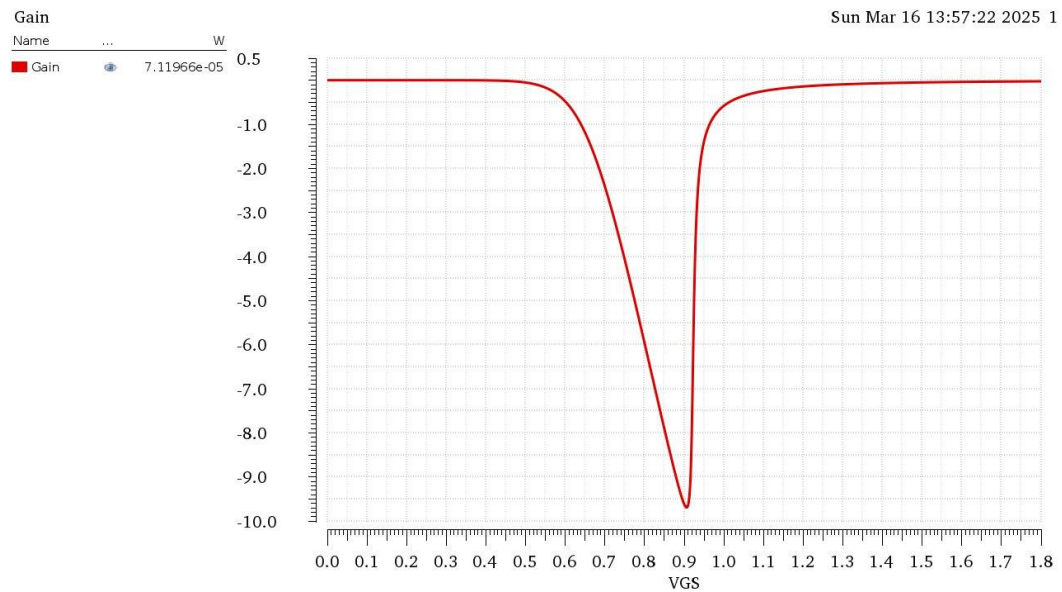


The gain is not linear as the relation between the input and gm is not linear as well but it can observe linearity around its operating point.

5-

Transient Analysis `tran': time = (0 s -> 2 ms)

1

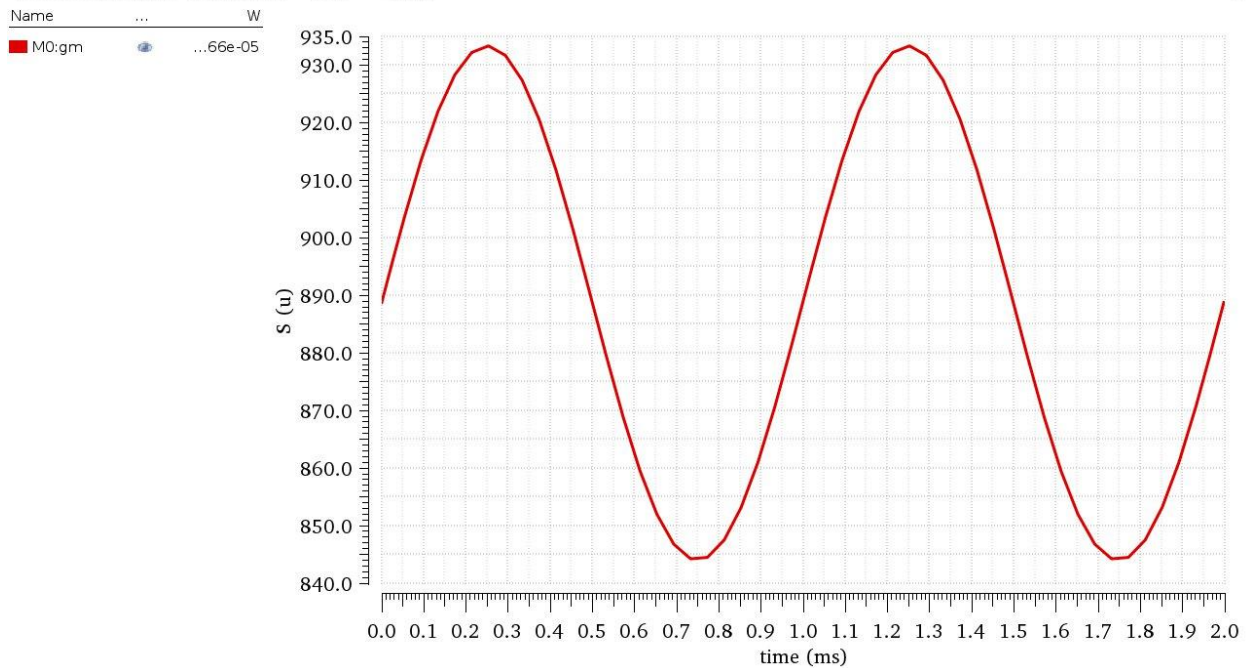

gm changes with time as it depends on the input voltage albeit the change is very small (0.1m peak to peak) and can be neglected for small signal analysis.

6- The CS Amplifier can be considered linear around its operating point as it meets the conditions.