

Analog IC Design

Lecture 11 Differential Amplifier

Dr. Hesham A. Omran

Integrated Circuits Laboratory (ICL)
Electronics and Communications Eng. Dept.
Faculty of Engineering
Ain Shams University

Outline

- ❑ Recapping previous key results
- ❑ Single-ended (SE) vs differential operation
- ❑ Pseudo differential amplifier
 - Common-mode (CM) and differential analysis
- ❑ Differential amplifier (differential pair)
 - Common-mode (CM) and differential analysis
- ❑ Effect of mismatch in load and input pair
 - Common-mode rejection ratio (CMRR)
- ❑ Frequency response of differential amplifier
 - Common-mode (CM) and differential analysis

Outline

- ❑ Recapping previous key results
- ❑ Single-ended (SE) vs differential operation
- ❑ Pseudo differential amplifier
 - Common-mode (CM) and differential analysis
- ❑ Differential amplifier (differential pair)
 - Common-mode (CM) and differential analysis
- ❑ Effect of mismatch in load and input pair
 - Common-mode rejection ratio (CMRR)
- ❑ Frequency response of differential amplifier
 - Common-mode (CM) and differential analysis

MOSFET in Saturation




- ❑ The channel is pinched off if the difference between the gate and drain voltages is not sufficient to create an inversion layer

$$V_{GD} \leq V_{TH} \text{ or } V_{DS} \geq V_{ov}$$


- ❑ Square-law (long channel MOS)

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \cdot V_{ov}^2 (1 + \lambda V_{DS})$$
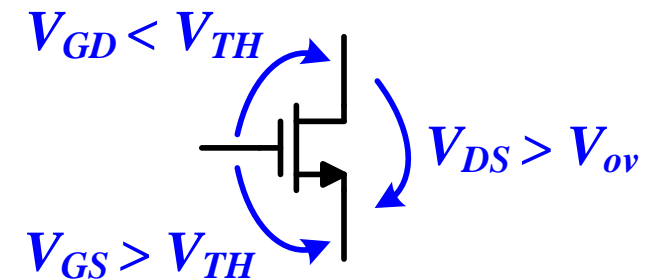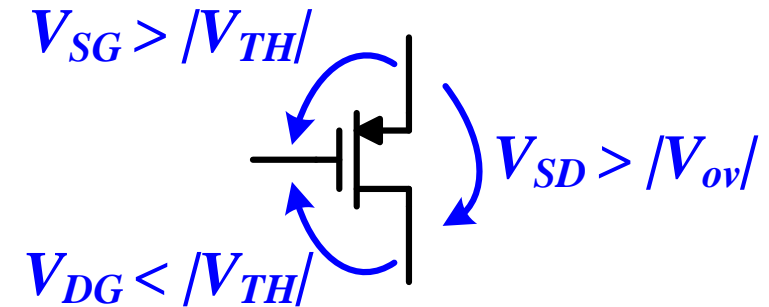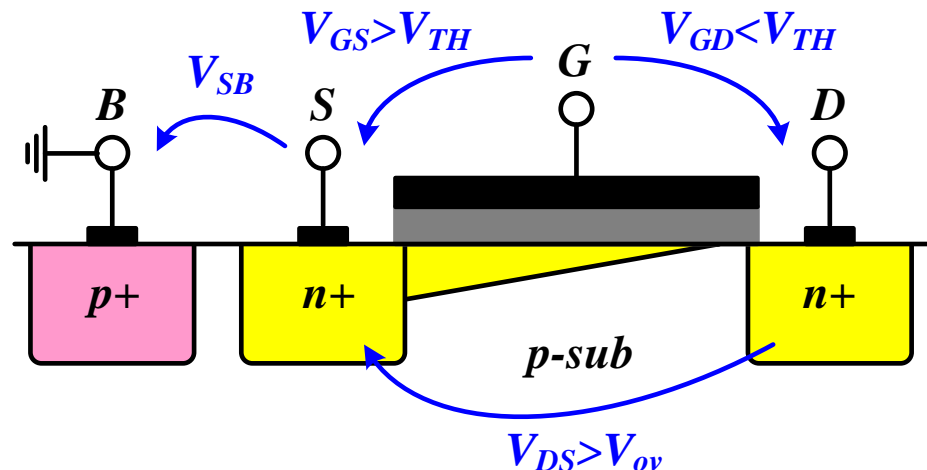
$$V_{SB} \uparrow \Rightarrow V_{TH} \uparrow$$



Regions of Operation Summary

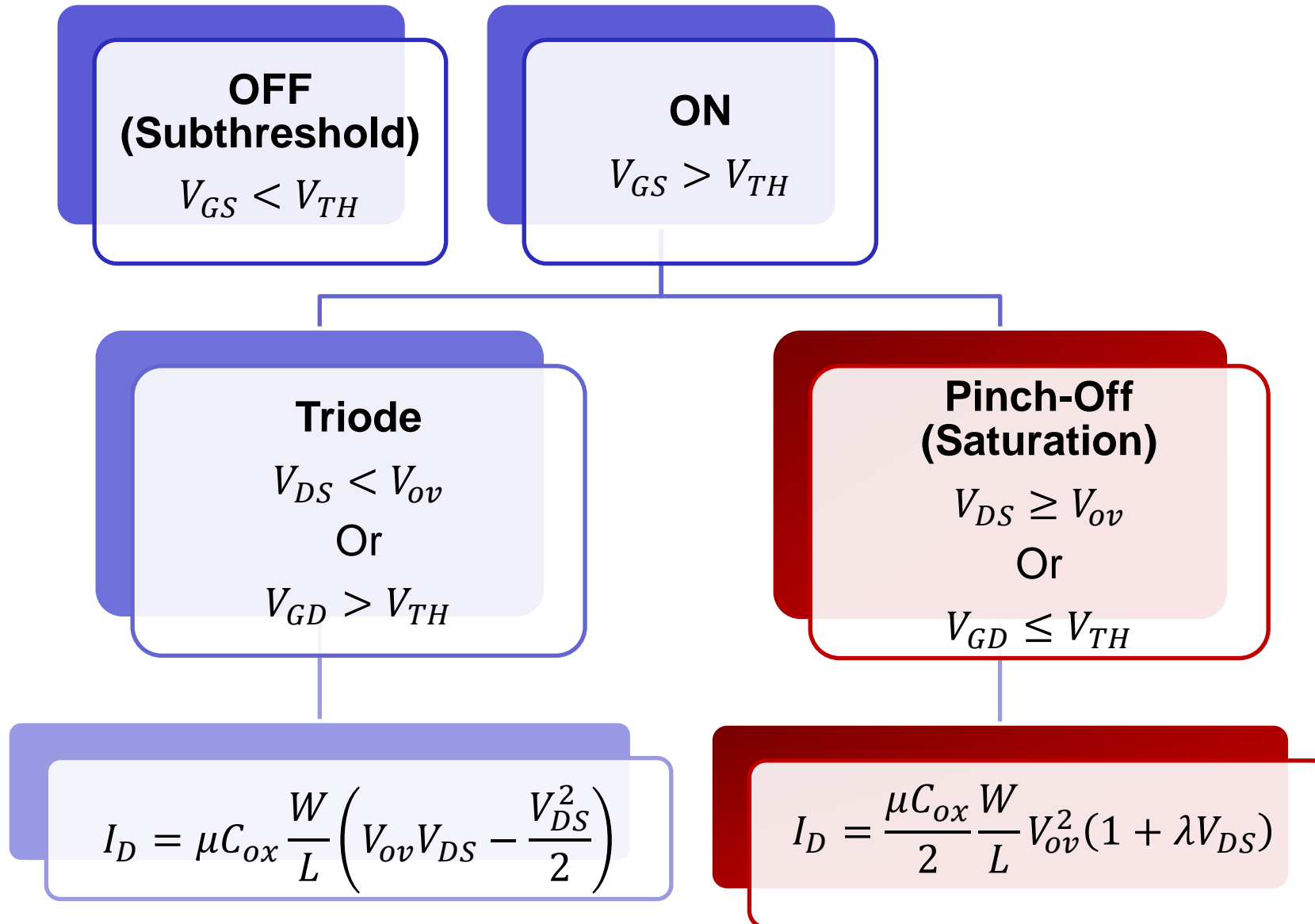

High Frequency Small Signal Model

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} V_{ov} = \sqrt{\mu C_{ox} \frac{W}{L} \cdot 2I_D} = \frac{2I_D}{V_{ov}}$$


$$g_{mb} = \eta g_m \quad \eta \approx 0.1 - 0.25$$

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{V_A}{I_D} = \frac{1}{\lambda I_D} \quad V_A \propto L \leftrightarrow \lambda \propto \frac{1}{L} \quad V_{DS} \uparrow V_A \uparrow$$


$$C_{gb} \approx 0$$

$$C_{gs} \gg C_{gd}$$




$$C_{sb} > C_{db}$$

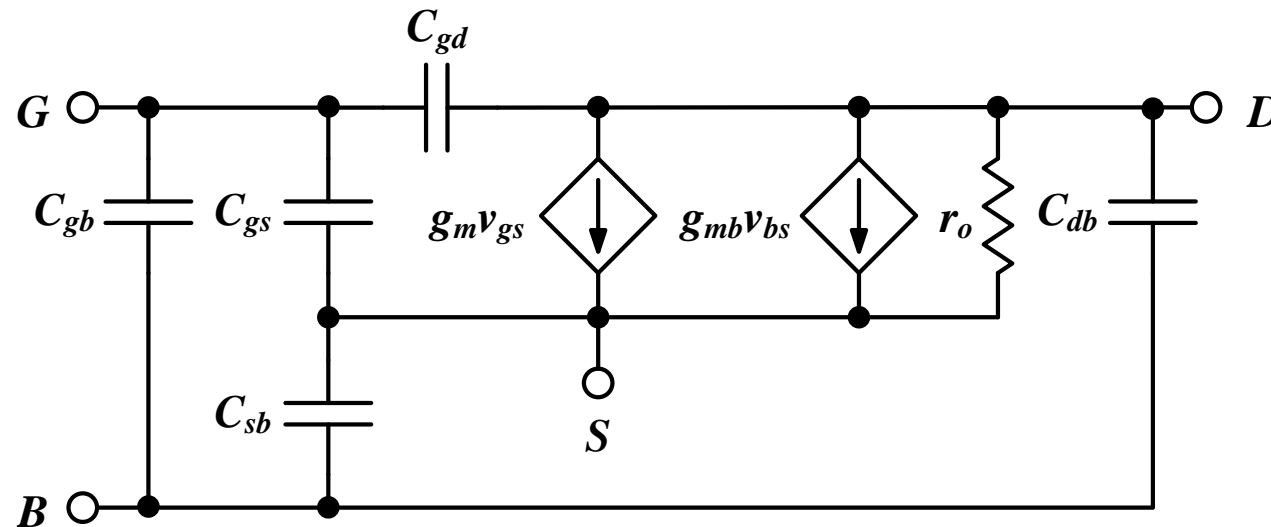

Rin/out Shortcuts Summary

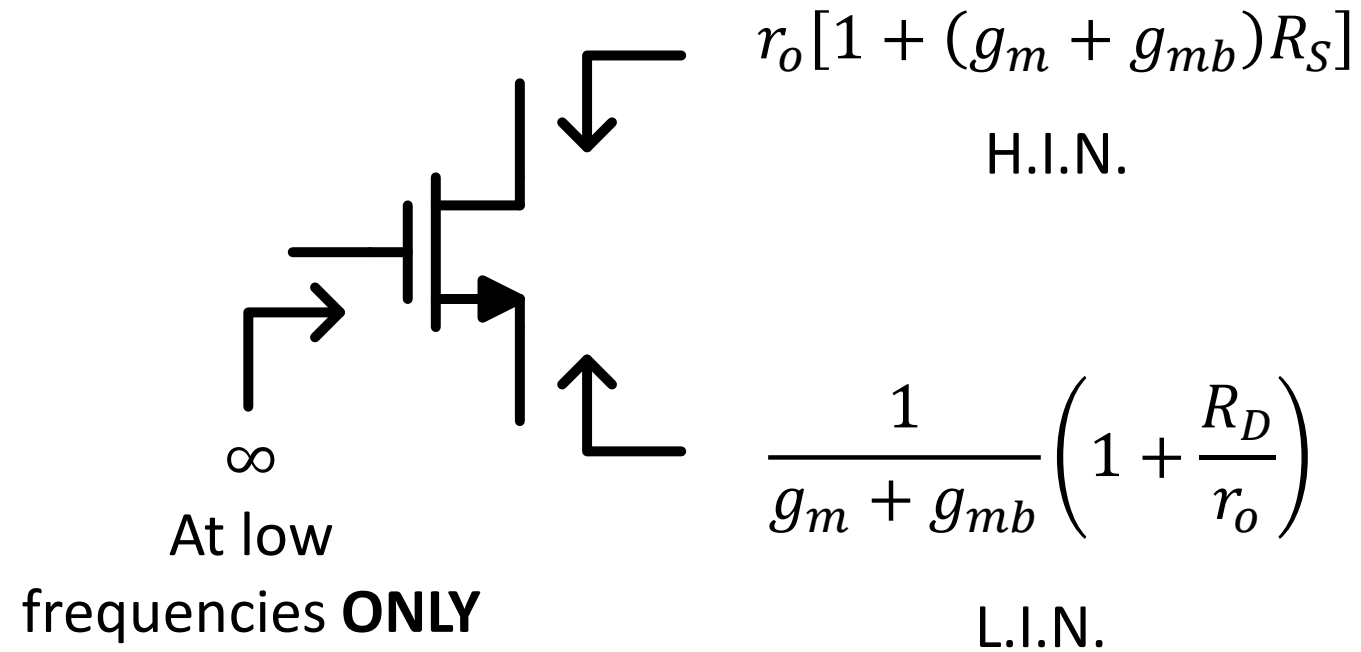

Summary of Basic Topologies

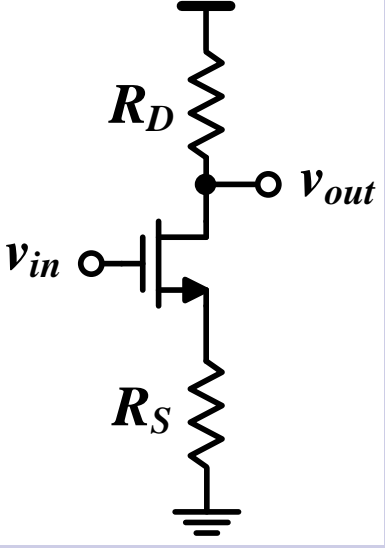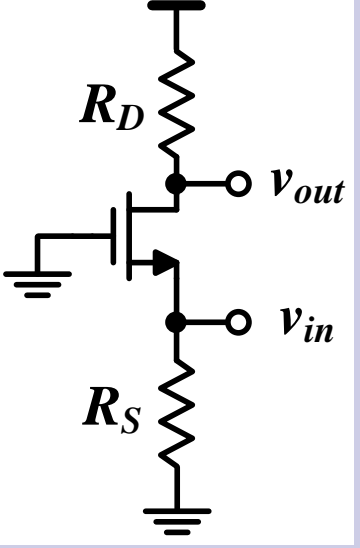
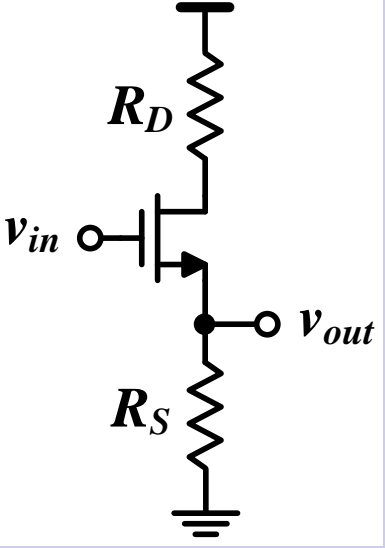
	CS	CG	CD (SF)
			
	Voltage & current amplifier	Voltage amplifier Current buffer	Voltage buffer Current amplifier
R_{in}	∞	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$	∞
R_{out}	$R_D \parallel r_o [1 + (g_m + g_{mb})R_S]$	$R_D \parallel r_o$	$R_S \parallel \frac{1}{g_m + g_{mb}} \left(1 + \frac{R_D}{r_o} \right)$
G_m	$\frac{-g_m}{1 + (g_m + g_{mb})R_S}$	$g_m + g_{mb}$	$\frac{g_m}{1 + R_D/r_o}$

Outline

- ❑ Recapping previous key results
- ❑ Single-ended (SE) vs differential operation
- ❑ Pseudo differential amplifier
 - Common-mode (CM) and differential analysis
- ❑ Differential amplifier (differential pair)
 - Common-mode (CM) and differential analysis
- ❑ Effect of mismatch in load and input pair
 - Common-mode rejection ratio (CMRR)
- ❑ Frequency response of differential amplifier
 - Common-mode (CM) and differential analysis

Have You Seen a Diff Amp Before?

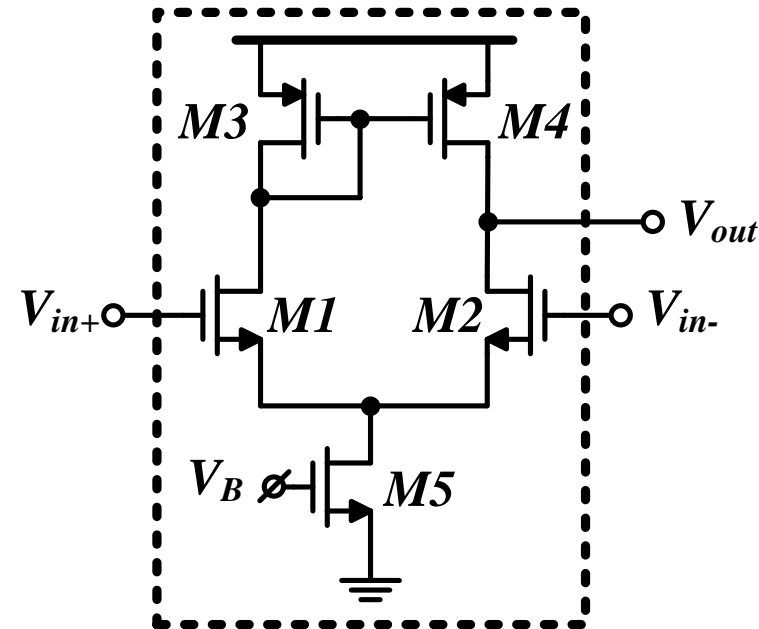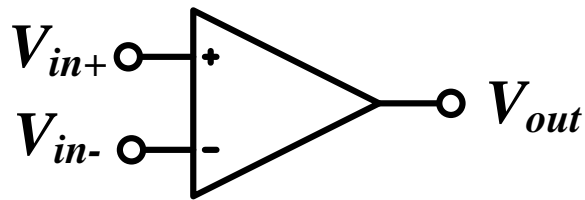- ❑ An op-amp is simply a high gain differential amplifier
 - The gain can be increased by using cascodes and multi-stage amplification
- ❑ The diff amp is a key block in many analog and RF circuits
 - DEEP understanding of diff amp is ESSENTIAL



Single-Ended (SE) vs Differential

- SE: measured with respect to a fixed potential (usually the ground)



$$V_{out,SE} = V_o \sin \omega t + V_{CM}$$

- Single-ended peak-to-peak swing is $2V_o$

- Diff: measured between two nodes that have **equal and opposite** signals around a common-mode (CM) level

$$\begin{aligned} V_{out,diff} &= V_X - V_Y \\ &= (V_o \sin \omega t + V_{CM}) - (-V_o \sin \omega t + V_{CM}) \\ &= 2V_o \sin \omega t \end{aligned}$$

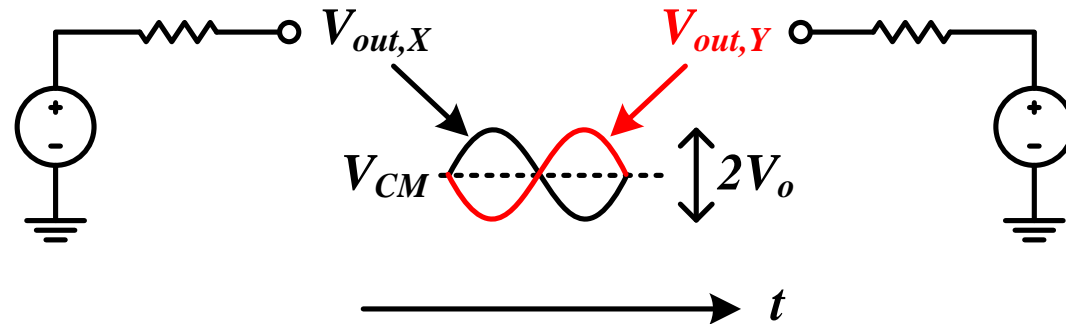
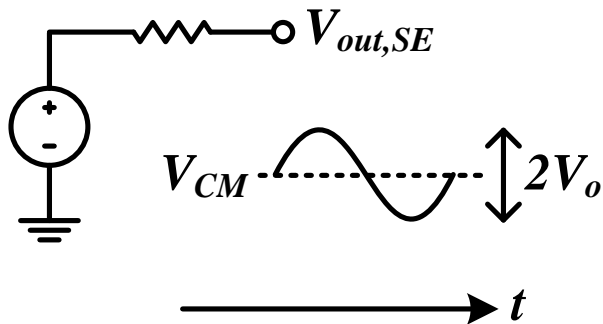
- Differential peak-to-peak swing is $4V_o$



Why Differential?

$$V_{out,SE} = V_o \sin \omega t + V_{CM} + V_{CMnoise}$$

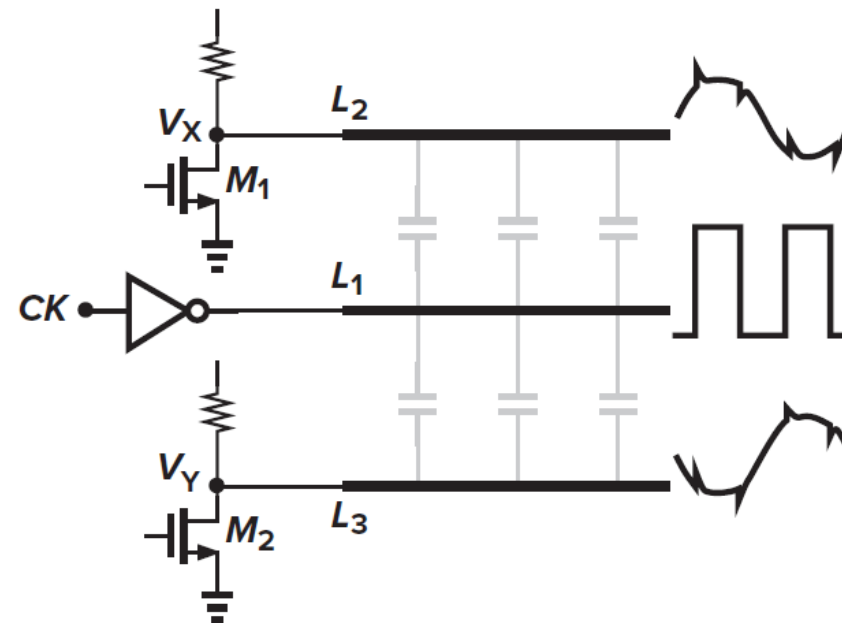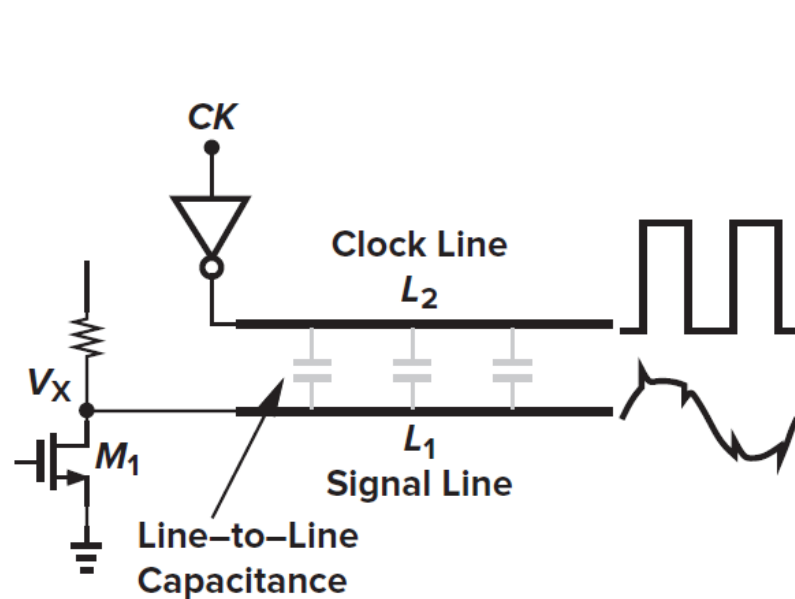
$$\begin{aligned} V_{out,diff} &= V_X - V_Y \\ &= (V_o \sin \omega t + V_{CM} + V_{CMnoise}) - (-V_o \sin \omega t + V_{CM} + V_{CMnoise}) \\ &= 2V_o \sin \omega t \end{aligned}$$



Why Differential?

$$V_{out,SE} = V_o \sin \omega t + V_{CM} + V_{CMnoise}$$
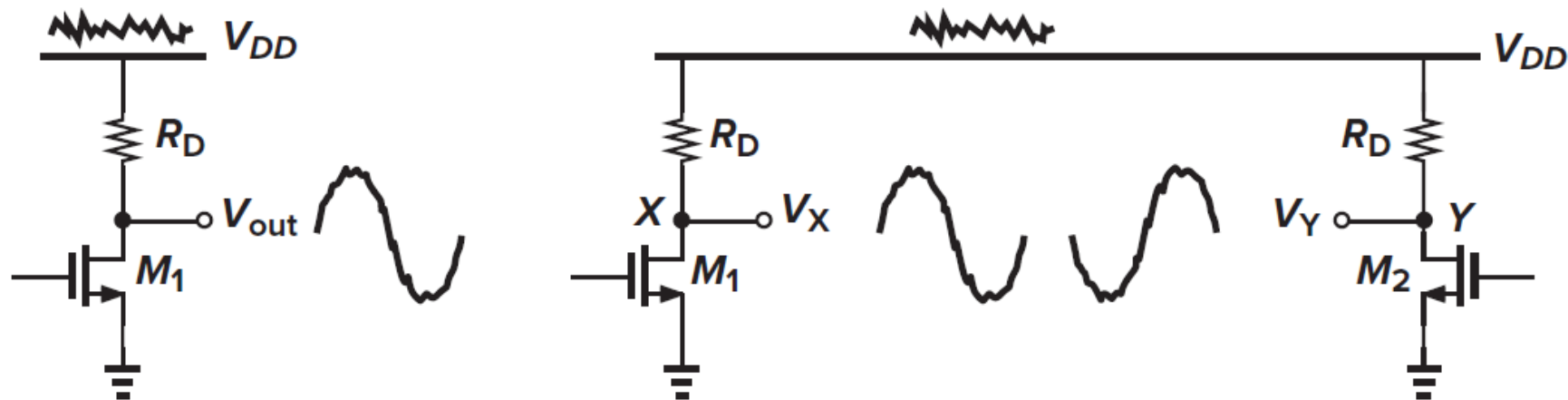
$$\begin{aligned} V_{out,diff} &= V_X - V_Y \\ &= (V_o \sin \omega t + V_{CM} + V_{CMnoise}) - (-V_o \sin \omega t + V_{CM} + V_{CMnoise}) \\ &= 2V_o \sin \omega t \end{aligned}$$



Why Differential?



Pros

- **Common-mode (CM) noise rejection**
- **Simpler biasing (no need for bypass or coupling capacitors)**
- Larger maximum signal swing
- Higher linearity



Cons

- Doubling the area
- Doubling the power consumption





The advantages of differential operation by far outweigh the disadvantages




Differential operation has become the de facto choice in today's high-performance analog and mixed-signal circuits

SE \leftrightarrow Differential

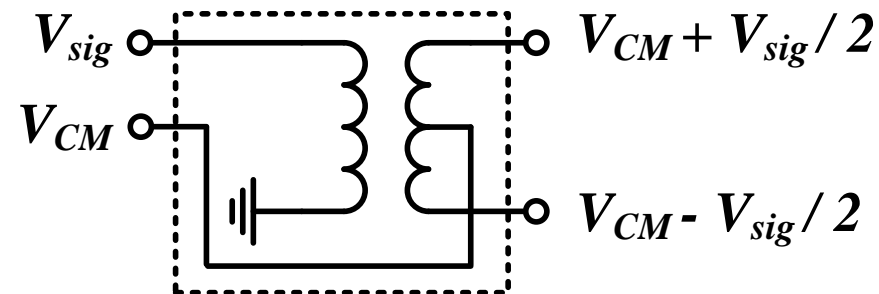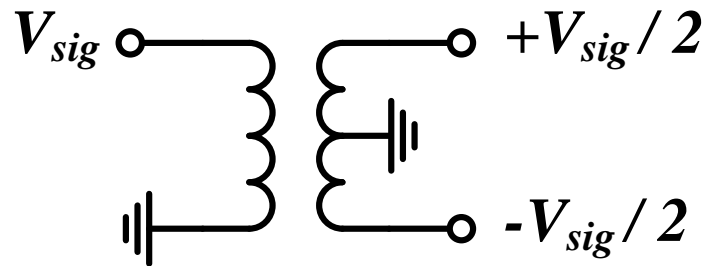
- ❑ A center-tapped transformer can be used for SE to differential conversion and vice versa.
 - Used frequently in simulation testbenches.
 - Also known as balanced-to-unbalanced conversion (balun).
 - Differential \rightarrow balanced
 - Single-ended \rightarrow unbalanced
- ❑ There are other circuits that can be used to achieve this goal.




Diff Amp with Arbitrary Inputs

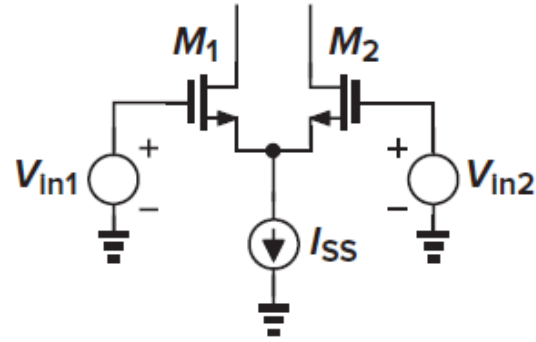


(a)

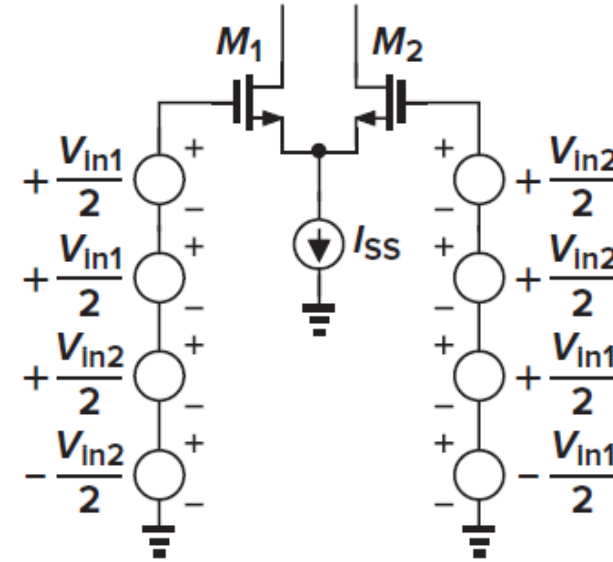

(b)

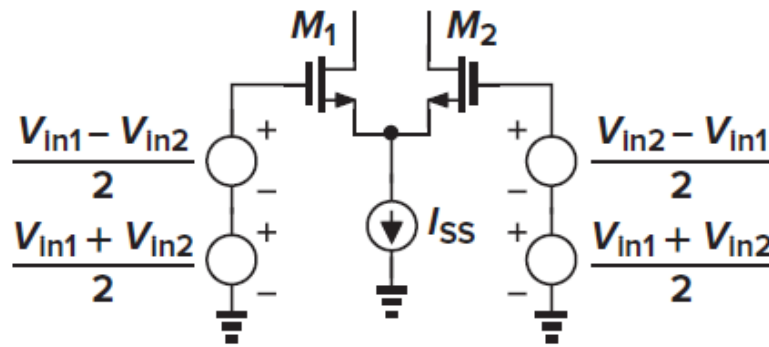

(c)

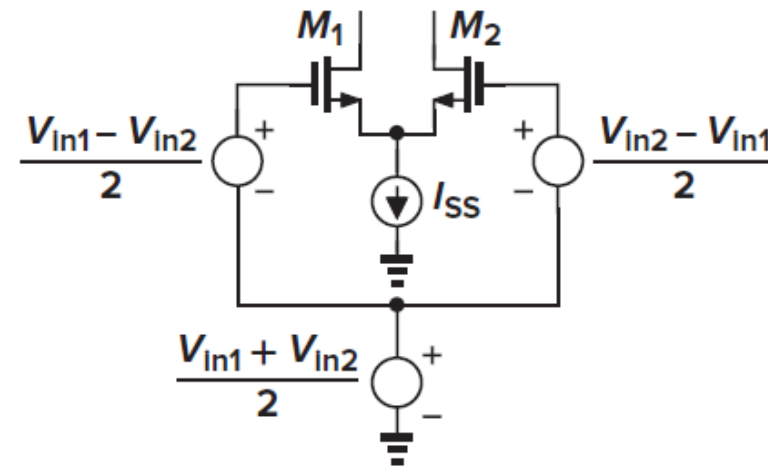



(d)

Separate CM and Diff by Superposition

$$v_{id} = v_{in1} - v_{in2}$$

$$v_{id1} = \frac{v_{id}}{2} \quad \text{and} \quad v_{id2} = -\frac{v_{id}}{2}$$
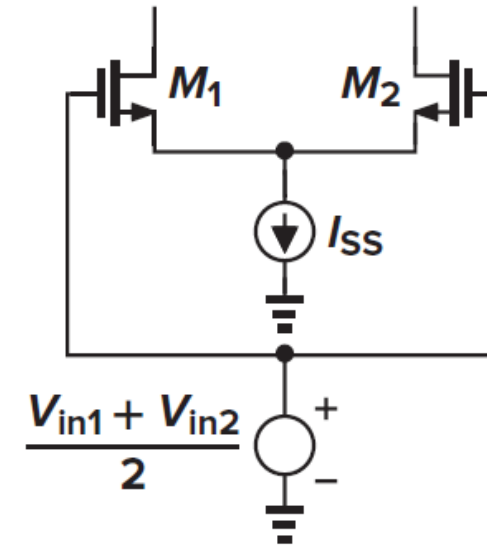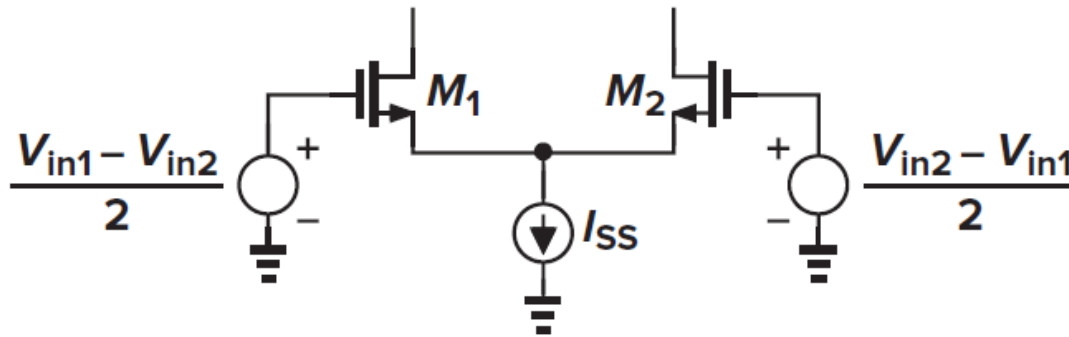
$$v_{iCM} = \frac{v_{in1} + v_{in2}}{2}$$




Outline

- ❑ Recapping previous key results
- ❑ Single-ended (SE) vs differential operation
- ❑ Pseudo differential amplifier
 - Common-mode (CM) and differential analysis
- ❑ Differential amplifier (differential pair)
 - Common-mode (CM) and differential analysis
- ❑ Effect of mismatch in load and input pair
 - Common-mode rejection ratio (CMRR)
- ❑ Frequency response of differential amplifier
 - Common-mode (CM) and differential analysis


“Pseudo” Diff Amp

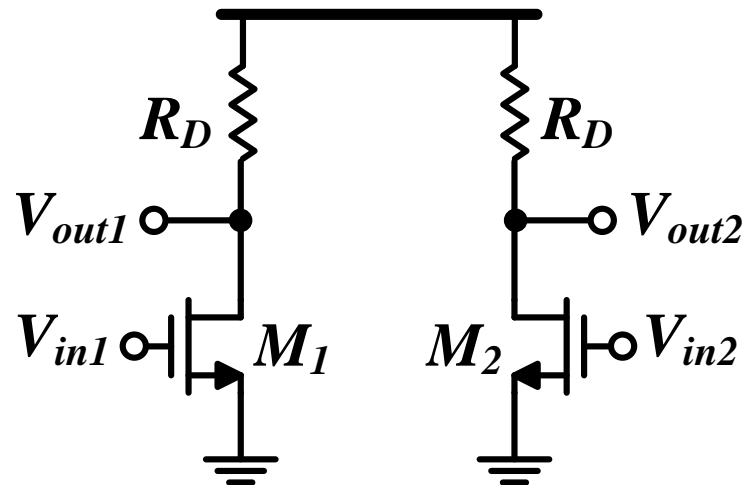- A. Small signal analysis
 - 1. Diff small signal analysis
 - 2. CM small signal analysis
- B. Large signal analysis
 - 1. Diff large signal analysis
 - 2. CM large signal analysis




A1. Diff Small Signal Analysis

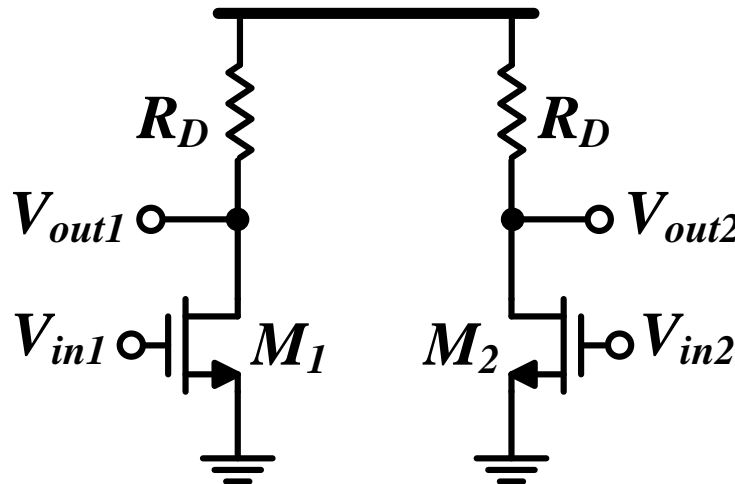- $v_{in1} = \frac{v_{id}}{2}$ and $v_{in2} = -\frac{v_{id}}{2}$
- $v_{out1} = -g_m R_D \left(\frac{v_{id}}{2} \right)$ and $v_{out2} = -g_m R_D \left(-\frac{v_{id}}{2} \right)$
- $v_{od} = v_{out1} - v_{out2} = -g_m R_D (v_{id})$
- $A_{vd} = \frac{v_{od}}{v_{id}} = -g_m R_D = \frac{v_{out1}}{v_{in1}} = \frac{v_{out2}}{v_{in2}} = A_{v,SE}$




A2. CM Small Signal Analysis

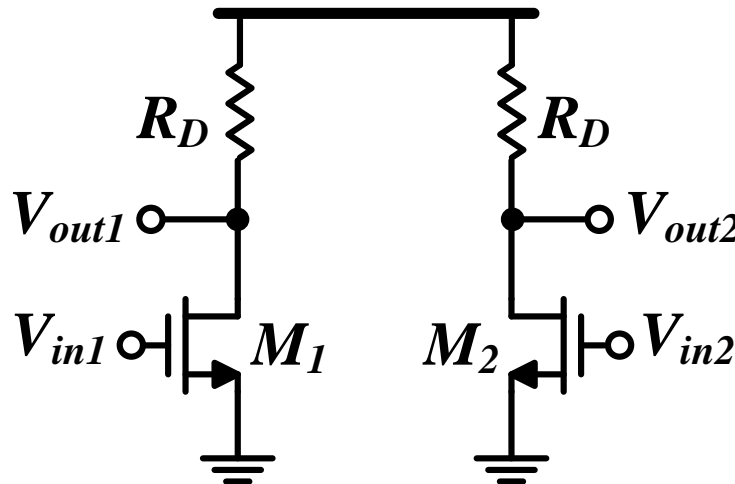- $v_{in1} = v_{iCM}$ and $v_{in2} = v_{iCM}$
- $v_{out1} = -g_m R_D (v_{iCM})$ and $v_{out2} = -g_m R_D (v_{iCM})$
- $v_{oCM} = \frac{v_{out1} + v_{out2}}{2} = -g_m R_D (v_{iCM})$
- $A_{vCM} = \frac{v_{oCM}}{v_{iCM}} = -g_m R_D = A_{vd} \rightarrow A_{vd} / A_{vCM} = 1$
- The output CM level is sensitive to the input CM level
- CM input is not “completely” rejected




B1. Diff Large Signal Analysis

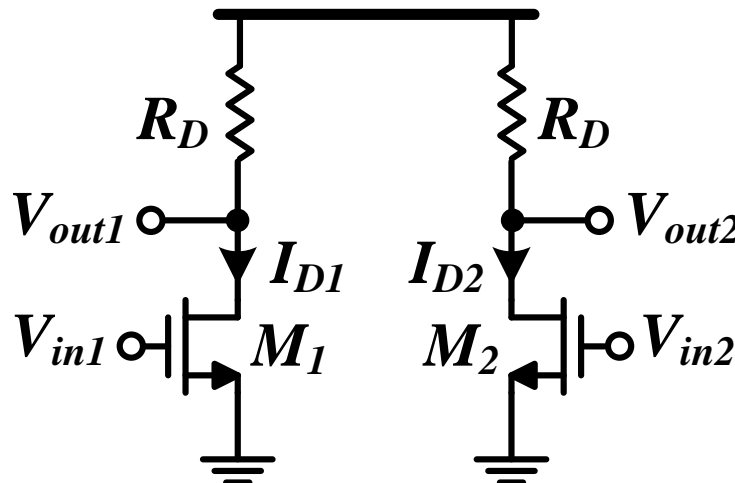- ❑ Assume large differential signal is applied
- ❑ The two sides act as two independent CS amplifiers
- ❑ Ex: $V_{in1} \uparrow$ and $V_{in2} \downarrow$
 - M2 will turn OFF: $I_{D2} = 0$
 - I_{D1} will increase following square law (expansive characteristics)
 - Eventually M1 goes out of saturation and I_{D1} saturates at $\frac{V_{DD}}{R_D}$



B2. CM Large Signal Analysis

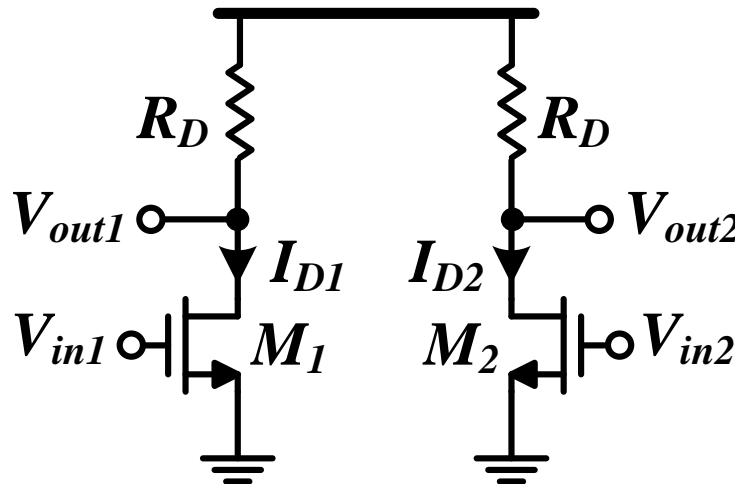- ❑ The two sides act as two independent CS amplifiers
- ❑ The transistors are biased by the input CM level
- ❑ The OP point is sensitive to the input CM level
- ❑ Ex: $V_{iCM} \uparrow = V_{in1} \uparrow = V_{in2} \uparrow$
 - I_{D1} and I_{D2} will increase following square law
 - Eventually M1 and M2 go out of saturation and $I_{D1,2} \approx \frac{V_{DD}}{R_D}$




Outline

- ❑ Recapping previous key results
- ❑ Single-ended (SE) vs differential operation
- ❑ Pseudo differential amplifier
 - Common-mode (CM) and differential analysis
- ❑ Differential amplifier (differential pair)
 - Common-mode (CM) and differential analysis
- ❑ Effect of mismatch in load and input pair
 - Common-mode rejection ratio (CMRR)
- ❑ Frequency response of differential amplifier
 - Common-mode (CM) and differential analysis


“True” Diff Amp (Diff Pair)

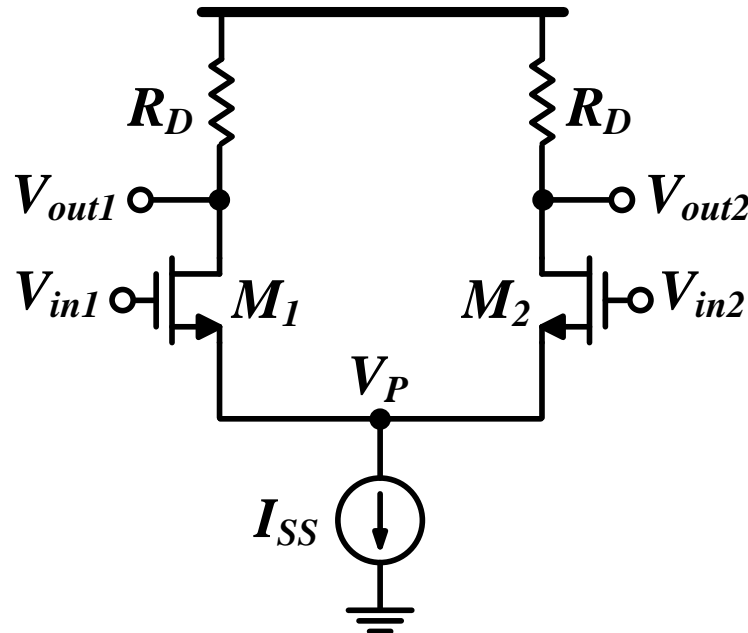- A. Small signal analysis
 - 1. Diff small signal analysis
 - 2. CM small signal analysis
- B. Large signal analysis
 - 1. Diff large signal analysis
 - 2. CM large signal analysis




Half-Circuit Principle (Differential Input)

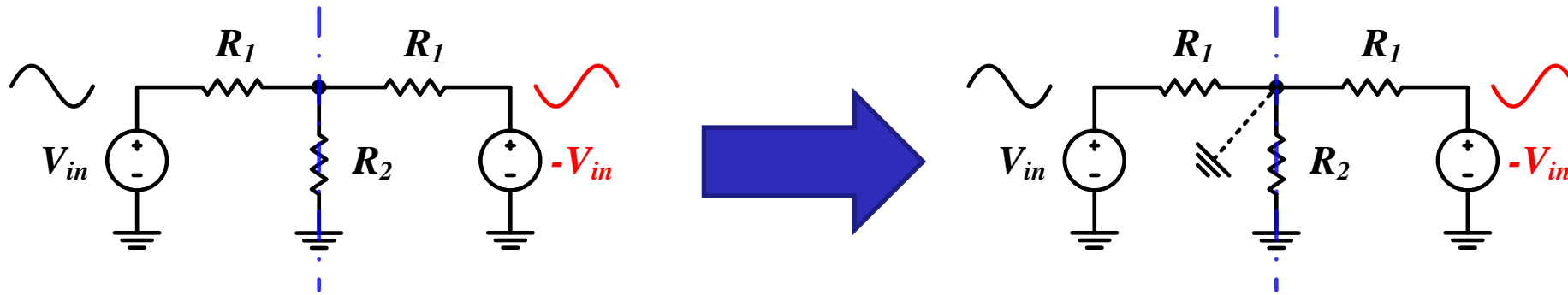- ❑ If a circuit is **perfectly symmetric**, the analysis can be greatly simplified by dividing it into two half-circuits.
- ❑ If the input to a symmetric circuit is DIFFERENTIAL
 - Any point ON THE AXIS OF SYMMETRY can be treated as a **virtual ground**.
- ❑ The circuit is divided into two identical half-circuits.





Half-Circuit Principle (CM Input)

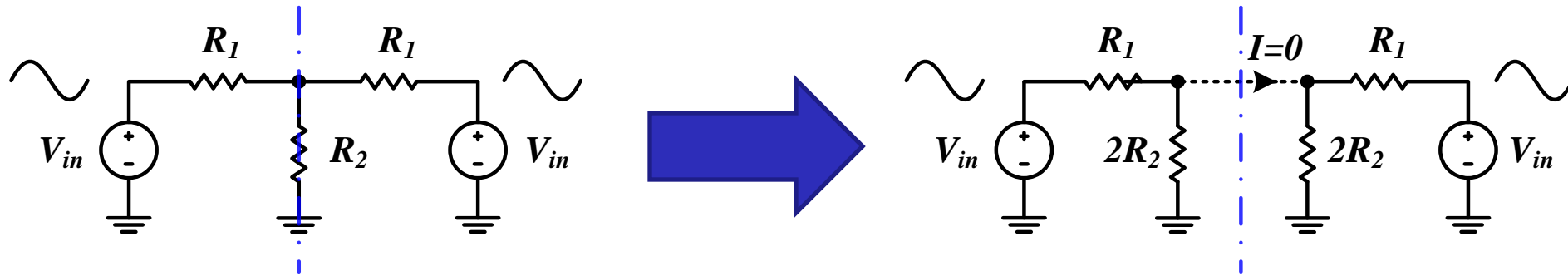- ❑ If a circuit is **perfectly symmetric**, the analysis can be greatly simplified by dividing it into two half-circuits.
- ❑ If the input to a symmetric circuit is CM
 - Any wire CROSSING THE AXIS OF SYMMETRY can be treated as **open-circuit**.
- ❑ The circuit is divided into two identical half-circuits.




A1. Diff Small Signal Analysis

- ❑ METHOD #1: Half-Circuit Principle (exploit symmetry)
- ❑ $v_{in1} = -v_{in2} = v_{id}/2$: V_P acts as virtual ground \rightarrow same as pseudo
- ❑ $v_{out1} = -g_m R_D \left(\frac{v_{id}}{2} \right)$ and $v_{out2} = -g_m R_D \left(-\frac{v_{id}}{2} \right)$
- ❑ $v_{od} = v_{out1} - v_{out2} = -g_m R_D (v_{id})$
- ❑ $A_{vd} = \frac{v_{od}}{v_{id}} = -g_m R_D = \frac{v_{out1}}{v_{in1}} = \frac{v_{out2}}{v_{in2}} = A_{v,half-circuit} = A_{v,SE}$

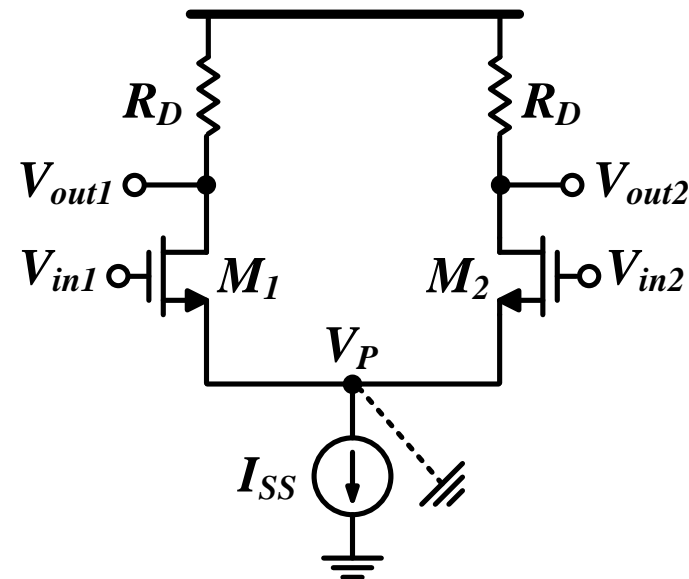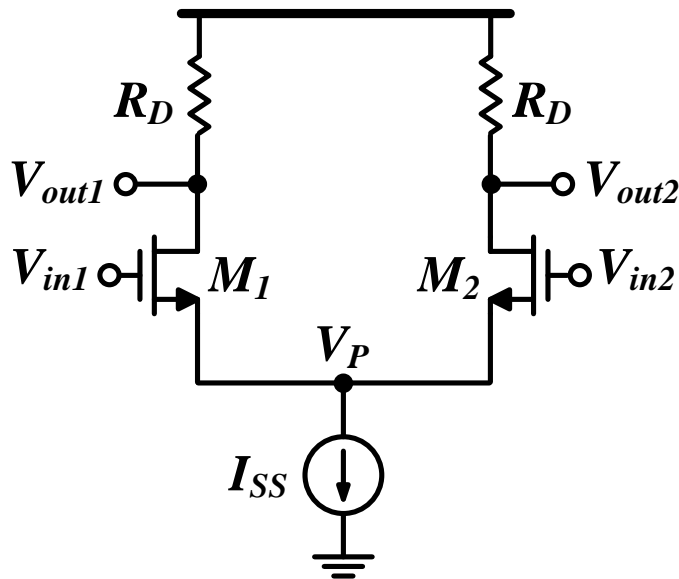


A1. Diff Small Signal Analysis

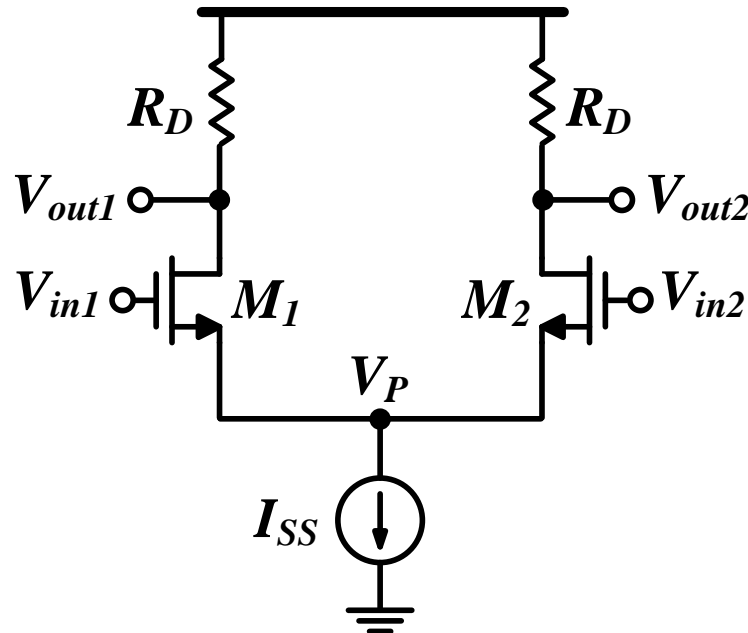- ❑ METHOD #2: **Super-position (H.W.)**
- ❑ For v_{in1} to v_{out1} : CS (M1) degenerated by M2
- ❑ For v_{in1} to v_{out2} : CD (M1) + CG (M2)
- ❑ Similarly for v_{in2}
- ❑ Same result as half-circuit principle
- ❑ Lengthy analysis! (but may be necessary if not symmetric)





A1. Diff Small Signal Analysis

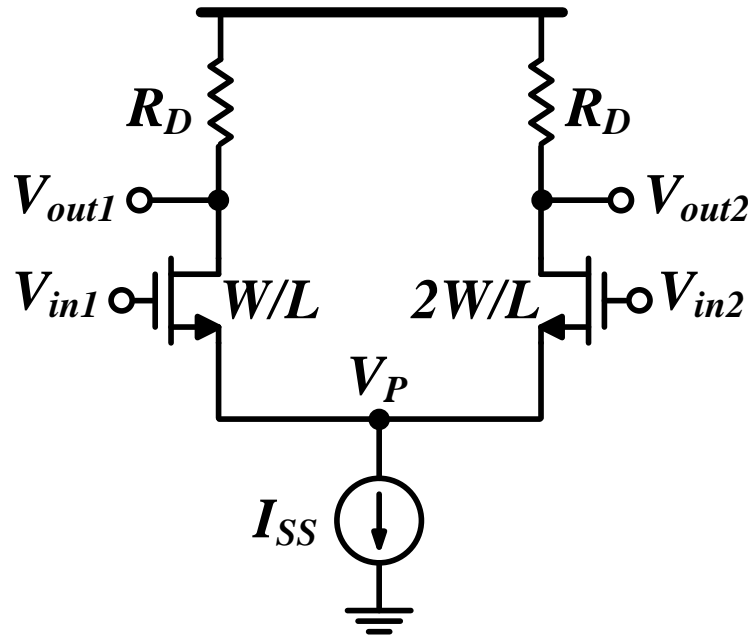- ❑ Half-circuit principle does not work in this case




A2. CM Small Signal Analysis

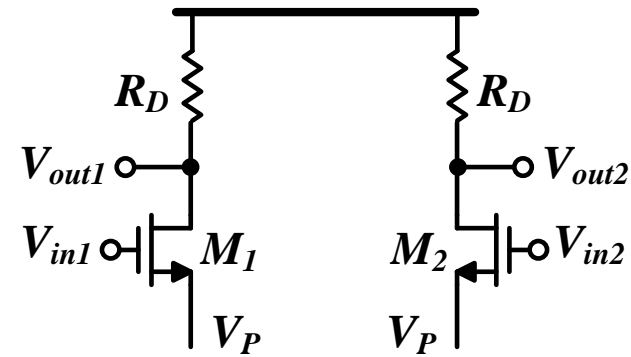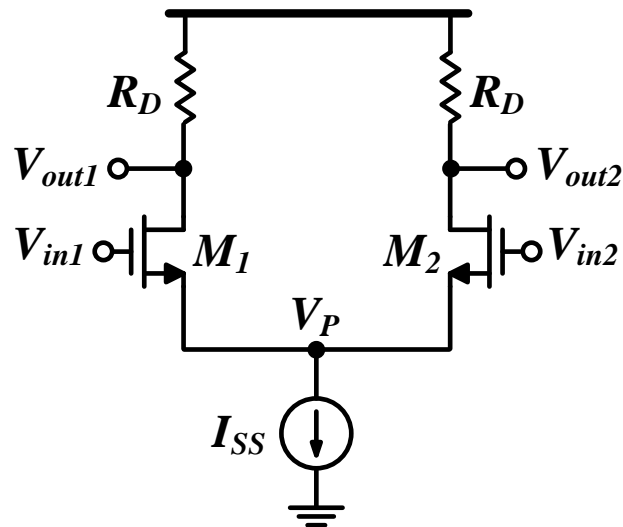- ❑ METHOD #1: Half-Circuit Principle (exploit symmetry)
- ❑ $v_{out1} = 0$ and $v_{out2} = 0$
- ❑ $v_{oCM} = \frac{v_{out1} + v_{out2}}{2} = 0$
- ❑ $A_{vCM} = \frac{v_{oCM}}{v_{iCM}} = 0 = A_{v, half-circuit} \rightarrow A_{vd}/A_{vCM} \rightarrow \infty$
- ❑ The CM output is NOT sensitive to the CM input
- ❑ CM input is “completely” rejected (compare with pseudo diff amp)






A2. CM Small Signal Analysis

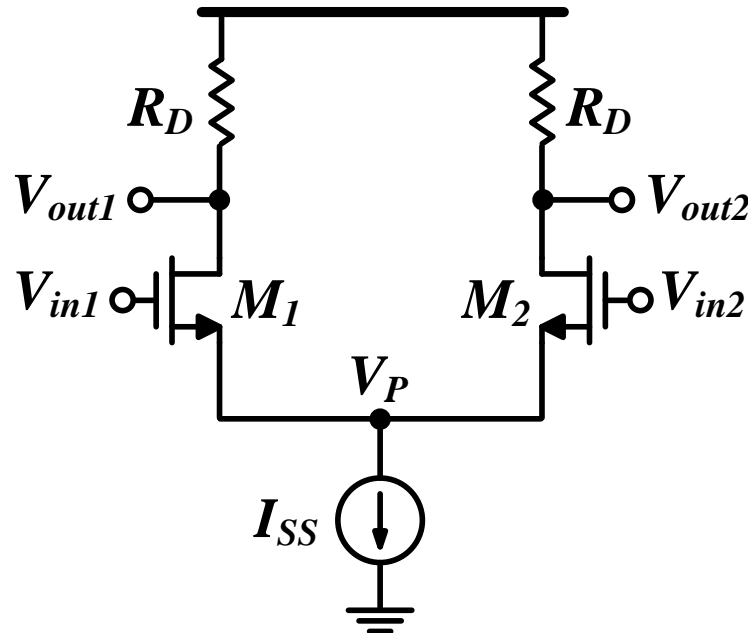- ❑ METHOD #2: **Super-position (H.W.)**
- ❑ For v_{in1} to v_{out1} : CS (M1) degenerated by M2
- ❑ For v_{in1} to v_{out2} : CD (M1) + CG (M2)
- ❑ Similarly for v_{in2}
- ❑ Same result as half-circuit principle
- ❑ Lengthy analysis! (but may be necessary if not symmetric)



A2. CM Small Signal Analysis ($R_{SS} \neq \infty$)

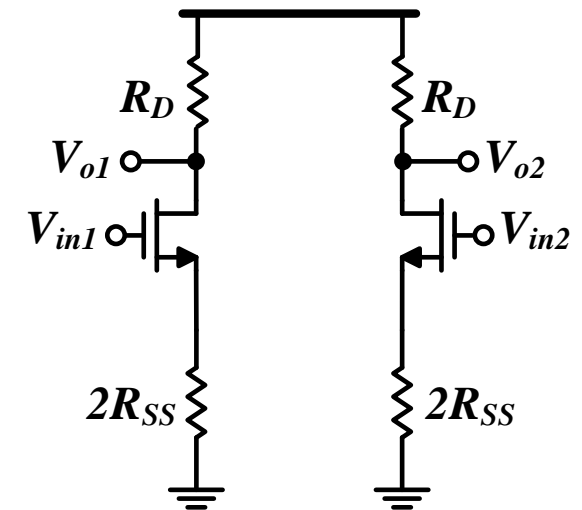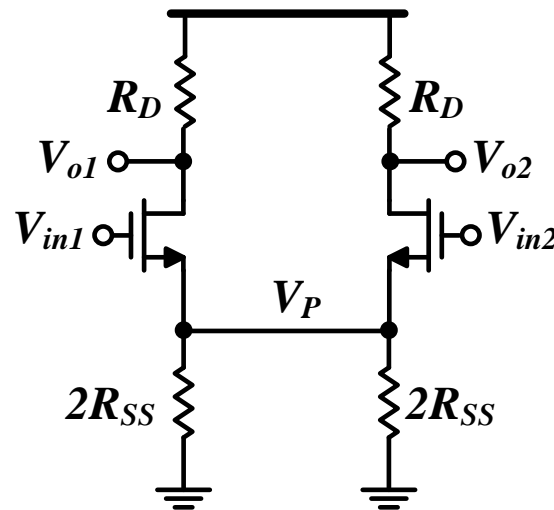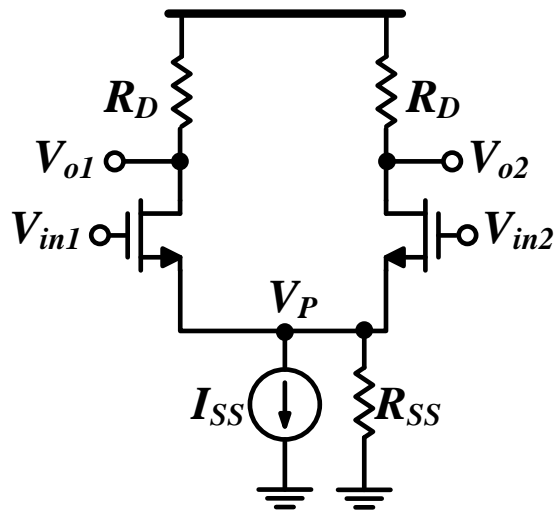- ❑ METHOD #1: Half-Circuit Principle (exploit symmetry)
- ❑ $A_{vCM} = \frac{v_{oCM}}{v_{iCM}} = \frac{-g_m R_D}{1 + 2(g_m + g_{mb})R_{SS}} = A_{v,half-circuit}$
- ❑ $A_{vd}/A_{vCM} \approx 2(g_m + g_{mb})R_{SS} \gg 1$
- ❑ CM input is “partially” rejected (compare with pseudo diff amp)




Recapping Small Signal Analysis

	Pseudo Diff Amp	Diff Pair (w/ ideal CS)	Diff Pair (w/ R_{SS})
A_{vd}	$-g_m R_D$	$-g_m R_D$	$-g_m R_D$
A_{vCM}	$-g_m R_D$	0	$\frac{-g_m R_D}{1 + 2(g_m + g_{mb})R_{SS}}$ < 1
A_{vd}/A_{vCM}	1	∞	$2(g_m + g_{mb})R_{SS}$ $\gg 1$


Quiz

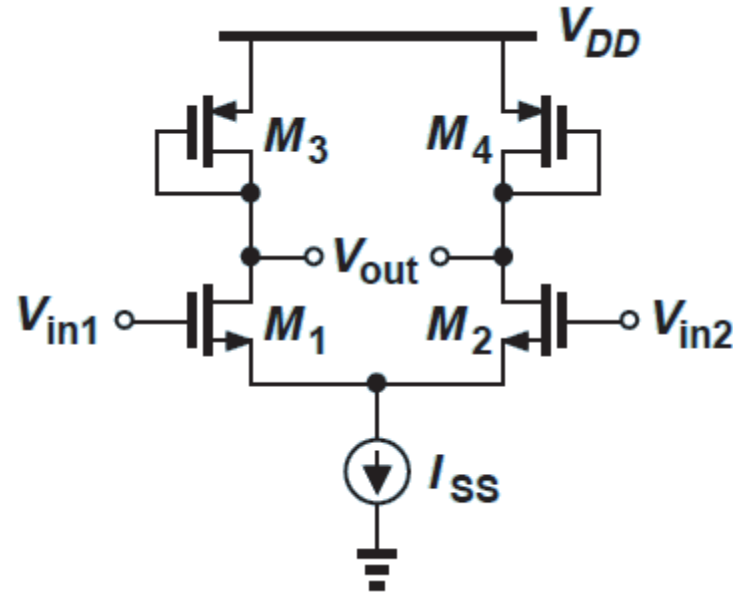- Assume symmetry and $g_m r_o \gg 1$. Calculate A_{vd} .




Quiz

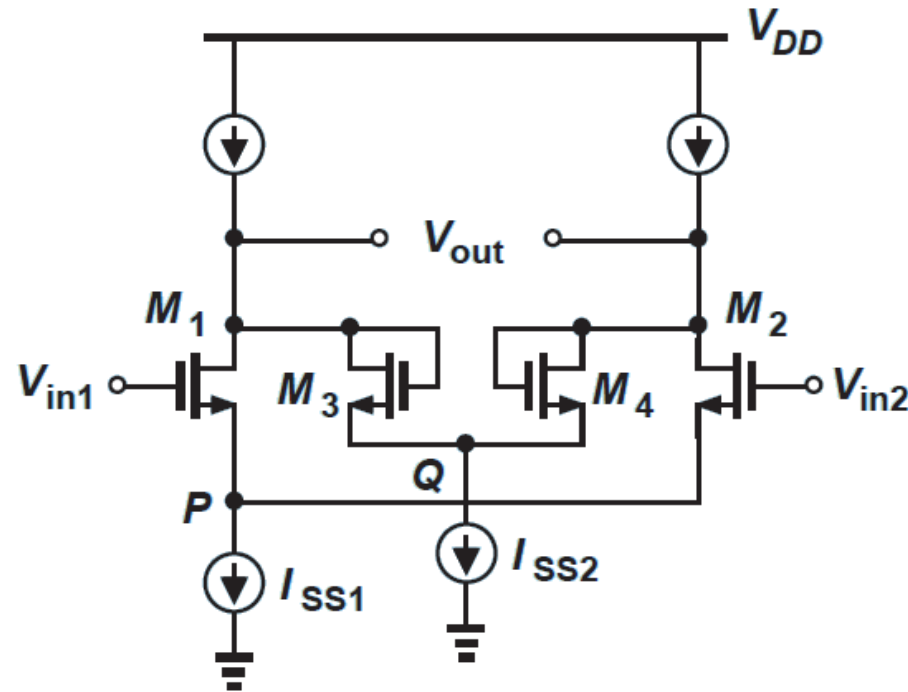- Assume symmetry and $g_m r_o \gg 1$. Calculate A_{vd} .




Quiz

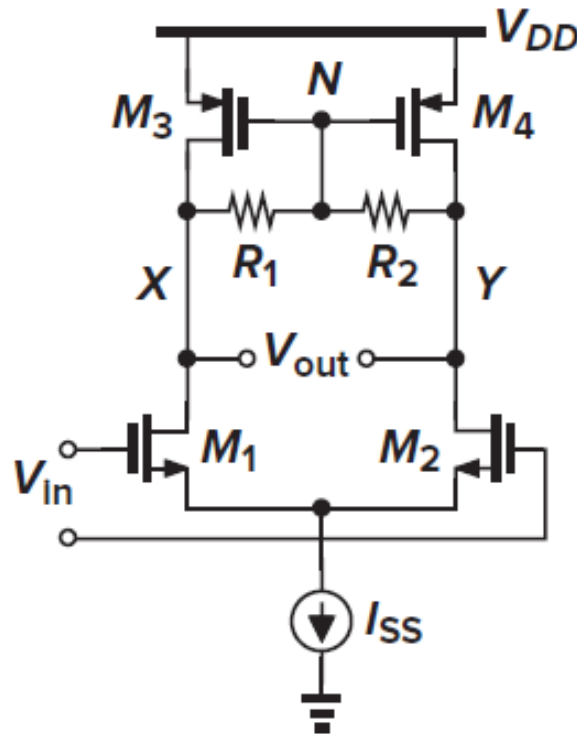- Assume symmetry and neglect channel length modulation (CLM). Calculate A_{vd} .




Quiz

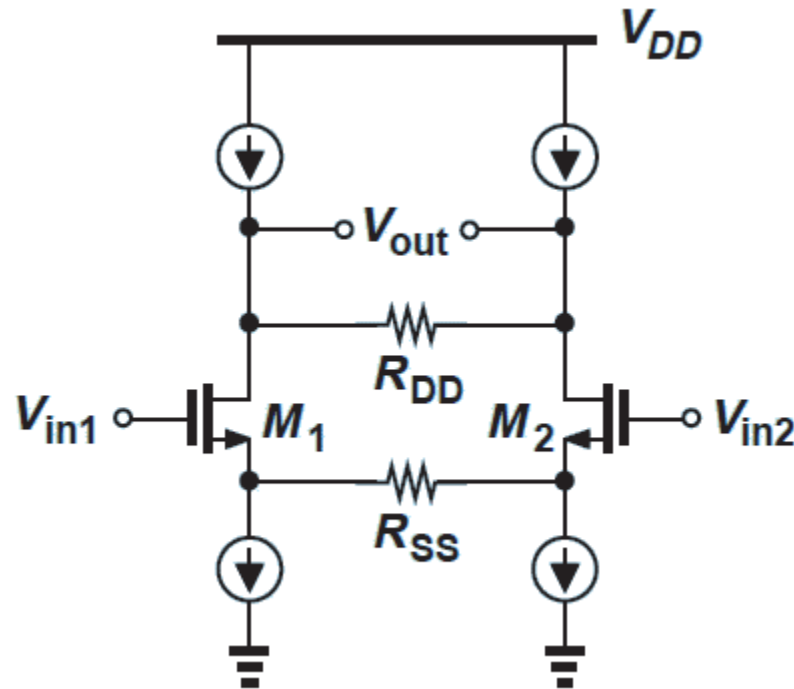- Assume symmetry and assume $g_{m1}R_{SS} \gg 1$. Neglect CLM and body effect. Calculate A_{vd} .





Quiz

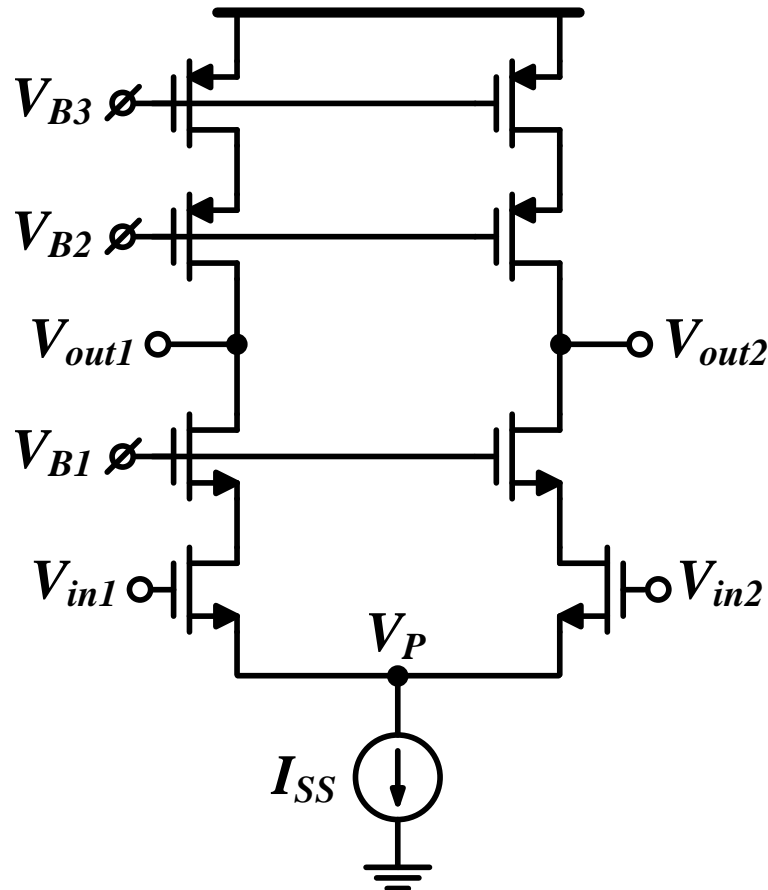- Assume symmetry, neglect body effect, and assume all transistors have the same g_m and r_o . Calculate A_{vd} .







B1. Diff Large Signal Analysis

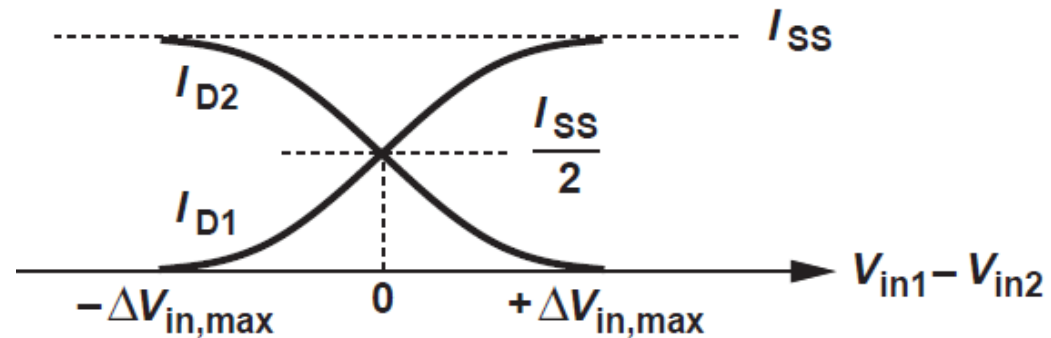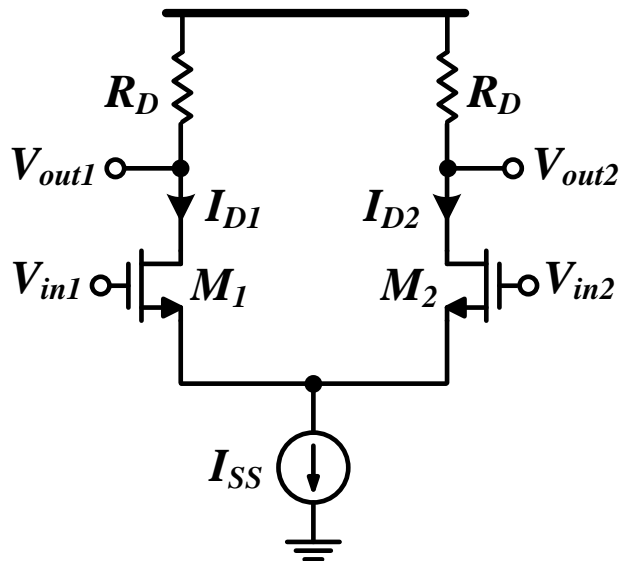- ❑ The large signal differential input voltage steers the tail current from one side to another
 - Current-steering
- ❑ Current fully steered at $V_{id} \approx \Delta V_{in,max} \approx \sqrt{2}V_{ov,eq}$ (why?)
- ❑ The current has compressive characteristics (compare to pseudo diff amplifier)
- ❑ The slope at $V_{id} = 0$ is equal to ...?




B1. Diff Large Signal Analysis

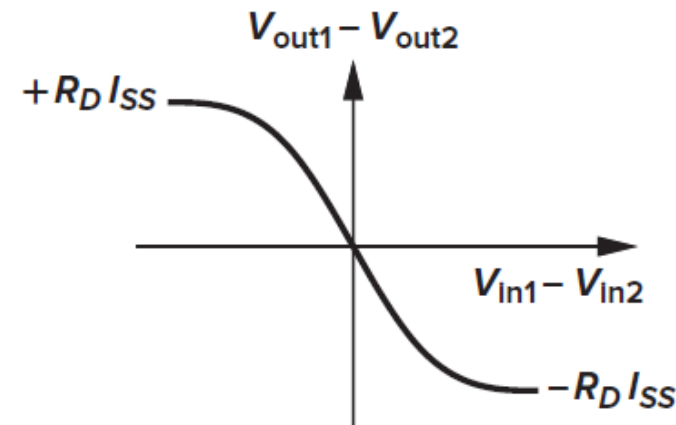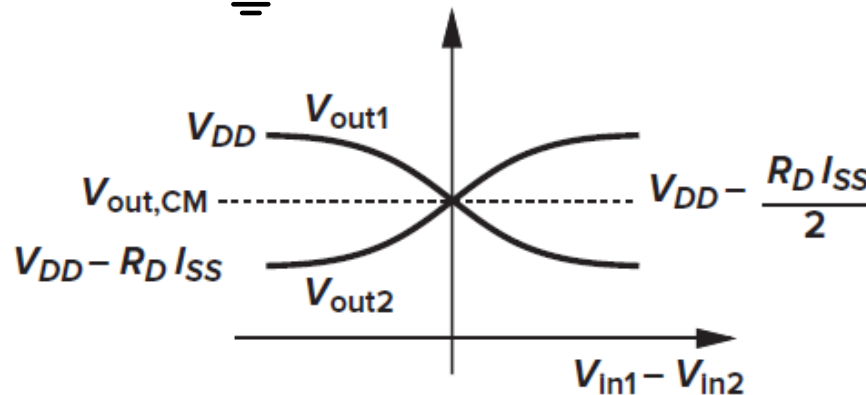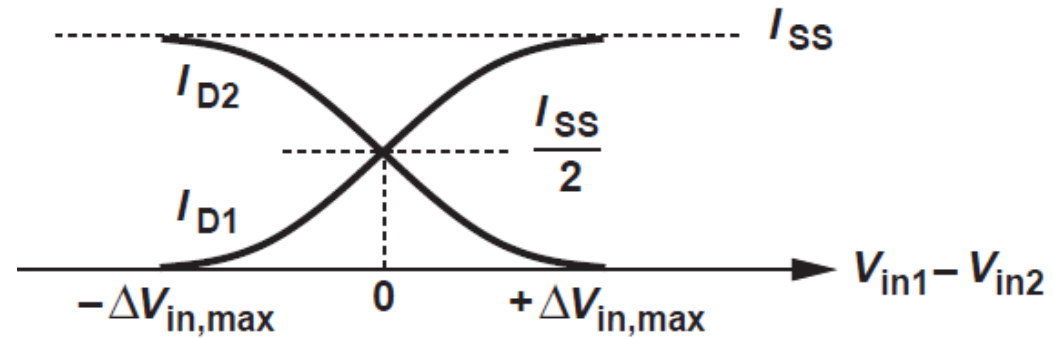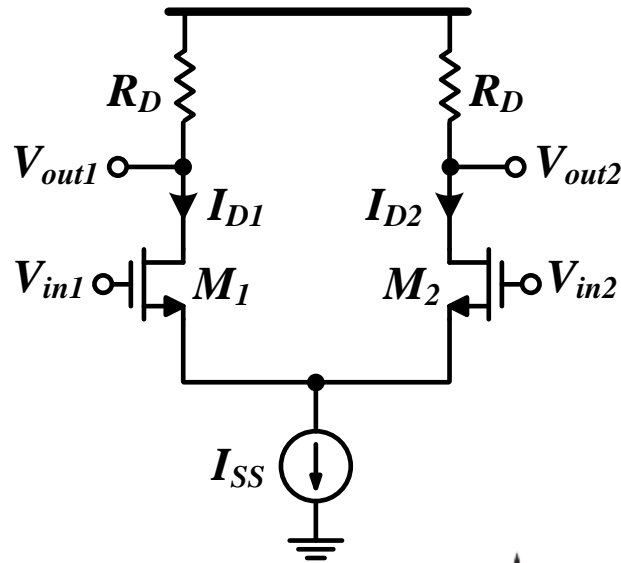- ❑ Maximum differential peak-to-peak output = $2I_{SS}R_D$
- ❑ The slope at $V_{id} = 0$ is equal to ...?




B1. Diff Large Signal Analysis

□ If tail current is doubled

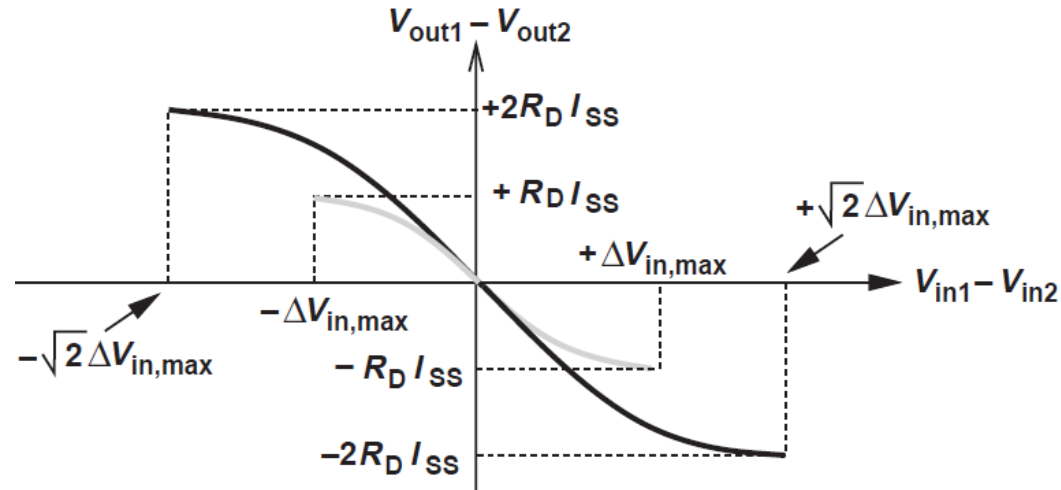

□ If aspect ratio is doubled


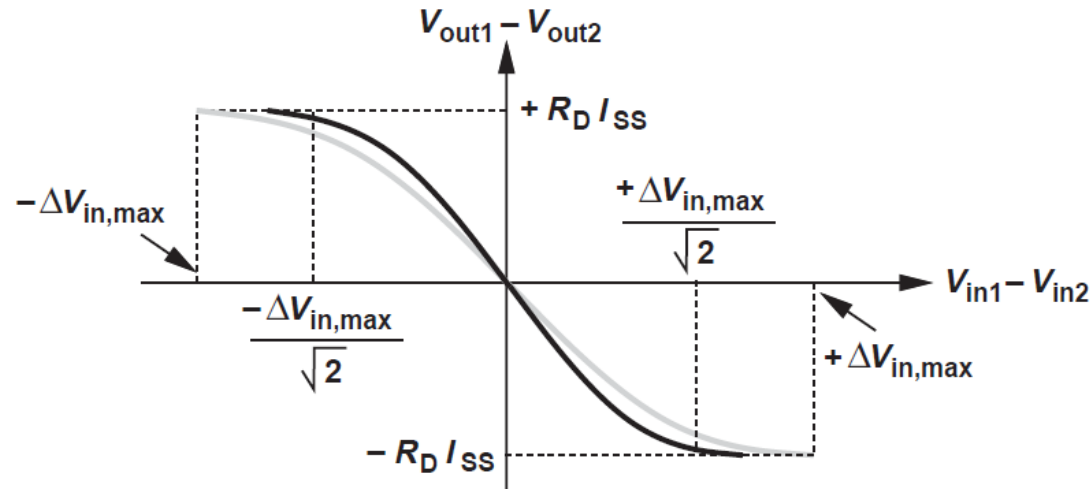


B1. Diff Large Signal Analysis

- The linear range can be increased by
 - Increasing $V_{ov,eq}$ (decreasing W)
 - Degeneration

$$\Delta V_{in2} = \Delta V_{in1} + I_{SS} R_S$$

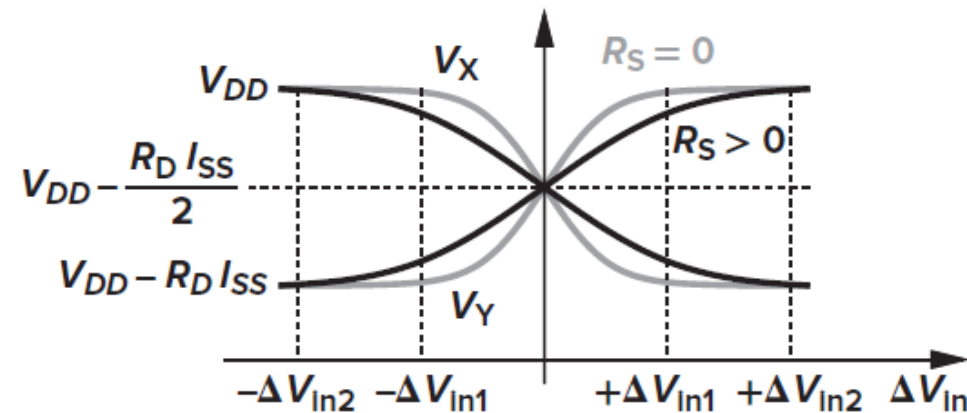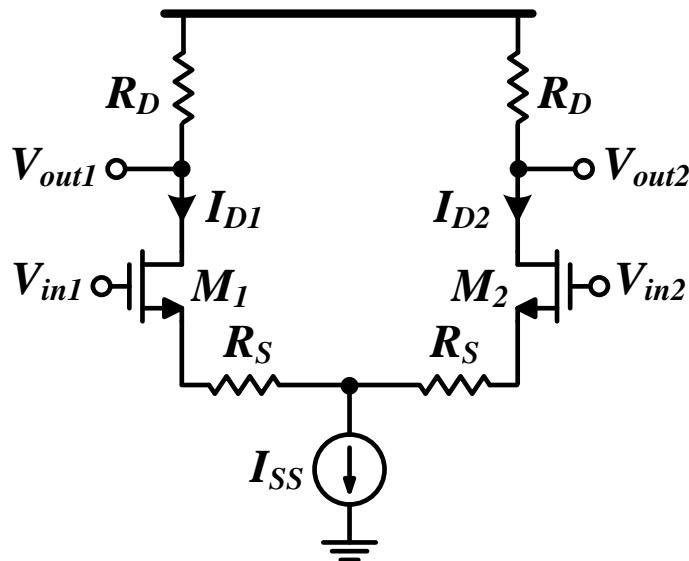- Linearity improved, but gain and headroom reduced



B1. Diff Large Signal Analysis


- Analytical large signal solution for $I_{D1,2}$ can be derived by solving two equations:

$$\begin{aligned}V_{in1} - V_{in2} &= V_{GS1} - V_{GS2} \\ I_{D1} + I_{D2} &= I_{SS}\end{aligned}$$

- Substituting with square law and solving (see [Sedra, 2015]):

$$I_{D1} = \frac{I_{SS}}{2} + \frac{I_{SS}}{V_{ov,eq}} \frac{V_{id}}{2} \sqrt{1 - \left(\frac{V_{id}/2}{V_{ov,eq}}\right)^2}$$
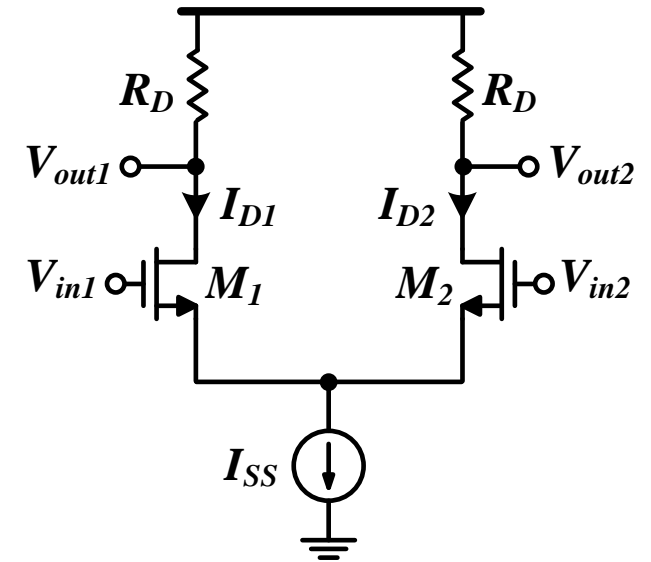
$$I_{D2} = \frac{I_{SS}}{2} - \frac{I_{SS}}{V_{ov,eq}} \frac{V_{id}}{2} \sqrt{1 - \left(\frac{V_{id}/2}{V_{ov,eq}}\right)^2}$$



B2. CM Large Signal Analysis

- ❑ The CM input ($V_{iCM} = V_{in1} = V_{in2}$) does not affect the bias point of M1,2 ($I_{D1,2}$) and the CM output level
 - Bias point is defined by the tail current source
 - No need for coupling capacitors between diff stages!
 - Compare to pseudo diff amplifier


- ❑ But all transistors must be in saturation

- ❑ M3 in sat:

$$V_{iCM} \geq V_{TH1} + V_{ov1} + V_{ov3}$$


- ❑ M1,2 in sat:
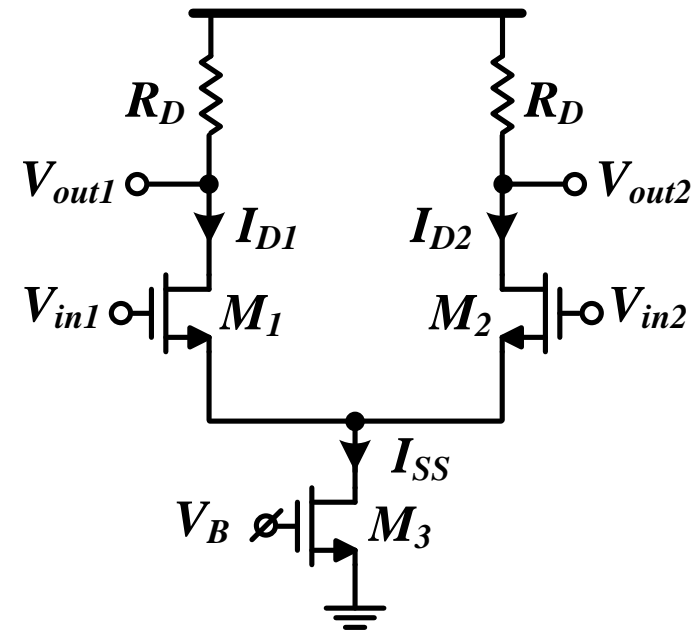
$$V_{iCM} \leq V_{DD} - \frac{I_{SS}}{2} R_D + V_{TH1}$$



Max Allowable Signal Swing

- ❑ Max output is V_{DD} : $V_{out,max} = V_{DD}$
- ❑ Min output is set by keeping M1,2 in sat: $V_{out,min} = V_{iCM} - V_{TH1}$
- ❑ Max peak-to-peak differential output swing
$$= 2 \times (V_{out,max} - V_{out,min}) = 2 \times (V_{DD} - (V_{iCM} - V_{TH1}))$$
- ❑ If V_{iCM} is set to its min value: $V_{iCM} = V_{TH1} + V_{ov1} + V_{ov3}$
$$= 2 \times (V_{DD} - V_{ov1} - V_{ov3})$$
- ❑ Deduced intuitively noting that M1 and M3 are vertically stacked
- ❑ For SE amp: Max peak-to-peak output swing = $(V_{DD} - V_{ov1})$

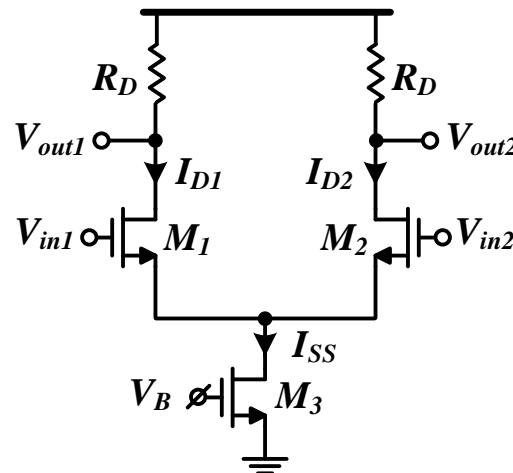

Outline

- ❑ Recapping previous key results
- ❑ Single-ended (SE) vs differential operation
- ❑ Pseudo differential amplifier
 - Common-mode (CM) and differential analysis
- ❑ Differential amplifier (differential pair)
 - Common-mode (CM) and differential analysis
- ❑ Effect of mismatch in load and input pair
 - Common-mode rejection ratio (CMRR)
- ❑ Frequency response of differential amplifier
 - Common-mode (CM) and differential analysis


Effect of Mismatch (in Load)

❑ Most dangerous effect: CM to diff conversion

❑ Example #1: Mismatch in load resistance

- If $\Delta R_D / r_o \ll 1$ then we can apply half-circuit principle at V_P
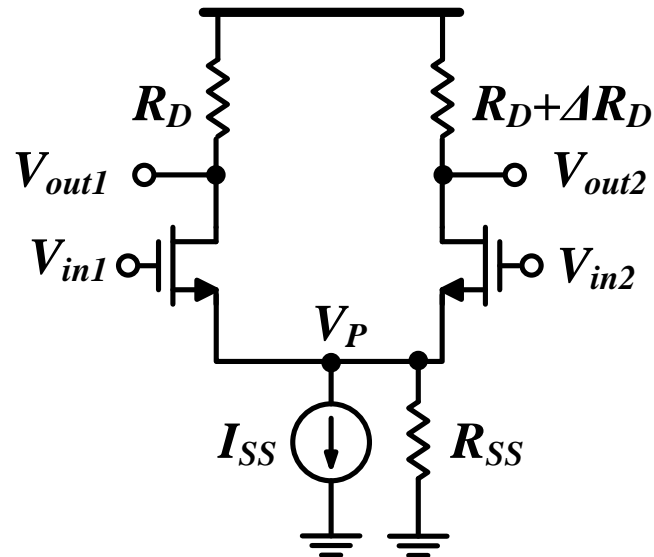
$$\begin{aligned} A_{vCM2d} &= \frac{v_{od}}{v_{iCM}} = \frac{v_{out1} - v_{out2}}{v_{iCM}} = - \left(\frac{g_m R_D}{1 + 2g_m R_{SS}} - \frac{g_m (R_D + \Delta R_D)}{1 + 2g_m R_{SS}} \right) \\ &= \frac{g_m \Delta R_D}{1 + 2g_m R_{SS}} \approx \frac{\Delta R_D}{2R_{SS}} \end{aligned}$$




Effect of Mismatch (in Load)

- ❑ Most dangerous effect: CM to diff conversion

$$A_{vCM2d} \approx \frac{\Delta R_D}{2R_{SS}}$$

- ❑ Common-mode rejection ratio (CMRR) (@low frequency!)

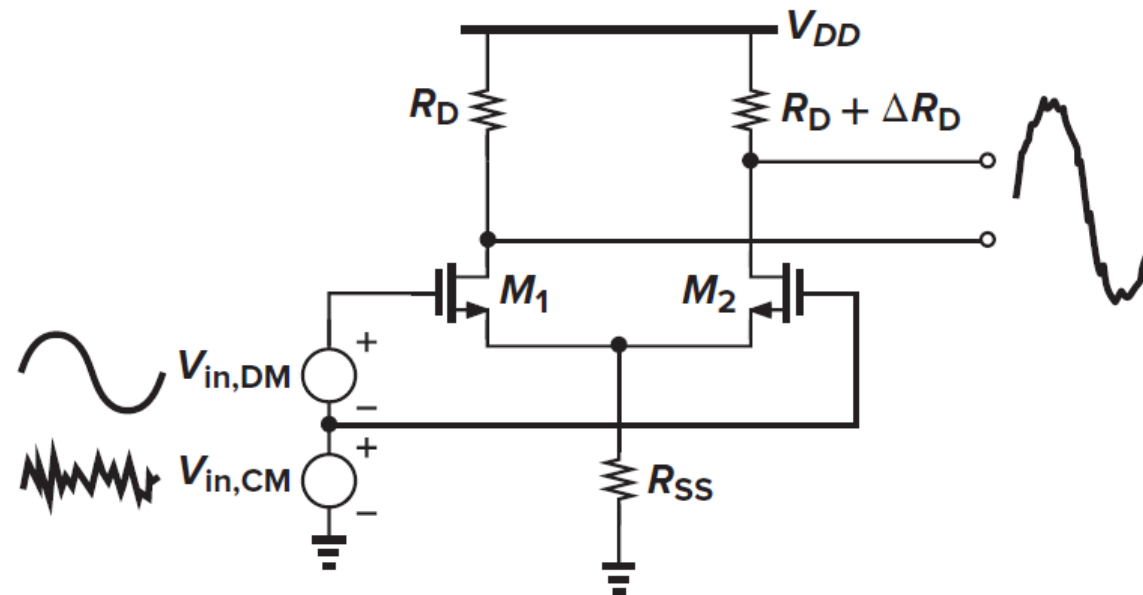
$$CMRR = \frac{A_{vd}}{A_{vCM2d}} \approx 2g_m R_{SS} \frac{R_D}{\Delta R_D}$$



Effect of Mismatch (in Input Pair)

- ❑ Most dangerous effect: CM to diff conversion
- ❑ Example #2: Mismatch in input pair: $g_{m2} = g_{m1} + \Delta g_m$
 - Half-circuit cannot be used → use superposition
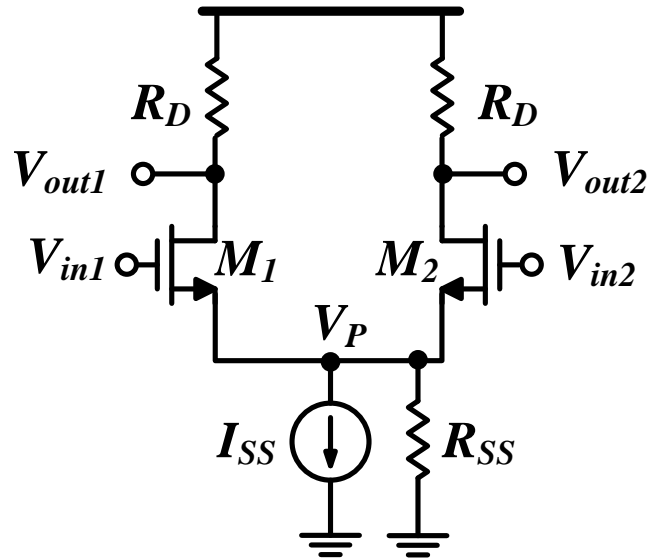
$$\begin{aligned} A_{vCM2d} &= \frac{v_{od}}{v_{iCM}} = \frac{v_{out1} - v_{out2}}{v_{iCM}} = -\frac{g_{m1}R_D}{1 + g_{m1}\left(\frac{1}{g_{m2}} \parallel R_{SS}\right)} + \frac{g_{m2}R_D}{1 + g_{m2}\left(\frac{1}{g_{m1}} \parallel R_{SS}\right)} \\ &= \frac{\Delta g_m R_D}{1 + (g_{m1} + g_{m2})R_{SS}} \approx \frac{\Delta g_m R_D}{2g_{m1,2}R_{SS}} \end{aligned}$$




Effect of Mismatch (in Input Pair)

- ❑ Most dangerous effect: CM to diff conversion

$$A_{vCM2d} \approx \frac{\Delta g_m R_D}{1 + 2g_{m1,2}R_{SS}} \approx \frac{\Delta g_m R_D}{2g_{m1,2}R_{SS}}$$

- ❑ Common-mode rejection ratio (CMRR) (@low frequency!)
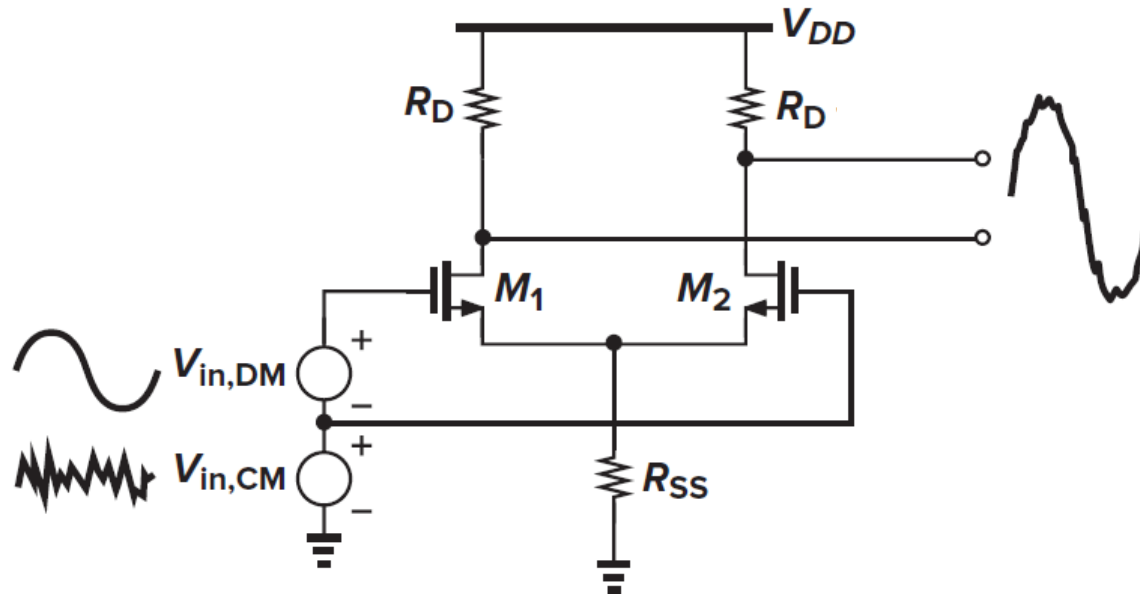
$$CMRR = \frac{A_{vd}}{A_{vCM2d}} \approx (1 + 2g_{m1,2}R_{SS}) \frac{g_{m1,2}}{\Delta g_m} \approx 2g_{m1,2}R_{SS} \frac{g_{m1,2}}{\Delta g_m}$$




Outline

- ❑ Recapping previous key results
- ❑ Single-ended (SE) vs differential operation
- ❑ Pseudo differential amplifier
 - Common-mode (CM) and differential analysis
- ❑ Differential amplifier (differential pair)
 - Common-mode (CM) and differential analysis
- ❑ Effect of mismatch in load and input pair
 - Common-mode rejection ratio (CMRR)
- ❑ Frequency response of differential amplifier
 - Common-mode (CM) and differential analysis



Diff Frequency Response

- The frequency response of the diff amp is itself the frequency response of the half-circuit
 - V_P is virtual ground
- Note that the number of poles/zeros in the diff amp is the same as the number of poles/zeros in the half-circuit
 - The two halves are added, not multiplied
 - Ex: $A(s) = \frac{A_o/2}{1+\frac{s}{\omega_p}} + \frac{A_o/2}{1+\frac{s}{\omega_p}} = \frac{A_o}{1+\frac{s}{\omega_p}}$ (what if there is mismatch?)

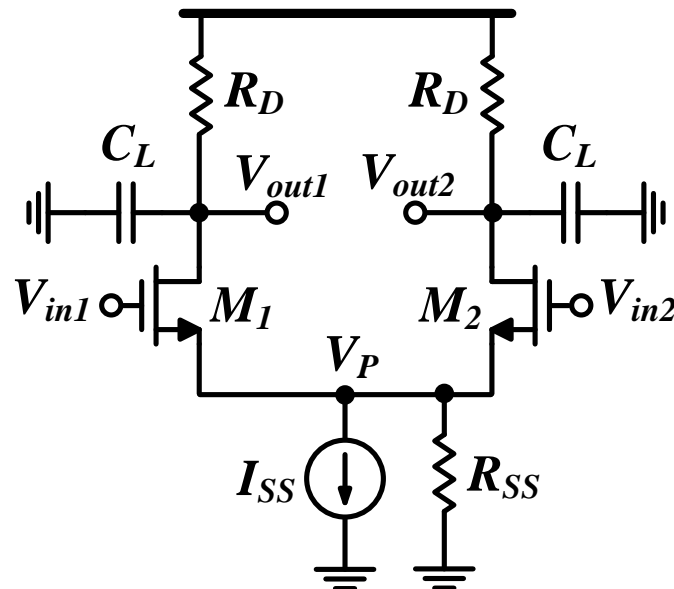

CM Frequency Response

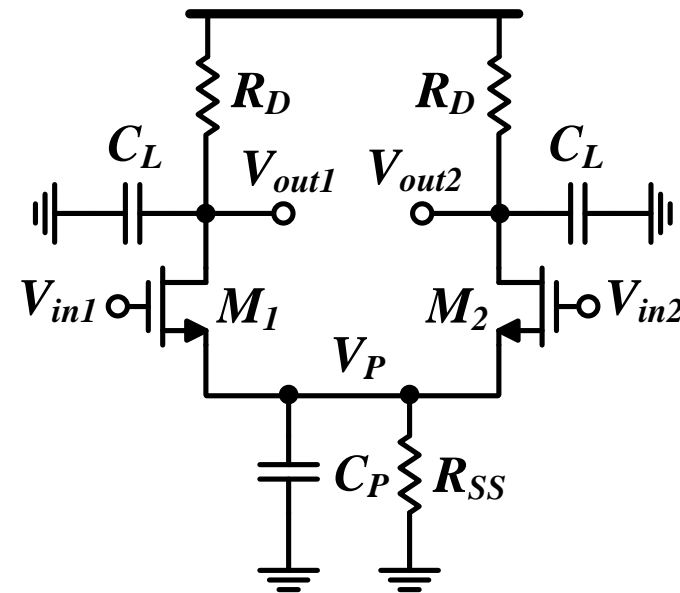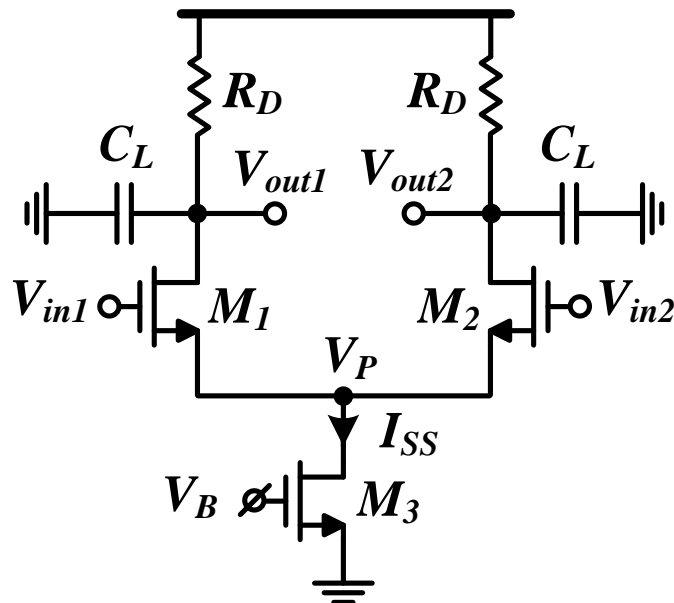- ❑ C_P degrades tail current source impedance at high frequency
- ❑ $C_P \approx C_{db3} + C_{gd3} + C_{sb1} + C_{sb2}$
- ❑ Trade-off between headroom and CMRR
 - M1-M3 are made wide to decrease $V_{ov} \rightarrow$ More g_m and more headroom
 - But C_P increases, and degrades CMRR
 - C_P resembles the bypass capacitor used in discrete CS amplifier





CM Frequency Response

- ❑ Mismatch in input pair (M1 and M2)

@Low frequency: $A_{vCM2d} \approx \frac{\Delta g_m R_D}{1 + (g_{m1} + g_{m2}) R_{SS}}$

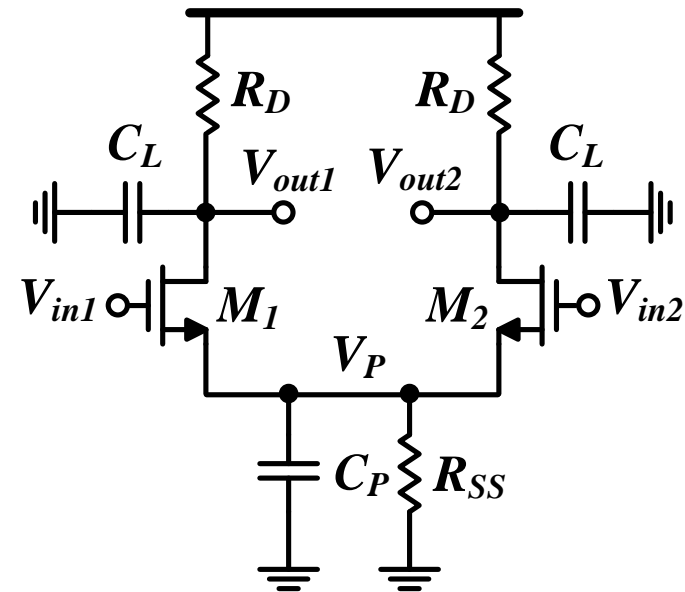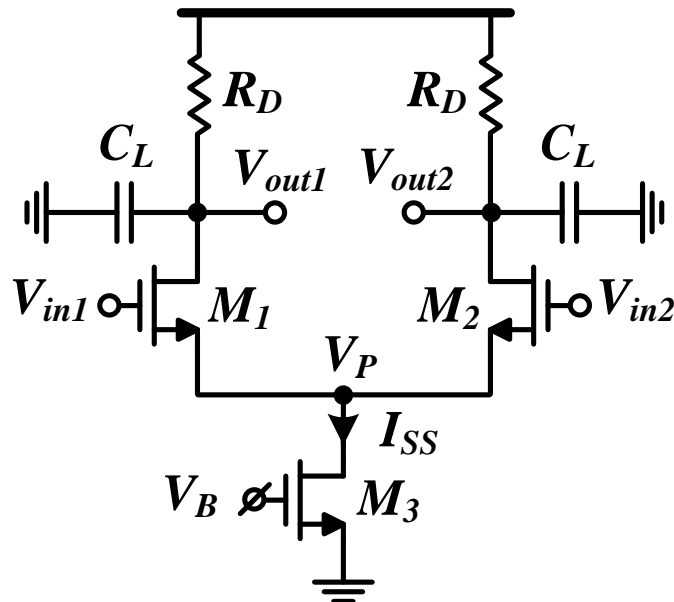@High frequency: $A_{vCM2d} \approx \frac{\Delta g_m \left(R_D \parallel \frac{1}{sC_L} \right)}{1 + (g_{m1} + g_{m2}) \left(R_{SS} \parallel \frac{1}{sC_P} \right)}$





CM Frequency Response

❑ Mismatch in input pair (M1 and M2)

@Low frequency: $CMRR = \frac{A_{vd}}{A_{vCM2d}} \approx (1 + 2g_{m1,2}R_{SS}) \frac{g_{m1,2}}{\Delta g_m}$

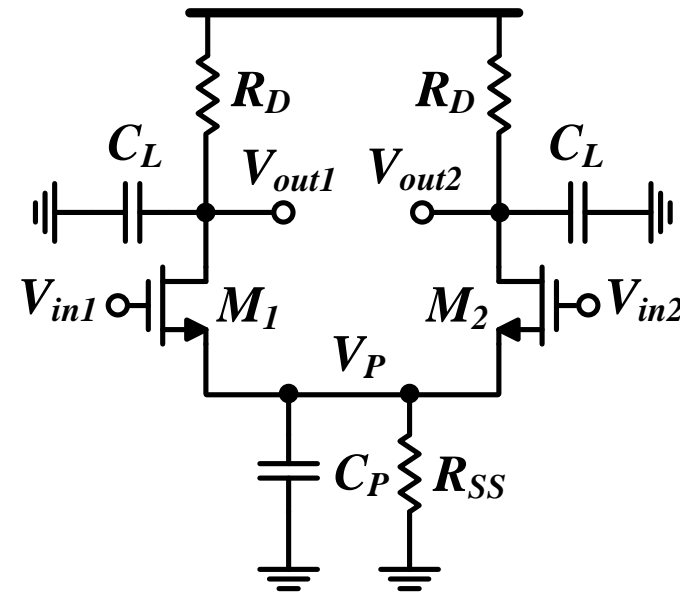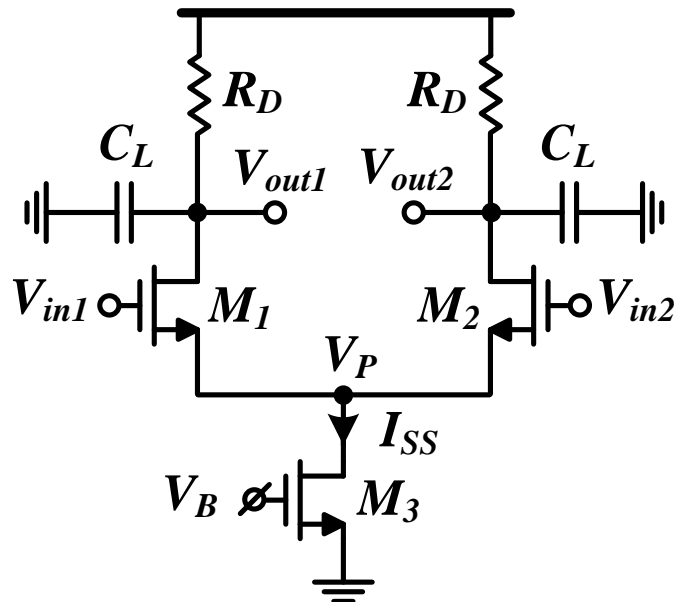
@High frequency: $CMRR = \frac{A_{vd}(s)}{A_{vCM2d}(s)} \approx \left[1 + 2g_{m1,2} \left(R_{SS} \parallel \frac{1}{sC_P} \right) \right] \frac{g_{m1,2}}{\Delta g_m}$



CM Frequency Response


- ❑ Mismatch in input pair (M1 and M2)
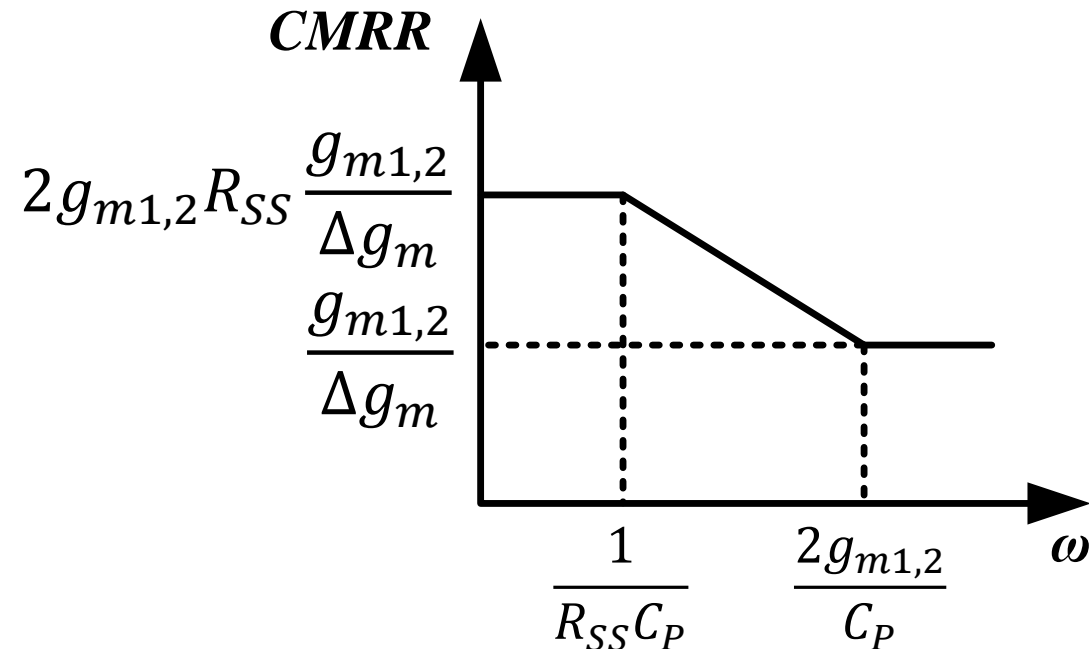
$$\begin{aligned} CMRR &= \frac{A_{vd}(s)}{A_{vCM2d}(s)} \approx \left[1 + 2g_{m1,2} \left(R_{SS} \parallel \frac{1}{sC_P} \right) \right] \frac{g_{m1,2}}{\Delta g_m} \\ &\approx \frac{1 + s \frac{C_P}{2g_{m1,2}}}{1 + sR_{SS}C_P} \cdot 2g_{m1,2}R_{SS} \frac{g_{m1,2}}{\Delta g_m} \end{aligned}$$



CM Frequency Response

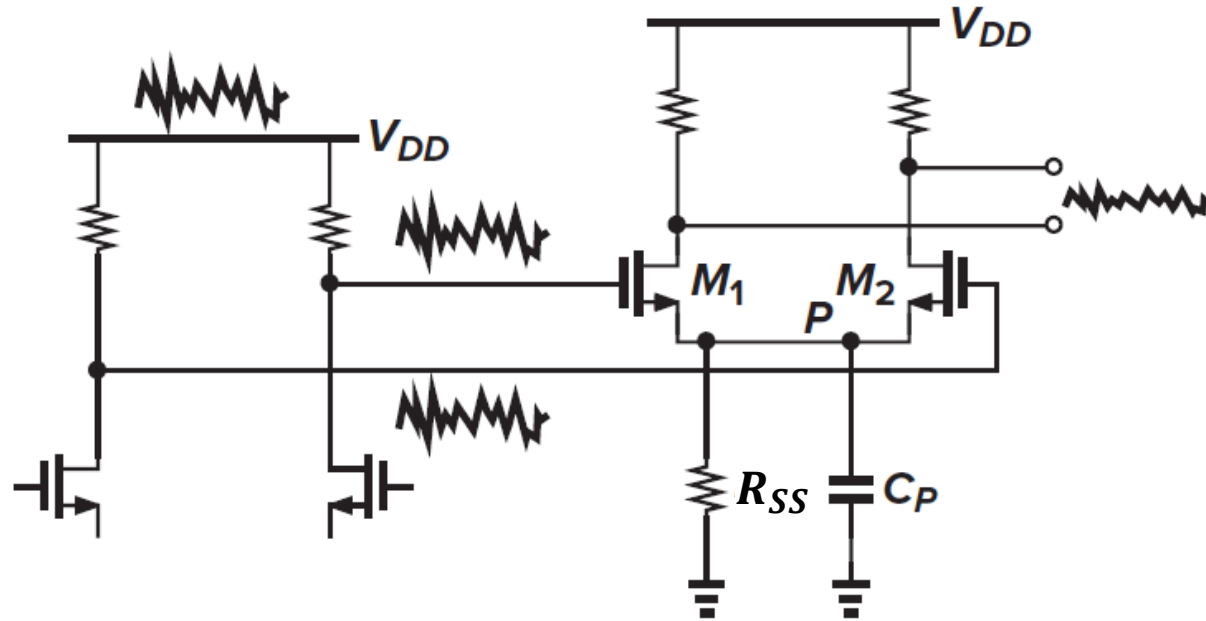- ❑ High frequency supply noise is a very serious issue
- ❑ Again: There is a trade-off between headroom (and g_m) and CMRR
 - More serious for low supply voltage



Thank you!

References

- ❑ A. Sedra and K. Smith, “Microelectronic Circuits,” 7th ed., Oxford University Press, 2015
- ❑ B. Razavi, “Fundamentals of Microelectronics,” 2nd ed., Wiley, 2014
- ❑ B. Razavi, “Design of Analog CMOS Integrated Circuits,” McGraw-Hill, 2nd ed., 2017
- ❑ T. C. Carusone, D. Johns, and K. W. Martin, “Analog Integrated Circuit Design,” 2nd ed., Wiley, 2012